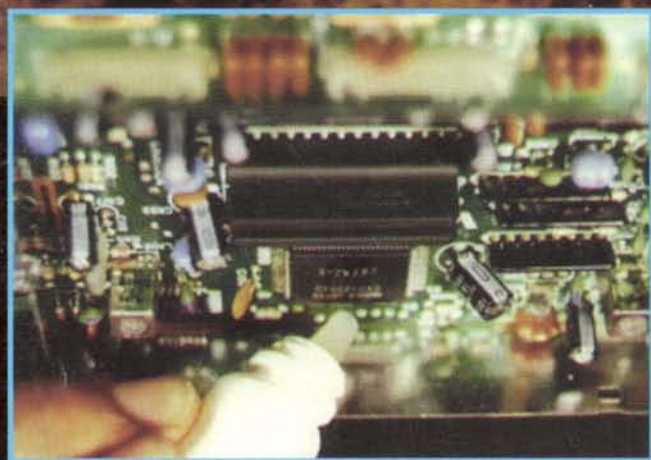


Nuts & Volts

Exploring Electronics And Technology For The Hobbyist And Professional


April 1999 Vol. 20 No. 4



SAFE AND SANE SMD REPAIR



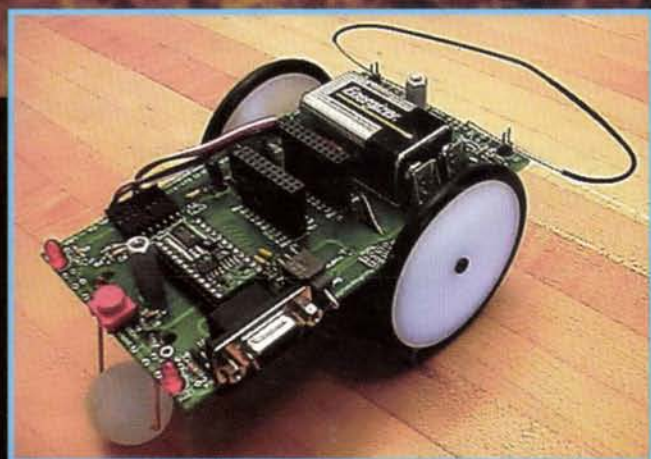MARINE ELECTRONICS FOR THE LAND RV MARKET



Amateur Robotics: GROWBOT

- Some Design Rules for Building Circuits
- One Step Beyond BASIC Stamp Application Notes
- Exploring Used Test Equipment Options

Plus Much More ...

U.S. \$3.50 CANADA \$5.00




**BOTH SINGLE AND DUAL
DRIVE MODELS AVAILABLE.**

**INTERNAL A/V HARD DRIVE
STORES DISC IMAGES FOR MULTIPLE
COPIES, AND CUSTOM AUDIO DISCS.**

**EXTERNAL SCSI-II PORT WORKS
LIKE A STANDARD CD WRITER
FOR CREATING CUSTOM DISCS.**

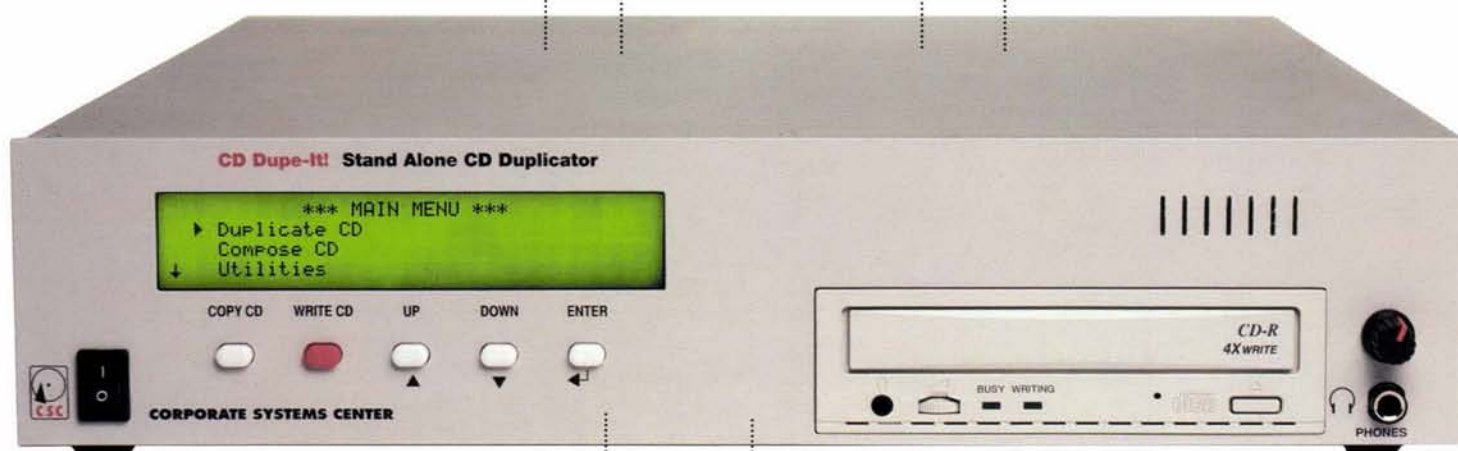**MAKE CUSTOM DISCS WITH
JUST THE MUSIC YOU LIKE.**



**TOTALLY SELF CONTAINED,
NO ADDITIONAL HARDWARE
IS REQUIRED**

**ADVANCED FORMAT DETECTION
PRODUCES PERFECT DUPLICATES
ON STANDARD CD-R MEDIA.**

COPY ANY CD NOW. NO PC REQUIRED.

DUPE-IT!

Instantly copy music and CD-ROM compact discs. Make backup copies of your favorite music and software on rugged, permanent CDs. Produce compact discs quickly and economically. No mastering or multimedia experience is required.

Insert your original CD and press "start." The multimedia processor quickly copies any disc to the internal A/V hard drive. Insert blank CDs and make as many copies as you like. You'll produce perfect duplicates. The system is totally self contained — no additional hardware is required.

**BUY DIRECT: FROM \$795!
100 BLANK CDs \$169!
408 330-5524**

Just plug in the power cord and press "start"—it's that easy.

You can even make your own custom music CD without a PC! Insert your original CD's, select the tracks you want, and Dupe-It will copy them to the internal hard drive. Then insert a blank CD, and you'll have a custom music CD with just the songs you want.

With the included CD mastering software, Dupe-It will work over-time as your personal CD design system. Just attach a SCSI cable

to your PC or Mac, and you're ready to design and create your own original CD's. Similar systems used in duplication houses cost over \$5,000. Now you can easily copy CDs yourself for a fraction of the price.



CORPORATE SYSTEMS CENTER
3310 WOODWARD AVE., SANTA CLARA, CA 95054
WWW.DUPEIT.COM

Musicians—ask about our pro-audio CD recorders. Software publishers—ask about our high-volume multi-drive duplication systems. Dupe-It is sold and intended for backup and in-house design purposes only. Copyright laws must be observed.

HSC Electronic Supply

Serving Silicon Valley since 1964!

...brings you a potpourri of high-tech goodies for the techno-tinkerer! For thirty years we have been your source for Silicon Valley exotica!

Tiny Color CCD Camera!

One of the world's smallest color cameras!
Camera-on-a-board measures 1.87" x 1.3", 1" thick!
Has glass micro-lens element, not pinhole lens
DSP on board for auto white-balance, shutter
Standard NTSC composite video output
350 lines horiz. resolution, good low-light sensitivity
uses 4 - 5 VDC, only 150 mA! Three AA batteries would power it for over six hours!
New in OEM pkg (no box), 90-day HSC warranty



HSC#17736 \$89.95

Pentium II Motherboard

Micronics C300 Mini-ATX (7.5" x 12") Motherboard!
For Intel Pentium II or Celeron 233 - 333 MHz CPU
Intel 440LX PIII 4 chipset, 3-3.3v. unbuffered 168-pin DIMM sockets, up to 384MB, ECC memory support
Dual channel PCI bus mastering Ultra DMA/33 EIDE
-AGP slot, 4-PCI slots, 1-ISA slot (1-PCI/ISA shared)
- USB ports, 2 SIO (16550 compatible), 1-PIO (ECP/PP/STD)
-DA compliant IR Header, SB-LINK header
AMI PCI BIOS on 1MB
Flash with Advanced Power Management 1.2
New, 90-day warranty, with CPU retention post, FD/HD ribbon cables, Driver CD, instruction manual via Adobe Acrobat Reader (Note: CPU not included!)



HSC#17809 \$75.00

Home Alarm Stuff!

These items are dealer-returned inventory (shelf worn packaging but unused) of home security components that were made by Telko Inc. Mix and match to create your own bargain security system! All items have mounting screws or adhesive pads, instructions, and alarm units have window warning stickers. All parts have 30-day warranty.

ST911 Automatic Phone dialer has screw terminals for sensor input, power adapter, and very long phone cord. Instantly contacts up to four pre-selected phone numbers with your own digitally recorded 16 second message.

HSC#17718 Phone Message Dialer \$27.50

S100M Magnetic entry sensors (mag-switch) have a reed-switch and magnet pair for door or window mounting, and approx. 50 feet of white hook-up wire.

Use with PIR units or Entry Guard below for additional protection. Switches may be used in series for multiple door/window protection.

HSC#17723 Magnetic Entry Sensor \$1.95

S002M Digital Control Motion Alarm has wall-mount keypad, PIR infrared motion detector with 110° coverage to 60 feet, programmable security code, 10 - 15 second entry delay, extremely loud alarm.

Uses 9V battery or AC Adapter (neither included)

HSC#17720 Digital Control Motion Alarm \$15.00

S008B Digital Control Motion Alarm with Safety Chime has wall-mount keypad, PIR infrared motion detector (same as S002M above) with very loud alarm OR safety chime alert.

Uses 9V battery or AC Adapter (neither included)

HSC#17721 Digital Motion Alarm/Chime \$17.50

S082X Entry Guard Alarm has wall-mount keypad, mag-switch activation (one switch included), programmable security code, 10 - 15 second entry delay, extremely loud alarm or pleasant door chime.

Uses 3 AAA batteries (not included)

HSC#17722 Digital Entry Guard Alarm \$12.50


Superior Motherboards!

High-quality Micronics motherboards for top-level performance! Both boards feature:

- ◆ Built-in Pri. & Sec. Mode4 IDE controller, floppy controller
- ◆ 2-USB ports at 12Mbps rate, connect as many as 127 devices to host system
- ◆ 2 SIO ports, 1 PIO port, Game/MIDI port, PS/2-style keyboard and mouse connectors
- ◆ Full support for the 'Green PC' specification

- ◆ "DUAL FORTRESS" has dual Intel Slot 1 sockets for Intel Pentium II chip at 233/266/300 MHz (CPU's not included)
- ◆ ATX motherboard has 4 PCI, 2 ISA slots, (one shared)
- ◆ Intel 440FX PClset, PIII 3, SMC FDC37C93X Ultra I/O
- ◆ Four 3.3V unbuffered 64-bit DIMM sockets, support for EDO, BEDO, Fast Page Mode (FPM) memory, ECC
- ◆ Yamaha OPL MIDI/sound on board w/ drivers
- ◆ New in box, 90-day warranty, with instruction book, CPU brackets, Win/DOS driver diskettes & cables

HSC#80469 \$99.00

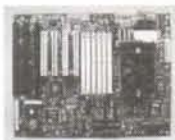

- ◆ M6MI "Pentium Pro" ATX motherboard has 4 PCI, 3 ISA slots, Intel 440FX PClset
- ◆ Comes with tested "Pentium Pro" 150 MHz CPU installed w/ heatsink, fan & VRM module
- ◆ Supports up to 384Mb memory (6 x 72-pin SIMMs)
- ◆ Support for EDO, Fast Page Mode (FPM) memory, ECC
- ◆ New in box, 90-day warranty, with instruction book

HSC#17625 \$129.00

PCMCIA Sound Card!

Media Vision PCMCIA Sound Card

- ◆ Great for Portables, Laptops with PCMCIA Slot
- ◆ External pod has joystick port, mic. input, line in & line out jacks, volume control.
- ◆ Install software, inst. included.
- ◆ Win 3.x, W95 compatible
- ◆ New in OEM pkg (no box), 90-day HSC warranty
- ◆ We had these before at \$39.95 and they went fast!

HSC#17036 \$29.95

Briefcase of Goodies!



- ◆ These handsome hardshell cases were used to carry a laptop-computer estimating system (laptop not included)
- ◆ They were used with a Compaq LTE laptop, and provided a SCSI port for a CD-ROM drive with battery back-up
- ◆ Large Nicad pack has 10 Sanyo Cadnica cells.
- ◆ Built-in 19VDC power supply for battery charging
- ◆ Tiny piggy-back PC board seems to be a SCSI interface
- ◆ Case measures 18" x 14" x 7", with several compartments
- ◆ SCSI II to CEN50 SCSI cable, many great parts inside!
- ◆ Buy either the whole assembly, or just the parts you want!
- ◆ Not guaranteed to function with laptops -- for parts only!

HSC#17180 Complete Laptop Case \$29.95

HSC#17182 Empty Hardshell Case \$15.00

HSC#17181 Nicad Pack, 12.5VDC, 5AH \$17.50

HSC#17179 SCSI II Cable, 1 ft. long \$12.50

CyberEye PC Camera!

- ◆ High-quality (nice looking too!) composite color camera
- ◆ 1/4 inch CCD sensor w/auto white balance control
- ◆ Resolution: NTSC video, 542 x 492
- ◆ Manual focus knob/ring, 5mm to infinity
- ◆ Power: 5.0 VDC @ 180 mA. Supply from PC or keyboard power...no external adapter needed!



HSC#17535 \$69.00

Compaq Docking Bay

- ◆ Compaq docking "Smartstation" for laptop computer (we don't know which!)
- ◆ Has two internal ISA slots
- ◆ SCSI port, network ports, serial, parallel, video, keyboard & mouse ports on back.
- ◆ Used, 90-day warranty



HSC#17713 \$39.00

PCI-Bus 56K Modem!

- ◆ Genica PCI-Bus 56K Modem at unheard-of price!
- ◆ Data, FAX, voice, full V.90 compatibility
- ◆ Voice from handset
- ◆ Windows 95/98 or NT only (Not Win 3.1 compatible)
- ◆ Uses latest Lucent chipset, comes with Lucent drivers
- ◆ New retail box, with Trio application software on CD
- ◆ 90-Day Warranty



HSC#17532 \$39.95

Ultimate Family Tree Deluxe Software

- ◆ Easiest and fastest software for cataloging and completing your family tree!
- ◆ Free professional genealogy family search
- ◆ Access to over 500,000,000 names and sources!
- ◆ Easy step-by-step instructions and tutorials included
- ◆ Lots of charts and reports!

HSC# 80471 \$9.95

Workhorse Hard Drives!

- ◆ Seagate with SCSI interface full-height drives
- ◆ Good, Reliable drives for many applications
- ◆ Choose from 670 or 330 MB size
- ◆ With 90-day warranty!



HSC#17556 ST4766N \$35.00

HSC#17557 ST4385N \$29.00

Video-hacker Dream!

- ◆ Logitech Videoman Video-conference camera & interface
- ◆ These units were sold with Hewlett Packard S-700 workstations for videoconference capability
- ◆ We do not have technical data, software or manuals
- ◆ All we have is cameras with stand, and SCSI-II interface
- ◆ The camera is on a weighted stand that extends from 13" tall to over 20" tall, and has a stereo microphone
- ◆ Color camera is digital output only (not NTSC) as far as we can tell -- but who knows?
- ◆ Interface box has two SCSI-II ports on back, and a DC power input (we do not have the adapter), and on the front it has a mic. out jack, composite video out (BNC), and the connector for the camera cable.
- ◆ Note: HP and Logitech will provide no information on these



HSC#17503 \$39.95

Get the Right Touch with ALPS Input Devices!

Get name-brand quality at bargain-basement prices with these premium keyboards and mice -- all are new and have a 90-day HSC warranty. Some quantities limited!

Alps Premium Keyboard

- ◆ 'AlpsTouch' (tm) Model: MCL-101
- ◆ Premium mechanical keyswitches
- ◆ Audible key clicks
- ◆ Industry-standard 101-key layout
- ◆ IBM AT, PS/2 and 100% compatible

HSC# 17828 \$14.95

Alps PS/2 - Style Keyboard

- ◆ Alps 'WB' series PC compatible keyboard
- ◆ 101 key, Windows layout
- ◆ Small footprint, low profile, lightweight

HSC# 17829 \$12.50

Alps Adjustable Mouse

- ◆ For Macintosh computers
- ◆ The first mouse that adjusts to you!
- ◆ Three programmable buttons!
- ◆ Sleek design for comfort, easy handling
- ◆ Chording -- Program multiple button combinations!
- ◆ Requires Mac OS 6.04 or later, available ADB port
- ◆ 400 dpi resolution, Made in U.S.A.

HSC# 17827 \$17.50

Alps 2-Button Mouse

- ◆ Two-button type with PS/2 plug
- ◆ Ergonomic shape for comfort, easy handling
- ◆ Ultima Driver software v1.3 diskette included
- ◆ 400 dpi resolution
- ◆ New, OEM package, 90-day warranty

HSC# 17830 \$3.95

Alps PS/2 Mouse

- ◆ Sleek two-button design
- ◆ Designed for comfort, easy handling
- ◆ Alps 'professional' series mouse
- ◆ 400 dpi resolution, Made in U.S.A.
- ◆ New, OEM package, 90-day warranty

HSC# 17831 \$4.95

Alps Glidepoint Touchpad

- ◆ Desktop pointer...replaces your mouse or trackball
- ◆ Three programmable buttons
- ◆ 'Taps' for instant selection (highlighting, clicking...etc!)
- ◆ Large touchpad for comfort and accuracy
- ◆ DOS, Windows 3.xx and 95 compatible
- ◆ Adjustable base for convenience and control

HSC# 17832 \$14.95

External SCSI Drive Cases

- ◆ Bargain case for 5.25" drives, brand new!
- ◆ 7" x 4.5" x 10.5" overall size
- ◆ 50-pin SCSI connectors
- ◆ SCSI ID switch
- ◆ 65W Power supply (lots of power for hard drives, etc.)
- ◆ Fan-cooled, uses standard IEC Power cord (not included)



HSC# 17130 \$39.95

Lead-Acid Rechargeables!

These are all new batteries by Tempest with tab terminals. Perfect for hobbies, security systems, battery back-up, etc.

- ◆ TR1.2-6, 6VDC at 1.2 AH, measures 3.75 x 1 x 2"
- ◆ TR1.2-12, 12VDC at 1.2 AH, measures 3.75 x 1.875 x 2"
- ◆ TR4-6, 6VDC at 4 AH, measures 2.75 x 1.75 x 4"

HSC#17589 \$3.95

HSC#17197 \$4.95

HSC#17588 \$4.95



Visit HSC's Website!

Pay us a virtual visit on the World Wide Web!
Simply point your browser to <http://www.halted.com>
Site is constantly being revised, please visit often!
Check out the amazing "Gizmo of the Week" feature!

HSC Catalog online!

- ◆ That's right, get HSC's catalog on the World-Wide Web!
- ◆ Simply go to www.halted.com and follow the big red link.
- ◆ Adobe .PDF files are available for download and viewing.
- ◆ Or drop on by and pick one up...we'd love to see you!

Some quantities limited; all items subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to .00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight!) by UPS Surface (P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee applies. Prepaid orders that include shipping charges will be shipped freight COD. There is a \$5.00 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1854 M-F 9AM to 5PM PST.

Halted
specialties co.

HSC Electronic Supply

Toll Free (Orders Only) 1-800-4 HALTED
Internet World Wide Web:
3500 Ryder St., Santa Clara, CA 95051
4837 Amber Ln., Sacramento, CA 95841
5681 Redwood Dr., Rohnert Park, CA 94928

(1-800-442-5833)
<http://www.halted.com>
(408) 732-1573
(916) 338-2545
(707) 585-7344

FAX your orders to:
(408) 732-6428



CATCH IT. HOLD IT. TUNE IT.

NEW

Tuning your receiver will never be easier. Introducing the all new Mini Scout Reaction Tuner. With a .001 second measurement time, the Mini Scout will not miss even the briefest of transmissions. While locking onto a frequency from up to 200 feet away (5w UHF), the Mini Scout automatically tunes the receiver* to the action

using its patented Reaction Tune capability. No manual tuning necessary.

*Compatible Receivers:

ICOM
7000, 7100, 8500, 9000, R10
AOR
8000, 8000B, 8200
Optoelectronics
Optocom, R11
Radio Shack
Pro2005/6 with OS456/Lite
Pro 2035/42 with OS535

No modifications necessary. Interface cables required.

Specifications Scout Mini Scout

10MHz - 1.4GHz
Reaction Tune
LCD Display
<3mV Sensitivity
Signal Strength Bargraph
Filter Mode
Capture Mode
Backlight
Beeper
Vibrator
400 Memories
255 Hits Counter

•
•
•
•
•
•
•
•
•
•
•



Are FM Broadcast signals a Problem?

Knock them out with the N100 Notch Filter. Blocks 88 - 108MHz, Connect between antenna and Scout or Mini Scout.....\$99



Patent No. 5,471,402

**Mini Scout
Reaction Tuner**
\$249



Patent No. 5,471,402

AR8200 Not Included

**Scout Frequency Recorder
Reaction Tuner**

\$349



SPECIAL
DB32 & CC30 \$29

Place your
Order anytime
at the
Optoelectronics
Cyber Store
www.
optoelectronics.
com

OPTODIRECT • 800-327-5912
OPTOELECTRONICS®

5821 NE 14th Avenue • Ft. Lauderdale, FL 33334
Phone: (954)-771-2050 Fax: (954)-771-2052 E Mail: sales@optoelectronics.com
Prices and Specifications are subject to change without notice or obligation.
DB32 Antenna shown on Scout and Mini Scout sold separately. AOR, ICOM, Radio Shack are all registered trademarks

Articles ...

SOME PRACTICAL LIGHT METERS — PART 2

Determine and construct the specific "lighting" system which suits your particular needs, and learn the details that apply to that system.

Evert Fruitman ... Page 6

SAFE AND SANE SMD REPAIR

Learn how to successfully remove and replace SMD chips.

TJ Byers ... Page 9

BUILD THE POT BOX

Useful to experimenters and circuit designers, this inexpensive decade potentiometer box allows you to conveniently determine the best value of resistance to use in a circuit.

Fred Blechman ... Page 19

THE "OPTO" IN OPTOELECTRONICS — PART 2

Learn the basic nature and behavior of optical prisms and lenses in this installment of a four-part series.

Ray Marston ... Page 31

BUILD A SEPIC REGULATOR FOR YOUR BATTERY-POWERED DIGITAL PROJECT

Portable power for your portable electronics is not a trivial consideration.

Fernando Garcia ... Page 66

MARINE ELECTRONICS FOR THE LAND RV MARKET

Electronics that go into boats and vehicles share a lot of common applications. Find out the advantages of technology exchanges between these two markets.

Gordon West ... Page 87

Columns ...

AMATEUR ROBOTICS NOTEBOOK

A GrowBot review, Breadbot code on-line, and SIMMStick Design Contest99 details.

Robert Nansel ... Page 89

ELECTRONICS Q & A

TJ Byers ... Page 74

OPEN CHANNEL

Some design rules for building circuits.

Joe Carr ... Page 14

RESOURCE BIN

Exploring used test equipment options.

Don Lancaster ... Page 83

STAMP APPLICATIONS

One step beyond the application note.

Lon Glazner ... Page 25

THE COMPUTER-CONTROLLED WORLD

Due to unforeseen circumstances, The Computer-Controlled World will be postponed for one more issue. We apologize for any inconvenience this may have caused.

Departments

Advertiser's Index ... 78
Classified Ad Info ... 78
Dealer Directory ... 30
Events Calendar ... 56
New Product News ... 93
News Bytes ... 35
NV AdMart ... 80-81
NV Bookstore ... 10
Prize Drawing ... 85
Reader Feedback ... 18
Tech Forum ... 37

Classified Ad Index

10. Ham Gear for Sale ... 39	90. Satellite Equipment ... 45	145. Robotics ... 49
20. Ham Gear Wanted ... 0	95. Military Surplus Electronics ... 0	150. Plans/Kits/Schematics ... 50
30. CB/Scanners ... 39	100. Audio/Video/Laser ... 46	155. Manuals/Schematics ... 51
40. Music & Accessories ... 40	110. Cable TV ... 46	Wanted ... 51
50. Computer Hardware ... 40	115. Telephone/Fax ... 48	160. Misc. Electronics For Sale ... 51
60. Computer Software ... 41	120. Components ... 48	170. Misc. Electronics Wanted ... 52
70. Computer Equip. Wanted ... 42	125. Microcontrollers ... 48	175. BBS & Online Services ... 0
80. Test Equipment ... 42	130. Antique Electronics ... 48	180. Education ... 0
85. Security ... 45	135. Aviation Electronics ... 49	190. Business Opportunities ... 52
	140. Publications ... 49	200. Repairs/Services ... 53

Published Monthly By
T & L Publications, Inc.
430 Princeland Court
Corona, CA 91719
(909) 371-8497
FAX (909) 371-3052

E-Mail
editor@nutsvolts.com
URL
<http://www.nutsvolts.com>

Subscription
Order ONLY Line
1-800-783-4624

PUBLISHER
Jack Lemieux N6ZTD

EDITOR
Larry Lemieux KD6UWV

MANAGING EDITOR
Robin Lemieux KD6UWS

ON-THE-ROAD EXHIBIT

COORDINATOR
Audrey Lemieux N6VXW

SUBSCRIPTIONS
Abby Madain

CLASSIFIED ADS
Natalie Sigafus

Copyright 1999

by
T & L Publications, Inc.
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princeland Court, Corona, 91719.

Nuts & Volts Magazine is published monthly for \$19.00 per year by T&L Publications, Inc., 430 Princeland Court, Corona, CA. **POSTMASTER:** Send address changes to Nuts & Volts Magazine, 430 Princeland Court, Corona, CA 91719.

Some Practical Light Meters — Part 2

by Evert Fruitman W7RXV

An old saying in photography goes no light, no picture.

Putting It Together

Last month, we went over several ideas regarding light meters in some detail. Now, as we start to construct the systems, we will go into

already soldered wires. Connect the wires to an ohmmeter, or connect a resistor from 1,000 ohms to 4,700 ohms, a battery, and a 0-1 milliamp meter in series. One side of the resistor

tion changes. Hooking the transistor up backwards in this circuit will not harm it.

You may use a CdS, light-dependent resistor for the photo cell instead of the photo transistor as I did in the final version of my

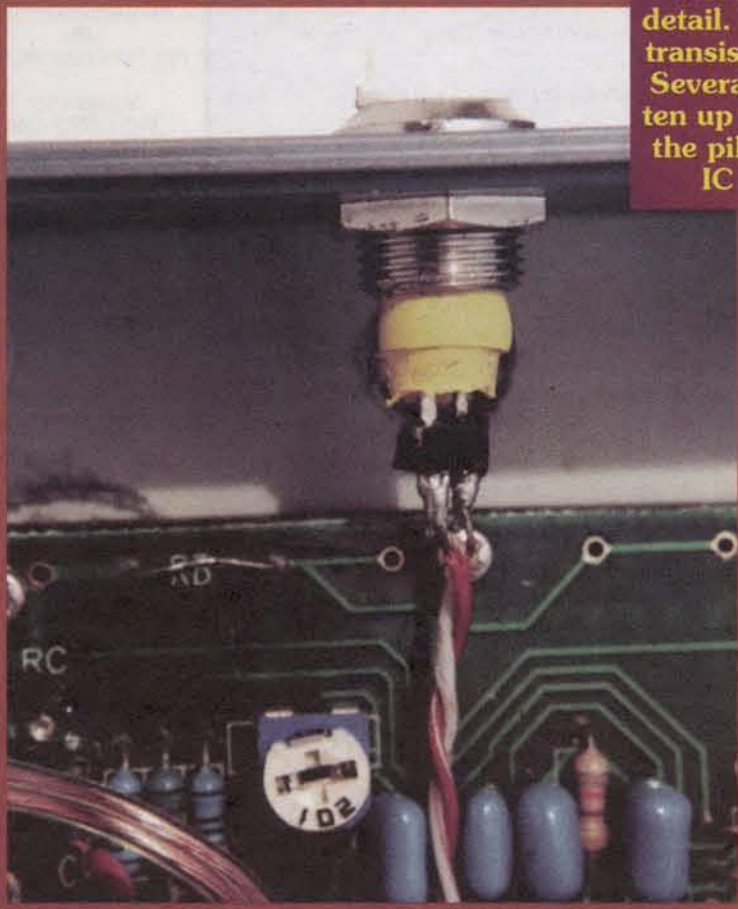


PHOTO A. Photo transistor mounting detail. In this case, digital display. Photo transistor will work with analog version. Several layers of heat shrink tubing fatten up the transistor enough to hold it in the pilot light holder. Two pins from an IC socket make the connections.

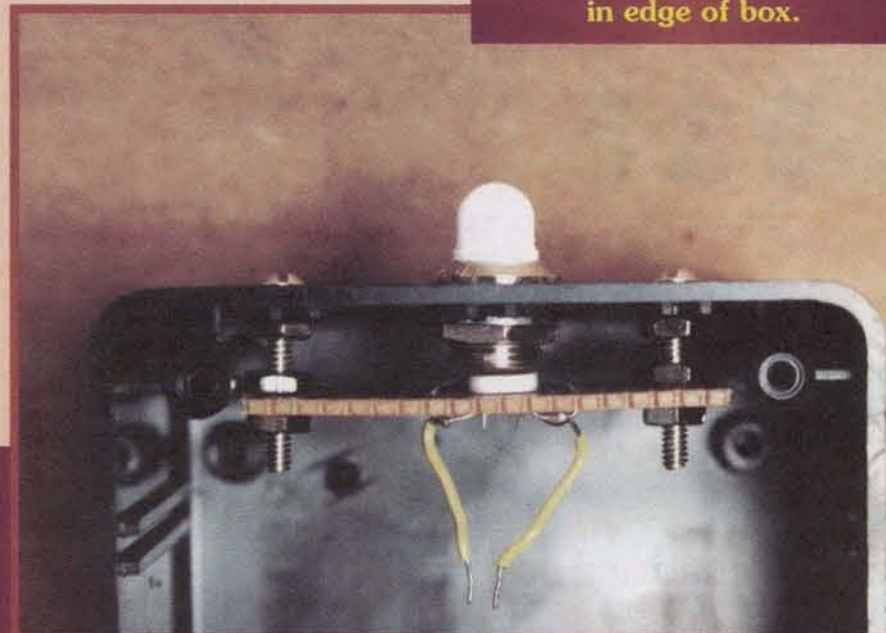


PHOTO B. Detail of CdS photo cell mounting. CdS cell mounted on perfboard. Board secured to box with small machine screws. Pilot light holder, used as diffuser, mounted in hole in edge of box.

specific details that apply to a particular system. We will start with the simpler, ambient light meter of Figure 1.

Simple Analog Meter for Ambient Light

This is about the simplest stand-alone unit you could make. It consists of three resistors, a photo cell, a regulator, a meter, a couple of switches, the battery, and the box. You could put the parts on a piece of perf board. The capacitors connect to the regulator just as shown in the diagram. Put an ON/OFF switch between the battery plus (+) and the input to the regulator.

You will have to determine which side of the photo transistor goes to plus and which side goes to the meter. Usually they mark the leads. You can verify that with an ohmmeter; either analog or digital. A DMM will show a marked change in resistance as you move the photo transistor into brighter light. The meter on an analog ohmmeter will tend to 'follow' the light changes if you have the leads correctly connected. Use an intermediate range, RX100 to RX1000 on an analog meter. Select something around 2,000 to 20,000 on a digital meter.

If you use the plug-socket arrangement shown in Photo A, you can determine the correct connections in a more convenient way. Plug the transistor into the socket, to which you have

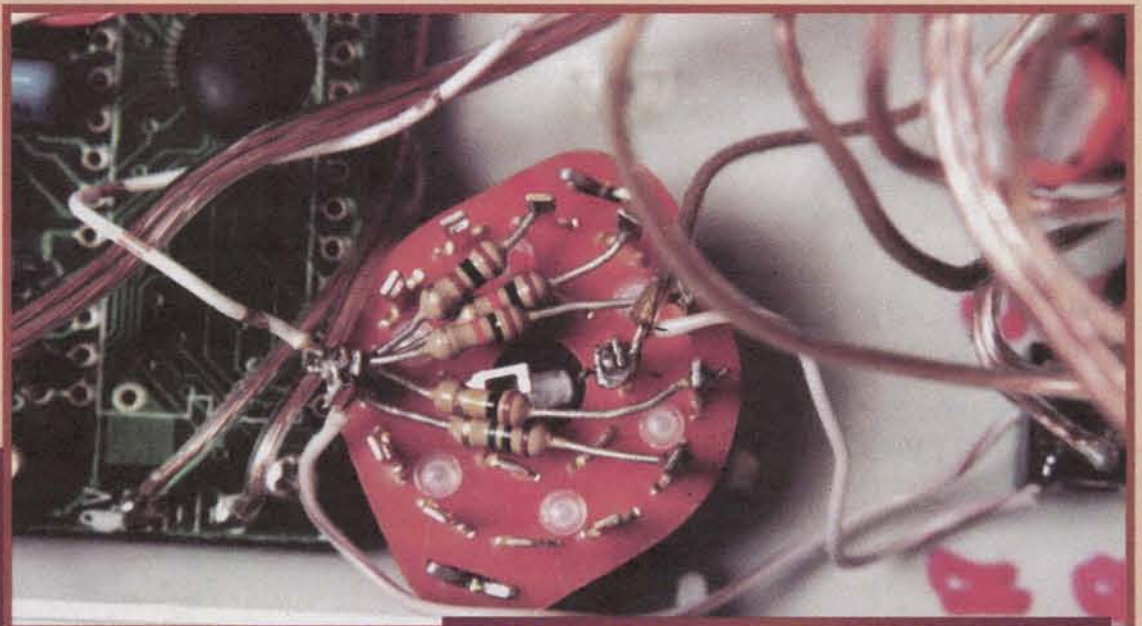


PHOTO C. Range switch detail, prototype version. Range resistors mount directly on switch to reduce the number of wires going to the board.

goes to one side of the transistor, the other side of the transistor goes to the battery, etc.

If the meter does not seem to follow the light changes, reverse the connections to the transistor and try it again. When you have the correct connections, it will definitely follow the light level changes. The socket allows convenient connec-

analog meter. The CdS cell does not care which lead connects to the battery plus. A socket still makes a handy way to connect to the photo cell. Photo B shows the mounting details for the CdS cell.

The socket consists of two pins cut off of a machine-pin IC socket. The red wire in Photo A indicates the collector lead. While that photo shows the photo transistor in the digital version, the photo transistor will work with either system. We will get to calibration later.

Simple Digital Meter for Ambient Light

Figure 2 gives the circuit of the light meter which is a step up in complexity. It uses a few more parts, but as explained earlier, it gives us a more sensitive instrument. Instead of a two-position range switch, it uses a six-position switch, although you could limit it to just two ranges and use the smaller, simpler switch.




The digital panel meter, possibly cheaper than its analog counterpart, needs a separate battery for its power. It also needs the voltage divider on the input to limit the voltage. The meter battery gives long life and, up to the point where the readout becomes too dim to read, the battery voltage does not seem to affect accuracy.

PHOTO D. Prototype version of analog board. Regulator and voltage adjust control, center left. Voltmeter balance control, lower left. FETs lower right. Diode, center right.

The voltage divider helps match the expected range of input voltages to the allowable range of input voltages. Most of these meters will have a basic sensitivity of 200 mV. They will read 199 or 199.9 mV. At 200 mV input or more, they show a 1 followed by a blank scale. Within reasonable limits, you may exceed the nominal 200 mV input without damaging the meter. I picked values that would keep the input voltage within that limit on some setting of the range switch, and with the light levels that it should see.

In the prototype version, for

PHOTO E. Analog board. Adjustable regulator, lower right, allows almost full use of 12 volts' worth of penlight batteries. Voltage adjust control, upper right, just in back of regulator. Balance pot upper left. FET voltmeter, lower left, right next to transistor used as diode.

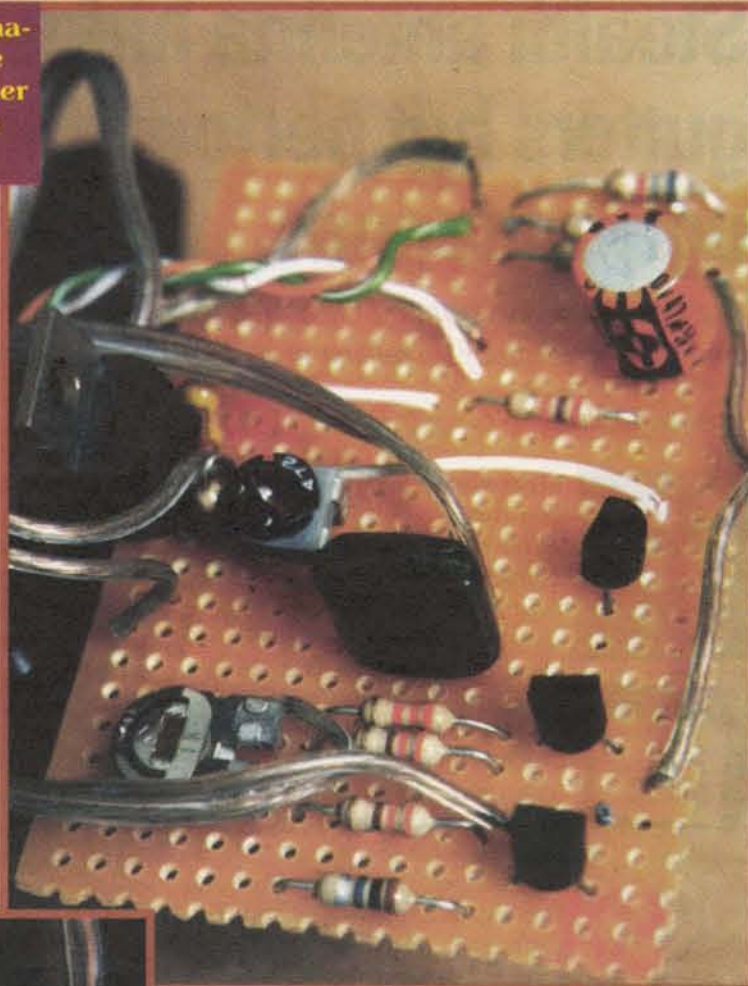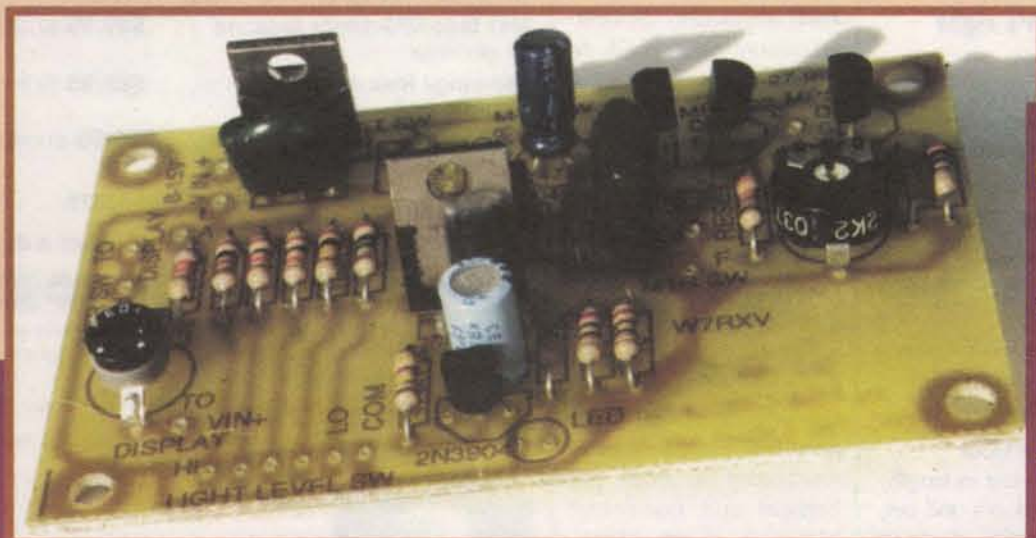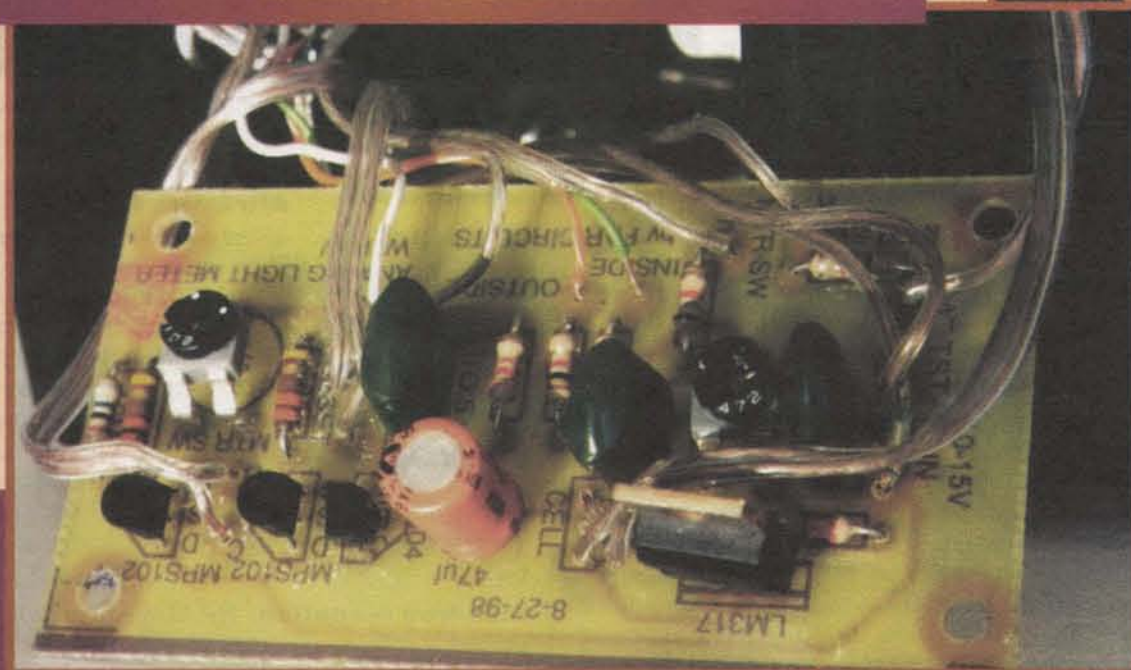

ease of mounting and to minimize the number of wires running around the box, I put the range resistors directly on the switch as shown in Photo C. From top to bottom, you have the resistors for the Highest light level to the Lowest. Note that we use only five resistors for six ranges. The two most sensitive ranges show only about a 10% difference in sensitivity. However, the last range costs nothing extra, so we may as well use it.

If you put the range resistors on the back of the RANGE switch, you will still need a piece of perf board for the 82 K resistor and the 10 K sensitivity control. When you get those wired, turn the sensitivity control to about the middle of its range. You will make the final adjustment later.

Wiring the Digital Panel Meter

The other parts in Figure 2 could go on a piece of perf board. Put an ON/OFF switch between the battery plus and the input to the regulator. Remember, the digital version needs a separate battery for the digital panel meter.

That means that the ON/OFF switch will have to have two poles: four contacts. With its greater sensitivity, the digital version uses a five-volt regulator and just a nine-volt battery. The adjustable regulator needs more parts around it in order to set the desired voltage. The five-volt regulator needs no adjustment; 7-30 volts in, 5 volts out, simpler wiring.

Packaging It

Select a box large enough to hold the DPM and, most likely, it

PHOTO F. Digital board. Ready to go into box. Five-volt regulator, upper left. Meter range-trim control, lower left. Auto-reset transistor, center. FET voltmeter, upper right. Voltmeter, balance control, center right.

Continued on Page 58

Stealth antenna hides under gutters but performs like big ugly antennas

The new Max Antenna by GE is the low-profile, high-gain way to get flawless reception of broadcast signals without expensive installation.

by Hope Chapman



The Max Antenna by GE is the ultimate TV antenna system.

Electronic engineers agree—you're television is only as good as the signal it receives. Unfortunately, antenna design has not kept pace with improvements in television quality and the features available. Both cable and satellite television systems have spent a great deal to improve the quality of their transmission, but they can be extremely expensive, they aren't available in all areas and may not provide access to local TV stations. The advent of digital broadcast television is about to change the face of television, and in the near future, broadcasters will begin transmission of these high definition signals. This will

mean that you won't need to pay outrageous cable bills or subscribe to satellite programming to get the perfect picture.

So people have headed back up to the attic and pulled their old rabbit ears out of storage. What they'll find is that although rabbit ears will provide reception of over-the-air signals, they are just as ugly and just as difficult to adjust as ever. Luckily, there is a new antenna from GE that will provide breakthrough performance without making your family room look like something out of the fifties.

Fuzzy outlook. If you subscribe to cable, you receive a quality picture on most channels, as long as storms or other factors don't disrupt your service. Unfortunately, the interference caused by the signal bouncing off buildings and other large objects, known as multipathing, often results in "ghosting" or "snow." If you'd rather

not pay a hefty monthly sum for the privilege of receiving a signal, your options have been limited, and your picture was likely to be distorted. You could always mount a huge antenna on your roof, but that's not even allowed in some neighborhoods. Then there's the problem of aiming the antenna at the broadcast source.

Clear alternative. The Max Antenna series from GE uses a revolutionary electromagnetic design to maximize installation flexibility and yield longer range reception of off-air VHF and UHF signals. Unlike a conventional dipole antenna, the Max Antenna can receive signals in both vertical and horizontal planes with minimum cross-polarization loss. This design allows for the first low-profile antenna solution that provides numerous installation options.

Superior components. The key to the superiority of this antenna is its ingenious use of the latest electromagnetic technology—providing high gain and full channel coverage as well as the greatest amount of mounting flexibility. First, the antennas were designed

around a wide band element to achieve the greatest amount of gain in a relatively small space. Next, an amplifier and matching network was designed to enhance the reception of weak signals. This amplifier also adds very little distortion to the strong signals, giving it a balanced amount of gain. A filter on the amplifier board will allow for good matching

between the antenna and amplifier. Special attention was paid to design an antenna-amplifier combination that would be completely compatible with the new digital transmission format. It has been designed for strong signal distortion rejection and a low amount of noise. The scientists who designed it followed certain optical principles to give the antennas good sensitivity in both the vertical and horizontal plane. It is omnidirectional and requires no adjustments, orienting



The best antenna you'll never see.

Would you rather have the "old-fashioned" unsightly antenna tower or get even better reception with one that you can mount horizontally or vertically.

or fine tuning during use. You simply install it, set it and forget it.

Attractive design. This antenna has been designed with your living space in mind. It features a durable textured surface that mounts easily and can be painted to match any decor. You can mount it vertically on your chimney or horizontally under the eaves of your

rooftop. If it weren't for the improved picture on your television, you would never know it was there.

Risk-free reception. The Max Antenna is the perfect way to get a perfect picture. It comes with Comtrad's exclusive risk-free home trial. If you are not completely satisfied, return it within 90 days for a full "No Questions Asked" refund.

Max Indoor/Outdoor Antenna . . . \$49.95 \$7.95 S&H
20-mile range

Mid-range Max Antenna . . . \$69.95 \$9.95 S&H
40-mile range

Super Max Antenna . . . \$99.95 \$11.95 S&H
60-mile range

Please mention promotional code 5731-15579.


For fastest service, call toll-free 24 hours a day

800-992-2966     

To order by mail, send check or money order for the total amount including S&H. To charge it to your credit card, enclose your account number and expiration date.

Virginia residents only—please include 4.5% sales tax.

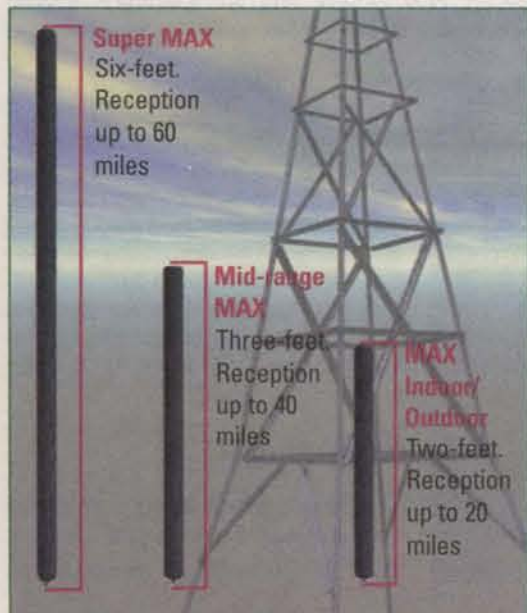comtrad industries
2820 Waterford Lake Dr., Suite 102
Midlothian, Virginia 23112



The range that's right for you...

With the right antenna, UHF/VHF reception is better than the cable broadcast of local network stations:

- The Super MAX Antenna is six-feet long and provides the maximum reception for up to 60 miles.
- The Mid-range MAX Antenna is three-feet and provides reception up to 40 miles.
- MAX Indoor/Outdoor Antenna is two-feet in length, can be used indoors and out, and has a reception range up to 20 miles.

Safe and Sane SMD Repair

How To Successfully Remove And Replace SMD Chips

For more years than I care to admit, I've troubleshooted and repaired all sorts of electronic devices, everything from appliances to car stereos to TVs to satellite equipment. Over the years, I've seen many changes — most of which require stronger eyeglasses as the size of the parts shrink. (Don't know about you, but spotting an eagle at 300 yards is easier than spotting a bad 10 mil solder joint.) This progress has also changed the way defective parts are replaced. The latest challenge is SMD — surface mount devices.

Unlike traditional DIP (dual in-line plastic) components — which are a

all sorts of materials. Let's take lead, one of the earliest discoveries, for instance. As a kid, I remember the stench of burning calking rope as my father ladled molten lead (like gravy at Thanksgiving) into the joints of a soon-to-be sewer pipe. It quickly solidified and made a water-tight seal (well, after a bit of pounding). My dad also used lead, in the form of solder, to weld copper water pipes and other plumbing fixtures.

In fact, the word plumber comes from the Latin word *plumbum*, which means lead (Pb in chemistry). Back in Roman times, lead — a very malleable, non-corrosive metal — pounded into the shape of pipes was used for both fresh water delivery and

There are many kinds of solder, all of which use tin as a base. To this is added various amounts of lead, silver, or other elements to characterize the melting point and strength of the bond. Table 1 shows the most popular blends.


Generally, the higher the melting temperature, the stronger the bond. Unfortunately, semiconductors are very sensitive to sustained high temperatures. As the temperature rises, so does the risk of failure.

Making An SMD Board

When an SMD board is manufactured, the surface mount chip is "glued" in place on the board using a

is placed in an oven, and the temperature raised until the solder melts. The temperature is then reduced and the board removed. Timing here is critical because you need enough heat to melt the solder, but not so much that'll damage the IC. Here's a brief overview of how each works (Figure 1).

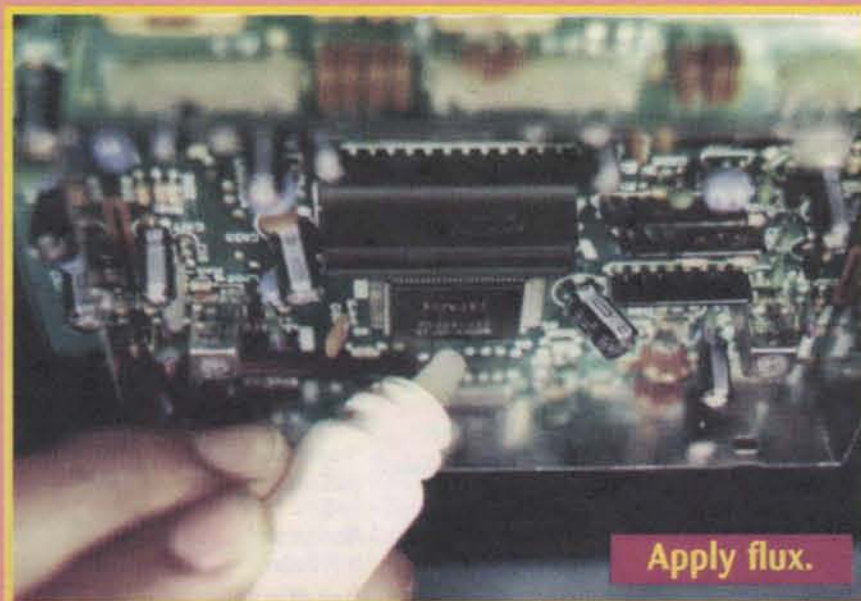Vapor-phase reflow soldering is currently the most popular and consistent method. It uses a liquid fluorinated compound for the heat-transfer medium. The board is inserted into a sealed chamber and the liquid is heated to its boiling point, at which point it turns into "steam." The temperature of the vapor is determined by the fluid type (Table 2). Dwell time in the



Apply flux.

challenge in themselves with plate-through solder pads — SMD parts have tiny, fragile leads that attach to tiny printed circuit board pads that are even more fragile than the leads themselves. Too much heat, and ... poof, the pad and its link to other pads/traces are history.


The mission, should you wish to accept it: How do you remove a defective SMD part from a multi-layer PC board and have the copper pads/traces survive? Simply lower the heat, the experts tell us.

It's All About Solder

Somewhere around the Bronze Age (3500BC), man learned how to extract and alloy metals to forge weapons, cast sculptures, and bond

waste disposal. Today, we know the deadly consequences of heavy-metal poisoning, and lead pipes have long given way to steel, copper, and plastics.

However, lead-based compounds are still used extensively in the electronics industry. For example, I use lead-solder every day to connect components to each other and tack them onto circuit boards. If you've ever tried it, though, you have discovered it takes a lot of patience and skill. The hardest part of getting a perfect solder joint is temperature control. Too little heat produces a solder joint that's grainy and brittle; too much heat, and you run the risk of destroying the parts you're trying to bond. How much heat you need depends on the type of solder.

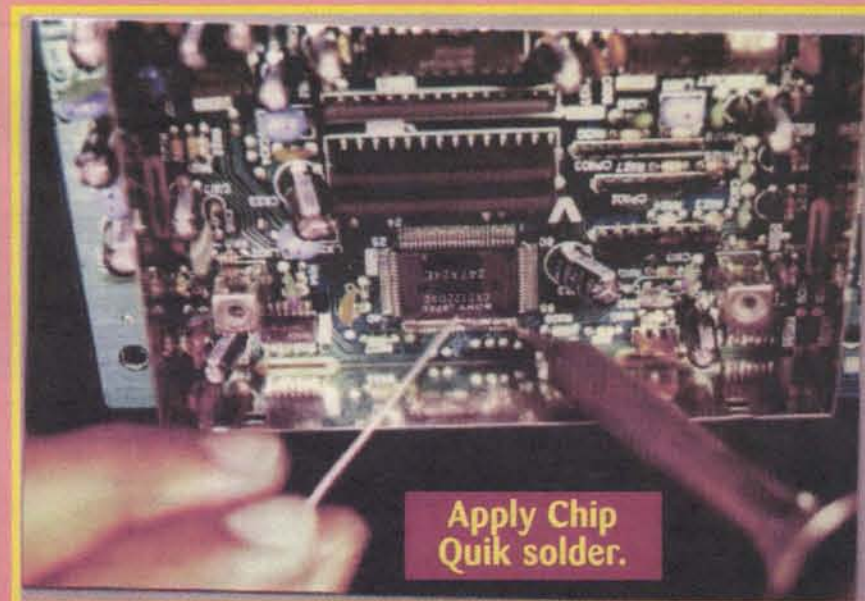

Apply Chip Quik solder.

solder paste. The board is then heated to the point where the solder melts and "reflows," that is, it becomes liquid and fills the voids between the lead and the circuit board pad. However, the reflow temperature is typically 419 °F (215 °C), well above the glass-transition temperature of epoxy (320 °F, 160 °C), where the material undergoes a transition from a solid to a plastic state. Fortunately, it takes longer for the epoxy case to melt than it does for the solder to reflow, so no damage is done if the heat isn't applied for too long — typically 15 seconds.

The two widely-used SMD soldering methods are infrared reflow and vapor-phase reflow. Both melt and reflow the solder through total board immersion. That is, the board


chamber is generally on the order of 15-30 seconds, depending on the mass and density of the board.

Infrared reflow uses air for the transfer medium, and is actually a mixture of infrared heating and convection oven technologies. The heating is generated by infrared lamps or panels, and the air circulated with a blower to prevent stratification. Because the medium is dry air rather than moist vapor, it takes longer to heat the board to reflow temperature. On the other hand, the method produces less thermal stress on the board.

Repairing SMD Boards

When replacing a defective SMD component, the hobbyist doesn't

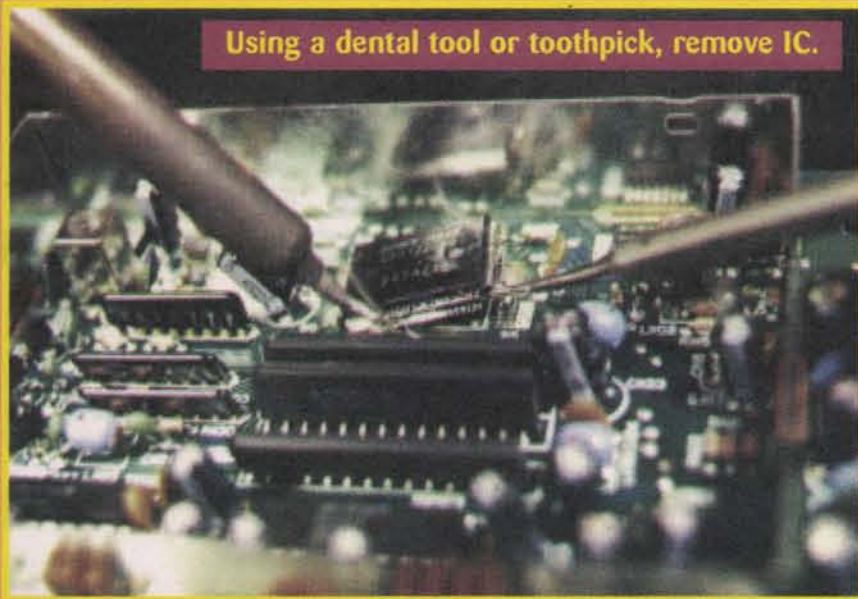Using a dental tool or toothpick, remove IC.



have the precise temperature control used to initially place the part. Obviously, the worry isn't the dead IC, but the traces on the PC board. If you apply too much heat, the adhesive that bonds the copper trace to the board will "melt" and let go. What you're left with is a dangling pad, or worse, no pad at all (you'll likely find it stuck to the tip of the soldering iron).


Until recently, the only SMD removal process economical enough for the hobbyist was done using flux-saturated braid, like the No-clean SMD Repair Kit from Kester, which is available from Jameco (1-800-831-4242; <http://www.jameco.com>), Mouser Electronics (1-800-346-6873;

<http://www.mouser.com>), and other supply houses.

The idea is to remove as much solder as possible, at least enough to weaken the solder bond, using the braid as a solder wick. Then a light touch of the soldering iron tip would, hopefully, pop the lead loose. This is no easy chore when a chip has the footprint of a centipede. Moreover, wedging the braid and hot iron tip into the limited space between SMD parts without breaking something is a formidable task.

The alternative is to clip out the IC with a pair of diagonal cutters, leaving the leads sprouting from the PC board like grass. One by one, the leads are removed using a soldering

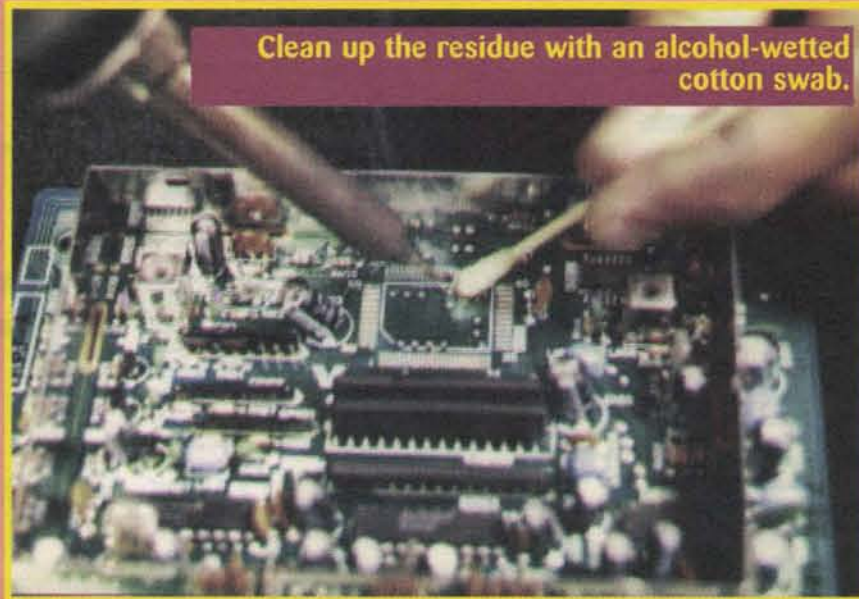Clean up the residue with an alcohol-wetted cotton swab.



iron and tweezers. In fact, it's the only way I've been able to successfully remove LSI (large scale integration) ICs using the Kester Repair Kit. Unfortunately, this method often damages delicate solder pads before heat is applied.

Removing SMDs The Safe Way

The new, smart way to remove SMDs is with a special solder made by **Chip Quik** (1-800-836-2447; <http://www.chipquikinc.com>). The solder is an alloy of tin, lead, indium, and bismuth. Bismuth is a heavy metal that's one step above lead on the periodic table, and is the most

diamagnetic of all metals with a thermal conductivity lower than any other metal, except mercury.

When tin and bismuth are "amalgamated," it reduces the melting point of the solder to a very low 136 °F, as opposed to the 361 °F melting point of 60/40 solder. When you melt the new solder with the old — the resultant alloy has a melting point of about 150 °F (well below the boiling point of water). At temperatures this low, it's nearly impossible to damage the solder pads.

The procedure is easy and painless. It involves four easy steps, which are outlined in Photos A through D. The process starts by applying a drop

Nuts & Volts Bookstore!!

As a paid subscriber to *Nuts & Volts*, you'll receive a **10% discount** off the listed price shown here!!

Build your electronics library at a price you can afford!! **Order now!!**



\$34.95

"Programming and Customizing BASIC Stamp Computers" by S. Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.



\$44.95

"Handbook of Radio and Wireless Technology" by S. Gibilisco

A comprehensive compendium on the entire field of radio and wireless technology.



\$34.95

"Electronic Troubleshooting" by D. Tormal and N. Widmer

Troubleshoot and repair any type of electronics with this comprehensive guide.



\$39.95

"Programming and Customizing the 8051 Microcontroller" by M. Predko

This tutorial/disk package details the features of the 8051 and demonstrates how to use these embedded chips to access and control many different devices.



\$39.95

"Encyclopedia of Electronic Circuits" by R. Graff

An extensive library of 1,000 circuits from the bestselling, six-volume "Encyclopedia of Electronic Circuits."



\$54.95

"Handbook of Microcontrollers" by M. Predko

This much-needed reference is the first to cover all the most common types of eight-bit microcontrollers.



\$39.95

"Circuit Troubleshooting Handbook" by J. Lenk

This handbook gives full descriptions of the operation of important circuits, and how each circuit's characteristics may figure in its failure or poor performance.



\$24.95

"How Electronic Things Work ... and What to Do When They Don't" by R. Goodman

Never again be flummoxed, flustered, or taken for a ride by a piece of electronic equipment with this fully illustrated, simple-to-use guide.

BOOKS PUBLISHED BY MCGRAW HILL

Call 1-800-783-4624 today!

WE ACCEPT VISA AND MASTERCARD

Send check or money order to Nuts & Volts, 430 Princeland Court, Corona, CA 91719. Include a complete shipping address (no P.O. Boxes, please). Shipping & handling \$4.50. CA residents add 7.75% sales tax. Or, call our toll-free order-only line at 1-800-783-4624 and use your MasterCard or Visa. **ALL ORDERS MUST BE PREPAID.**

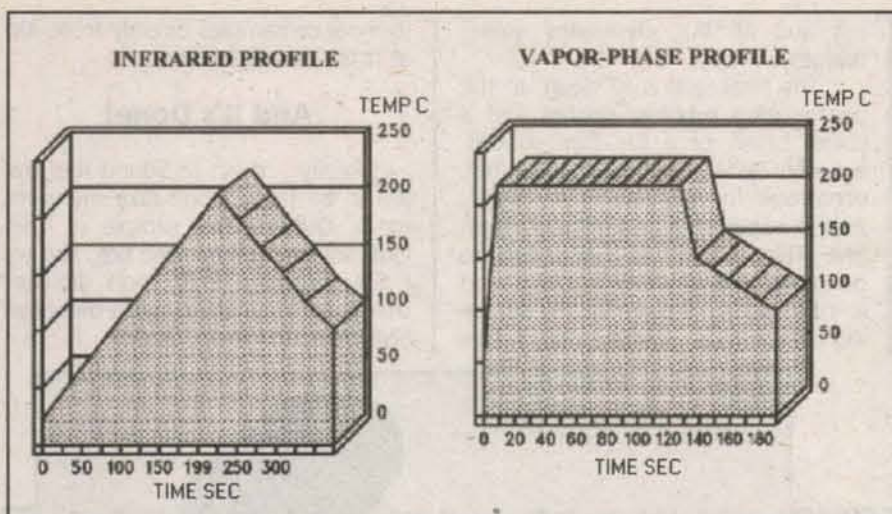


FIGURE 1 — Temperature control is important. The two leading and safest SMD reflow soldering methods are infrared and vapor-phase.

of flux from the included syringe to each lead of the part to be removed (Photo A).

Next, melt a dab of Chip Quik solder on each to the leads using a small (30W) soldering iron — just pretend like you're soldering the chip in place rather than removing it. Be liberal with the Chip Quik solder (Photo B), and don't worry about solder bridges (slipovers).

Once the leads are treated, apply heat to the leads until the new solder is molten, and lift the SMD off the board using a dental tool (Photo C) or vacuum pick.

After the part is removed, you'll notice an unsightly mess left behind. This is solder "ash," a result of the interaction between the ChipQuik solder and the old solder, which has to be removed to expose the pad underneath. Clean-up is done with a

Sources Mentioned

3M
http://www.3m.com

Chip Quik
25 Nicholas Rd.
Framingham, MA 01701
1-800-836-2447
http://www.chipquikinc.com

Digi-Key Corp.
701 Brooks Ave. South
Thief Falls, MN 56701
1-800-344-4539
http://www.digikey.com

Howard Electronic Instruments
6222 N. Oliver
Kechi, KS 67067
1-800-394-1984
http://www.heinc.com

Jameco
1355 Shoreway Rd.
Belmont, CA 94002
1-800-831-4242
http://www.jameco.com

Mouser Electronics, Inc.
2401 Hwy. 287 North
Mansfield, TX 76063
1-800-346-6873
http://www.mouser.com

cotton swab dipped in flux (Photo D), followed by an alcohol wipe. The Chip Quik SMD-1 SMD Removal Kit contains enough solder to remove 8-10 44-pin SOIC packages.

SMD Replacement

What's left is a clean footprint, ready to accept the new SMD. The

new part can be soldered in place using any number of techniques. My favorite is wetted solder paste, like the R244 formula from Kester (available from Digi-Key, 1-800-344-4539; http://www.digikey.com). This paste is a blend of 90 percent solder and 10 percent gooey flux that is applied in a bead along the newly-cleaned pads using a syringe.

With a pair of tweezers and magnifier, carefully align the new SMD in place so that it lands squarely on the pads. Let it set for a few hours to harden the paste. Use a low-wattage iron — about 15 watts — with the smallest chisel-tip you can buy (RadioShack 64-2055, or equivalent) to solder the

TABLE 1 — PHYSICAL PROPERTIES OF ELECTRICAL SOLDER

RadioShack	% Tin (Sn)	% Lead (Pb)	% Silver (Ag)	Melting Point (°F)	Bond Strength
—	98	—	—	450	Very high
—	—	98	—	608	Low
64-001	60	40	—	361	Medium
64-015	63	37	—	361	Medium
64-013	62	36	2	354	High
64-025	95	—	4	421	Very high
64-027	97	—	3% Cu	410	Medium
Chip Quik	48	28	21% In, 3% Bi	136	Very low

Davilyn
CORP.

13406 Saticoy Street
North Hollywood, CA 91605
800-235-6222
818-787-3334 • F-818-787-4732
HTTP://WWW.DAVILYN.COM/Electronics
CALL FOR FREE CATALOG



THE BEST PRICE EVER
ON THIS INDUSTRY FAVORITE
\$1.095 + SHIPPING

HP 8640B SIGNAL GENERATOR OPT 003



CONDITION CODE "A"

Frequency: 500KHz to 512MHz. Indicates to 1024MHz. Requires external frequency doubler for 1024MHz (supplied with unit). Readout can be used as a frequency counter. Accuracy: 6.5 digits expandable to X10 and X100. Output: -145dBm to +19dBm (0.5 to 512MHz). Modulation: AM, FM, pulse, 400 and 1KHz, 1mV to 1V internal. Has input and output of modulation sources. PRICE: \$1,095

EXCEPTIONAL
CONDITION

LIMITED SUPPLY
DUE TO OVER-
WHELMING
DEMAND

HP 200CD Oscillator\$95
HP 312B Selective Voltmeter ..\$695
HP 331 Distortion Analyzer ...\$249
HP 400E Voltmeter\$325
HP 412A Voltmeter\$95
HP 415E Voltmeter\$125
HP 3435A Multimeter\$295
HP 8160A Generator\$2,800
Krohn-Hite Model 4300A
Oscillator\$395
PRD Type 2020 Vector Voltmeter
w/sampling heads\$250
Syston Donner Spectrum Analyzer
Consists of tuning unit Model
809-1, display unit Model
712-1\$1,995
Watkins Johnson WJ-8628-4
Receiver\$8,500

AN/URM-120 50 OHM THRU-LINE RF WATTMETER

Frequency range: 2MHz to 1000MHz. Power range: 10 watts to 1000 watts. USWR≤1.08 to 1. Uses three plug-in coupler elements (included). CU-753 2 to 30MHz 50 to 100 watts CU-754 25 to 250MHz 10 to 500 watts CU-755 200 to 1000MHz 10 to 500 watts. Connector: Type N. Case included. Size: 7"Wx6-5/8"Hx7-1/5"D. Weight: 6.5 lbs. Price: \$395

TEKTRONIX 2336YA DUAL TRACE 100MHz PORTABLE OSCILLOSCOPE



Price: \$795

Vertical: DC to 100MHz band with 5 mV per div. to 5V per div. maximum sensitivity of 2mV/div. Horizontal: Time Base A: 0.05 uS/div. 0.5 sec/div. X10 to 5 ns/div. Time Base B: 0.05 uS/div. to 50 mS/div. X10 to 5 ns/div. Has digital readout of delta time, delayed sweep, and XY input div.

LAMBDA LK344A-FM POWER SUPPLY

Front panel voltage and current meters. Convection-cooled, no blower. Voltage adjustable from 0 to 60 VDC at a maximum current of 4A. Regulation 0.015% or 1mV. Line or load. Series/parallel operation. Remotely programmable by voltage or resistance. Less than 500µV RMS ripple. Constant current/constant current. NEW Price: \$395



HP 180A SCOPE (MIL SPEC AN/USM-281A)



Includes vertical plug-in 1801A (PL1186), horizontal plug-in 1821A (PL1187). Tested. Manual Reproduction: 15

GREAT PRICE \$195

TELEGRAPH KEYER

Unique item for military collectors. J37 telegraph key, new in original government package. \$49.95



JONES MODEL 1600-1 TACHOMETER

Instrument tachometer centrifugal mechanical tach measures RPM scale 0-500 RPM, coupling shaft 1/8" accessories, various size rubber tipped drive couplings, case new. Also Jones Model 1600-7 RPM scale 0-11,000 RPM w/accessories new. \$35/ea. or 2 for \$50

SEXTANT

Aircraft or marine navigation. No case. \$50



SINGER CSM-1 COMMUNICATIONS SERVICE MONITOR



horizontal, AM/FM. Outputs: audio, tone, RF functions: generate 2mV to 2mV. AGC: manual or auto. \$395

CT SYSTEMS 3000B SERVICE MONITOR



\$2,500

MORGAN DATA SYSTEMS MODEL 8609



Constant voltage or current power supply voltage range: 0 to 50 volts. Current range: 0 to 1.5A. Readout: 3 digit with 0.1 volt and 1mA current resolution. Regulation: linear; input voltage: 115V/220V. Adjustments: voltage and current has remote control adjustment capability. NEW. Price: \$95



**BOX
\$15**

FIBERGLASS, WATERPROOF
Exterior size 20-1/2 (L) x 14-1/4 (W) x 10-1/2 (H)

NICKEL CADMIUM BATTERY



G.E. Catalog No. 42B004KA01. Nominal volts 12 rated capacity 4.0Ah, wt. 5 lbs. NEW \$55



**TS-723A
SPECTRUM
ANALYZER**
Frequency range 20Hz to 20KHz. Noise measurement — full scale 300 microvolts, minimum -75dBm, frequency -10Hz to 20KHz. Power supply — 115V/230V, 50 to 100Hz, 90 watts.

\$95

TABLE 2
POPULAR VAPOR-PHASE SOLVENTS

Solvent	Boiling Temperature
FC-70	419 °F 215 °C
FC-71	487 °F 253 °C
FC-5312	419 °F 215 °C

chip in place. Begin by tacking down two or three of the corner leads. This prevents the chip from shifting while you heat the remaining leads.

A trick of the trade is to heat the bottom side of the circuit board to about 150 °F with a hair dryer or hot

air gun before soldering the chip. This reduces the amount of time it takes for the solder to reflow when touched by the soldering iron, thereby lowering the heat transferred to the IC and reducing the risk of damage.

Another trick is to drag the solder tip parallel to the body of the IC (perpendicular to the leads) at a rate just slow enough to melt the solder along the way.

Never touch the pads or the pins; let the ball of solder carry the load of the work for you. Combining these two techniques minimizes chip heat-

ing and all but eliminates solder bridges.

The final step is to clean up the board using rubbing alcohol and a solder brush or a CFC-free solvent, like HFE-71DA — a hydrofluoroether, azeotrope formulation with trans-1, 2-dichloroethylene and ethanol, from 3M. This mixture is well-suited to defluxing and degreasing tasks, and is intended to replace ozone-depleting compounds. You can obtain free

four-ounce samples directly from 3M at <http://www.3m.com>.

And It's Done!

Really — that's it. Sound too simple to be true? Don't take my word for it. Order a free sample of Chip Quik solder via their web site, and try it for yourself. You'll soon discover that there's still life in those defective SMD toys and tools. **NV**

Inexpensive SMD Repair Kit

Howard Electronic Instruments has put together a very inexpensive package for removing and replacing SMD components at a very low temperature. The package contains an EDSYN 951SX temperature-controlled soldering station outfitted with a Mini-Wave Soldasip tip, and contains a Chip Quik SMD-1 SMD Removal Kit.

The EDSYN 951SX soldering station has a wattage rating of 15W to 220W, very delicate to heavy-duty soldering, with an adjustable tip temperature of 400 °F to 800 °F, ±5 °F. The patented Mini-Wave Soldasip solder tip, also from EDSYN, is a cylindrical tip cut at a 45-degree angle on the end. The tip end is cupped, or convex, so that it will hold solder in the cup.

To install a SMD part, flux is applied to the leads of the IC and the Mini-Wave cup filled with regular wire solder. Holding the iron at a 45-degree angle, simply drag the solder tip parallel to the body of the IC (perpendicular to the leads).

As you move down the line, solder is applied to the leads, making a permanent bond between the IC's leads and the PC board's pads.

The price of the package is \$99.00, and comes with a 15-day free trial (30 days if you prepay). **Howard Electronic Instruments (1-800-394-1984; <http://www.heinc.com>)** is located at 6222 N. Oliver, Kechi, KS 67067.



BRIGAR ELECTRONICS

7-9 ALICE ST.
BINGHAMTON, NY 13904


OPEN 7:30 TO 4:30 PM
MONDAY THRU FRIDAY
SATURDAY 7:30 AM TO NOON

Send For Free Catalogue


PHONE: (607) 723-3111
FAX: (607) 723-5202
E-MAIL: BRIGAR2@aol.com
VISIT OUR WEB PAGE AT
<http://members.aol.com/brigar2/brigar.htm>



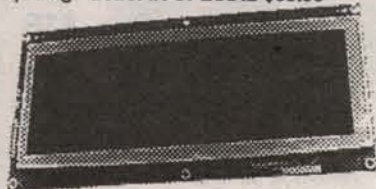LCD GRAPHIC DISPLAY
EPSON LCD DISPLAY #ECM-A0451
640 X 240 Blue Super-Twist (Passive/Mono)
Electro-Luminance Back-Light
Size Viewing screen: 9-1/2" x 2-3/4"
complete with six Hitachi HD61200, and
two Hitachi HD61203 drivers. The board
uses a 10 pin card edge conn. with .100"
spacing. **BRIGAR SPECIAL \$69.95**



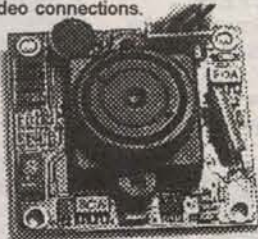WELDEX Video camera # WDPR-2000
1/3" CCD Board camera B&W Pinhole
lens. compact 30mm x 30 mm (Approx
1"sq.) High performance & picture quality of
a full featured camera on a compact board.
0.03 Lux min. illumination - RCA connectors
for power & Video connections.
430 lines
resolution.
8-12 Vdc
input.
**Brigar
Special
\$79.95**




ULTRASONIC LIGHT SWITCH MFG: LITRONIC
Replaces existing wall switch - Great for home alarm
systems or controlling lights & small appliances, ON-
OFF Switch-LED TRIP Indicator COLOR: WHITE
SIZE: 5"W x 5"H x 1-3/8"D
● VOLTAGE 120 OR 277VAC 50/60HZ
● MIN LOAD 80 WATT 120V
● MAX LOAD 1000W 120V
Sensor Low Power Ultrasonic 25KHZ
● ADJUSTMENT: Sensitivity &
Time out (0 TO 25 MINUTES)
● Documentation & schematic
included. **ENERGY SAVINGS**
30 TO 60%
ORIGINAL PRICE \$100.00
SPECIAL SALE PRICE
\$6.95



NMB 12 VOLT DC FAN 28 CFM
Model # 3110KL-04W-B17
3.16" SQ. x 1" TH (80mm x 26mm)
0.13 Amp - 7 blade - Phenolic Blade
& housing - DC Brushless - Ball
bearing -
12" wire leads -
UI & CSA -
Noise: 25 (dba) -
List Price ... \$9.95
BRIGAR PRICE
... **\$4.25**



ROTARY VANE AIR COMPRESSOR
GAST Model# 0522-P167-G451DX
Oil-less rotary vane air compressor directly
connected to motor. Compressor rated at
3.2 to 4 Cfm @ 10 psig max.
Motor rating:
3/4 H.P. 60 Hz 115 Vac 1 PH 1725 RPM
Code H - 7.40 A - SF 1.00 - FR 56 Cz Amb 50 c
Time Rating: Cont. Insul Class B - Thermally Prot.
Motor Size: 14"L X 6-1/2"Dia. Weight: 40 Lbs.
Shaft Size: 2-1/8"L x 5/8"Dia. (Fluted)
BRAND NEW FACTORY BOXED \$119.95

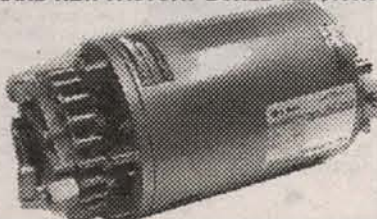

GENERAL ELECTRIC
DC POWER SUPPLY
PART # 9T63Y2396
INPUT: 115V 60 Hz 80VA
OUTPUT #1 3.7 KV, 376 µA
OUTPUT#2 6.0 TO 7.0 KV .05 mA DC
Size: 10"L x 6"W x 3-3/4"H Weight 14 Lbs.



MULTIMETER

MFG: PHASTRON Analog meter
movement 50 Micro Amp D.C. full
scale. Large 4.5" diam - 3.5" viewing
area. Zero adjustment knob. White
face. Scales: In Green, Black, and
Blue letters. Three AC & three DC
Volt Scales. 0 - 2.5, 5 and 10. One
resistance scale from 0 to infinity.
Includes mounting hardware.
REDUCED PRICE \$4.95



ANALOG PANEL METER
PART # 40-013857

120 VOLT AC 10 AMP TOROID
ISOLATION TRANSFORMER
Mfg: BANNER MAGNETICS # 169257
INPUT: 120VAC (Blk, Gry)
Output: 70v 12 amp (Red, Red)
120vac 10amp (Violet, White)
12 V 1amp (Brown, Brown)
Size: 3-1/2"H x 5"Dia.
Weight: 12 lbs. **PRICE... \$59.95**



AC TO DC WALL TRANSFORMER
MFG: AUDIOVOX PART# CNR405
INPUT: 120VAC 60Hz 11W
Output: 12 VDC 300mA
Polarity: Center pos.
comes complete
with 6' zip cord
2.5 mm Female
receptacle.
UL & CSA APPR.
SALE PRICE ...
\$1.50



INTEL # P8052AH
40 PIN CPU 8 BIT 256
BYTES RAM, Timer/counter
and I/O
PRICE... \$1.75
10 PCS. @ \$1.00 EA.



REAL BEAUTIES They Could be Yours Netcom since 1983

WEB Surfer

Compaq LTE LITE 486 DX433

8.5" Active Matrix Display (Sharper & Brighter) *Wow!*
 12M Ram / Includes Internal 14.4k FAX Modem &
 External 28.8k Modem *Wow!*
 -or- (External 33k Modem \$29 option)
 230m Standard Hard Drive -or- (810meg \$19 option)
 3.5 Floppy / Standard Ports on rear
 (1S, 1P, Vga, Kbd) *only a few left*
 Hydride Battery (2X the Power)
 That's a \$150 Value FREE
 Includes Power Supply
 LIFETIME Compaq Tech Support
 Internet Ready
 Owners Manual Software & Win



WOW 2 easy payments of
\$199!
 0% Financing!
 On Credit Cards only

orig
~~\$1,995~~

0%
 Financing
 ENDS
 Soon

ACTIVE COLOR
 a \$300 Value FREE

Web Surfer

CRUISER & Work Horse

Compaq LTE ELITE 486 DX475

9.5" Active Matrix Display (Sharper & Brighter than standard display)
 810m Standard Hard Drive -or- (1gig \$29 option)
 16M Ram Standard -or- (24M \$19 option / 32M \$39)
 28.8k FAX MODEM -or- (33k \$15 option)
 2-PCMCIA Expansion Slots & All Standard Ports
 (1S, 1P, 1VGA, 1Kbd)
 Hydride Battery (2X the Power) \$150 Value FREE
 EJECTABLE: Battery, Hard Drive & Ram
 Expandable & Upgradable / Lifetime Compaq Tech Support
 Built-in Power Supply / Optional Case (has tons of pockets \$29)
 Internet Ready / Owners Manual Software & W95



ACTIVE COLOR
 a \$300 Value FREE

Excellent

WOW 2 easy payments of
\$288!
 0% Financing!
 On Credit Cards only

orig
~~\$2,695~~

MAXIMUM ABUSE

strictly for professionals

Blazing Sunlight or Rain Storm

Instant ON - ZERO boot up time!

FOR HARSH ENVIRONMENTS
Out-Doors or In-Doors

Use it in a Rain Storm! (4"/hr Rain w/ 40 MPH Winds)

Drop it 3' to Concrete!

Silicone Rubberized & Diecast Case!

Ultra Shock Mounted 1GIG EIDE Hard Drive!

ESD / EMF & RF Resistant, Works from -4 to 120 Deg F
 & Vacuum to 15,000 ft

1- PCMCIA (type 1, 2 or 3), Serial & Parallel Ports in rear
 3.5 Floppy, 16m Ram / 1m Video / Local Bus 486-50 mhz &
 Math Co-processor, 28.8k Modem (Internet Ready)
 Built-in Speaker Phone, Long Lasting Hydride Battery
 (\$150 Value)

Built-in Sound & Microphone
 8.25" Display-64 Shade Monochrome REFLECTIVE
 Includes Touch Screen **with** Handwriting Recognition
 Roxanne's Voice Annotates all Windows 3.X Functions
 Compatible with W95 / Optional 12V Car cord \$29

This was a unique (one shot) purchasing opportunity
IT'S NOT OPEN STOCK
WHEN THEY'RE GONE, THEY'RE GONE FOR GOOD
 Sold till recently by IBM at \$4,699 & \$6,912 as equipped here.

See the details and pricing on the IBM web site:
www.networking.ibm.com/2489/2489prod.html

IBM ROAD WARRIOR

WOW 2 easy payments of
\$399!
 0% Financing!
 On Credit Cards only



Sturdy Handle

Rubber Slides

only a few left



Oh - My - GOD!
 Buy a Computer, get an IC MASTER for

\$29!!
 ICMaster

IC MASTER

Bible
 of the IC Industry
 Every Cross-reference
 3 Volume Set with Tons of Information

	with computer	alone	regular
ICMaster \$195 Publisher	\$29 95 edition	\$49	\$69
	\$39 96 edition	\$59	\$89
	\$49 97 edition	\$69	\$129

Mega Sale Ends Soon

Ask About REFERENCE Semiconductor Cross-Reference Software for a Quarter Million Transistors, Diodes & IC's Includes 4 HUGE Consumer Electronics Parts Co. Directories

NETWORK READY WORKSTATION

Compaq LTE ELITE Pentium 90

10.5" ACTIVE Display (Sharper & Brighter)
 24M Ram / 810 Meg Hard Drive / CD Rom
 2-PCMCIA, Infrared, & All Standard Ports on rear w/ Microphone
 33k FAX-MODEM / Stereo Sound / LIFETIME Compaq Tech Support
 EJECTABLE: Battery, Hard Drive, Floppy, CD & Ram
 Hydride Battery (2X the Power) \$150 Value FREE
 Includes 2 Power Supplies (1 in Docking Station)
 Internet Ready / Owners Manual Software & W95

INCLUDES DESKTOP Docking Station
 (a \$500 Value) Converts your laptop to a desktop

2-PCMCIA Ports & 2-Bays for optional drives (any type!)
 Stereo Speakers / Infrared Port / System Status Lights
 2-types of Network connection RJ & Coax
 Monitor Platform included

Includes Desktop
 Network Ready
 Docking Station

WOW 2 easy payments of
\$448!
 0% Financing!
 On Credit Cards only



Superb
ACTIVE COLOR
 a \$300 Value FREE



2 PAYMENT PLAN with Credit Card -or- Layaway ONLY 843-650-5700 For Questions -or- email: netcomd@aol.com
 COD's SINGLE PAYMENT ONLY ORDERS ONLY 800-733-3733 ORDERS ONLY FAX 843 650 5777 Hours 10-9 7 Days

Open Channel

Some Design Rules

by Joseph J. Carr

One of the facts of life that affects many people in amateur science and electronics is the fact that they must (or prefer to) build some of their own circuits (unless they are rich, or lucky in the surplus market). Even in schools and colleges, budgets are rarely so generous as to permit unlimited instrument buying. Some homebrewing, adaptation, improvising, and out and out chicanery is sometimes needed.

If you peruse the adverts in *Nuts & Volts* like I do every month, then you will note a large variety of high quality pieces and parts, along with complete instruments, offered for sale at good prices. With a war chest full of these items, a little ingenuity, and a bit of thinking, there is little reason why you couldn't cobble together something that works.

Sometimes, ingenuity asserts itself in funny ways. For example,

some years ago television tuners became voltage controlled. It was one way to cope with problems that TV designers faced, and allowed them to make a phase-locked loop (PLL) controlled receiver. A guy named Murray Barlowe in Bethpage, NY saw that tuner not in terms of TV, but as the basis for a spectrum analyzer. We will be discussing Murray's "Poor Man's Spectrum Analyzer" in these pages in the near future. In the meantime, if you want a pre-look, use your web browser to find "Science Workshop" in Bethpage, NY ... and visit Murray's web site.

The process of designing electronic instrumentation circuits or projects is a logical step-by-step process that can be learned. Like any skill, design skill is improved with practice, so one is cautioned against both excessive expectations "first time at bat" and discouragement if the

process did not exactly work out as planned the first time.

Some of the material in this column may be called "philosophy," and that may be a fair label to attach. Although many technical people claim to disdain "philosophy," we all have it and use it. It's just that some people think about it a lot, others think about it either a little or at only a few times, while others don't think about it at all — they take actions based not on a logically considered viewpoint, but rather, by dumb luck and pure default.

A Design Procedure

The procedure that one adopts to designing may well be different from what is presented below, and that's alright. The purpose of offering a procedure is to systematize the process. While it is conceivable that one can successfully design a circuit or instrument by a process similar to Brownian motion (Figure 1), it is the systematic approach (Figure 2) that most often yields success. This procedure assumes a product that is a one-of-a-kind instrument, as in a scientific laboratory or plant. Designing a product for production and sale follows a similar procedure, but involves marketing and production problems as well. The steps in the procedure — some of which are iterative with respect to each other — are offered below:

1. Define and tentatively solve the problem. Create multiple tentative solutions wherever feasible. In systems engineering this is called "eliciting requirements."
2. Determine the critical attributes required of the final product; incorporate these into a specification and a test plan that determines objective criteria for acceptance or rejection.
3. Determine the critical parameters and requirements.
4. Attempt a "block diagram" solution.
5. Apportion requirements (e.g., gain, frequency response, etc.)

to the various blocks.

6. If appropriate, make a first-cut guess at which functions ought to be in software and which in hardware.

7. Perform analysis and do simulations on the block diagram to test validity of the approach. If you are designing an electronic circuit, then software such as Electronic Workbench is useful. The manufacturer of this software has a website at <http://www.electronicworkbench.com>, or can be reached via ewb@interactive.com, or by phone at 1-800-263-5552.

8. Design specific circuits to fill in the blocks.

9. Build and test the circuits, and write the software.

10. Combine the circuits with each other on a breadboard ("integrate" the elements).

11. Test the breadboarded circuit according to a fixed test plan.

12. Build "brassboard" that incorporates all changes made in the previous steps. A brassboard is a full-up working model. For one-off amateur models, it may actually be the final article. In either event, it should be built the way you want the end product to look like.

13. Test brassboard and correct problems.

14. Integrate software and hardware.

15. Design and construct final configuration.

16. Test final configuration.

17. Put the product into service and enjoy it!

Solving the (Right) Problem

The purpose of the designer is to solve some problem or another using analog circuits, digital circuits, a computer, or whatever else is available in the armamentarium. There are two related problems often seen in the efforts of novices.

First, it is often the case that the designer will have a tentative favorite approach in mind before the problem is properly understood. Decisions are made based on what the designer is most comfortable doing. For example, many younger designers are likely to select the digital solution in a knee-jerk manner that excludes any consideration of the analog solution. Both should be evaluated, and the one that best fits the need selected.

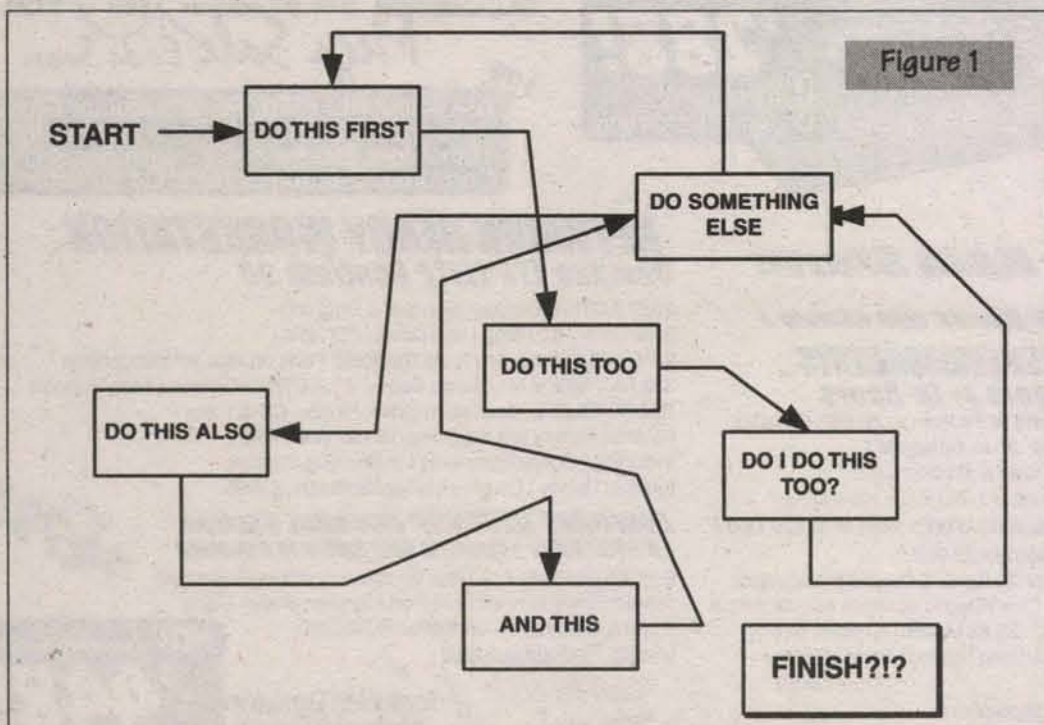


Figure 1

QUALITY KITS

Complete Source for Electronic Kits

Kits for the Novice or the Professional

Secure On-Line Ordering: www.qkits.com

64 MHz PC Oscilloscope
Laboratory PSU Kits
Hi Fi Audio Amp Kits
Stereo Valve Amp Kits
PIC Books & Programmers
1/4" CMOS Camera Modules
Transmitters & Receivers
PC I/O Kits, 1.3 GHz Video Link Kit
Polaroid Ranging Modules & Much More

• MOST COMPLETE VELLEMAN KIT LINE
• MAPLIN DISTRIBUTOR & DIY KITS

Quality Kits

49 McMichael Street
Kingston, ON., K7M 1M8
Info Phone: 613-544-6333
FAX: 613-544-4944

We accept VISA, AMEX, MC

1 888 464 5487
ORDER LINE ONLY

E-Mail: Sales@qkits.com
Send \$3.00 for catalog

WIDGETS

Sensors to RS232, 422 or 485

Starting at \$199

PRESSURE
THERMOCOUPLE
RTD
VOLTAGE
CURRENT
MOTION
GASES
RH
And more

Each system comes complete with one sensor, 10, 12 or 14 bit resolution w/ 7 extra channels of A/D, 30k of remote data storage, power supply, serial cable and WINLP-Lite data acquisition software (trending, storing and display)

1-888-597-3588 (530) 647-2028

LEMON-PLADD INC. FAX (530) 647 8951
PO Box 1683 POLLOCK PINES CA. 95726
WWW.LEMONPLADD.COM

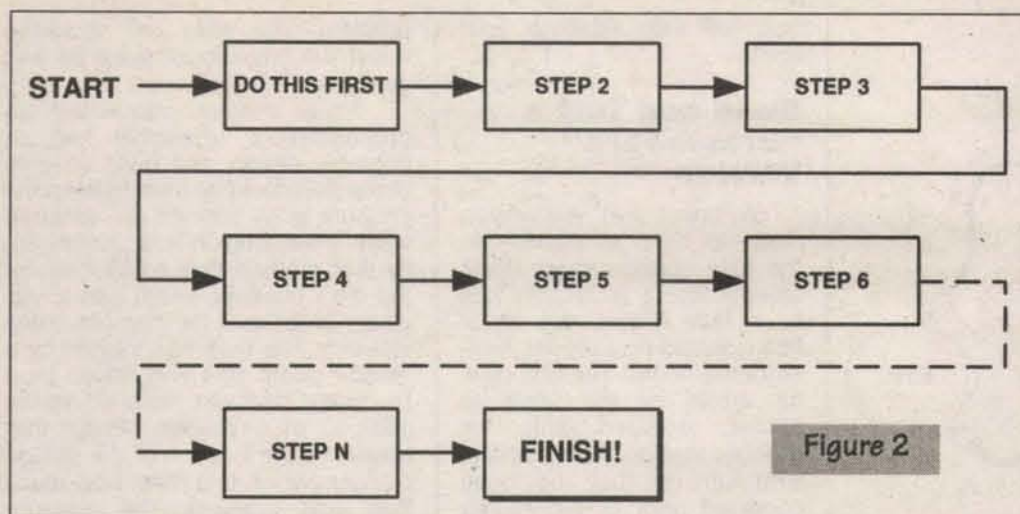


Figure 2

Second, be sure you understand the problem being solved. While this advice seems trivial, it is also true that failure to understand the problem at hand often sinks designs before they have a chance to manifest themselves. There are several facets to this problem. For example, a natural tendency of techies is to think that an elegant solution is complex and large-scale. If this mistake is made, then it is likely that the product will be over designed and have too many whistles and bells. It was, after all, designed to solve a much harder problem than was actually presented.

Another aspect to understanding the problem is to understand the final end use for the thing being designed. It is all too easy to get caught up in the specification, or our own ideas about the job, and overlook altogether what needs to be accomplished with the product.

An example is derived from the years I worked in the field of biomedical instrumentation. A physiologist requested a pressure amplifier that would measure blood pressures over a range of 0 to 300 mmHg (Torr). What the salesman never told the plant was a) it would be used on humans (safety and regulatory issues); b) that blood would come in contact with the diaphragm (cleaning and/or liquid isolation issues); and c) that it would occasionally be used for measuring 1 to 5 mmHg central venous pressures (which implies severe low-end linearity issues). The product that was delivered could not be used on anything living, human or animal.

Part of the problem in determining the level of complexity, or the specific design's function, is miscommunication between the end user and the designer. That makes for a funny conversation when these two "stakeholders" are the same person! Although miscommunications occur frequently between in-house designers and their "clients," it is probably most common between distant customers and engineers in the plant. Of course, marketing people may never let the engineer and customer get together (either from ignorance or a fear that the salesman's little lies will surface: "The reason I hate engineers is that, under duress, they usually blurt out the truth").

The proper role of the designer is to scope out the problem at hand, understand what the circuit or instru-

ment is supposed to do, how and where the user is going to use it, and exactly what the user wants and expects from the product.

Determine Critical Attributes

This step is basically the fruit of understanding and solving the correct problem. From the solution of the problem one can determine, and write down, a set of attributes, characteristics, parameters, and other indices of the product's final nature.

It is at this point that one must jot down a specification that documents what the final product is supposed to do. The specification must be clearly written so that others can understand it.

A concept or idea does not really exist, except in the mind of the originator. One must create operational definitions for the attributes of the product. One cannot simply say "it must measure pressure to a linearity of one percent over a range of 0 to 100 p.s.i."

Rather, it might be necessary instead to specify a test method under which this requirement can be met. There might be, after all, more than one standard for pressure and measurement, and there is certainly more than one definition of linearity. The operational definition serves the powerful function of providing everyone with the same set of rules; basically it levels the playing field.

Sometimes, the operational definition becomes standardized, and is the only way to "get a handle" on the problem. For example, how do you measure the conductivity (G) of water? A marine biologist I knew once tried to dip the problems of an ohmmeter into the water, and then take the reciprocal of the resistance ($G = 1/R$). He was trying to measure salinity. But his results were at odds with other researchers in the same college. They standardized on a method that defined the size, shape, spacing, and material composition of electrodes ... and whadayaknow ... the results were consistent.

Part of making an operational definition is to write a test procedure for the final product. It is here that one determines (and in business often contractually agrees) exactly what the final product will do, and defines the objective criteria of goodness or badness that will be used to judge the product.

Determine Critical Parameters and Requirements

Once the product is properly scoped out, it is time to determine the critical technical parameters that are needed to meet the test requirements (and hopefully the user's needs — if the test requirements are properly written). Parameters such as frequency response, gain, and so forth tend to vary in multi-mode instruments, so one must determine

the worst case for each specification item and design for it.

Attempt a Block Diagram Solution

The block diagram is a signal's flow or function diagram that represents stages, or collections of stages, in the final instrument. In large instruments, there might be several indexed levels of block diagrams, each one going finer in detail.

Apportion Requirements to the Blocks

Once the block diagram solution is on paper, tentatively apportion system requirements to each block. Distribute gain, frequency response, and other attributes to each block. Keep in mind that factors such as gain distribution can have a profound effect on dynamic range. Also, the noise factor and drift of any one amplifier can have a tremendous effect on the final performance — and that it's in these types of parameters (where critical placement of one high quality stage may be sufficient) that added cost and complexity often arise.

Analyze and Simulate

Once the block diagram is set, and the requirements apportioned to the various stages, it is time to analyze the circuit and run simulations to see if it will actually work. A little "desk checking" goes a long way towards eliminating problems later on when the thing is first prototyped. Plug in typical input values, and see what happens on a stage-by-stage basis. Check for the reasonableness of outputs at each stage. For example, if the input signal should drive an output signal to, say, 17 volts, and the operational amplifiers are only operated from five-volt power supplies, then something is wrong and will have to be corrected.

Design Specific Circuits for Each Block

In this step, fill in those blocks with real circuit diagrams.

Built and Test the Circuits

At this point one must actually

JFETS

ULTRA LOW NOISE

LS843 - 3nV/Hz typ

TIGHT MATCHING

LS843 - 1 mV max

- ◇ N & P Channel
- ◇ Duals & Singles
- ◇ Custom Screening
- ◇ Die, SMT, Thru-Hole
- ◇ No Order Minimum
- ◇ COD's Accepted


Second Source for Domestic & Foreign JFETs & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

LINEAR SYSTEMS

4042 Clipper Court
Fremont, CA 94538
510-490-9160/510-353-0261 (Fax)
E-mail: 3623671@MCI.COM


Write in 66 on Reader Service Card.

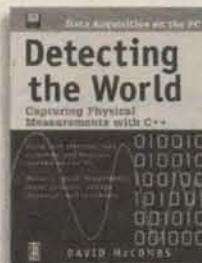

by D. McCOMBS

Capture and analyze speed, temperature, force, pressure, voltage, amperage, and resistance with cost-effective PC-based systems. Includes C++ Code operable under Windows 95 or DOS.

360pp, disk included
ISBN 0-87930-559-2 | \$44.95

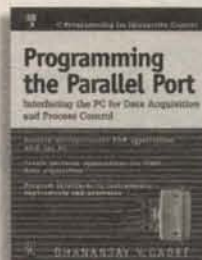

by D. V. GADRE

Key topics include: the Enhanced Parallel Port, Extended Communications Port, Analog/Digital Converters, adding bits, hosting an EPROM emulator, connecting to an external microprocessor, and digital waveforms.

360pp, disk included
ISBN 0-87930-513-4 | \$44.95

CALL 800-500-6875 | FAX 408-848-5784

R&D BOOKS

Nuts & Volts Magazine/April 1999 15

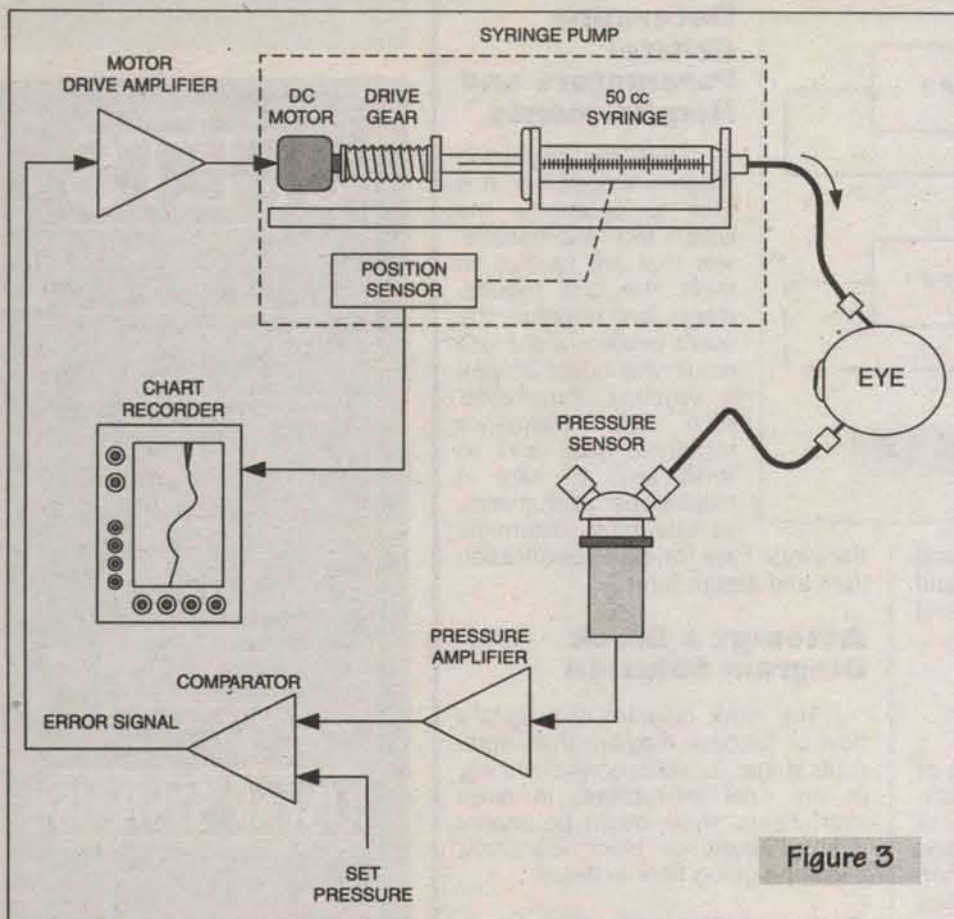


Figure 3

construct the individual circuits, and test them to make sure they work as advertised (unless, of course, the circuit is so familiar that no testing is needed). Keep in mind that some of your best ideas for simplified circuits may not actually work — and this is the place to find out. Use a benchtop breadboard that allows circuit construction using plug-in stripped end wires.

Combine the Circuits in a Formal Breadboard

Once the validity of the individual circuits is determined, combine them together in a formal breadboard. Whether built on a benchtop breadboard (as above), or on a prototyping board, make sure that the layout is similar to that expected in the final form.

Test the Breadboard

Test the overall circuit according to a formally established objective criteria. This test plan should be developed earlier in step two. As problems arise and are solved, make changes and/or corrections — and document the results. It is, perhaps, the main failing of inexperienced designers that they do not properly document their work, even in an engineer's or scientist's notebook. The reason for documenting the process is that it helps when you go back a little while later to make changes, repair the instrument, or even attempt to understand it. It's remarkable how fickle human memory is. It is also necessary to be able to communicate your intent to anyone else who does these chores. If you decide to patent your invention, then the documenta-

tion will help establish your rights.

Build and Test a "Brassboard" Version

A "brassboard" is a version made as close as possible to the final configuration. While breadboarding techniques can be a little sloppy, the brassboard should be a proper printed circuit board. The test criteria should be the same as before, updated only for changes that occurred. If problems turn up, they should be corrected prior to proceeding further. Keep in mind that the most common problems that occur in leaping from breadboard to brassboard are layout (e.g., coupling between stages), power distribution, and ground noise (these are the areas of difference between the two configurations).

Design, Build, and Test Final Version

Once all of the problems are known, solved, and changes incorporated, it is time to build the final product as it will be given to the end user. It is at this point that they reputation of the designer is made or broken, because it is here that the product is finally evaluated by the client.

Deliver, install, and use the instrument!

Parting Words

Whenever you design and build anything — whether it is an electronic instrument, a complex system — or an addition to your house, you need to first capture the requirements. There is no step more important to success! After all, if you don't know what the product is going to do, then you can't even think about making it right. The medical pressure monitor problem mentioned above was basically a requirements capture

problem. The sales rep should've asked the physiologist what he was going to use it for!

I saw another case where an ophthalmology researcher had an engineer design and build a servo pump that could be used to keep the pressure in an animal's eye constant while measuring in-flow (Figure 3). By that method they could measure the eye's out-flow, which was a necessary bit of data for their glaucoma research. The fluid was infused by a syringe pump that was driven by a DC motor, and was modified by the addition of a position sensor that measured the location of the syringe plunger (which told them how much fluid was infused). The pressure inside the eye was measured by a pressure sensor of standard design.

Finally, a comparison amplifier (i.e., a differential amplifier) monitored the difference between a set pressure value and the actual pressure. The difference became an error signal that drove the motor of the syringe pump. Simple, huh? I spent a lot of time modifying the design later on because the engineer did not take into consideration some critical factors.

First, the doctor's office had an even temperature, the lab did not. Drift was huge, mostly from the pressure sensor. Second, the metal used for the syringe pump corroded easily because of the fluid that leaked from the syringe during assembly. Finally, the unit was tested using a lemon as a surrogate for an eye ... and lemons don't have an out-flow facility. As a result, the pump "hunted" because the engineer did not have the opportunity to notice that the AC response of the servo loop was too high.

A little more communication between the user and the designer, and a bit of requirements capture effort might've saved me a lot of trouble later on. **NV**

Connections ...

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA 22041, or via E-Mail at CARRJJ@AOL.COM.



EPROM+

A device programming system for design, repair and field service

◆ EXCEPTIONAL POWER FOR THE PRO
◆ EASY-TO-USE FOR THE NOVICE

Here's what you get: A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters*. Comprehensive, easy-to-use software which is specifically designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

Broad device support: Including FIRST GENERATION EPROMS (2708, TMS2716*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080)(8 MEG), 40 and 42 PIN EPROMS* (27C1024-27C160)(16 MEG) EEPROMS (2816-28C010) PLUS ER5901, FLASH EPROMS (28F, 29C, 29EE, 29F)(32 MEG), NVRAMS (12, 20, X2210/12) 8 PIN SERIAL EPROMS* (24, 25, 85, 93, 95, 80011A) PLUS ER1400/M58657* BIPOLAR PROMS* (74S/825), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS* (874X, 875X, 87C5X, 87C75X, 89C) ATMEL MICROS*(89S, 90S)(AVR) PIC MICROS* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS* (68705P3/U3/R3, 68HC705CB/C9/J2/P9, 68HC711E9/D3)

\$289

Includes step-by-step tutorial plus explanation of EPROM fundamentals
1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE
*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)

\$5.00 SHIPPING • \$5.00 C.O.D.
VISA • MASTERCARD • AMEX

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150
(513) 831-9708 FAX (513) 831-7562
website - www.arlabs.com email - arlabs@worldnet.att.net MADE IN THE U.S.A.

WHOLESALE CABLE

COMPLETE LINE OF CABLE PRODUCTS

- ✓ Quality merchandise by brand name manufacturers
- ✓ Satisfaction guaranteed
- ✓ Free gift on first order
- ✓ Technical support
- ✓ 2 year warranty on new converters
- ✓ COD shipping & overnight shipping by request
- ✓ Experience where it counts
- ✓ Volume pricing

PLAIN CONVERTERS: ZENITH, OAK, PANASONIC, PIONEER, EAGLE, HAMLIN, STARGATE, PLUS MORE.

REMOTE CONTROLS: ALL MAJOR BRANDS, INCLUDING 2-4 FUNCTION UNIVERSAL REMOTES

WHOLESALE CABLE M-F 11am-6pm EST (718) 206-0879
(718) 262-0900 • FAX (718) 657-4015 • (718) 297-9221

No NY sales. Federal and local laws provide criminal and civil penalties for unauthorized use. Check with your cable providers for permission to use equipment. Must be paying for all services you receive. Order by model number only. Some equipment refurbished as new.



Tell us the best price you were offered, where you got it from, and let us try to beat it.

FAT HIGH VOLTAGE CAPS!

Two 820µF 250V radial electrolytics soldered on a PC board with other goodies.
99P001 \$4.95

LOCTITE REMOVEABLE THREADLOCKER

Type 242. 0.34-oz. (10ml) bottle.
99Z001 \$2.49 each

NEC NE710 FET

Ku-K Band GaAs.
92S073 \$9.95

JEWELERS' SCREW-DRIVERS

Six small screwdrivers (four straight blade and two Phillips) come in handy storage box.
750SD \$1.85/set

10 POSITION LED BAR GRAPH

Seven amber and three red.
98L001 \$1.95 each

HEAT SINK GRABBAG

Popular sizes and shapes. Representative sample shown.
92Z036 50 for \$3.95

PLASTIC & METAL KNOBS

Assortment of sizes and colors, similar to sample.
92Z026 50 for \$3.99

MINI PROJECT BOX

Amarex unibox. 2"x2.75"x0.625"; with 0.125" hole in both ends.
92U065 49¢ ea.
96U010 12 for \$5.00

24V DIAPHRAGM AIR PUMP

24VDC @ 400mA (max.). Free air 0.3 CFM. Max. pressure approx. 11 lbs. Max. vacuum approx. 28"Hg. Dimensions 4"W x 4 1/2"L x 3 1/2"H.
99U002 \$19.95 each

24VDC @ 25A LAMBDA SWITCHING POWER SUPPLY

24VDC @ 25A (up to 40°C). Input 187-250 VAC, 790W, 0.7pF (260-350 VDC). Size 4.5" x 5" x 13". Weight approx. 9.5 lb.
98E027 \$74.95

POWERSONIC AUTOMATIC CHARGER

For 12V gel cell. Input: 120VAC, 60Hz, 0.11A. Output: 12VDC @ 0.3A.
98E025 \$9.95 each

"Semiuniversal" RCA 39-BUTTON REMOTE CONTROL

This "semi-universal" unit works on several products and brands. Just press desired function button and enter the 3-digit code provided. Requires four AAA batteries (not included). Unused.
97V010 \$9.95 each

SIX-WIRE UNIPOLAR STEPPER MOTOR

7.5°/step, 48s/rev, 36 Ohms. With brass gear 2-3/16" dia. x 1" thick. Nippon Pulse # PF55-48C5.
97M009 \$2.49 each

PLUG PARADISE!

Molex, Amp, Cannon, Viking, etc. A great assortment of connectors.
92J048 5 Lbs for \$5.00

28VAC 2A TRANSFORMER

Model PPT-054. Schematic included.
98N006 \$8.95 each

TYGON TUBING

Fifty foot roll, formula R-3603, 1/8" ID, 1/4" OD, 1/16" wall.
98U005 \$7.95/roll

SOLAR-POWERED ROBOT BUG KIT

No batteries required! It uses photosensitive eyes to seek light and dual feelers to avoid obstacles. Kit includes circuit board, solar cells, miniature motors, all parts and easy-to-follow instructions. Body approx. 3"L x 2"W.
98K001 \$59.00 each

TRANSCIEVER MODULE

3W Mobile transportable type, 12 pin transceiver to handset/control head jack. 4-pin battery contacts for power 3.5mm mic and speaker jack. T-type antenna connector. Dual NAM capability. OKI 1200 cellphone, Model 6025. Style UX4.
99U004 \$14.95

SWITCH BONANZA

Assorted switches. May include rotary, toggle, slide, "micro," breaker, pushbutton and weird.
92B012 50 for \$4.95

SEMIPOTPOURRI

One pound of mixed transistors and diodes. Big assortment of signal, power, UHF, RF, Schottky - all kinds of goodies.
95Z013 \$19.95

PHONE FM TRANSMITTER

This small but powerful circuit attaches to a phone line and transmits the conversation into the FM band. It uses the phone line itself as an antenna. No battery is required since power is drawn from the phone line. Easily adjusted to transmit outside the commercial FM band for greater security. Sold only as a testing device.
Kit 16 \$12.99 each

2x40 CHARACTER LCD DISPLAY

Has 14-pin interface with documentation to help you interface to your microcontroller projects.
94L005 \$14.95 each

REMOVABLE HARD DRIVE

Syquest S0555 44MB removable SCSI cartridge hard drive. (Removed during upgrade)
97C024 \$9.95 each

NEC AMPLIFIED SPEAKERS

Size: 11"H x 4.5"W x 4.75"D. Power: ±15VAC @ 1A, 3-pin mini-DIN socket. Input: 1/8" stereo phone jack, line level. Outputs: 1/8" stereo phone jacks, line out & earphone. RCA phono cord connects speakers. Simple schematics to build your own power supply included.
98V013 \$9.95/pr.

Visit our website for Vacuum Tubes, Test Equipment, HAM Gear, and more!
<http://www.alltronics.com>

HOLD-VAC® SURFACE MOUNT TOOL

This pen-style vacuum tool is delivered to you with five different size vacuum cups - ideal for handling and manipulating various components during assembly or placement operations, and it's guaranteed ESD-safe.
HV-8901 \$64.00 each

INCREDIBLE, INEDIBLE HARDWARE ASSORTMENT

Nuts, bolts, screws, brackets, springs, standoffs, arms, pawls, gears, pulleys and lots of indescribable metal stuff from Silicon Valley surplus to complement anyone's hardware hoard.
92Z038 10 Lbs. for \$10.00

ATARI 1020 COLOR PRINTER

For all Atari 8-bit computers. (Not PC-compatible!) Package includes: printer, power supply, software, pens, paper and interface cable. These are new units in factory sealed boxes.
94C037 \$14.95 each

3 1/2" to 5 1/4" FLOPPY DRIVE ADAPTER

94C028 \$4.95 each

TRANSPARENT 3-BUTTON MOUSE

Watch your mouse in action! Selectable 2- or 3-button operation. Fully compatible with Mouse Systems and Microsoft. 300 DPI opto-mechanical encoder. Six-ft. cable with DB-9 connector. FCC approved. Easy-to-follow instructions and software on 5.25" floppy disk.
MUS3C \$7.95 each

DB25-M to RJ11

98J004 79¢ each

DB25-F to RJ11

98J005 79¢ each

HEAVY DUTY INSTRUMENT CASES

Unit splits apart for ease of access. ABS plastic used for flexibility and strength. Complete with black front and rear panels. IC115B includes ventilation slots and speaker recess.
• 2.5" x 8" x 6.4"
IC115A \$6.20
• 3.1" x 10" x 7.4"
IC115B \$8.20

LONGWAVE UV LAMP

This pocket-sized longwave ultraviolet light may be used for detecting invisible inks, minerals in rocks, etc. It's the size of a pocket pager and even has a belt clip to keep it handy. Runs on two "AA" batteries (not included). 3.25"W x 1.75"H x 1"D.
95L007 \$7.95 each

SUPER MAGNET

Rectangular, 2.5" long x 1.125" wide by 0.375" deep. These 2000 gauss magnets will definitely hold your calendar up! Not a toy!
98N013 \$5.95 each

COMPUTER CASE & POWER SUPPLY

Mini tower case with 250W power supply, two 5.25" and two 3.5" external bays, plus one internal bay for hard drive. LEDs for power, turbo and HDD.
97C001 \$24.95 each

TV AUDIO DEMODULATOR

Originally used in cable TV application, this sub-assembly takes channel 3, 4 or 5 signal and demodulates the audio. Comes with documentation and schematics, plus additional schematics to build add-on video demodulator board.
92A028 \$9.95 each

EMERGENCY SURVIVAL COMMUNICATIONS

How to Build and Power Your System Keys to survival news. Shortwave radio. World of amateur radio. Scanning. CB/Citizens Band. Personal com-munications systems. Satellite radio and guide. Alternate power sources. Free playing radios. Weather information. Radio antennas. Source lists. paper, 182pp, 8.5 x 11.
98X008 \$19.95

U.S. GOVERNMENT SPY ANTENNA

Marked "Confidential Antenna & Reel." 24 feet of open ladder line plus 18 feet of flexible braid. Hook to antenna tuner and load up any frequency. P/N 5666-1H-B1-1-10.
94A007 \$9.95 each

PLUG & PLAY IDE CD-ROM INTERFACE CARD

System requirements: IBM PC 386SX and higher or 100% compatibles; plug and play operating system (Windows 95), or a Configuration Manager driver (INTEL CM for WIN 31/DOS), or 100% PnP BIOS; 16-bit ISA bus slot. Supports up to two CD-ROM drives. Supports all ATAPI compliant IDE CD-ROM drives. No DMA support. 16-bit I/O polled CD-ROM interface external connector. Hardware settings: IDE Interface Interrupt (IRQ): 10, 11, 12, 14, 15; IDE Interface Port: Secondary, Tertiary, Quaternary (Note: all settings are PnP settable. More may be available). External Connectors: 16-bit I/O polled CD-ROM interface. Sold by box of 20 only.
98C007 20 for \$19.95

UNIPOLAR STEPPER MOTOR DRIVER IC

UCN5804. Drives a unipolar stepper in one of three operating modes: single phase, two phase or half step. Up to 1.25 Amps per phase. Step and direction input. Drive with a 555 timer, parallel port, etc. Build your own robot, anything that requires precision positioning.
93I002 \$4.50 each

PULSE MOTOR

42mm dia., 22mm thick. Shaft: 3mm dia. x 12mm long, with 13-tooth gear approx 16.6mm dia x 5mm thick. 7.5°/step, 48s/rev., 12VDC, 50Ω, 6-wire. With spec sheet.
92M010 \$3.95 each

COMBO PACK!

One 93I002 IC and 92M010 motor (both shown above) with schematics.
93I003 \$7.95/set


ALLTRONICS

2300-D Zanker Road - San Jose, CA 95131-1114

World Wide Web: <http://www.alltronics.com>

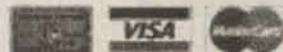(408) 943-9773 - Fax (408) 943-9776

Store Hours: 9-6 M-F & 10-3 Sat. - Pacific
Visa, M/C, AmEx Accepted.
All Sales Final.
California Residents Add Sales Tax.
Shipping Additional on All Orders.
Prices Good 60 Days from Date of Publication



Send \$2.00 For Our Latest Catalog!
\$4.00 Foreign. Refundable on First Order.

010499

reader FeedBack

Dear Nuts & Volts:

I am a loyal reader of your magazine and have been for years because of your interesting articles, sources, and columns.

In your Feb. '99 issue, I saw an article about AT&T's decision to stop offering SSB phone service.

This article seems to be geared more towards those users who do not want to give up their faithful SSB systems and not to those who really want reliable inexpensive communications.

The fact is, today's technology offers many options to radio systems at a lower cost and higher reliability and quality.

In the article, the mention of the Inmarsat Mini M alter-

native, makes people fear this system with the warning of high rates and monthly fees. Comsat, for example, has many pricing plans available, many of which do not have a monthly fee.

When compared to \$4.99/min that AT&T use to get in the US, the rates I can offer you with Comsat (as low as \$2.15/min to the US and Canada) are much lower.

Using Mini M also gives you the ability to send and receive basic E-Mail from your computer without extra equipment or modifications.

As for the price of equipment, the \$5000.00+ price you mention is for a complete marine system with a stabilized antenna designed for the rough seas. Less fre-

quent users and those on shore may be able to cover their needs with a portable unit (Our Planet 1 phone is about the size of a small laptop computer) for about \$2,500.00.

I was recently in St. Martin covering the Heineken regatta from one of the race committee boats. During one of the finishes, we were in a bad area for cellular reception and too far for VHF, we were able to use my Planet 1 Mini M phone to call in the race results and even do a live radio interview.

I also used it to send E-Mail from my hotel room on the French side of the island because I could not connect to the strange French telephone system and they wanted about \$4.00 just to connect a call.

Maybe you can do an article on the new satellite technology in the near future. We should let the users see all options available and decide which systems works best for

them. Please visit the Comsat web site at www.comsat.com for more information on Planet 1 (Mini M) and other services available from Comsat. Feel free to contact me with any questions or comments.

Vincent Valldeperas
Comsat Mobile Communications

Hi,

I've just discovered the N&V web site. I don't know if you do any articles on SMD's and SM construction. Perhaps your readers would be interested in my web page at <http://www.billssmd.mcmail.com> I have worked on taming SMD's for hobby use for some years and there is a list of articles on SM on my site, mostly for EPE magazine.

I'll be asking for a trial copy of Nuts & Volts it looks just the job.

Best regards from UK

Bill Mooney
em bijpm@mcmail.com

INTERNET SECURITY CELLPHONE/CORDLESS GUIDE STOPPING POWER METERS MANY MORE TITLES!

The latest tricks and methods hackers use on the Net to pirate software (warez), and hack websites. Includes examples, countermeasures, password defeats, Packet-Switched Networks, UNIX, Sprintnet, X.25, anonymous FTP, brute force techs, lots of tips. **More! \$29. wds=29.4K**

INTERNET TRACKING & TRACING: Scammers, spammers, stalkers, infectors, and others hide behind the Internet's anonymity to commit serious offenses. Learn from master hackers best methods to track, trace IDs and origins, and to protect your own privacy. **More! \$29. wds=17.0K**

INTERNET FRAUDS DATABOOK: Internet cons, scams and related frauds now rake in \$2+ Billion annually! Most are done anonymously with impunity. Details how they're done, how to ID them, how to protect yourself. **More! \$25. wds=19.1K**

THE COOKIE TERMINATOR: Many websites track your every move! Browser cookie, history and cache files contain personal data readily accessible to Internet predators, scammers, spammers and snoops. Your financial, medical, political, habits, lifestyle, future plans data is exposed to the world! Step-by-step how to remove and stop cookies from destroying your privacy. **\$25. wds=8.4K**
Any 2 for \$49, 3 for \$64, all 4 for \$79!

PBX SECURITY
PBXs hacking losses of \$5-\$10 Billion/yr! Detailed vulnerabilities (especially for out-dial), countermeasures. Exclusive author interview in Forbes! **\$24. wds=17.4K**

ATM SECURITY
100+ ATM crimes, abuses, vulnerabilities, defeats exposed - TEMPEST, mag stripes, false fronts, supercool. **More! Case histories, labeled internal photos, figures. \$39. wds=41.0K**

TOP SECRET
Full Web Catalog: www.tsc-global.com Special Projects: spaf-spp.html

Established in 1971 by John Williams, MSEE, former DOD weapons engineer and NIH physicist. Featured on CBS "60 Minutes," Forbes, New York Times. Add \$5 total S/H (US, Canada). **Postal MO is fastest! VISA, MC OK. No CODs. 10% OFF all Orders over \$100; \$2.00 OFF all New Orders over \$20 placed by Mail or Fax. wds=Estimated Word Count**
Sold for legal educational purposes only. Some publications are controversial! We take no responsibility for anything we publish. See Catalog for WARRANTY, SPECIAL PROJECTS and all other applicable policies.

How cellphones operate; mods. Vulnerabilities to hack attack; countermeasures. Cloning details for NAMs, ESNs, etc. control data formats, computing encoded MINs, ESNs, SIDHs, Op Sys, PROMs, forcing ACK, test mode and resets, cable diagrams, scanning, tracking, scanner restorations, freq allocations, roaming, step-by-step to keypad-reprogram 100+ popular cellphones. One FREE database search. Plus much on Cordless phones. **More! \$49. wds=80.0K**

PAGER (BEEPER) MANUAL: How Pagers work, different types and uses, freqs, advantages over and uses with cellphones, and tips and tricks. How phreaks hack Pagers; countermeasures. Plus plans for a **Personal Pocket Paging System** (xmitter and receiver). **More! \$29. wds=11.7K**
Both for only \$69!

CALLER ID & ANI SECURITY
How they work and the many vulnerabilities of Caller ID, ANI, *69, *57, Call Blocking, *67, et al. Describes ESS, SS7, CN/A, CAMA, DNR, Diverters, Centrex! **\$25. wds=15.2K**

FAX MACHINE SECURITY
All known methods used to hack faxes and countermeasures. Includes computer fax modems, crimes, interceptions, fax servers, fax-on-demand, protocols, parameters, compression, encryption, and fax surveillance-type mods. **More! \$29. wds=29.0K**

VOICE MAIL SECURITY
VMSs are hacked to penetrate PBXs to make outgoing calls, get free VMB usage, secretly read/change/delete messages, control or damage the VMS (or its PBX) itself. Details how hackers do it, countermeasures. A must for users, sysops, security personnel! **\$29. wds=14.2K**

CATALOG \$1 WITH ORDER, \$3 W/O
2430 Juan Tabo, NE, #259, ABQ, NM 87112
P.O. Box 23097 ABQ, NM 87192
Fax: 505-292-4078 (all hours, orders only) Voice: 505-237-2073 (9-7 M-S)

As reported on "60 MINUTES"! 6th Edition!

Details devices that can slow down (even stop) power meters while loads draw full power - great science projects! Devices plug into one outlet and normal loads into other outlets. Describes meter creep, overload droop, pole meters, etc. **\$29. wds=10.4K**

SPM THE VIDEO: Now its easier to learn about KW-HR Power Meters than ever before! This educational video shows you how they work and their anatomy. Demonstrates SPMEM device and external magnetic methods used to slow and stop meters! Hosted by a top expert in the field. From the novice to the pro, an excellent source of info on these exciting devices! Great in combo with our SPM-related manuals! **\$29. (20 min)**

THE I.G. MANUAL: Details external magnetic ways (applied to meters) outlaws use to slow down and stop power meters while drawing full loads. **\$25. wds=4.9K**

KW-HR METERS: How watt-hour energy meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow, stop power meters by others. **\$25. wds=24.2K**
Any 2 for \$49, 3 for \$64, all 4 for \$79!

COMPUTER SECURITY
Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - much more! Manual + PC Disk! **\$39. wds=49.5K**

THE HACKER FILES: Expose 3 HD PC disks filled with choice raw, colorful, highly informative hacker, phreaker text files covering many topics! **\$39. Both for only \$69!**

BEYOND VAN ECK TEMPEST
Remote eavesdropping plans of TV video "noise" signals. Range up to 1 KM. Describes how van Eck systems work, and are also used in surveillance of computer systems. Plus TVRO vs phone privacy detailed! **\$29. wds=14.9K**
Van Eck Demo Tape is \$29. (15 min). Both for only \$49!

(See Catalog for prices & descriptions)
BEYOND PHONE COLOR BOXES
ANSWER. MACHINE SECURITY
CASINO SECRETS
CHECK & M.O. SECURITY
CREDIT CARD SECURITY
CONS & SCAMS DATABOOK
SOCIAL ENGINEERING
POLYGRAPH SECRETS
BY AN ORDER OF THE MAGNITUDE
ULTIMATE SUCCESS MANUAL
STEALTH TECHNOLOGY
SIMPLE/CHEAP SECURITY ELEC.
SECRET & SURVIVAL RADIO
THE "GOLDFINGER"
THE "SILKWOOD"
SECRETS OF SOLDERLESS BBS
HIGH VOLTAGE DEVICES
MIND CONTROL
UNDER ATTACK!
RADIONICS MANUAL
HEAL THYSELF!
SECRET & ALTERNATE IDS
CRYPTANALYSIS TECHNIQUES
GOVERNMENT LAND GRAB
ROCKET'S RED GLARE
SURVIVAL GUNS & AMMO
THE ULTIMATE DRIVER

THE DIRTY-2 Dozen!
24+ Hot Hack/Phreak Expose Disks!
See CATALOG!

SPECIAL PROJECTS

We will design & build just about anything electronic! Hardware done as **SPECIAL PROJECTS**. Send #10 SASE or \$1 for SP Application Form, else get at: www.tsc-global.com/spaf-spp.html

Build the Pot-Box

by Fred Blechman

Useful to experimenters and circuit designers, the "Pot-Box" allows you to conveniently determine the best value of resistance to use in a circuit, as well as to test various components that must be used with resistance. You can build it for under \$25.00 from all new parts.

The Pot-Box is essentially a potentiometer substitution box. It contains five linear-taper decade-stepped potentiometers, each selected by a rotary switch, and two clip leads. Each "pot" has a pointer knob, so the potentiometer resistance at any position can be estimated. For greater accuracy, the lead resistance can be measured directly.

How many times have you had to hunt through your "junk box" looking for a potentiometer of just the right value when designing, testing, or repairing a circuit? Finally, finding one you hope will do, you precariously perch the "pot" on the workbench and gingerly attach it to the circuit with clip leads. Then, ever so gently (for fear of upsetting the whole "rat's nest" of wires), you rotate the potentiometer shaft.

Sometimes this takes a screwdriver and three hands, but somehow you manage. After trying two or three different potentiometers, you finally find one that's the proper range, and set it to the position that



Box is intended for low-power hobbyist and experimenter circuitry, not Boulder Dam repairs!

Finding the Parts

On the face of it, this seems like a simple project — and it was, over 30 years ago when I designed and built my first Pot-Box. In those days, with Lafayette Radio, Olson Radio, Allied Radio, and other suppliers as a ready source of inexpensive parts for hobbyists and experimenters, it was simple to find the necessary parts at low cost.

Things have changed. There seem to be fewer sources for low-cost parts, and the variety is very limited. RadioShack stocks only the most popular parts. Most mail-order

A Decade Potentiometer Box

gives the desired circuit effect. Now you'll probably want to replace the potentiometer with a fixed resistor — but what value? Out comes the ohmmeter and more lead maneuvering ...

What Is It?

Well, with the "invention" of the "Pot-Box," many of the difficulties just described are eliminated. As

shown in the Figure 1 schematic, the Pot-Box is essentially a potentiometer substitution box. It contains five linear-taper decade-stepped potentiometers, each wired to a rotary selector switch. Two clip leads are the connection to the outside world. Oddly, as useful as I've found this device, no one seems to manufacture one — but you can easily make your own for under \$25.00.

In use, the clip leads are merely

connected to the test circuit, the selector switch is used to determine the potentiometer to be used, and the selected potentiometer knob is turned to vary the resistance. Each pot has a pointer knob, so the potentiometer resistance at any position can be estimated. More on this later.

Note: The potentiometers in the Parts List are rated for 0.4 watts, adequate for today's typical integrated and transistorized circuits. The Pot-

firms have minimum orders and high shipping/handling costs.

When I recently decided to write up my Pot-Box as a project for *Nuts & Volts*, I was dismayed at not being able to find a source for the parts at a reasonable cost. Everyone (including RadioShack) has knobs, switches, clip leads, and cabinets. But finding inexpensive linear-taper decade-value potentiometers of the same type was a real challenge — until I

32 FIBER JACKETED FIBER OPTIC CABLE

High quality flexible black vinyl jacket fiber optic cable contains 32 clear plastic fiber optic strands. Here's your chance to stock up on fiber optic strands at a giveaway price. Strands can be easily pulled out of the jacketed cable. New high quality perfect for making colorful displays, high quality flexible light pipes, communications etc.

G1128 \$2.00/ft • \$8.00/5ft • \$35.00/25ft

PICO 5VDC TO 75VDC CONVERTER

Small converter takes 5VDC in and puts out about 75VDC. Perfect for applications where you want to use low voltage DC to light neon lamps, fluorescent displays, etc. Size only 1 1/8" L x 1 1/16" W x 1/4" H. Has 4 pins for hookup. Part # PICO 5B48S.

G1303 \$2.00 ea.

9 VOLT SUPER HEAVY DUTY BATTERY

Great for powering all sorts of electronic devices these standard size 9V batteries are super heavy duty types made by GP. Part #16045 9V. We believe the date code might be from the end of 1997 but they are full power batteries that are mercury free so they are better for the environment.

G9973 2/\$1.00

BLINDING OUTPUT RED JUMBO LED

Made by Everlight these clear 5mm T1 3/4 case LEDs produce a blinding red light. Prime long lead units on tape and reel.

G1124 5/\$1.00
Factory reel of 1000/\$175.00

BRIGHT BLUE T1 LED

Prime bright blue LED type 264UBD features a light blue diffused lens. Brand new!

G9831 69¢ ea. 100/\$59.00

GREENPLUG® ELECTRICITY SAVER TYPE 1 FOR REFRIGERATOR/FREEZERS

Brand new highly sophisticated electronic device which contains special IC circuitry to help reduce electricity usage. Simple to use just plug into any standard 120V 3 slot AC outlet and then plug your refrigerator or freezer into the GreenPlug. The type 1 is designed for any 120VAC refrigerator or freezer with up to a 7amp (840watts max) draw manufactured before 1992. Not for use on models with LED digital displays. Brand new with instructions.

G9946 \$3.98 ea.

BACKLIGHTED LARGE LCD DISPLAY

Intelligent LCD display features a 2 5/16" X 4 5/16" active display area and an overall size of about 3 1/2" X 5 1/4". These are part#HG12603-A made by Hyundai. They have 10 IC's on the reverse side and a 17 pin connector. Unfortunately we have no specs or hookup data. They do have a slide control on the front that we suspect is for contrast or brightness. These are brand new — prime but we are selling them "as is" because we have absolutely no info.

G1308 \$4.95 ea.

GIANT CDS CELL

Giant light sensitive 1" Dia. CDS cell with dark res. in megohms and light res. less than 1kohm. Prime!

G1296 \$1.00 ea.

Send for our new
96 page catalog!
Free to USA addresses
or send \$5 if out of US.

WE ALSO OFFER OVER 150 DIFFERENT ELECTRONIC KITS.

ELECTRONIC GOLDMINE
PO Box 5408
Scottsdale, AZ 85261

<http://www.goldmine-elec.com>

NOTE: All items subject to prior sale; All prices expire 6-01-99

For Phone Orders Call: 800-445-0697

or Fax Your Orders to: (602) 661-8259

For a Free Catalog Call: (602) 451-7454

Foreign catalog request: send \$5.00

Minimum Order: \$10 (plus min. \$5 Shipping and Handling). We accept MasterCard, Visa and personal checks. However, we cannot accept personal checks on orders outside the U.S. Minimum Foreign Order Amount: \$50 (plus a minimum \$10 S&H)

POTTER & BRUMFIELD DUAL IN-LINE PACKAGE 5VDC DRY REED RELAYS

We have 2 different types of the small dip relays. Each has a coil voltage of 5VDC. The JWD-107-1 has a coil resistance of 500Ω, a minimum operating voltage of 3.8VDC, and a maximum operating voltage of 19VDC. Contacts are 1 form A (SPST) rated 10W max. The JWD-172-155 has a coil resistance of 200Ω, a minimum operating voltage of 3.8VDC and a maximum operating voltage of 12VDC. Contacts are 1 form C (SPDT) rated 3W max. Both relays fit into a standard 14 pin IC socket. Brand new marked with the Potter & Brumfield part #.

JWD-107-1 G1307 69¢ ea • 100/\$60.00
JWD-172-155 G1308 \$1.00 ea • 100/\$90.00

**Great Books for Hobbyists,
Students, Engineers . . .**

**Simple, Low-Cost Electronics
Projects**

by Fred Blechman

Learn electronics with Fred Blechman's exciting new book. Begin with simple designs and progress to more sophisticated projects. Each project comes with a complete discussion of circuit theory and parts list, as well as information on troubleshooting and testing. Build voltmeters and multimeters, inductance and semiconductor testers, variable frequency audio oscillators, a photoelectric counter, and much more!

1-878707-46-9/224 pages/\$19.95



Controlling the World with Your PC

by Paul Bergsman

PC Disk Included! Connect your computer to the real world and make it do useful work like controlling stepper motors, turning appliances on and off, or monitoring fluid levels. PC disk contains software files in ready-to-use form.

1-878707-15-9/208 pages/\$35.00



**The Forrest Mims Engineer's
Notebook**

by Forrest Mims III

This revised edition of Forrest's classic book includes hundreds of useful circuits built from integrated circuits and other parts available from convenient sources.

1-878707-03-5/156 pages/\$19.95



**The Integrated Circuit Hobbyist's
Handbook**

by Thomas R. Powers

Covers the major types of integrated circuit devices—linear, TTL, and CMOS—and provides complete details and theory about their operation. Contains lots of useful application circuits—an essential reference for every hobbyist.

1-878707-12-4/256 pages/\$19.95



Order on the Web!

For these and other great books
on electronics, visit:

www.LLH-Publishing.com

or

call 1-800-247-6553 to use a
major credit card, or send check or
money order to:

LLH

Technology Publishing
3578 Old Rail Road
Eagle Rock, VA 24085



All the parts for the Pot-Box are shown
here, and are available from
Tech America.

discovered Tech America!


Tech America is primarily a mail-order operation with a huge over-500-page FULL COLOR catalog. They have NO MINIMUM ORDER, with shipping only a flat \$4.00 in most cases! And their large selection of parts is perfect for hobbyists and experimenters.

I found EVERY PART for this project in the Tech America catalog, or their monthly flyers, for a total cost under \$25.00! In particular, the potentiometers are perfect for this project: small, linear, easy to mount, and in decade values — 100 ohms, 1K, 10K, 100K, and 1M — for only \$1.75 each. (Unfortunately, I could not find a similar 10-ohm pot or I would have also used that.)

The rotary switch, cabinet, and knobs were almost as I would have designed them myself for this project — although the rotary switch had one unused position, and the inside of the cabinet needed some minor modifications (described later).

The only electrical parts are the potentiometers and switch. If you order the potentiometers in the Parts List, you'll get the right parts, WITH a mounting nut. When I first ordered the potentiometers for this project, they came without mounting nuts, and the mounting bushing was a METRIC size. I spent hours vainly looking for matching nuts. When I complained to Tech America, they made arrangements to now include the nut with each of these potentiometers. They are REALLY into customer service!

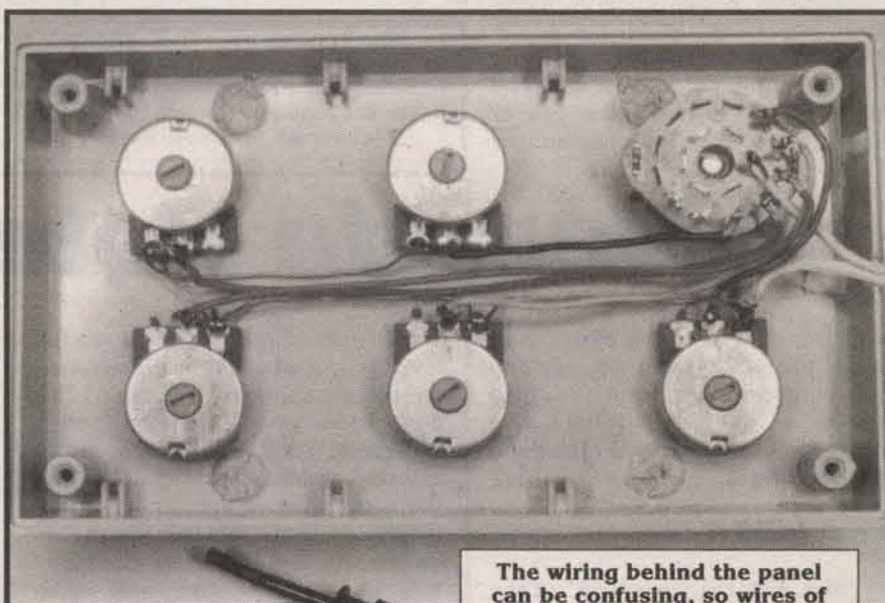If you should order the potentiometers from another source, make sure they are "linear-taper" rather than the more common "audio-taper." The linear-taper pots have a resistance that varies proportional to their rotation, while audio taper pots as they are rotated follow a logarithmic resistance curve.



The wiring behind the panel
can be confusing, so wires of
different colors are used.

I used subminiature IC test clips to make the external connections, since these have tiny hooks at the end for holding onto small leads. You may prefer regular or mini alligator clips, or you may even prefer to use binding posts on the cabinet.


Incidentally, my original over-30-years-ago Pot-Box used dial plates that made it easy to estimate

ingly backward approach of starting with the highest value pot (1M) and ending with the lowest value (100 ohms). But think about it. When using the Pot-Box, you want to start with the HIGHEST resistance (lowest current) for safety, and go to lower resistance (higher current) from there. Therefore, it seems reasonable to use clockwise orientation for increased current. Arguments can be made for other layouts, so suit yourself, since you will be the user.

The entire project is assembled in the upper half of the cabinet. The potentiometers and rotary switch are mounted through holes in the top panel and held in place with the mounting nuts provided.

Looking at the photo of the inside of the Pot-Box, note that the potentiometers and switch can be oriented so that their terminals face toward the center of the box. This simplifies wiring. The switch has a small locking tab to prevent turning; a small hole in the panel is needed for this tab.

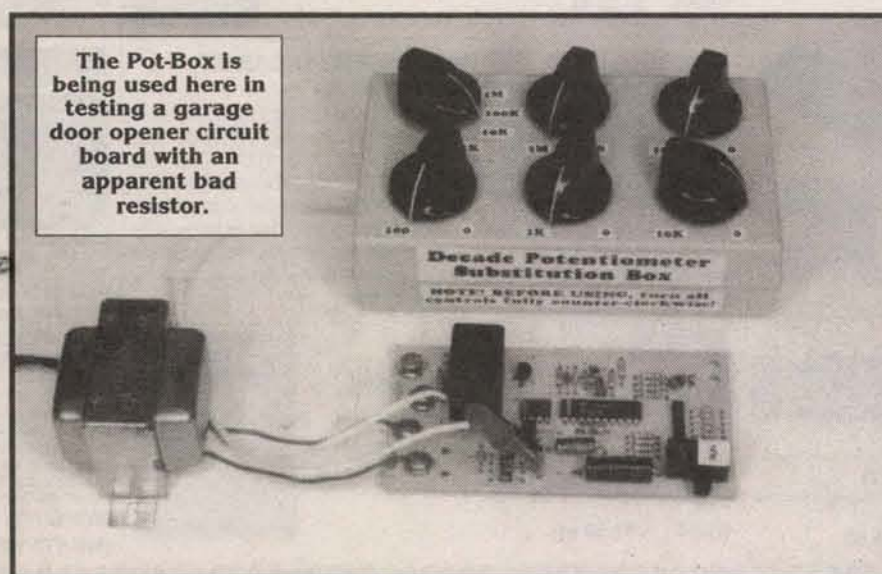The particular BUD cabinet specified in the Parts List has four



The Pot-Box is
being used here in
testing a garage
door opener circuit
board with an
apparent bad
resistor.

internal bosses apparently intended for mounting a circuit board. These interfered with the potentiometers, so using a hot soldering iron, I melted and cut these bosses away.

When wiring, I used bare wire for the "common" connection to each pot. (Looking at the back of the pot, with the terminals at the top, the rightmost terminal is the common for this project.) To eliminate wiring errors to the individual pots, I used a different colored wire (stripped from ribbon cable) between each pot and its center terminal.

Use an ohmmeter to determine the switch terminals for each position. Turning the switch to its full CLOCKWISE position, wire the lowest valued pot (100 ohms) to the active terminal, and then the others in decade sequence. (Using the seven-position switch specified in the Parts List, you'll have two unused terminals.)

Use insulated wire from the wiper terminal of the switch and the potentiometer common connection to the red and black clip leads, P1 and P2. Although there is no real significance here to the black or red test clip, since no polarity is

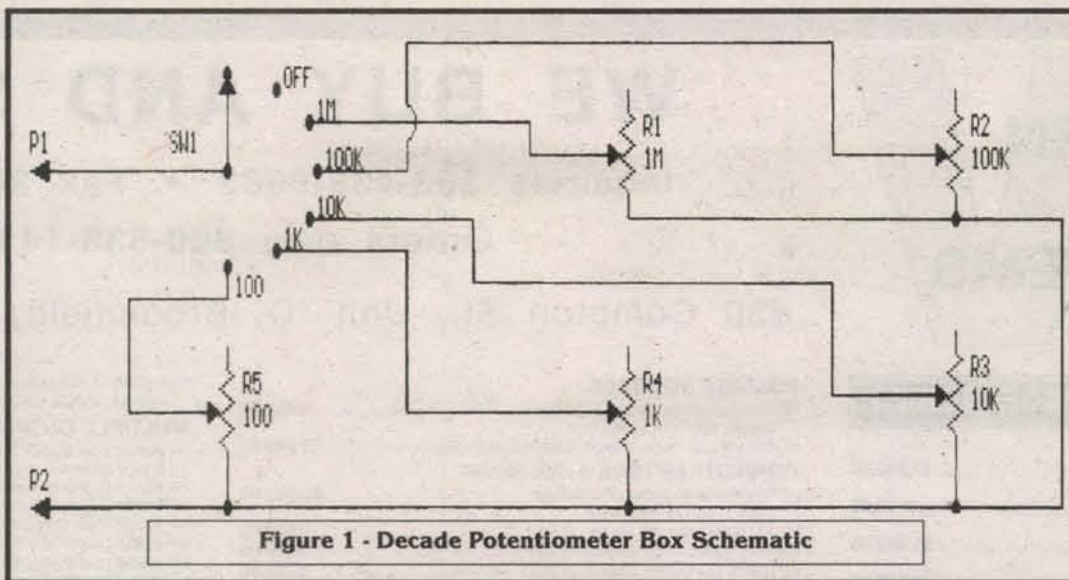


Figure 1 - Decade Potentiometer Box Schematic

involved, I prefer to have the "common" black. A small notch in the edge of the cabinet allows the test clip leads to exit the cabinet.

Now it's just a matter of turning the switch and each pot fully counterclockwise and installing the knobs as shown in the photographs.

Panel markings may be dry-transfer letters, tape labels, or your favorite method. I used a computer desktop publishing program to print the labels, and pasted them to the cabinet with rubber cement.

pots, the knob position gives you a fair indication of value.

Don't be alarmed if your ohmmeter does not show exactly one megohm at one end and zero at the other. These are not expensive, high-accuracy potentiometers.

Once again, I have chosen to start with the highest resistance in the counterclockwise position, so that turning clockwise lowers the resistance. You may prefer to do this the opposite way, in which case you simply wire the common to the OTHER (leftmost) terminal of each potentiometer.

Next, turn the switch to each position and check the resistance reading of each of the pots, both for value and direction of lesser resistance.

Using the Pot-Box

If you are designing a circuit, but not quite sure of the proper resistance to use at a particular place, use one of the pots in the Pot-Box. Set the switch to a pot value higher than your expected resistance and work down from there. After making sure the pot knob is fully counterclockwise, connect the two clip leads from the Pot-Box to the appropriate point in your circuit.

The convenience of the Pot-Box is hard to appreciate until you use it. Since being built over 30 years ago, I've used it repeatedly, from checking meter movements (use a pot in

series with a battery and a known good milliammeter; start with a high value pot and work down), to establishing proper transistor biasing resistor values, finding the right resistance for a desired frequency in an oscillator circuit, and watching the effect of varying the resistance in test circuits of all kinds.

In critical circuits, where a resistance substitution box jumps the gap between the value you need and the next higher or lower box value, the Pot-Box lets you "zero-in" on just the value you

want!

Be aware that the Pot-Box and its leads are not shielded, and may cause oscillation or detuning of high-frequency circuits. Audio circuits should pose no problem.

About the only other precaution you should observe is to stay within the power rating of the potentiometers you use. If you use the suggested 0.4 watt potentiometers, this means not pushing more than about 60 milliamperes through the 100-ohm pot (which only takes 6.0 volts if nothing else is in series) or 20 milliamperes through the 1K pot (about 20 volts). The higher resistance pots would require higher voltages to exceed 0.4 watts.

Still concerned? Then, before connecting the Pot-Box to your circuit, measure the voltage that will be applied to the pot terminals. Multiply that voltage by itself, and divide the result by the maximum pot resistance. The result should not exceed the pot wattage rating. Example: voltage is 9 volts, pot is 1000 ohms; $9 \times 9 = 81$, divided by 1000 equals .081 watts.

Except for the 100-ohm pot, circuits powered by nine-volt transistor radio batteries are no threat, but be careful about how much current you try to shove through the Pot-Box from automobile circuits, which typically draw amperes, or from 117VAC wall power! Although modest in cost and effort to build, the Pot-Box is an experimenter's delight. NV

Parts List

All Part Numbers are from **Tech America**, P.O. Box 1981, Fort Worth, TX 76101-1981. No minimum order, \$4.00 total shipping. Orders: 1-(800) 877-0072; Fax: 1-(800) 813-0087; Support: 1-(800) 876-5292. Internet: www.techam.com.

All potentiometers (R1-R5) are 20mm diameter, 0.4 watts, linear taper, and come with mounting nut. Current price is \$1.75 each:


- R1 - 1M ohm (Tech America 900-5977)
- R2 - 100K (Tech America 900-5974)
- R3 - 10K (Tech America 900-5971)
- R4 - 1K (Tech America 900-5968)
- R5 - 100 ohm (Tech America 900-5965)
- SW1 - Single-pole seven-position non-shortening rotary switch (Tech America 900-7104 \$1.99)
- P1 - Red subminiature test clip (Tech America 910-0229 \$1.30)
- P2 - Black subminiature test clip (Tech America 910-0230 \$1.30)
- Cabinet, 5.63"x3.25"x1.5" (Tech America 910-1245 \$3.74)
- Six Pointer Control Knobs (Tech America 900-2546 \$.64 each)
- Wire, solder, label material

Checkout

Turn all knobs to the extreme counterclockwise position. For the switch, this is straight up. For the pots, this should be at about the seven-o'clock position. Connect an ohmmeter to the test clips. If the wiring is correct, the Pot-Box is OFF, so there should be no resistance reading.

Turning the switch clockwise, the next switch position is also OFF. The next switch position enables the 1M potentiometer. As the 1M pot is rotated clockwise, the resistance should drop from one megohm to about 500K at mid-point, and near zero at the extreme clockwise position.

Since these are linear



Professional 10 HOUR RECORDER

"BUILT LIKE A BATTLESHIP"

- Heavy duty commercial recorder - NOT improvised from consumer models
- 12, 14, and 16 hour models also available
- BUILT-IN voice activation (add \$30)
- Applications information included
- Dimensions: 11.5 x 7.0 x 2.75"

SPECIAL Nuts&Volts Price.. \$159

FREE 40-PAGE SPECIAL EQUIPMENT CATALOG!

COD's OK. Sorry, no credit cards. Free catalog USA only; other countries \$5. Price includes UPS to 48 States on Pre-Paid Orders

Viking International 150 Executive Park Blvd. #4600 San Francisco, CA 94134
Phone: (415) 468-2066 • Fax: (415) 468-2067 • Web: www.vikingint.com

SATELLITE TV - HACKERS 'BIBLE'!

The SECRETS are REVEALED!

- The principles of security
- Descrambler building blocks
- Smart cards, information wars & stupid mistakes
- Cracking codes (includes DirecTV source code)
- Installing and hooking up descramblers
- Video manipulative systems...and much more...

www.baylin.com
or... call 800-483-2423

ORDER via Internet or Send \$60 plus \$4 s/h to:
Baylin Publications, 1905 Mariposa, Boulder, CO 80302
MASTER, VISA & AMEX / COD orders accepted

FREE CATALOG - Satellite TV books, videos and software



576 pages, 6" x 8-1/2"

NEW!
5th Edition

Telephone: 303-449-4551
FAX: 303-939-8720

WESTERN TEST SYSTEMS

WE BUY AND SELL

Inquiries 303-438-9662 • Fax 303-438-9685

Orders only 800-538-1493

530 Compton St., Unit #C, Broomfield, Colorado 80020

OSCILLOSCOPES & ACCESSORIES

OSCILLOSCOPES

HP 54501A 100 MHz 4-ch. Digitizing Oscilloscope, 1 MHz single shot	\$1,250.00
TEK 2236 100 MHz 2-ch. Oscilloscope, w/voltmeter & counter-timer	\$900.00
TEK 2247A 100 MHz 4-ch. Oscilloscope, w/voltmeter & counter-timer	\$1,600.00
TEK 2465 300 MHz 4-channel Oscilloscope	\$2,250.00
TEK 7104 1 GHz Oscilloscope, with 7A29, 7A29-04, 7B10, 7B15	\$3,500.00
TEK 7844 400 MHz Dual Beam Oscilloscope, with 7A24, 7A26, 7B80, 7B85	\$900.00
TEK 7854 400 MHz Waveform Processing Scope, w/7A24, 7A26, 7B80, 7B87	\$1,500.00
TEK 7904 500 MHz Oscilloscope, with 7A24, 7A26, 7B80, 7B85	\$900.00
TEK SC502 15 MHz Dual Trace Oscilloscope, TM500 series	\$375.00
TEK TAs475 100 MHz 4-channel Oscilloscope	\$1,200.00

PROBES

HP 1122A Probe Power Supply	\$150.00
TEK 1101A Accessory Power Supply, for FET probes	\$200.00
TEK P6046 100 MHz Differential Probe	\$650.00
TEK P6150 9 GHz 10X/3 GHz 1X 50 Ohm Probe, SMA(m) output	\$400.00
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$450.00
TEK P6202A 500 MHz 10X FET Probe	\$250.00
TEK P6203 1 GHz 10X Active Probe, for 11000 series	\$375.00
TEK P6701-opt.02 O/E Converter, 450-1050 nm/0-1 mW: DC-700 MHz, ST conn.	\$175.00

CALIBRATION

TEK SG503 Level Generator, 250 kHz-250 MHz, TM500 series	\$600.00
--	----------

WAVEFORM GENERATORS

FUNCTION

HP 3312A 13 MHz Function Generator	\$600.00
HP 3325A 21 MHz Synthesized Function Generator, HP1B	\$1,000.00
HP 3325A-002 21 MHz Function Generator, high voltage output option	\$1,500.00
HP 165A-002,003 Prog. Signal Source, 1 mHz-50 MHz, log sweep, rear out	\$1,750.00
TEK AWG5102 Arb. Waveform Gen., 20 MS/s, 12 bits, 50ppm synthesis <1MHz	\$900.00
TEK AWG5105-opt.02 Arbitrary Waveform Generator, dual channel option	\$1,250.00
TEK DD501 Digital Delay & Burst Gen., for function & pulse gen's	\$275.00
TEK FG501 1 MHz Function Generator, TM500 series	\$225.00
TEK FG502 11 MHz Function Generator, TM500 series	\$300.00
TEK FG503 3 MHz Function Generator, TM500 series	\$250.00
TEK RG501 Ramp Generator, TM500 series	\$175.00
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB	\$750.00

PULSE

BERKELEY NUCLEONICS 7085B Digital Delay Generator, 0-100 mS, 1 nS res., 5 Hz-5 MHz	\$750.00
HP 8007B 100 MHz Pulse Generator	\$650.00
HP 8012B 50 MHz Pulse Generator, variable transition time	\$600.00
HP 8015A-002 50 MHz Dual Output Pulse Generator, gated burst option	\$750.00
HP 8080A/81A/83A/84A 300 MHz Word Generator	\$800.00
HP 8080A/91A/92A/93A 1 GHz Single Channel Pulse Generator	\$950.00
HP 8082A 250 MHz Dual Output Pulse Generator	\$1,250.00
HP 8110A/2x 81103A 150 MHz Dual Output Pulse Generator, HP1B	\$9,000.00
HP 8115A 50 MHz Dual Channel Pulse Generator, HP1B	\$2,750.00
TEK PG502 250 MHz Pulse Generator, Tr<1nS, TM500 series	\$600.00
TEK PG505 100 kHz Pulse Generator, 80 V peak, TM500 series	\$275.00
TEK PG508 50 MHz Pulse Generator, TM500 series	\$500.00
WAVETEK 191 20 MHz Pulse / Function Generator	\$500.00
WAVETEK 802 50 MHz Pulse Generator	\$300.00

VOLTAGE & CURRENT

VOLTMETERS

FLUKE 845AR High Impedance Voltmeter / Null Detector	\$400.00
HP 3456A 6-1/2 Digit Voltmeter, HP1B	\$500.00
HP 3478A 5-1/2 digit Voltmeter, HP1B	\$700.00
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB	\$900.00
SOLARTRON 7081 8-1/2 digit Voltmeter	\$3,250.00
TEK DM5010 4-1/2 digit Multimeter, TM5000 series plug-in	\$300.00
TEK DM501A 4-1/2 digit Multimeter, TM500 series plug-in	\$225.00

CALIBRATION

FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA	\$450.00
FLUKE 515A Portable Calibrator, DC/AC/Ohms, line & battery power	\$900.00
FLUKE 5220A Transconductance Amplifier, DC-5 kHz, 0-20 A	\$3,000.00
FLUKE 731B DC Reference Standard	\$400.00
VALHALLA 2703 AC Volt. Std., 0-120V/10 Hz-100 kHz/120-1200V/10 Hz-1 kHz	\$1,750.00

VOLTAGE SOURCES

HP 6115A Precision Dual Range Power Supply, 50V 0.8A / 100V 0.4A	\$850.00
KEITHLEY 228 Programmable Voltage/Current Source	\$2,500.00

CURRENT METERS & SOURCES

HP 4140B Picometer / DC Voltage Source, without test fixture	\$2,000.00
HP 6177C DC Current Source, to 50 V, 500 mA	\$500.00
HP 6181C DC Current Source, to 100 V, 250 mA	\$500.00
HP 6186B DC Current Source, to 300 V, 100 mA	\$300.00
HP 6186C DC Current Source, to 300 V, 100 mA	\$750.00
KEITHLEY 225 Current Source, 0.1 uA-100 mA, 10-100 V compliance	\$500.00
KEITHLEY 227 Current Source, 1 uA-1 A, 0-50 V compliance	\$800.00
KEITHLEY 261 Picoampere Source	\$375.00
TEK A6303 AC/DC Current Probe, 500 Amps peak	\$850.00
TEK AM503/A6302/TM501 AC/DC Current Probe System	\$1,000.00
TEK CT-5 -opt.05 High Current Transformer for P6021/A6302, to 1000A	\$300.00
TEK P6022 AC Current Probe w/termination, 935 Hz-120 MHz, 6 A pk	\$275.00

IMPEDANCE & COMPONENT TEST

L.C.R.

BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH	\$550.00
BOONTON 72BD 1 MHz Capacitance Meter, 3-1/2 digit display	\$650.00
GR 1689-M 5 digit LCR Meter, 12 Hz-100 kHz	\$1,900.00
HP 4262A-101 3-1/2 digit LCR Meter, 120 Hz/1 kHz/10 kHz test, HP1B	\$1,750.00

STANDARDS

E.S.I. SR1010 Resistance Transfer Standards, 1 Ohm-100 K/step	\$550.00
E.S.I. SR1050-1M Resistance Transfer Standard, 1 Megohm/step	\$2,000.00
GR 1404-A 1000 pF Reference Standard Capacitor	\$700.00
GR 1406 Standard Air Capacitors, GR900 connector, 0.1% acc.	\$375.00
GR 1432-U 4-Decade Resistor, 0-111.10 Ohms, 0.01 Ohm resolution	\$100.00
GR 1433-G 7-Decade Resistor, 0-1.111.10 Megohms, 0.1 Ohm res.	\$275.00
GR 1433-J 4-Decade Resistor, 0-11.110 Ohms, 1 Ohm resolution	\$150.00
GR 1433-K 4-Decade Resistor, 0-1.110 Ohms, 0.1 Ohm resolution	\$150.00
GR 1433-L 4-Decade Resistor, 0-111.100 Ohms, 10 Ohms resolution	\$150.00
GR 1433-N 5-Decade Resistor, 0-11.111 Ohms, 0.1 Ohm resolution	\$200.00
GR 1433-X 6-Decade Resistor, 0-111.110 Ohms, 0.1 Ohm res.	\$250.00
GR 1482-series Standard Inductors	\$200.00
VALHALLA 2724A Programmable Resistance Standard, 0-11 Gigaohms, GPIB	\$1,250.00

HI & LO RESISTANCE

HP 4328A Milliohmeter	\$1,200.00
T.D.R.	
TEK 1502-opt.04 Time Domain Reflectometer, 0-2,000 feet, chart recorder	\$1,400.00
TEK 1503-opt.04 Time Domain Reflectometer, 0-50,000 feet, chart recorder	\$1,400.00

POWER SUPPLIES

SINGLE OUTPUT

HP 6002A-001 0-60 V/0-10 A/200 Watts max. Autoringing Power Supply	\$750.00
HP 6011A Autoringing 0-20 V 0-10 A Power Supply, 1000 W max.	\$1,400.00
HP 6200B Dual Range Supply, 0-20 V 0-1.5 A/0-40 V 0-750 mA CV/CC	\$200.00
HP 6201B 0-20 V 0-1.5 A CV/CC Power Supply	\$175.00
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply	\$200.00
HP 6256B 0-10 V 0-20 A CV/CC Power Supply	\$250.00
HP 6260B-027 0-10 V 0-100 A CV/CC Power Supply, 208 VAC line	\$675.00
HP 6261B-027 0-20 V 0-50 A CV/CC Power Supply, 208 VAC line	\$675.00
HP 6263B 0-20 V 0-10 A CV/CC Power Supply	\$400.00
HP 6266B 0-40 V 0-5 A CV/CC Power Supply	\$400.00
HP 6267B 0-40 V 0-10 A CV/CC Power Supply	\$500.00
HP 6269B-028 0-40 V 0-50 A CV/CC Power Supply, 230 VAC line	\$900.00
HP 6271B 0-60 V 0-3 A CV/CC Power Supply	\$400.00
HP 6281A 0-7.5 V 0-5 A CV/CC Power Supply	\$150.00
HP 6289A 0-40 V 0-1.5 A CV/CC Power Supply	\$175.00
HP 6299A 0-100 V 0-750 mA CV/CC Power Supply	\$200.00
HP 6384A 4.0-5.5 V at 8 A CV/CC Power Supply	\$125.00
HP 6434B 0-40 V 0-25 A CV/CC Power Supply	\$800.00
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply	\$450.00
KEPCO ABC-1500M 0-1500 V 10 mA CV/CL Power Supply	\$125.00
KEPCO ATE 36-30M 0-36 V 0-30 A CV/CC Power Supply	\$900.00
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply	\$375.00
LAMBDA LK-352-FM 0-60 V 0-15 A CV/CC Power Supply	\$600.00
SORENSEN DCR 20-25B 0-20 V 0-25 A CV/CC Power Supply	\$550.00
SORENSEN DCR 600-0.75B 0-600 V 0-750 mA CV/CC Power Supply	\$600.00
SORENSEN SRL 20-12 0-20 V 0-12 A CV/CC Power Supply	\$400.00
SORENSEN SRL 60-8 0-60 V 0-8 A CV/CC Power Supply	\$600.00

TEK PS501-1 Power Supply, 0-20 V, 2 mV res., 400 mA, TM500 series	\$175.00
---	----------

MULTIPLE OUTPUT

HP 6205C Dual Output Supply, 0-40 V 300 mA or 0-20 V 600 mA	\$300.00
HP 6227B Dual 0-25 V 0-2 A CV/CC Power Supply	\$450.00
HP 6228B Dual 0-50 V 0-1 A CV/CC Power Supply	\$450.00
HP 6236B Triple Output Supply, to +/-20 V 0.5 A & 0-6 V 2.5 A	\$375.00
HP 6253A Dual 0-20 V 0-3 A CV/CC Power Supply	\$450.00
HP 6255A Dual 0-40 V 0-1.5 A CV/CC Power Supply	\$450.00
LAMBDA LPD-422-FM Dual 0-40 V 0-1 A CV/CC Power Supply	\$300.00
LAMBDA LPT-7202-FM Triple Output Power Supply	\$450.00
TEK PS5010 Programmable Triple Power Supply, TM5000 series	\$650.00
TEK PS503A Dual Power Supply, TM500 series	\$200.00

MISCELLANEOUS

ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max.	\$350.00
ELGAR 1751B/461 AC Power Source, 0-135 VAC, 1750 Watts, fixed freq. osc.	\$2,000.00
HP 59501B HP1B Isolated DAC/Power Supply Programmer	\$175.00
HP 6825A Bipolar Power Supply/Amplifier, +/-20 V 2 A	\$800.00
KEPCO BOP 20-20M Bipolar Op Amp/Power Supply, to 20 V 20 A	\$675.00
KEPCO BOP 36-5M Bipolar Op Amp/Power Supply, to 36 V 5 A	\$400.00
KEPCO BOP 50-2M Bipolar Op Amp/Power Supply, to 50 V 2 A	\$400.00
TRANSISTOR DEVICES DAL-50-15-100 Programmable Load, 0-50 V, 0-15 A, 100 Watts max.	\$200.00

TIME & FREQUENCY

UNIVERSAL COUNTERS

HP 5315A-001 100 MHz/100 nS Universal Counter, TCXO reference option	\$450.00
HP 5315A-002,003 100 MHz/100 nS Univ. Counter, batt. power & 1 GHz C-ch.	\$650.00
HP 5315A-003 100 MHz/100 nS Univ. Counter, 1 GHz C-channel option	\$550.00
HP 5315B 100 MHz/100 nS Universal Counter	\$500.00
HP 5316A 100 MHz/100 nS Universal Counter, HP1B	\$600.00
HP 5316A-001,003 100 MHz/100 nS Univ. Counter, HP1B, TCXO, 1 GHz C-ch.	\$750.00
HP 5316B 100 MHz/100 nS Universal Counter, HP1B	\$750.00
HP 5334B-010,060 100 MHz Universal Counter, HP1B, OCXO	\$250.00
HP 5335A 200 MHz Universal / Statistical Counter	\$500.00
HP 5364A Microwave Mixer / Detector, for modulation domain an.	\$3,000.00
HP 5371A 500 MHz Frequency & Time Interval Analyzer	\$1,500.00
PHILIPS PM6666 120 MHz/100 nS Universal Counter, GPIB	\$375.00
TEK DC5004 Programmable 100 MHz/100nS Counter/Timer, TM5000 series	\$250.00
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer, TM5000 series	\$400.00
TEK DC5010 350 MHz / 3.125 nS Universal Counter, TM5000 series	\$950.00
TEK DC503A 125 MHz/100 nS Universal Counter, TM500 series	\$275.00
TEK DC509 135 MHz/10 nS Universal Counter, TM500 series	\$275.00

FREQUENCY COUNTERS

EIP 575 18 GHz Source Locking Counter, GPIB	\$1,250.00
FLUKE 7220A-010,131,351 1.3 GHz Counter; battery power, OCXO, and res. mult.	\$500.00
HP 5340A 18 GHz Frequency Counter	\$450.00
HP 5343A-001 26.5 GHz Frequency Counter, OCXO reference	\$3,500.00
HP 5345A/5355A/5356B 26.5 GHz CW/Pulse Frequency Counter	\$3,500.00
TEK DP501 1.3 GHz Prescaler, divide by 16, TM500 series	\$225.00

STANDARDS

HP 105B Quartz Oscillator, 0.1/1.0/5.0 MHz, battery power	\$1,500.00
HP 5061A Cesium Frequency Standard, 0.1/1.0/5.0/10.0 MHz outputs	\$6,500.00
HP 5065A-002 Rubidium Frequency Standard, 0.1/1.0/5.0/10.0 MHz out	\$3,500.00
HP 5087A Distribution Amplifier, 12 outputs at 1 MHz	\$1,500.00
HP 5087A-opt.032 Distribution Amplifier, 12 outputs at 5 MHz	\$1,750.00
HP 5087A-opt.033 Distribution Amplifier, 12 outputs at 10 MHz	\$1,750.00

AUDIO & BASEBAND

SPECTRUM ANALYZERS

HP 3586C Selective Level Meter, 50 Hz-32.5 MHz, 50 & 75 ohms	\$1,500.00
TEK 7L5/L3/R7603 Spectrum Analyzer, 20 Hz-5 MHz, 10 Hz min. res., w/frame	\$1,500.00

DISTORTION ANALYZERS


HP 339A Distortion Analyzer, built-in low distortion osc.	\$750.00
HP 8903A-001 Audio Analyzer, 20 Hz-108 kHz, rear panel input	\$1,500.00
HP 8903B-001,013,051 Audio Analyzer, 20 Hz-100 kHz, C-message, CCITT	\$1,750.00
TEK DA4084 Programmable Distortion Analyzer	\$750.00

RMS VOLTMETERS

FLUKE 8920A True RMS Voltmeter, 180 uV-700 V, 10 Hz-20 MHz	\$450.00
--	----------



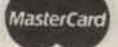90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



FLUKE 8922A True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz \$450.00

OSCILLATORS

HP 209A Sine/Square Wave Generator, 4 Hz-2 MHz, 5 VRMS max \$225.00
HP 3336C Synthesizer / Level Generator, 10 Hz-21 MHz \$1,400.00
TEK SG5010 Programmable Oscillator, 10 Hz-163.8 kHz \$2,750.00
TEK SG502 Sine/Square Osc, 5 Hz-500 kHz, 70 dB step atten., TM500 \$200.00
HP 3575A-003 Gain/Phase Meter, 1 Hz-13 MHz, dual display \$850.00
HP 461A Amplifier, 20/40 dB, 1 kHz-150 MHz, 0.5 V/50 Ohms \$125.00

MISCELLANEOUS

KROHN-HITE 3103 High/Low Pass Filter, 10 Hz-3 MHz, 24 dB/octave \$350.00
KROHN-HITE 3202 Dual HP/LP/BP/BR Filter, 20 Hz-2 MHz, 24 dB/octave \$450.00
KROHN-HITE 3342R Dual HP/LP Filter, 0.001 Hz-99.9 kHz, 48 dB/octave \$900.00
KROHN-HITE 3750 LP/HP/BP/BR Filter, 0.02 Hz-20 kHz, 6/12/18/24 dB/oct. \$600.00
KROHN-HITE DCA-10R 10 Watt Amplifier, 20 dB gain, DC-1 MHz, 600-1000 Ohms \$450.00
ROCKLAND 852 Dual Highpass/Lowpass Filter, 0.1 Hz-111 kHz \$900.00
TEK AM502 Differential Amplifier, 0.1 Hz-1 MHz, TM500 series \$475.00

RF & MICROWAVE

SPECTRUM ANALYZERS

HP 11517A/18A/19A/20A Mixer Set, 12.4-40.0 GHz, for HP 8555A/8569A \$600.00
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz \$1,100.00
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz \$1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz \$1,400.00
HP 11970U WR19 Harmonic Mixer, 40-60 GHz \$1,400.00
HP 853A-001 Spectrum Analyzer, Display, bench/rack mount config. \$1,250.00
HP 8565A-100 Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. \$4,500.00
HP 8568B Spectrum Analyzer, 100 Hz-1.5 GHz, 10 Hz min. res. \$8,500.00
HP 8569B Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. \$7,500.00
TEK TR502 Tracking Generator, 0.1-1800 MHz, for 7L13/7L14 \$950.00
TEK WM782V WR15 Harmonic Mixer, 50-75 GHz \$1,500.00

NETWORK ANALYZERS

HP 11650A Network Analyzer Accessory Kit, APC7 \$600.00
HP 35676A Reflection/Transmission Test Kit, 5 Hz-200 MHz \$1,000.00
HP 4195A Network / Spectrum Analyzer, 10 Hz-500 MHz \$15,000.00
HP 8405A Vector Voltmeter, 1-1000 MHz \$450.00
HP 85020A Directional Bridge, 10-4300 MHz, N(f) test port \$650.00
HP 85021A Directional Bridge, 0.01-18 GHz, APC7 test port \$1,000.00
HP 85021C Directional Bridge, 0.01-18 GHz, N(f) test port \$1,000.00
HP 85025C Detector Adapter, for HP 8757 series \$375.00
HP 85027A Directional Bridge, APC7 test port, 10 MHz-18 GHz \$2,000.00
HP 8502A-H26 Reflection/Transmission Test Set, 4-2600 MHz \$600.00
HP 85044A Reflection/Transmission Test Set, 300 kHz-3 GHz \$1,500.00
HP 8756A Scalar Network Analyzer \$2,500.00
HP R85026A WR28 Detector, 26.5-40 GHz, for HP 8757 series \$1,200.00

SIGNAL GENERATORS

FLUKE 6060A Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB \$1,900.00
FLUKE 6060A/AN Synthesized Signal Gen., 10 kHz-520 MHz, 10 Hz res., GPIB \$1,500.00
FLUKE 6060B/AK Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB \$2,250.00
GIGATRONICS 1018 Synthesized Signal Gen., 50 MHz-18 GHz, 1 MHz res. \$4,500.00
GIGATRONICS 600/10-18 Synthesized Source, 10-18 GHz, 1 MHz res., GPIB \$2,500.00
GIGATRONICS 600/16-12 Synthesized Source, 6-12 GHz, 1 kHz res., GPIB \$2,500.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm \$2,500.00
GIGATRONICS 875/86 Levelled Multiplier, 26.5-40.0 & 50.0-75.0 GHz outputs \$3,750.00
GIGATRONICS 900/2-8 Synthesized Signal/Sweep Gen., 2-8 GHz, 1 MHz res., GPIB \$2,500.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio \$450.00
HP 3335A Synthesizer / Level Generator, 200 Hz-81 MHz \$4,500.00
HP 85100V Frequency Mult., 10-15 GHz in / 50-75 GHz out >0 dBm \$3,750.00
HP 8640B Signal Generator, 0.5-512 MHz, AM, FM, pulse modulation \$1,000.00
HP 8656B-001 Synth. Signal Gen., 0.1-990 MHz, 10 Hz res., OCXO ref. \$2,500.00
HP 8657A-002 Signal Generator, 0.1-1040 MHz, 10 Hz res., HP1B \$3,250.00
HP 8660C/86602B-002 Synth. Sig. Gen., 1-1300 MHz, FM / Phase mod., w/86635A \$2,750.00
HP 8660C/86603A-002 Synthesizer, 1-2600 MHz, FM / Phase Mod., w/86635A \$3,750.00
HP 8672A Synthesized Signal Generator, 2-18 GHz \$6,000.00
HP 8673C Synthesized Signal Generator, 50 MHz-18.6 GHz \$16,500.00
HP 8673G-004, 008 Synth. CW Signal Generator, 2-26 GHz, >+8 dBm output \$12,500.00
HP 8684B Signal Generator, 5.4-12.5 GHz, AM, WBFM, Pulse \$3,500.00

SWEEP GENERATORS

HP 8350A/83545A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step attenuator \$4,000.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, +20 dBm levelled \$400.00
HP 8620C Sweep Oscillator Frame \$550.00
HP 86222B-002 RF Plug-in, 10-2400 MHz, +13 dBm levelled, 70 dB atten. \$1,250.00
HP 86230B RF Plug-in, 1.8-4.2 GHz, +10 dBm unlevelled \$400.00

HP 86240C RF Plug-in, 3.6-8.6 GHz, +16 dBm levelled \$700.00
HP 86241A-001 RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled \$300.00
HP 86242D-004, 008 RF Plug-in, 5.9-9.0 GHz, +10 dBm levelled \$300.00
HP 86250D RF Plug-in, 8.0-12.4 GHz, +10 dBm levelled \$500.00
HP 86260A RF Plug-in, 12.0-18.0 GHz, +10 dBm unlevelled \$500.00
HP 86260A-H04 RF Plug-in, 10.0-15.0 GHz, +10 dBm unlevelled \$500.00
HP 86290A RF Plug-in, 2.0-18.0 GHz, +7 dBm levelled \$1,750.00
HP 86290C RF Plug-in, 2.0-18.6 GHz, +13 dBm levelled \$2,250.00
WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, +12 dBm univld. \$1,250.00
WILTRON 6619A Sweep Generator, 2-8 GHz, +10 dBm levelled \$1,500.00

POWER METERS

ANRITSU MA72B Power Sensor, -20 to +20 dBm, 0.01-18 GHz \$200.00
ANRITSU MP-81B/ML-83A Power Meter, 75-110 GHz (WR10), -20 to +20 dBm \$2,500.00
BOONTON 4200-01A, 03/8-4A x2 Dual Channel Microwattmeter, w/(2) 1 MHz-7 GHz sensors \$950.00
BOONTON 42B/41-4B Analog Power Meter, with 1 MHz-12 GHz sensor \$375.00
BOONTON 42B/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor \$500.00
GENERAL MICROWAVE 476/4240A Power Meter & Sensor, 0.01-18 GHz, -35 to +10 dBm \$300.00
HP 435B/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz \$900.00
HP 435B/8482B Power Meter, 0 to +43 dBm, 100 kHz-4.2 GHz \$1,750.00
HP 435B/8482H Power Meter, -10 to +34 dBm, 100 kHz-4.2 GHz \$900.00
HP 436A-002, 022/8481A Power Meter, rear input & HP1B options, with sensor \$1,250.00
HP 8477A Power Meter Calibrator, for HP 432 series \$500.00
HP K486A WR42 Thermistor Mount, 18.0-26.5 GHz, for 432 series \$350.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/6/7/8 \$1,500.00
HP R486A WR28 Thermistor Mount, 26.5-40 GHz, for 432 series \$350.00
HP R8486A WR28 Power Sensor, 26.5-40 GHz, for HP 435/6/7/8 \$1,500.00

RF MILLIVOLTMETERS

BOONTON 92B-opt.05 RF Millivoltmeter, 10 kHz-1.2 GHz, 75 Ohms scale \$500.00
RACAL 9303 TRMS Level Meter, 10 kHz-2 GHz, -77 to +23 dBm, GPIB \$875.00

AMPLIFIERS, MISCELLANEOUS

AMPLIFIER RESEARCH 1W1000 Amplifier, 30 dB gain, 1-1000 MHz, 1 Watt output \$650.00
BOONTON 82AD-opt.01A Modulation Meter, AM, FM, 10-1200 MHz, GPIB \$750.00
HP 415E SWR Meter \$200.00
HP 465A Amplifier, 20/40 dB, 5 Hz-1 MHz, 1/2 Watt/50 Ohms \$125.00
HP 8447A Amplifier, 20 dB, 0.1-400 MHz, 5 dB NF, +6 dBm output \$375.00
HP 8447E Amplifier, 22 dB, 0.1-1300 MHz, +13 dBm output \$750.00
HP 8447F Preamp/Power Amplifier, 0.1-1300 MHz \$1,200.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz \$2,500.00
HP 8901B-1, 2, 3 Modulation An., 0.15-1300 MHz, rear input, OCXO, ext. LO \$3,000.00
HP 8970A Noise Figure Meter \$4,000.00
HUGHES 1177H02F000 TWT Amplifier, 4.0-8.0 GHz, 10 Watts output \$1,500.00
MICROWAVE SEMI-CORP. MC5112 Noise Source, 25.5 dB ENR, 1.0-12.4 GHz, N(m), +28 VDC \$175.00
ROHDE & SCHWARTZ ESH2 Test Receiver, 9 kHz-30 MHz \$5,000.00

COAXIAL & WAVEGUIDE

AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) "NEW" \$95.00
AVANTEK AMT-400X2 WR28 Active Doubler, 13-20 GHz +10 dBm in, +10 dBm out \$450.00
BAYTRON 3-28-300/10 WR28 Directional Coupler, 10 dB, 26.5-40 GHz \$300.00
BIRD 6735-300 1 kW Load, 25-1000 MHz, LC(f), with wattmeter \$650.00
CONTINENTAL MW. RAE28-K-M WR28 x K(m) Endfire Adapter \$225.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(m/f) \$125.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz \$400.00
GR 900-Q GR900 14mm Interseries Adapters \$125.00
HP 11590A-001 Bias Network, 1.0-18.0 GHz, APC7 \$450.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz \$800.00
HP 3321K Programmable Step Atten., 0-70 dB, DC-26.5 GHz, 3.5mm \$475.00
HP 3332L-006 Programmable Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm \$1,200.00
HP 774D Dual Directional Coupler, 20 dB, 215-450 MHz \$275.00
HP 777D Dual Directional Coupler, 20 dB, 1.9-4.1 GHz \$275.00
HP 778D Dual Dir. Coupler, 20 dB, 100-2000 MHz, N test port \$450.00
HP 778D-011 Dual Dir. Coupler, 20 dB, 100-2000 MHz, APC7 test port \$450.00
HP 8431A 2-4 GHz Band Pass Filter, N(m/f) \$150.00
HP 8470B Crystal Detector, 10 MHz-18 GHz, neg. pol., APC7 \$250.00
HP 8472A Crystal Detector, 10 MHz-18 GHz, neg. pol., SMA \$150.00
HP 8472B Low Barrier Schottky Det., 10 MHz-18 GHz, neg. pol., SMA \$200.00
HP 8494A-001 Step Attenuator, 0-11 dB, DC-4 GHz, N(f/f) \$350.00
HP 8494G-002 Programmable Step Attenuator, 0-11 dB, DC-4 GHz, SMA \$350.00
HP 8495H-002 Programmable Step Attenuator, 0-70 dB, DC-18 GHz, SMA \$400.00
HP 8497K-004 Programmable Step Attenuator, 0-90 dB, DC-26.5 GHz \$750.00
HP K281C-012 WR42 x APC3.5(m) Adapter \$300.00
HP K382A WR42 Direct Reading Attenuator, 0-50 dB, 18-26.5 GHz \$2,900.00

HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz \$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz \$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz \$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz \$300.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz \$650.00
HP R382A WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz \$2,000.00
HP R422A WR28 Crystal Detector, 26.5-40 GHz \$400.00
HP R532A WR28 Frequency Meter, 26.5-40 GHz \$500.00
HP R752A WR28 Directional Coupler, 3 dB, 26.5-40 GHz \$450.00
HP R914B WR28 Moving Load, 26.5-40 GHz \$250.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz \$750.00
HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz \$650.00
HP X870A WR90 Slide Screw Tuner \$150.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz \$900.00
HUGHES 45721H-1000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz \$900.00
HUGHES 45732H-1200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz \$250.00
HUGHES 45772H-1100 WR22 Thermistor Mount, -20 to +10 dBm, 33-50 GHz \$400.00
HUGHES 45775H-1100 WR12 Thermistor Mount, -20 to +10 dBm, 60-90 GHz \$800.00
HUGHES 47316H-1111 WR10 Tuneable Detector, 75-110 GHz, positive polarity \$600.00
HUGHES 47323H-1211 WR19 Flat Broadband Detector, negative, 40-60 GHz \$650.00
HUGHES 47974H-1000 WR15 SPST PIN Switch, 250 MHz speed, 60-62 GHz response \$375.00
KRYTAR 2616S Directional Detector, 1.7-26.5 GHz, K(f/m)/SMC \$200.00
M/A-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, 40-60 GHz \$450.00
MIDWEST MICROWAVE 3537 DC Block, 0.1-12.4 GHz, SMA(m/f) "NEW" \$40.00
MINI-CIRCUITS ZFDC-20-4 Directional Coupler, 19.5 dB, 1-1000 MHz, SMA(f) \$25.00
MINI-CIRCUITS ZHL-42 Amplifier, 30 dB gain, 0.7-4.2 GHz, +28 dBm, 15V, SMA \$400.00
NARDA 3000-SERIES Directional Couplers \$150.00
NARDA 3024 Bi-Directional Coupler, 20 dB, 4-8 GHz \$300.00
NARDA 3090-SERIES Precision High Directivity Couplers \$225.00
NARDA 368BNM Coaxial High Power Load, 500 Watts, 2.0-18 GHz, N(m) \$500.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz \$1,000.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz \$1,000.00
NARDA 4000-SERIES SMA Miniature Directional Couplers \$75.00
NARDA 4245-10 Directional Coupler, 10 dB, 4-12 GHz, SMA(f) \$100.00
NARDA 4799 Level Set Attenuator, 0-15 dB, 4-18 GHz, SMA(f) \$135.00
NARDA 5070-SERIES Precision Reflectometer Couplers \$300.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f) \$165.00
NARDA 769-30 30 dB Attenuator, 150 Watts, DC-6 GHz, N \$275.00
NARDA 792FF Variable Attenuator, 0-20 dB, 2.0-12.4 GHz \$375.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8 GHz \$375.00
OMNI-SPECTRA 2085-6010-00 Crystal Detector, 1-18 GHz, negative polarity, SMA(m/f) \$50.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz \$250.00
SONOMA SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz \$75.00
SPACEK LABS K-2X Frequency Doubler, 9.0-13.25 GHz in / 18.0-26.5 GHz out \$350.00
TRANSCO 705C90100 Latching DPDT Transfer Switch, DC-26.5 GHz, 28 V \$150.00
TRG B528 WR22 Direct Reading Phase Shifter, 0-360 deg., 33-50 GHz \$1,250.00
TRG V551 WR15 Frequency Meter, 50-75 GHz \$600.00
TRG W551 WR10 Frequency Meter, 75-110 GHz \$750.00
WAVELINE 100080 WR28 Terminated Crossguide Coupler, 30 dB \$200.00
WEINSCHEL 1515 Power Divider, 2-Way, DC-18 GHz, SMA(m/f) \$125.00
WEINSCHEL DS109 Double Stub Tuner, 1-13 GHz, N(m/f) \$150.00
WEINSCHEL DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(m/f) \$150.00
WILTRON 60A50-opt.1 SWR Bridge, 5-2000 MHz, APC7, 46 dB directivity \$450.00

COMMUNICATIONS

HP 4935A-003 Transmission Test Set, 20 Hz-110 kHz, battery power \$600.00
HP 59401A HP1B Bus Analyzer \$700.00
TEK 1410R NTSC Gen., w/SPG2 sync generator, TSG7 color bars \$800.00
TEK 1411R PAL Gen., w/SPG12 sync, TSG11 color bars; TSG13 linearity \$750.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16 \$1,000.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG12, TSG13, TSG15, TSG16 \$1,100.00
TEK 1411R-opt.04 PAL Test Gen., w/SPG12, TSG11, TSG11, TSG13, TSG15, TSG16 \$1,400.00
TEK 1420 NTSC Vectorscope \$600.00
TEK 147A NTSC Test Signal Generator, with noise test signal \$800.00
TEK 148 PAL Insertion Test Signal Generator \$700.00
TEK 520A NTSC Vectorscope \$750.00
TEK 521A PAL Vectorscope \$750.00

MISCELLANEOUS

FLUKE 2625 Hydra Data Logger \$1,250.00
P.A.R. 5206-95, 98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB \$1,500.00
P.A.R. 5209 Lock-in Amp., 0.5 Hz-120 kHz, 130 dB dynamic reserve \$2,000.00
TEK TM5006 5000-series 6-slot Programmable Power Module \$600.00
TEK TM504 500-series 4-slot Power Module \$175.00
TEK TM506 500-series 6-slot Power Module \$250.00
TEK TM515 500-series 5-slot Traveller Power Module \$275.00

COMPUTER CIRCULATION CENTER, Inc.

dba: Alltech Electronics

2618 Temple Heights Drive.

Oceanside, CA 92056

Phone Order Hours 9AM - 5:30PM Mon-Fri

Phone Orders

760/724-2404

\$25 -Min. Order -



9350 Clairemont Mesa, San Diego - 619/573-0411

1401 El Camino Real. Oceanside - 760/721-0093


1300 E. Edinger. Santa Ana - 714/543-5011

2018 W. Lomita BLVD. Lomita - 310/539-2260

We buy surplus & excess computer inventory as well as scrap electronics related inventory.

Save on your Point of Sale systems with these refurbished and new components.
 9" Monochrome VGA NEC "NEW" 640 x 480 \$79.00
 10" SVGA COLOR View Magic .26 dp Refurb (upto 1024 x 768) \$139.00
 10" SVGA Color (Open Frame - Build a custom enclosure) \$119.00
 Fujitsu Cash Drawer NEW w/dtl. 24VDC Trigger for drawer \$79.00
 Cash Drawer - Epson Printer - 9" Mono VGA \$199.00
 Cash Drawer - Epson Printer - 10" Color SVGA .26 dp \$299.00
 Compact footprint 83 Key keyboard - PS/2 Type \$14.95
 Epson TM300PD Parallel Receipt Printer (2 Color) Refurb \$89.99

Point of Sale Hardware

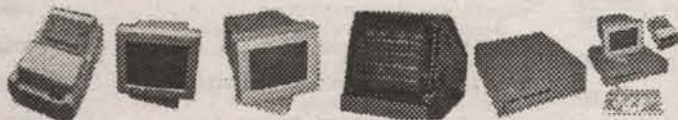

Be sure to check our Web Site for more information on these and other products!

www.allelec.com

Mitsubishi DJ-1000 Digital Camera

Pocket Size

Holds up to 15 images

320 x 240 or 504 x 378

PCMCIA Required for image downloading.

Windows 95/98 Compatible

See the web for more details



\$79

NEC Mini 486



Need a Linux Box?
\$29.00

Mini footprint
3.5" x 11.5 x 13
486 SX 25 CPU
4MB On board
2 ISA Slots
IDE, FD, 2
COM, 1 LPT &
512K VGA
Great for a
Firewall box.

10" Color SVGA!

Up to 1024 x
768 pixels
110V AC
operation.

ViewMagic



Refurb:
\$139.00

Intergraph 4MB PCI Intense 3D 100


\$35.00

Rendition
V1000e



3D Accelerated
Video Card for
Windows 95/NT
See Web for
more details

Color Scanner

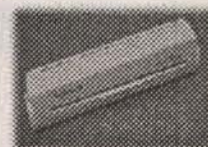

24 Bit • 300 dpi
Parallel Port
with pass
through for
printer.
Windows
95/98, 2.2lbs.
Great for
Laptops!

\$39.00



\$39.00

Supports both
Macintosh and
SVGA Monitors.
Upgradable to
4MB

Macintosh 2MB PCI
ATI Mach64 Video Card



\$29.00

Home network?
Cable Modem?
Linux Box?
Various Brand
10BaseT 8 Port
Hubs.

Refurb 8 Port Hub

Motorola Flip Phone Data Adapter



\$39.00

RJ-11 (Dial Tone)
Generator and Ring
Generator. Use any
standard land line
device with your cell
phone. Modem, credit
card terminal,
answering machine...

External SCSI Cases \$29.00 & Up



5.25" Closed HH \$29.
5.25" Open HH \$35.
5.25" Open FH \$45.
3.5" Open for Zip,
Syquest, etc... \$29.
3.5" Lunchbox \$19.
All cases have two 50
pin centronics
connectors.



Small 105V 40 RPM Motor. 2.7W

\$9.95



Motor with spin-
dle. Items can be
press fit. Shaft
has a through
hole with a rod
stuck in it.



\$9.95

Robotic
Attachments?
Arms, etc?
With rubber o-
ring on 5" dia.
disc.

Small DC Motor
w/gear box & Wheel

Large AC Motor.
Use for robotic
drive or ??
Has 5" disc
attached with a
rubber O-Ring.

\$9.95



Reversible 110V AC
Motor with brake



\$69.00
24 pcs

360 degree
rotatable. Ball
Bearing for
durability.
These were
from heavy
duty mobile
storage units

Used 3" Dia. Wheels

CPUs


486SX 25/33 \$3.00 ..\$5.00
486SX2-66 \$8.00
486DX25/33 \$5.00 ..\$8.00
486DX2-50/2-66 \$14.00 ..\$19.00
486DX4-100 \$39.00
Pentium 75/90 \$39.00 ..\$49.00
Pentium 100 / 133 \$59.00 ..\$69.00
Pentium 166 \$79.00

Upgrade
Your
System



EPROMs

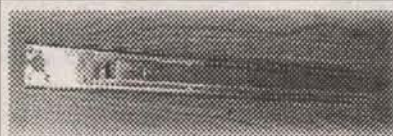2716 /2732 \$1.25
2764 /27128 \$1.25
27256 /27512 \$1.50
1Meg \$2.50
2 Meg \$2.50



6 pair for
\$29.00

Extends to 2'
past. Two slide
telescopic
extension

Ball Bearing Drawer Slide

IDE Hard Drives

420 Meg \$49.00
320 Meg \$39.00
270 Meg \$29.00
120 Meg \$20.00
80 Meg \$15.00
40 Meg \$10.00



PC Oldies but Goodies

EGA/CGA Card -or- ISA Super I/O \$14.95
2 Meg AT Memory Card - or - Parallel/Mono Card \$9.00
Floppy Controller -or- Serial / Parallel Card \$6.95
VLB 1 Meg VGA Card - or - 386 Motherboard w/2 Meg \$19.95
16 Bit (ISA) VGA w 256/512/1 Meg \$9.00 / \$12.00 / \$14.95
VLB Super I/O \$12.95
8 Bit VGA Card - or - XT Motherboard w/640K \$9.95

See Our Website for
for more details on these
industrial surplus items.

Robot Competition? Feeling
creative? Build something!

CD ROM & Sound Cards


4x IDE Internal \$19.00
8x IDE Internal \$29.00
24x IDE Internal with Yamaha Sound Card (ISA) \$49.00
4x SCSI Internal \$25.00
4x SCSI External \$49.00
Universal Audio Cable (CD ROM to Soundcard) \$4.95

HTTP://WWW.ALLELEC.COM

VISIT OUR WEB PAGE DAILY FOR SPECIALS & MORE INFO. ON THESE ITEMS

STAMP APPLICATIONS

by Lon Glazner

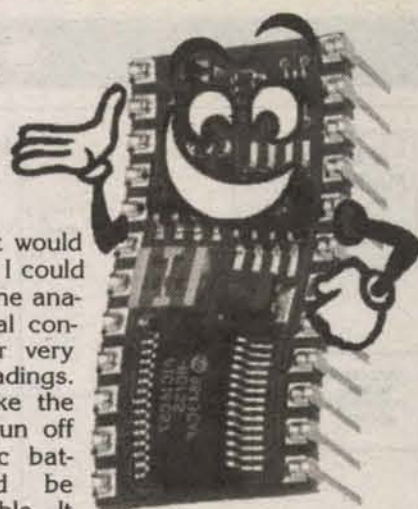

Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

One Step Beyond the Application Note

Overview

Application notes are generally a good starting off point for many designs. It's always nice if you can learn from example. There's nothing wrong with learning from your own mistakes, but it's usually beneficial if you can avoid as many as possible. More importantly, there's no reason to re-invent the wheel, especially in electronic engineering.

I'd like to share with you a process that I use when starting a design, and then walk you through an example. When I'm embarking on a design that utilizes an IC or processor that's new to me, I try to ensure that I do three things before any actual design work begins.

First, I download or order the data sheets for the part in question. If the part is not going to meet your design requirements, you will probably find this out by reading the first few pages of the data sheet.

The general description on the first page is usually a glowing report detailing all of the wonderful things that the device can do. This description overtly avoids any discussion of a particular part's shortcomings. Rest assured the information is available, it's just not on the front page. What you can find out from the general description are the key features of a product. If these features seem to meet your design's needs, then you've cleared the first hurdle.

Next, check the maximum ratings of the part in question. Supply voltages, operating current, and operating speeds can all be found either in the maximum ratings section or in the electrical characteristics that usually follow in table form. When dealing with families of parts that are all fairly similar, the manufacturer usually has a selector guide with a cross-reference. This selector guide can be useful in weeding out undesirable parts.

Second, once a cursory overview has shortened the parts list, I always search for application notes that reference the parts I am interested in. Often times, the list of application notes is pretty large. This is the case with the BASIC Stamp. Not only does Parallax provide application notes and

kits for use with the BASIC Stamp, there are also third party sources for application notes (see Figure 6).

Sitting down and actually reading all of the application notes for a particular product would be time consuming and inefficient. I definitely don't recommend that path to anyone. But it is usually a good idea to familiarize yourself with the application notes that are available. Being able to reference source code or connectivity information from an application note can cut hours out of your design time, and reduce the possibility of errors in the final product.

The third — and final — step in the process of selecting a chip is to look for an errata sheet for the part. An errata (error-data) sheet will usually state errors in the original data sheets and/or provide updates due to bugs in the part's silicon. These can KILL you. Primarily because they won't be listed in hard copies of the data sheet that you might already have. This allows functional problems to seep into your design or create hours of misguided debugging attempts. Always look for an errata sheet! Most manufacturers make these available as soon as the problem is defined. I also check to be sure that any part I am selecting has not been placed on an obsolete part list. There's nothing worse than completing a design that can't be produced.

For the Stamp enthusiast, some of this stuff doesn't matter. For example, if you're designing a pump controller for your fish tank, you're better off using what you have on hand. In other words, who cares if you're using an obsolete part, if it's free and already in your tool box, you might as well use it.

Defining The Design

I just started designing a new product. In our company, we usually go through a complete paper design, cost estimate, and functional overview prior to any parts hitting the breadboard. I'm still in that paper design phase but, of course, I'm looking ahead at the testability of my prototype. And that's where the BASIC Stamp comes in.


I need a device that will take voltage measurements of a single AA NiCad battery. Initially, the accuracy of the measurement doesn't need to be that stellar.

But later it would be great if I could fine tune the analog-to-digital conversion for very precise readings. I would like the tester to run off of a 9Vdc battery, and be semi-portable. It should also be expandable. For starters, I need to measure at least two voltages; future expansion of up to six voltages is desirable. The voltage data should be transferable to a PC for graphical analysis. And finally, I would like to be able to adjust the period between voltage measurements (the sample period). If I were to list the functions I'm looking for they would appear as they do below.

- Eight-bit analog-to-digital (A/D) conversion
- 2-6 A/D measurements
- 0-2Vdc range for each measurement
- Single supply derived from 9Vdc
- Serial data capability
- Adjustable sample period

Beyond the functional description, I need to be a little concerned about pricing. This is a test set-up for a product that may or may not go into production. So spending too much on the set-up would be a bad idea. In that same vain, spending too much time on the design would tend to eat up company resources. To me, this design has BASIC Stamp written all over it. It's usually good to have a block diagram of all functionality in a design. Figure 1 is the initial block diagram that I came up with.

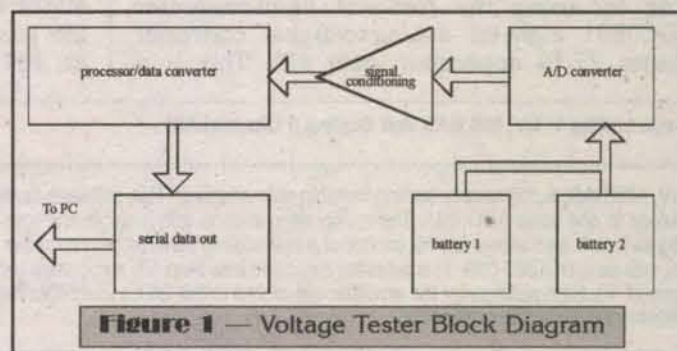There are a couple of things that immediately become apparent from the block diagram. The first is that the BASIC Stamp can suffice as both the processor/data converter and the serial data



MoTron Electronics
PO Box 2748
Eugene OR 97402-0280
(541) 687-2118
<http://www.motron.com/>

The Auto-Kall® AK-32 Radio Telemetry/Control Boards are designed for remote control applications where direct wiring is impractical. By implementing a radio interface, the AK-32 offers both a wireless and economical solution. The AK-32 boards work in pairs and can be used for bi-directional control and contact monitoring applications. The AK-32 will work with any FM Communications or Amateur Radio transceiver (Appropriate licenses required.) The AK-32 features 16 inputs and 16 open-collector outputs designed to control 12V relays. Outputs can be connected to any of the MoTron line of Relay Boards. Programming the boards is accomplished with any DTMF source, and will retain the data in the EEPROM until reprogrammed. For additional information, visit our website, or call us at (541) 687-2118.




Info: (541) 687-2118


Visa, MasterCard, American Express, Discover and Government Purchase Orders accepted.
S/H: \$8 USA; \$11 Canada; \$16 Foreign.
Se Habla Español. Pida Por Don Moser.

Orders: (800) 338-9058 Fax: (541) 687-2492

\$249.00
plus shipping

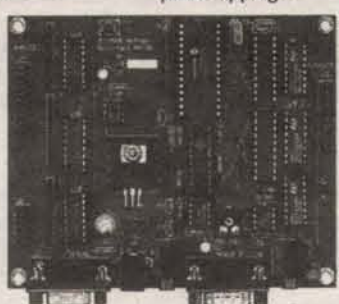

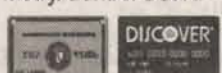Auto-Kall® AK-32
Radio Telemetry/Control Board



Model PTS-10
\$55




LIFETIME WIRE STRIPPER, a breakthrough in wire stripping technology. Extremely fast tool will strip PVC insulation #14 to #30 AWG from solid, stranded or shielded wires. High quality strip is achieved by patented stripping element (.008" thick) which thermally cuts the insulation all the way to the conductor without nicks. Five year test, with over 2 million stripped wires, using the same element, speaks for itself. The stripper has won a —

"FIVE STAR PRODUCT OF THE MONTH"
award in DESIGNFAX magazine. Strippers for TFE, KAPTON, KYNAR, SILICONE RUBBER, etc. and rechargeable, battery powered strippers also available.

PATCO Service, Inc., 2515 Glencoe Rd., Baltimore, MD 21234
(410) 444-4010 Fax (410) 254-9566

STAMP APPLICATIONS

Figure 2
MM74HC4051
Functional
Diagram

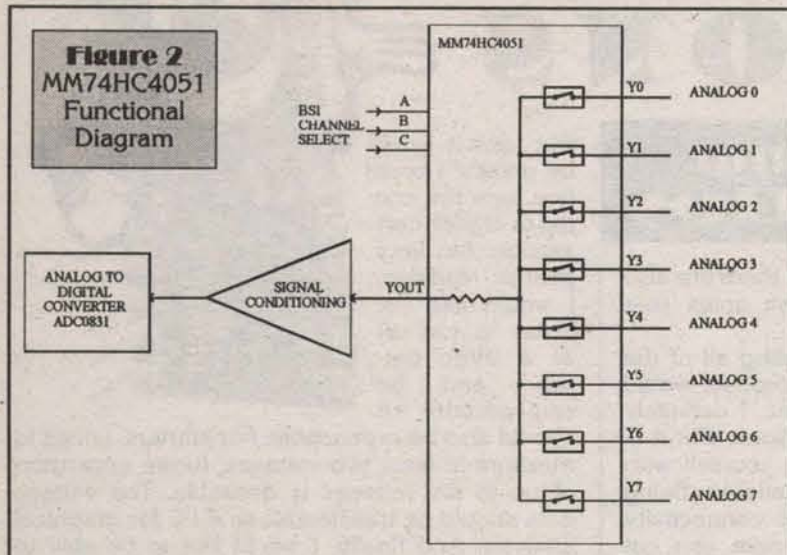

out block. I want the data to be sent to a PC in ASCII format. In this way, I can easily read it as a terminal program displays the data. This should also be something that the BASIC Stamp can accomplish.

I also realized from the block diagram that I will either need multiple A/D converters or some means of multiplexing the analog signals onto a single A/D. The latter concept is the least costly in parts so, for now, I'll be leaning towards that method. This device will likely require some conditioning of the analog voltage to be measured. The signal conditioning may be filtering, amplification, just plain buffering, or all of the above. To further minimize pricing, I'll be using the BASIC Stamp I (BS1). Most, if not all, of the functionality I desire can be derived from the BS1. So, at this point, I went to work scribbling furiously and perusing data sheets, and this is what I came up with.

Analog Multiplexing

Here's where the application notes come in. I know from being familiar with my Parallax BASIC Stamp manual that there is an application note for using the National Semiconductor ADC0831 eight-bit analog-to-digital converter (pages 77-79 application note #2). This is a

single supply, single channel, eight-bit A/D. I just happen to have a few of these lying around, so that definitely fits my budget.

These parts utilize a serial data protocol that is compatible with NSC MICROWIRE, and is easily interfaced to the BS1. Since these parts can share serial data and clock lines, I could easily just hook-up six ADC0831 and, with a little "glue logic," I could select the A/D I want to read a voltage from with the BS1. But not only would this require multiple A/Ds, I would also have to duplicate my signal conditioning for each A/D. There is a

better way. With a low-cost chip — the MM74HC4051 from Fairchild Semiconductor — I can multiplex up to eight analog signals onto a single A/D device.

Figure 2 is a functional diagram of how the MM74HC4051 fits into the circuit. With this chip, you can easily multiplex analog signals to a single A/D converter. There is an internal resistance that is associated with each switch. This creates the need for the signal conditioning circuit to possess at least a voltage follower as its first element. More discussion on this comes later. The logic family that I chose allowed signal levels from +6Vdc to -6Vdc to be passed by the analog switch. There were other forms of this chip (different logic families) that could operate off of +15Vdc, which I have to say intrigues me. But I'll leave that for a later date.

Signal Conditioning

As mentioned earlier, the analog multiplexer requires a voltage follower, or buffer, to ensure that the next section of my signal conditioning is not affected by the analog switch resistance. In reading through the data sheets for the MM74HC4051, I noticed that the resistance of the analog switch varies with the input voltage, as well as the voltage differential between the

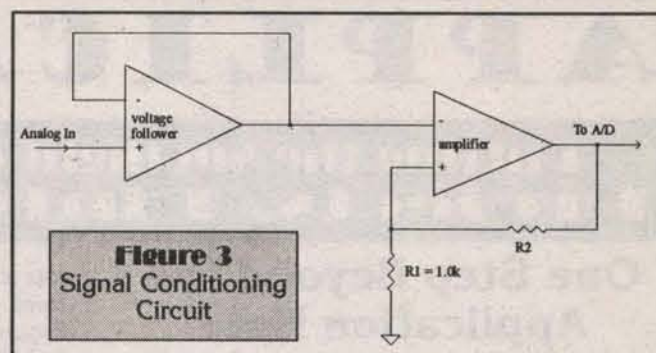


Figure 3
Signal Conditioning
Circuit

lower rail of the analog switch and its upper rail. This kind of characteristic is what you should look for in the data sheet. It tells me that unless I isolate this resistance from any filters or amplifiers, I will probably lose some accuracy in my measurements.

I chose the signal conditioning circuit in Figure 3 for a couple of reasons. The previously mentioned analog switch resistance explains the voltage follower. But the voltage follower is also in place to prevent the analog switch resistance from affecting the gain of my amplifier block. I realized early on that if the eight-bit A/D was measuring over a 5Vdc range, and my input signal was less than 2Vdc, about half of the A/D's measurement range would be unused. For that reason, I included a non-inverting amplifier stage. The gain for this amplifier can be defined as $1 + R2/R1$. For instance, if I set R2 to 1.0K ohms, then my gain would be $1 + (1000/1000) = 2$. So if my input signal was 1.5V, the signal I would be measuring would be 3.0V.

It was at this point in the design that I recalled a BASIC Stamp application note written by Scott Edwards, of Scott Edwards Electronics fame. Scott also used to write this column for *Nuts & Volts*. The application note that I'm speaking of described the Dallas Semiconductor DS1267 digital potentiometer, which just happens to use a serial interface similar to the ADC0831. Since both of these devices use the same communication interface, it's feasible to place them on the same bus (share the clock and data lines). Furthermore, it dawned on me that by replacing R2 in the signal conditioning circuitry with a digitally-controlled potentiometer, I could have an intelligent amplifier. This amplifi-

Code Listing 1: NV_499.BAS Self Scaling 8 Channel A/D

'NV_499.BAS: Automatically scaling variable gain amplifier. This software multiplexes 8 analog input values to one serial ADC0831. The multiplexing is done with a single low cost MM74HC4051 analog switch. It also allows for the control of a self scaling variable gain amplifier based on an LM358 as well as a DS1267-010. This amplifier exhibited less than 5% error when using its maximum gain of 10. Gain settings for the amplifier are stored in the BS1's EEPROM memory, and were determined in the lab empirically.

'BS1 Pin Definitions:

SYMBOL	CLK	= 7	'Serial clock line
SYMBOL	DAT	= 6	'Serial data line
SYMBOL	DATpin	= pin6	'Symbol for data line pin
SYMBOL	CS_AD	= 5	'Chip select for ADC0831
SYMBOL	CS_POT	= 4	'Chip select for DS1267-010
SYMBOL	SDATA	= 3	'Pin reserved for serial data output
SYMBOL	C	= 2	'A/D channel select MSB pin
SYMBOL	B	= 1	'A/D channel select pin
SYMBOL	A	= 0	'A/D channel select LSB pin

'BS1 Variable Definitions

SYMBOL	DSpots	= W0	'Word variable for DS1267-010 dual pot settings
SYMBOL	DSpots0	= B0	'Pot 0 settings variable
SYMBOL	DSpots1	= B1	'Pot 1 settings variable(not used in this code)
SYMBOL	AD_sel	= B3	'A/D channel select variable
SYMBOL	Clocks	= B4	'Clock bit counter variable for serial communication
SYMBOL	AD_in	= B5	'A/D input variable used to store A/D measurements
SYMBOL	Gain	= W3	'Stores EEPROM address of pot settings for various gains
SYMBOL	AD_data	= W4	'Displays voltage in 100's of micro-volts

START:


WRITE	8,235	'Pot 0 setting for a gain of 10 stored at EEPROM address 8
WRITE	7,214	'Pot 0 setting for a gain of 9 stored at EEPROM address 7
WRITE	6,186	'Pot 0 setting for a gain of 8 stored at EEPROM address 6
WRITE	5,158	'Pot 0 setting for a gain of 7 stored at EEPROM address 5
WRITE	4,126	'Pot 0 setting for a gain of 6 stored at EEPROM address 4
WRITE	3,98	'Pot 0 setting for a gain of 5 stored at EEPROM address 3
WRITE	2,66	'Pot 0 setting for a gain of 4 stored at EEPROM address 2
WRITE	1,38	'Pot 0 setting for a gain of 3 stored at EEPROM address 1
WRITE	0,10	'Pot 0 setting for a gain of 2 stored at EEPROM address 0

GOSUB	ANALOG	'Load first analog measurement
AD_SEL	= 0	'Pre-set A/D channel to 000
PAUSE	1000	'Allow a little time for power up

BEGIN:		
GOSUB	SELECT_AD	'Select A/D channel with pins A,B,and C
GOSUB	SET_GAIN	'Set gain and take A/D measurement
GOSUB	TRANSLATE_DATA	'Translate data into 100's of micro-volts and display
GOTO	BEGIN	

'SELECT_AD: This subroutine cycles through the 8 different analog channels. The pin values are 'reset with each pass through to ensure that the correct A/D is selected. The channel being 'accessed is located in the variable AD_sel.

SELECT_AD:		
PINS	= %11101000	'Clear lowest three bits, pins A,B, and C
PINS	= PINS + AD_sel	'Add AD_sel(0-7) to PINS register
DEBUG	AD_sel	'Display current channel selected
AD_Sel	= AD_sel + 1	'Increment channel number for next time through
IF	AD_sel = 8 THEN Zero_AD_sel	'Make sure AD_sel never exceeds 7
RETURN		
Zero_AD_sel:		

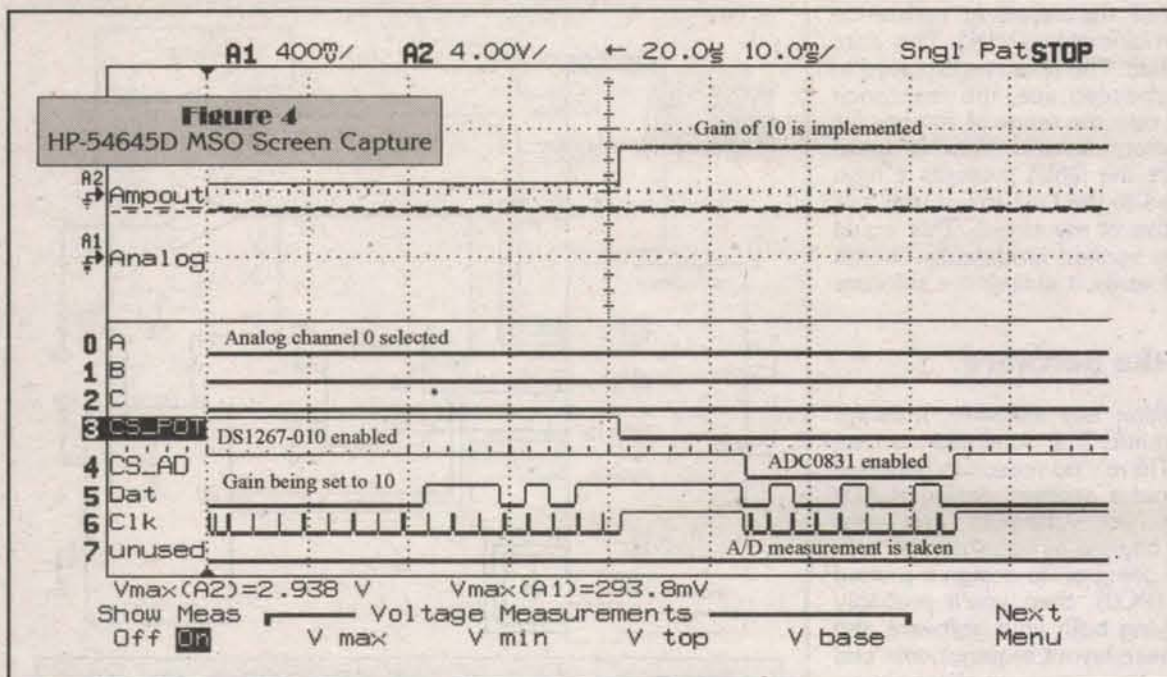

er could scale its gain up or down for more accurate measurements. Now things started to get interesting.

Before going any further, I needed to select a low-cost operational amplifier (op-amp) for my signal conditioning circuit. Ideally, the op-amp should come in a dual or quad pack (two or four op-amps per chip). It should also be capable of single supply operation. Finally, an op-amp with rail-to-rail output (output ranges from roughly 0Vdc to +5Vdc) would be desirable to give me access to the full range of the A/D's eight-bit measurement.

There are a handful of other important characteristics useful in selecting an op-amp. These range from operating current to gain-bandwidth. Since I'm just amplifying DC voltages, most other characteristics are not entirely relevant to my design. I found a National Semiconductor part — the LM358 dual op-amp — that seemed to fit the bill for this design. In choosing this part, I opted to live without a rail-to-rail output. This is just another example of the kind of trade-off you

typically make during a design. I made sure that this part was pin-for-pin compatible with other rail-to-rail output op-amps in case I changed my mind at a later date.

The DS1267 digital potentiometer that I used was the 10K ohm version. There's a bit of a trick to using these parts for a design like this. When I first used this part, I measured the resistance across the part at both of its end points (with the pot set to 0 and 255 by the BS1). I found the resistance ranged from 500 to 9500 ohms. This led me to deduce that the wiper resistance was roughly 500 ohms. In reading the data sheet, I found that the wiper resistance for these parts can range from 400-1000 ohms. The actual resistance exhibited is related to the voltage at the wiper, which is related to the setting of the digital pot. But guess what, there's no place in the data sheet that actually described how this resistance was related to the voltage on the wiper. This required a little lab work.

I modified the DS1267 application note to step through resistance settings in steps of 10,

Online Sources for Application Notes:

The following companies and individuals provide online application notes for use with the BASIC Stamp. If you're looking for a forum to ask questions about BASIC Stamps, try joining the Stamp List that is hosted by Parallax. You can find out more about this list at Parallax's website.

Parallax — www.parallaxinc.com

Parallax created the BASIC Stamp. BASIC Stamps, application notes, third-party products, and kits are available from Parallax.

Nuts & Volts — www.nutsvolts.com

Nuts & Volts provides copies of the Stamp Applications article all the way back to 1996 at their website.

Solutions Cubed —

www.solutions-cubed.com

Solutions Cubed provides application notes for Miniature Engineering Modules to be used with the BASIC Stamp.

Scott Edwards Electronics —

www.seetron.com

Scott Edwards Electronics has application notes, products, and kits all for use with the BASIC Stamp.

Al Williams (AWC) — al-williams.com

Al (AWC) provides the Stamp Project of the Month, as well as an FAQ list and products for use with the Stamp.

Bob Blick —

www.bobblick.com/bob/stamp/

Bob's got quite a few cool applications for BASIC Stamps, as well as a site ripe with interesting uses of technology.

Beau Schwabe —

www.ionet.net/~bschwabe/index.html

Beau's one of the resident answer guys on the Stamp List; he's also got a list of application notes longer than my arm..

```

AD_sel = 0          'Return AD_sel to 0
RETURN

*****
'TRANSLATE_DATA: This subroutine translates the A/D data into a value in 100's of micro-volts.
'This is done to retain maximum resolution of the measurement. Simply divide the result returned in
'AD_data by 10,000 to determine the measurements value in volts.

TRANSLATE_DATA:
LET AD_Data = AD_in * 196 'Scale up A/D measurement by 10E3*8 bit A/D step(19.6mV/step)
LET AD_data = AD_Data / Gain 'Divide measurement by Gain value (10 to 2)
DEBUG AD_data,CR 'Display result to debug screen
RETURN

*****
'SET_GAIN: The SET_GAIN routine cycles through the gain values from 10 to 2. Any measurement
'that is returned that is below the upper rail of the op-amp is considered valid. The LM358 upper rail
'is 3.5V. With a minimum gain of two the greatest voltage that can be measured is 1.75Vdc. By
'changing to a rail-to-rail output op-amp such as the LMC6132 this range can be increased to
'2.5Vdc. A voltage divider could also scale down voltages, and allow larger voltages to be measured.

SET_GAIN:
Gain = 9 'Start gain test at (9-1+2) or 10
Gain_test:
IF Gain = 0 THEN Done_with_gain
LET Gain = Gain - 1
READ Gain,DSpots0 'Check for minimum gain setting
GOSUB OUTPUT 'Subtract one from exiting Gain register
GOSUB ANALOG 'Use result as address pointer for EEPROM READ
IF AD_in > 178 THEN Gain_test 'Set potentiometer to desired gain level
Done_with_gain: 'Read analog to digital converter
LET Gain = Gain + 2 'Test for value greater than 3.5V(op-amp upper rail)
DEBUG Gain,CR 'Actual gain is Gain reg. + 2
PAUSE 10 'Display Gain selected
RETURN

*****
'OUTPUT: This subroutine was taken directly from a Scott Edwards application note. It is also simi-
'lar to the analog subroutine except that 17 bits are transmitted.


OUTPUT:
LET DIRS = %11111111 'Make all pins outputs
HIGH CS_POT 'Select DS1267-010
LOW CLK
LOW DAT
PULSOUT CLK,10
FOR CLOCKS = 0 TO 15
LET DATpin = BIT15
PULSOUT CLK,10
LET DSpots = DSpots * 2
NEXT
LOW CS_POT
HIGH CLK
PAUSE 10
RETURN

*****
'ANALOG: This subroutine was taken directly from the Parallax application note #2 from their data
'sheet. Notes on this application note can be found on pages 77-79 of the Parallax BASIC Stamp
'data book.

ANALOG:
LET DIRS = %10111111 'Make DAT pin an input
LOW CLK
LOW CS_AD 'Select ADC0831
PULSOUT CLK,10
LET AD_in = 0
FOR CLOCKS = 0 TO 7
LET AD_in = AD_in * 2
PULSOUT CLK,10
LET AD_in = AD_in + DATpin
NEXT
HIGH CS_AD 'De-select ADC0831
HIGH CLK
RETURN

*****END:
'End of program space
    
```


Order Today!

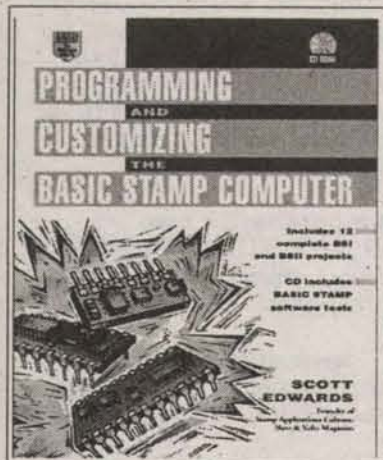

"PROGRAMMING AND CUSTOMIZING BASIC STAMP COMPUTERS"

by Scott Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.

ONLY \$34.95

As a paid subscriber to *Nuts & Volts*, you'll receive **10% off the list price!!**

(See ad page 10 for details.)

Look Ma, No BASIC Stamp*

PicBasic Compiler - \$99.95

Put BASIC Stamp I programs right into a PIC microcontroller - no BS1 module necessary! The programs run faster and can be longer. You also get more variables and extra instructions. For mid-range PIC12C67x, 16C55x, 6xx, 7xx, 8x, 9xx.

PicBasic Pro Compiler - \$249.95

PicBasic Pro is BASIC Stamp II compatible, and like the standard compiler above, eliminates the need for a BS2 module. Pro adds built-in LCD support, interrupts in BASIC, arrays, program size to 8K, real I/O. Then...Else and I/O to any PIC pin. For mid-range PIC12C67x, 16C55x, 6xx, 7xx, 8x, 9xx.

*BASIC Stamp is a trademark of Parallax Inc.

EPIC Plus PIC Programmer - \$59.95



Programs PIC12C50x, 67x, 16C55x, 6xx, 7xx, 8x, 9xx. Optional ZIF adapters for DIP, SOIC, MQFP, PLCC. Runs off two 9-volt batts or optional AC adapter. Includes programming software and assembler.

PICProto Prototyping Boards

Get it wired quicker! High-quality blank prototyping boards for PICmicros. Holds 5V reg, caps, osc, DB9-25, large proto area. \$8.95 - \$17.95



microEngineering Labs, Inc.

Box 7532 Colorado Springs CO 80933
(719) 520-5323 (719) 520-1867 fax

http://www.melabs.com
email: info@melabs.com

STAMP APPLICATIONS

and I measured the resulting resistance with a digital multimeter (DMM). This data was then graphed. The result is displayed in Graph 1. As you can see, the resistance remains linear over the range of settings for the digital potentiometer. This is good news, but since the DMM presents a high impedance load to the DS1267, it may not be representative of my circuit. This would still have to be verified empirically. Which means I could verify it during the software design.

Designing the Software

Before writing any software, I always create a schematic. The schematic is usually in pencil. There's no reason to generate it with a computer assisted design (CAD) program just yet. Chances are your schematic will change as you write the software. If you're going on to design a printed circuit board (PCB), then you'll probably end up modifying both your software and schematic to ease layout requirements and reduce noise.

It's also a good idea to generate a flow chart of some sort for your software prior to sitting down to write it. Quite often my BASIC Stamp


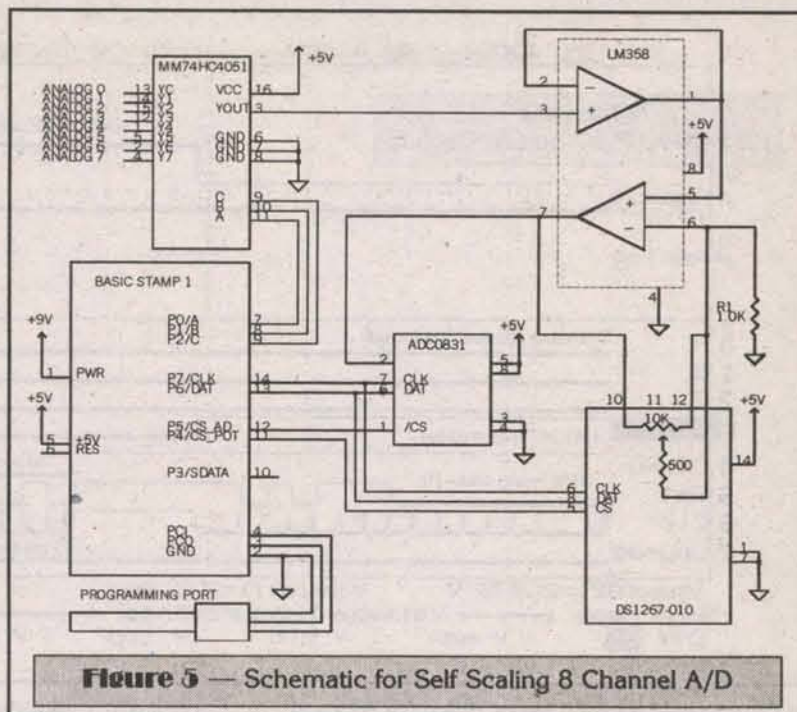


Figure 5 — Schematic for Self Scaling 8 Channel A/D

DS1267-010 Resistance VS. Setting

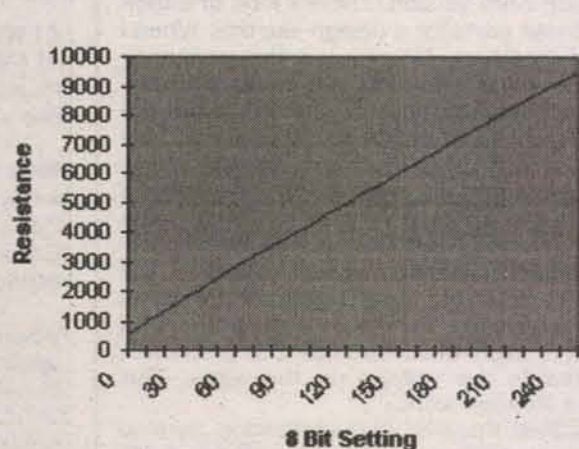

programs are relatively short. For this reason, I often forego the flow chart in lieu of a list of subroutines. If your program is long and has quite a few branches, gosubs, or gotos, then flow charting before and after you write the software is something I would recommend.

Originally, I had envisioned being able to set the gain of the amplifier block in my software with an equation. But, in the end, I opted for maintaining the gain settings by storing them in EEPROM. The BS1 Write and Read commands make it simple to implement indirect addressing to access stored constants. This also allowed me to modify the potentiometer settings to exactly match desired gain values.

During initial testing, I've found that the voltage measurements are typically within 2-3% of the actual voltage. It would be possible to utilize both of the potentiometers in the DS1267-010 in order to increase the resolution of the gain setting function. Doing this would remove some of the error exhibited by this voltage measurement technique. It would also be possible to have a

Network Service Tool Set

Popular installation and service tools for networks, modems and telephones. All hand tools are professional heavy duty type.

Use the compact tester on 10BASE-T (UTP & STP), thin Ethernet (BNC), 8-position Token Ring, AT&T 258A and EIA/TIA 568A/B. Automatically scans cables for continuity, wiring sequence and polarization. Tests STP cable ground. Testing installed cables is easy with Remote Terminator and gender changers (UTP and BNC). 9V battery included.

- Coax Stripping Tool, RG-58 & RG-59
- BNC Crimping Tool, RG-58 & RG-59
- Modular Cutting/Stripping/Crimping Tool (4, 6 & 8-Position)
- Multi-Network Cable Tester
- AC Receptacle Tester
- Cable Cutter

Order No. 55625 \$197.00



PC Service Tool Set

Contains all tools needed to troubleshoot & service IBM-compatible PCs. Set includes:

- AMI Diagnostic Software
- POST Card
- Logic Probe
- Digital Multi-Meter
- AC Receptacle Tester
- Serial Adapter
- Serial & Parallel Loopback Connectors
- DIP IC Puller
- PLCC IC Puller
- Grounding Wrist Strap
- Key Top Puller

PC Diagnostic Tool Set

- AMI Diagnostic Software
- POST Card

Order No. 55555 \$89.00

Network Installation Tool Set

- Network Tool Set 55625 without the Multi-Network Cable Tester.

Order No. 55600 \$99.00

Call for your FREE Catalog
Graymark®

P.O. Box 2015 Tustin, CA 92781
http://www.labvolt.com

Order No. 55000 \$198.00



CALL TODAY!

800-854-7393



STAMP APPLICATIONS

SOURCES

For more information on the BASIC Stamp, contact:

Parallax, Inc.

3805 Atherton Road, #102
Rocklin, CA 95765
phone (916) 624-8333
<http://www.parallaxinc.com>

Scott Edwards Electronics, Inc.

2700 E. Fry Blvd. Suite A4
Sierra Vista, AZ 85635
phone 520-459-4802
fax 520-459-0623

www.seetron.com info@seetron.com

Solutions Cubed

Lon Glazner
3029 Esplanade Suite F
Chico, CA 95973
E-Mail: lon@solutions-cubed.com
www.solutions-cubed.com
Phone: 530-891-8045
Fax: 530-891-1643

reference voltage at one of the analog inputs.

By using a known reference voltage, a sub-routine could easily be written that would adjust the gain values to be stored in EEPROM to the correct values. For instance, with a reference voltage fixed at 250mV, the routine could set the gain to 2 and adjust the potentiometer value up or down until the A/D reading was closest to 500mV. This new value could then be stored in EEPROM. This could continue until all gain values have been modified. Afterwards, the regular program would commence. This kind of self-adjustment would be useful in removing errors

induced by temperature fluctuations or component tolerances.

This kind of system can be easily devised with the versatile BASIC Stamp. The source code used for this design is listed in Code Listing 1: NV_499.BAS.

The software was simplified considerably due to the inclusion of both of the application notes provided by Parallax and Scott Edwards. Other than a little research, and some short sub-routines, this design was painless. There's still some work to be done as far as getting the voltage measurements into a PC. And guess what? There's an application note for that described in the Parallax BS1 SEROUT command (pages 63-65 of the BASIC Stamp manual). I haven't yet implemented the serial communication routines, although this should not pose a problem. It is most likely that I will use a quickBASIC program to store and convert the incoming data. The resulting data file will then be opened with Microsoft Excel and the data will be graphed.

Figure 4 provides an oscilloscope screen capture of both the gain setting and the A/D measurement. You can actually see the communication to the DS1267-010 and the resulting increase in the amplifier's gain. This is followed closely by the A/D measurement. The analog channel 0 input is measured by the oscilloscope as 293.8mV. The output of the op-amp amplifier is 10 times the voltage at analog channel 0, or 2.938V. These measurements are displayed at the bottom of the screen capture.

The oscilloscope used was the Hewlett Packard 54645D - MSO. This oscilloscope has some neat features that allow you to monitor digital lines like a logic analyzer would, as well as display the analog channels.

Figure 5 is a schematic of the finished project. Keep in mind that the serial output has not been completed, but I left a pin available for this function. The sample rate is also not adjustable at this point, but simply adding a PAUSE command, or increasing the ones already in the program would suffice as an adjustable sample rate.

In Closing

It was my hope to show a couple of things in

this month's column. Primarily, I wanted to emphasize the use of application notes in engineering. Usually you can find an application note that can answer some of your questions, and point you in the right direction. I run into people now and again that expect to find an application note that will fit their needs, and solve all of their design woes. That's just plain unrealistic.

When working with electronics, you can expect to face certain hurdles. In many cases, somebody has already cleared the hurdle that you can't seem to get over. If it's a common problem, there may be an application note for solving it. If it's an uncommon problem, there's only one thing you can do. Get out your tools, engineering resources, pencil, and paper, and get to work. Whether your efforts culminate in success or failure, you're bound to learn something, and that's not a bad thing.

The design completed here was accomplished with two application notes, both of which were nearly identical. It took a little creativity, and a few hours of research but, in the end, it's something that I can use in the lab. There were no revolutionary concepts derived from integrals or squeezed out of linear algebraic functions. I'm not going to show up at the next COMDEX with 10,000 units of BS1-based battery voltage testers and make a mint with this design.

What I did do was build something that would help me get my design work done, and hopefully allow me to build a better product. And I think that's the true power of the BASIC Stamp. It allows you to put technology to work at a minimum cost. Not to mention I tend to get a kick out of the idea that that little BASIC Stamp is making decisions and cranking out precise analog measurements while I type away at the PC. And I don't have to pay it a dime. NV

.....
Lon Glazner is a partner and Engineer at Solutions Cubed. Solutions Cubed is an innovative group of design engineers who specialize in embedded control design. They also produce a line of BASIC Stamp compatible products called Miniature Engineering Modules.

BE A DISTRIBUTOR FOR NUTS & VOLTS MAGAZINE.

Sell Nuts & Volts in your store or on your newsstand.

FOR COMPLETE INFORMATION, ASK FOR OUR NEW DISTRIBUTOR FLYER.

Nuts & Volts Magazine

430 Princeland Court
Corona, CA 91719
phone 909-371-8497
fax 909-371-3052
E-Mail distributors@nutsvolts.com

AMAZING PRODUCTS!

BOX 716 AMHERST, N.H. 03031

INFORMATION

UNLIMITED DEPT GEN 01198 <http://www.amazing1.com>

VISIT OUR "ACTION" WEB SITE@

LASER WINDOW BOUNCE LISTENING SYSTEM

Remarkable concept allows user to hear sounds within a premise over a beam of laser light reflected from a window or similar surface. Experimental device provides hours of interesting and educational use. Utilizes a visible red laser that simplifies alignment and discourages illegal use. Usable range will vary-expect about 20 to 50 meters. Optional lens will increase range 200 to 400 meters! Further range requires expensive optics. Basic system setup requires patience in alignment and a sturdy video tripod (not incl.)

LWB5 Plans.....\$20.00 LWB5K Kit/Plans.....\$149.95
LWB50 Basic System Assembled and Tested.....\$199.95
LWB70 Higher Performance Version With High Coherence Laser Gun Sight, Extending Lens, Deluxe Headsets.....\$299.95

LASERS

SUPER BRIGHT VISIBLE RED POINTERS

- *Signaling Beacon Visible Over 25 Miles!
- *Over 1/2 Mile Pointing Range
- *Light Up a Low Level Cloud
- *Great Fun At The Mo
- *Drive The Cat Nuts!!
- *6Hrs On AAA Batteries
- *5 5/8X1 1/2" All Metal

LAPN65 15 mw equiv 2000ft.....\$24.95
LAPN63 30 mw equiv 4000ft.....\$49.95
LAPN63F Above Focussable.....\$54.95

NEW LASER "LIGHT SHOW" POINTERS

- *#LAPN6512...12 Design Show.....\$29.95!
- *#LAPN6524...24 Design Show.....\$34.95!
- *#LAPN6540...40+Design Show.....\$39.95!!!

FM TRANSMITTER KITS

ALL PARTS TO BUILD 6 LONG RANGE WIRELESS DEVICES

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter
- 2 1 Mile+ Telephone Transmitter
- 3 Line Powered Telephone Transmitter Never Needs Batteries!!
- 4 Tracking/Homing Beacon "Beeping Transmitter"
- 5 Transmitter Rebroadcasts Video or Audio Outputs
- 6 Short Range TV/FM Disrupter NEAT PRANK!!! Discretion Advised

All 6 Above Kits Plus FREE Info Data Pack on "HELPFUL HINTS Building and Tuning" Wireless Devices

COMBOX Parts and Plans for above.....\$59.95
COMBOP Plans for all the above.....\$10.00

KINETIC ELECTRIC GUN

PIONEER A FUTURISTIC WEAPON!

500 Joules Energy Storage
Constant Current Charging
Triggered Spark Switch
Ballistic Velocities
Handheld Battery Operated
Labeled A Dangers product

EGUN1 Plans with Parts List.....\$20.00
All Parts are Individually Available

10-14" of Explosive Bolts of Lightning

250KV TESLA COIL

Transmit Wireless Energy
Strange and Bizarre
pyrotechnical effects.
Ion Motors Anti-Gravity
Size 20" H x 8" Sq
Weight - 25 Pounds
115 Volts/2 Amps AC
Labeled "Use Caution"

BTC3 Plans.....\$15.00
BTC3K Kit/Plans.....\$399.95
BTC30 Ready to Use.....\$499.95
BTC4 Plans 24 to 30" Sprk.....\$20.00

3 MI FM BROADCAST TELEPHONE TRANSMITTER

Tunable On FM Broadcast. Excellent Telephone Project. Only Transmits When Phone is Used

VWPM7K Kit/Plans.....\$39.95
BEEP1K Beeper Alert Kit.....\$19.95

HIGH POWER STUNGUNS

STUN100 100KV StunGun.....\$19.95
STUN200 200KV StunGun.....\$39.95
STUN300 300KV StunGun.....\$49.95

ION RAY GUN

Star Wars Technology Demonstrates Weapons Potential! See Ions in Motion!

IOG79 Plans.....\$10.00
IOG7K Kit/Plans.....\$99.95
IOG70 Assembled and Tested.....\$149.95

HIGHER POWERED DEVICE

IOG9K Kit/Plans.....\$149.95
IOG90 Assembled and Tested.....\$199.95

ATTENTION! HIGH VOLTAGE EXPERIMENTERS

Battery Powered Mini Sized Modules for research in: HOVERCRAFT, ION GUNS, FORCE FIELDS, SHOCKERS

MINIMAX4 4KV@10ma.....\$19.95

GRAVITY GENERATOR

Demonstrates a unique phenomena of electrical reactions that produce the effect of "anti-gravity". You build and levitate a small mock space ship from simple materials. Excellent scientific demonstration of a fascinating method of levitation. **Levitate an Object!**

GRA1 Plans and Book.....\$20.00
GRA1K Pwr Sup Kit/Plans.....\$99.95
GRA10 Assembled Pwr Sup.....\$149.95

SHOCK FORCE FIELD/VEHICLE OBJECT ELECTRIFIER

Hand Shock Balls, Wands, Electrify Objects, Great Payback for Those Who Squeal!

SHK1K Kit of Pwr Module.....\$19.95

CAUTION Monstrous Is Illegal!

1 800 221 1705 ORDERS ONLY! FAX 1 603 672 5406 INFO 9-5pm 1 603 673 4730 FREE CATALOG ON REQUEST
 Pay by MC, VISA, Cash, Chk, MO, COD. Please Add \$5.00 S&H plus \$5.00 if COD. Overseas Please Contact for PROFORMA

DEALER DIRECTORY

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

ALABAMA

Little Professor Book Center
2717 S. 18th St.
Birmingham 35209
RT Systems
Amateur Radio Supply
8207 Stephanie Dr.
Huntsville 35802

ARIZONA

Batteries Plus #330
3014 N. Dobson
Chandler 85224
Batteries Plus #334
1155 S. Power Rd. #108
Mesa 85206
Batteries Plus #331
2404 E. Bell Rd.
Phoenix 85032
Batteries Plus #332
3415 W. Glendale Ave. Ste. 4
Phoenix 85051
Batteries Plus #333
1829 E. Southern Ave.
Tempe 85282
Elliott Electronic Supply
1251 S. Tyndall Ave.
Tucson 85713
The Electronic Thrift Store
12329 N.W. Grand Ave. #F
El Mirage 85375
Tower Records
3 E. 9th St.
Tempe 85281

AUSTRALIA

DonTronics
P.O. Box 595
29 Ellesmere Cres.
Tullamarine 3043
www.dontronics.com

CALIFORNIA

Abletronics
9155 Archibald Ave. Unit E
Cucamonga 91730
Advanced Computer Products, Inc.
1310 "B" E. Edinger Ave.
Santa Ana 92705
All Electronics
905 S. Vermont Ave.
Los Angeles 90006
14928 Oxnard St.
Van Nuys 91411
Allen's To Go
13461 Hwy. 88
Lockeford 95237
Alltronics
2300-D Zanker Rd.
San Jose 95131
Brand Newsstand
234-1/2 N. Brand Blvd.
Glendale 91203
Centerfold International
716 N. Fairfax Ave.
Los Angeles 90046
Del Amo Books & News
3758 Sepulveda Blvd.
Torrance 90505
DSS Satellite Comm.
411-E 18th St. #C
Oakland 94606
Electro Mavin
2985 E. Harcourt St.
Rancho Dominguez 90221
Ford Electronics
8431 Commonwealth Ave.
Buena Park 90621
Harding Way News
113 W. Harding Way
Stockton 95204
Harold's Newsstand
524 Geary St.
San Francisco 94102
HdB Electronics
2860 Spring St.
Redwood City 94063

HI-FI Doctor

1814 E. Ball Rd.
Anaheim 92805
HSC Electronic Supply
4837 Amber Ln.
Sacramento 95841
3500 Ryder St.
Santa Clara 95051
5681 Redwood Dr.
Rohnert Park 94928
Hyatt Electronic Surplus
371 N. Johnson Ave.
El Cajon 92020
JK Electronics
6395 Westminster Ave.
Westminster 92683
Laurel Park News
4346 Laurel Canyon Blvd.
Studio City 91604
Lion Electronic Labs
4948 E. Townsend Ave.
Fresno 93727
Netseller
7207 Arlington Ave. Ste. G
Riverside 92503
Op Amp Technical Books
1033 N. Sycamore Ave.
Los Angeles 90038
Panorama Electronics
8737 Van Nuys Blvd.
Panorama City 91402
Sandy's Electronics Supply, Inc.
20655 Soledad Cyn. Rd. #15
Santa Clarita 91351
Sav-On Electronics
13225 Harbor Blvd.
Garden Grove 92643
SIERRA MADRE NEWSSTAND
55 N. Baldwin Ave.
Sierra Madre 91024
The Red Barn
Hwy. 299
Bieber 96009
Tower Books
211 Main St.
Chico 95928
7840 Macy Plaza Dr.
Citrus Heights 95610
1280 E. Willow Pass Rd.
Concord 94520
630 San Antonio Rd.
Mountain View 94040
1600 Broadway
Sacramento 95818
5950 Florin Rd.
Sacramento 95823
2538 Watt Ave.
Sacramento 95812

Tower Magazines/News

885 Riverside Pkwy.
West Sacramento 95605
Tower Records/Video
220 N. Beach Blvd.
Anaheim 92801
2520 Durant
Berkeley 94704
212 F St.
Davis 95616
5703 Christie Ave.
Emeryville 94608
2052 Redwood Hwy.
Greenbrae 94904
6310 E. Pacific Coast Hwy.
Long Beach 90803
2280 Market St.
San Francisco 94114
3205 20th Ave.
San Francisco 94132
2525 Jones St.
San Francisco 94133
871 Blossom Hill Rd.
San Jose 95123

1205 W. Covina Pkwy.
West Covina 91790
Video Electronics
3829 University Ave.
San Diego 92105

CANADA

Com-West Radio Systems Ltd.
8206 Ontario St. #100
Vancouver, BC V5X 3E3
Muir Communications Ltd.
3214 Douglas St.
Victoria, BC V8Z 3K6

COLORADO

TH Electronics
216 Commerce Dr., Unit 2
Ft. Collins 80524
Tower Records/Video
2500 E. 1st Ave.
Denver 80206
Western Test Systems
530 Compton #C
Broomfield 80020

CONNECTICUT

Archway News
64 Bank St.
New Milford 06776
Electronic Service Products
437 Washington Ave.
North Haven 06473

DELAWARE

Newark Newsstand
70 E. Main St.
Newark 19711

DISTRICT OF COLUMBIA

Tower Records
2000 Pennsylvania Ave.
Washington 20006

FLORIDA

Alfa Electronic Supply
1502 S. St. Rd. #7
Hollywood 33023
AI's News
8219 S.W. 124th St.
Miami 33156
Bob's News & Books
1515 S. Andrew Ave.
Fort Lauderdale 33316
Clarks Out of Town News
303 S. Andrews Ave.
Fort Lauderdale 33301
Mike's Electronic Distributing Co.
1001 N.W. 52nd St.
Fort Lauderdale 33309
Skycraft Parts & Surplus, Inc.
2245 W. Fairbanks
Winter Park 32789
Sunny's At Sunset, Inc.
8260 Sunset Strip
Sunrise 33322

GEORGIA

Tower Records
3400 Around Lenox Dr.
Atlanta 30326

HAWAII

SolarWorks!
525 Lotus Blossom Ln.
Ocean View 96737
Tower Records
4211 Waialae Ave.
Honolulu 96816
611 Keekaumoku
Honolulu 96814

IDAHO

The Current Source
5159 Glenwood
Boise 83714

ILLINOIS

Tower Records/Video/Books

383 W. Army Trail Rd.
Bloomington 60108
2301 N. Clark St. #200
Chicago 60614

1209 E. Golf Rd.
Schaumburg 60173

INDIANA

Harbourtown Sales
108 Park 32 W. Dr.
Noblesville 46060

KANSAS

Hollywood At Home
9063 Metcalf Ave.
Overland Park 66212
Lloyd's Radio & Electronic, Inc.
220 W. Harry St.
Wichita 67213

LOUISIANA

Lakeside News
3323 Severn Ave.
Metairie 70002

MARYLAND

Silicon Valley Electronics
2014-A Industrial Dr.
Annapolis 21401
Tower Records/Video
2566 Solomons Island Rd.
Annapolis 21401
1601 Rockville Pike #210
Rockville 20852

MASSACHUSETTS

Full Spectrum Communications
244 Essex St.
Salem 01970
Newsbreak, Inc.
579 G.A.R. Hwy. Rt. 6
Swansea 02777
Tower Records #172
360 Newbury St.
Boston 02115

MICHIGAN

Little Professors Book Center
22174 Michigan Ave.
Dearborn 48124
MW Electronics
229 E. Michigan Ave.
Paw Paw 49079
Purchase Radio Supply, Inc.
327 E. Hoover Ave.
Ann Arbor 48104
Tower Records
1214 S. University Ave.
Ann Arbor 48104

MINNESOTA

Radio City, Inc.
2633 County Road 1
Mounds View 55112

MISSOURI

Accurate Instruments
11201 E. 24 Hwy.
Independence 64054
Electronics Exchange
8644 St. Charles Rock Rd.
St. Louis 63114

NEVADA

Amateur Electronic Supply
1072 N. Rancho Dr.
Las Vegas 89106
Less Buster's Electronics
2930 N. Las Vegas Blvd.
VSTG-22
North Las Vegas 89030
Radio World
1656 Nevada Hwy.
Boulder City 89005
Tower Records/Video
4580 W. Sahara Ave.
Las Vegas 89102
6450 S. Virginia
Reno 89511

NEW JERSEY

JR Tech Systems
1309 Hwy. 71
Belmar 07719

NEW MEXICO

Newsland Bookstore
2112 Central S.E.
Albuquerque 87106

NEW YORK

All Phase Video Security, Inc.
70 Cain Dr.
Brentwood 11717
Ham Central
3 Neptune Rd.
Poughkeepsie 12601
Hirsch Sales Corporation
219 California Dr.
Williamsville 14221
Tower Records/Video
105 Old Country Rd.
Carle Place 11514
350-370 Route 110
Huntington 11746
1961 Broadway
New York 10023
383 Lafayette St.
New York 10003

OHIO

Compustuff
241 Great Oaks Trl.
Wadsworth 44281
Digital One
7603 Mentor Ave.
Mentor 44060
Footsteps
4925 Jackman Rd. Store #58
Toledo 43613
Hostell Electronics, Inc.
2700 Sunset Blvd.
Steubenville 43952
Keyways, Inc.
204 S. 3rd St.
Miamisburg 45342
Leo's Book Shop
330 N. Superior St.
Toledo 43604
Powermaxx, Inc.
1587 U.S. Route 68 N.
Xenia 45385

OKLAHOMA

Steve's Books & Magazines
2612 S. Harvard
Tulsa 74114

OREGON

News & Smokes
2295 W. Main St.
Medford 97501
News & Smokes #8
259-C Barnett Rd.
Medford 97501
Norvac Electronics
7940 S.W. Nimbus Ave. Bldg. 8
Beaverton 97005
960 Conger
Eugene 97402
1545 N. Commercial N.E.
Salem 97303
Powell's Technical Bookstore
33 N.W. Park
Portland 97209
Taylor News & Books
133 W. Main, Ste. 102
Oklahoma City 73102
Tower Books
1307 N.E. 102nd Ave.
Portland 97220

PENNSYLVANIA

Bedford St. News
308 Bedford St.
Johnstown 15901
Genes Books, Inc.
King of Prussia Plaza
King of Prussia 19406

Lehman Scientific
2997-F Cape Horn Rd.
Red Lion 17356

Monico Electronics & Computers
2555 Industry Ln. Ste. D
Norristown 19403

Surplus AI
RR 1 Box 337
Hunlock Creek 18621

Tower Books
425 South St.
Philadelphia 19147

Tower Records
340 W. Dekalb Pike
King of Prussia 19406

SOUTH CAROLINA

555 Electronics
5646 Farrow Rd.
Columbia 29203

TENNESSEE

Tower Books
204 W. End Ave.
Nashville 37203

TEXAS

BDL News, Inc.
809 Pierce
Houston 77002
Electronic Parts Outlet
3753-B Fondren Rd.
Houston 77063
Mouser Electronics
958 N. Main St.
Mansfield 76063
Tanner Electronics
1301 W. Beltline #105
Carrollton 75006
Tower Records
2403 Guadalupe
Austin 78705

VIRGINIA

American Computer Clearance
1609 Rhoadmiller St.
Richmond 23220
Satellite Headquarters
7920 Timberlake Rd.
Lynchburg 24502
Tower Records/Video/Books
4110 W. Ox Rd. #12124
Fairfax 22033
1601 Willow Lawn Dr.
Richmond 23230
8389 E. Leesburg Pike
Vienna 22182

WASHINGTON

A-B-C Communications, Inc.
17541 15th Ave. N.E.
Seattle 98155
Bohica Concepts
214 2nd St.
Morton 98356
Cody Books Ltd.
1125 Fir Ave.
Blaine 98230
Service Request
3304 W. Rowan Ave.
Spokane 99205
Tower Books
10635 N.E. 8th St.
Bellevue 98004
20 Mercer St.
Seattle 98109
WISCONSIN
Amateur Electronic Supply, Inc.
5710 W. Good Hope Rd.
Milwaukee 53223
Greenfield News & Hobby
6815 W. Layton Ave.
Greenfield 53220
Cudahy News & Hobby Ctr.
4758 Packard Ave.
Cudahy 53110

THE 'OPTO' IN OPTOELECTRONICS (Part 2)

Most of last month's opening episode of this mini-series described the basic nature and behavior of light, with particular regard to its use in modern optoelectronic systems. The remaining part of that episode dealt with two types of light-beam manipulators, namely, mirrors and retroreflectors.

This month's episode continues the 'light-beam manipulators' theme by describing the nature and behavior of optical prisms and lenses.

LIGHT-BEAM MANIPULATORS

PRISMS

In optics, a prism is a block of transparent material having two or more plane (flat) surfaces. Prisms have an innate ability to bend the paths of light. A flat sheet of glass is a very simple prism.

When light travels through a transparent material or medium other than free space, its velocity (v) and wavelength (λ) are lower than those that pertain in free space (v_0 and λ_0). The ratio v_0/v or λ_0/λ is known as the medium's *refractive index*, and is denoted by the symbol n .

Figure 1 lists some typical n values for various transparent media, including normal glass ($n = 1.5$ to 1.9), which is transparent to all visible light and much of the lower IR spectrum, but blocks most of the UV spectrum.

Figure 2 illustrates the effects that 'refraction' has on a light ray when it travels through a pane of glass with (for simplicity) an n value of 2. In Figure 2(a), the beam enters the glass at an incident angle of 0° , is slowed down (thus reducing the light's wavelength, but *not* its frequency) as it passes through the glass, and then returns to normal 'through air' speed as it leaves the glass at an angle of 0° .

In Figure 2(b), the dashed lines represent the *normal* or zero degrees angular reference line. In this diagram, the ray enters the glass at an incident angle (α_i) of (say) 30° and then, as it passes from the thinner medium (air) to the denser one (glass), the ray *bends towards the normal* by a refractive angle (α_r) of about 15° ; when the ray passes from the

denser to the thinner medium again as it leaves the glass, the ray *bends away from the normal* again, returning to its original angle of 30° , thus obeying the basic Laws of Refraction. The values of α_i , α_r , and the n values of the incident (n_i) and refractive (n_r)

the same glass surface — are subject to this type of parallax error.

Most prisms have plane surfaces that are angled away from each other, as shown in Figure 3, in which two prisms each have their major surfaces angled at 30° to one another. This diagram

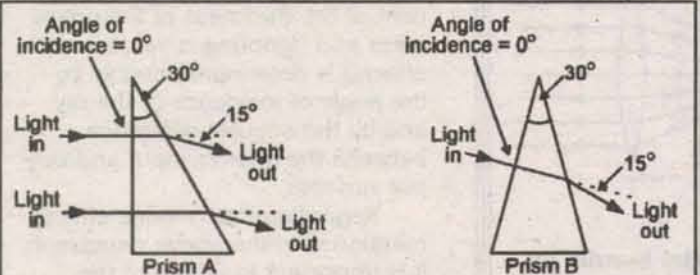


Figure 3. Diagram illustrating some important ray-bending features of a simple prism.

Substance	Refractive Index
Free Space	1.000 000
Air	1.000 293
Ice	1.31
Water at 20°C	1.333
Glass	1.5 to 1.9
Diamond	2.42

Figure 1. Table listing typical refractive index values for various transparent media.

regions are related by Snell's law of refraction, which states that $n_r/n_i = \sin \alpha_i / \sin \alpha_r$.

Note in Figure 2(b) that the light ray leaving the glass is shown parallel with — but offset from — the path of the original input ray, which is indicated by the dotted line. The degree of offset (parallax error) increases with the angle of incidence and with the thickness of the glass. Simple mirrors — in which light rays enter and leave the mirror via

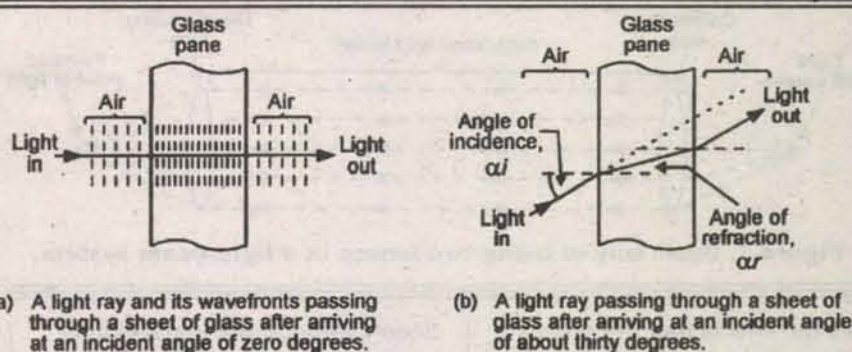


Figure 2. Diagrams illustrating the effects of refraction through a sheet (pane) of glass.

BIG POWER LOW COST



Domino 1 features:

- Full floating-point ROMed BASIC
- 32-KB SRAM and 32-KB EEPROM
- 12 bits of parallel I/O
- 2 PWM outputs
- IIC bus
- 2-channel 12-bit ADC
- Serial port: 19.2-kbps RS-232A, RS-422, or RS-485
- +5 V @ 15 mA

Domino 2 has:

- everything in Domino 1 plus
- 16 more bits of high-current parallel I/O
- Hardware clock/calendar
- Wide-range power operation
- Hardware PWM output

\$99 to \$139

Visit our Web site for complete datasheets

www.micromint.com

To Order Call: **1-800-635-3355**




4 Park St., Vernon, CT 06066
(860) 871-6170

Write in 77 on Reader Service Card.


MORE POWER! 68HC11, 80C51 & 80C166

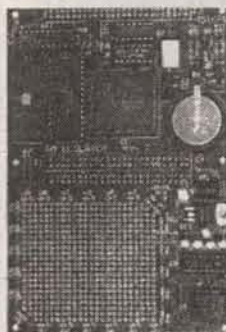AM Research supports over 30 of the most popular Embedded controllers with both *hardware* and *software*.



- ✓ More Microcontrollers
- ✓ Faster Hardware.
- ✓ Faster Software.
- ✓ More Productive.
- ✓ More Tools & Utilities.
- ✓ IIC Peripherals.
- ✓ Single Chip Capable.
- ✓ Outstanding Support.
- ✓ Custom designs.

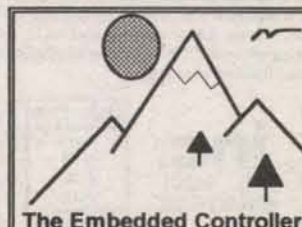Call or email for a free full line brochure



Orders (800) 949-8051
Info (916) 652-7472
fax (916) 652-6642
www.amresearch.com

AM Research, Inc.
PO Box 43
Loomis, CA 95650

The Embedded Controller Experts

Write in 76 on Reader Service Card.

April 1999 31

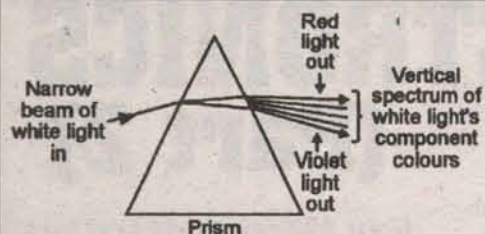


Figure 4. Exaggerated diagram showing a prism splitting a beam of white light into its component colors.

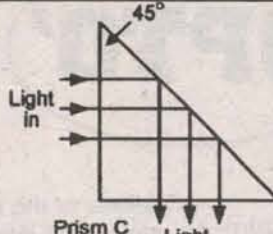
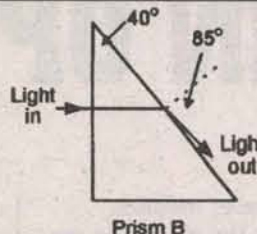
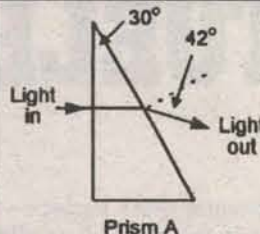


Figure 5. Diagram illustrating the phenomenon of total internal reflection in a prism.

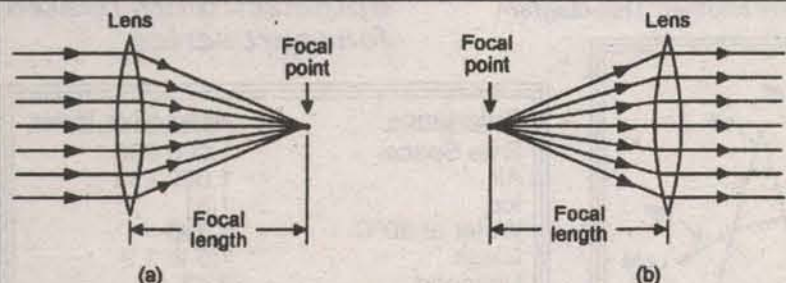


Figure 6. A simple lens can (a) focus a parallel bundle of rays onto a single point, or (b) convert the rays from a single point source into a parallel (collimated) beam of light.

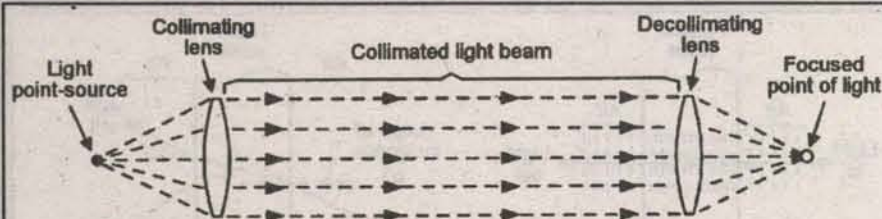


Figure 7. Basic way of using two lenses in a light-beam system.

shows the effects that the prisms have on a light ray that arrives at an incident angle of zero degrees. In both cases, the ray passes

cleanly through the glass without bending but, on leaving the glass, the ray bends away from the normal by about 15°, thus obeying

the basic Laws of Refraction.

Note in Figure 3 that the degree of ray bending is independent of the thickness of the prism glass and (ignoring n value effects) is determined mainly by the angle of incidence of the ray and by the angular difference between the prism's input and output surfaces.

Regarding the ' n value effects' mentioned in the above paragraph, it is important to note that the refractive index values of all transparent media other than free space vary with the wavelength of a light, and increase as wavelength shortens. The refractive index of glass is normally measured using a yellow sodium light with a wavelength of 589nm; the actual index value is higher than normal to violet light (400nm wavelength) and lower to red light (700nm wavelength).

Figure 4 shows, in exaggerated form, the results of passing a narrow beam of white light through a symmetrical triangular prism. White light contains all the colors (wavelengths) of the

visible spectrum, and the prism thus (because its refractive index is wavelength-dependent) bends each individual color of the beam by a different amount, giving the least bend to red light and the greatest bend to violet light. The prism's output thus takes the form of a vertically-expanded colored spectrum. This scatter-

ing of white light's component colors is known as *dispersion*.

When a ray of light passes through air and enters a prism, it bends by an amount determined by its angle of incidence and by the refractive index value of the glass. When the ray leaves the prism again and returns to the air, it bends by an amount determined by its angle of incidence and by the refractive index of the air (1.0) divided by that of the glass (say 1.5), and this value is invariably less than zero (0.667 in this example). Figure 5 shows the actual amounts of output refraction that occur on three different prisms that each have a refractive index of 1.5.

In Figure 5, the ray strikes the output surface of prism A at an incident angle of 30° and leaves the prism at a refractive angle of 42°; this prism thus bends the ray downwards by 12°. In the case of prism B, the ray strikes its output surface at an incident angle of 40° and leaves at a refractive angle of 85°, thus bending the ray downwards by 45°.

Note in the case of prism B that the ray leaves the prism at an angle that is only 5° less than the angle of slope of the prism's output face, and it is obvious that if the angle of incidence is increased much more, the ray will be unable to penetrate the prism's output surface. The angle of incidence at which this occurs is known as the surface's *critical angle*, and is dictated by the n value of the glass; the critical angle is 43° at an n value of 1.5, 36° at an n value of 1.7, and 32° at an n value of 1.9.

Figure 5 shows, in the Prism C diagram, what happens to the light rays when they strike the prism's output face at an incident angle of 45°, i.e., at an angle greater than the critical angle of the surface. Under this condition, a phenomenon known as *total internal reflection* occurs and makes the internal surface act like a mirror that bends the rays by double their angle of incidence, thus (in this case) bending them through a 90° angle and projecting them through the lower face of the prism.

The internally-reflecting type-C prism thus acts like a mirror that bends light through 90°, but (since the light passes through separate

World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind; this is information you need to know!

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the Primer as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)

Examples Include:

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

EMAC, inc.
11 EMAC WAY, CARBONDALE, IL 62901
618-529-4525 Fax 457-0110 BBS 529-5708
World Wide Web: <http://www.emacinc.com>

1985 - 1998
OVER
12
YEARS
OF SERVICE

TONER CARTRIDGE RECHARGE

& Laser Printer Supplies

CALL NOW
FOR YOUR
FREE
CATALOG #13!



Instruction Manual
Free with
starter kit



Video Training
Tapes
choose from
our library



Catalog #13
100 pages
FREE!



Marketing
Flyers
with
customized
pricing



Printer/Copier/Fax
Cross Reference
68 pgs-Free
with any order

- Black, Color & MICR Toners
- Tools and Accessories
- Technical Support

- Cartridge Parts
- Video Training Tapes
- OPC Drums and Belts

- InkJet Refill Supplies
- Graphic Black Toner Kits
- MICR Toner Kits

- Fast, Same Day Shipping
- Mail-in Cartridge Service
- Export Orders
- Monthly Sales Specials
- Marketing Flyers

Visit our website at

www.chenesko.com

for all the free tech
documents, Sales Specials
and the latest industry news!

CP
CHENESKO
PRODUCTS

Chenesko Products Inc.
2221 Fifth Ave., Suite 4,
Ronkonkoma, NY 11779
Fax: 516-467-3223
E-Mail: chenesko@aol.com
<http://www.chenesko.com>

800-221-3516

input and output surfaces) does not suffer from parallax errors. This type of prism is widely used in high quality optical instruments and devices such as reflex cameras, binoculars, and automatic laser-aiming controllers.

Total internal reflection can occur whenever one transparent material interfaces with another that has a lower refractive index, thus giving a less-than unity refractive index and a positive critical angle value at the interface junction. All modern fiber optic cables rely on this 'internal reflection' basic principle for their very efficient low-loss operation (fiber optic cable principles will be described in Part 3 of this series).

LENSES

Normal optical lenses are light-bending refractive devices that are related to prisms but have curved (rather than flat) faces. Figure 6 shows the classic profile of a simple lens that has two parallel faces that are each radially curved in two dimensions, to form a section of a sphere. This type of lens can focus a parallel bundle of light rays onto a single point (the focal point), as shown in Figure 6(a); the distance between the center of the lens and the focal point is the focal length of the lens.

If a light point-source is spaced from the lens by a distance equal to the focal length of this type of lens, the lens converts the light into a parallel ('collimated') beam of light, as shown in Figure 6(b).

Figure 7 shows the basic way of using two simple lenses in a light-beam alarm or communication system. At one end of the system, the left-hand lens converts the transmitter's light point-source into a collimated (parallel) light beam and, at the other end of the system, the right-hand lens converts the collimated beam back into a point of light, which is applied to the receiver's light-sensitive input. Identical lenses are used in the collimating and decollimating processes.

Systems of the above type only generate a perfectly parallel beam if the light point-source is infinitely small, and this is an impossibility. In practice, the beam widens with distances after leaving the collimating lens; the amount of widening is proportional to the width of the light source and inversely proportional to the diameter of the lens. For minimum widening, the lens diameter must be large relative to that of the source.

Simple lenses with one or both faces shaped as a section of a

sphere are known as *spherical lenses* and are available in *convergent* and *divergent* types; convergent types make a parallel beam of light converge towards a common focal point; divergent types make a parallel beam of light diverge outwards. Figures 8 and 9 show a variety of lenses of these types.

Figure 8 shows four simple types of convergent spherical

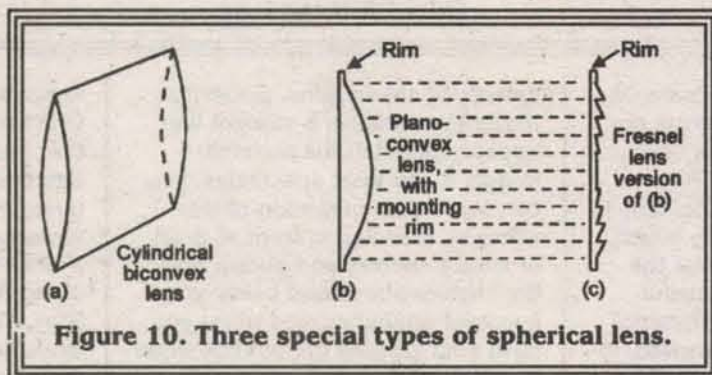


Figure 10. Three special types of spherical lens.

lens. The thin biconvex lens shown in (a) is the same type as shown in Figure 6; it operates equally well either way around, but its sharp edges are rather fragile. The thick biconvex type shown in (b) gives the same performance as the (a) type, but is more rugged.

The plano-convex type shown in (c) has one flat and one curved face and must be used the correct way around, with the flat face pointing in the direction of the parallel light beam and the curved face aimed towards the light's focal point. The convex meniscus type shown in (d) has a very long focal length; it

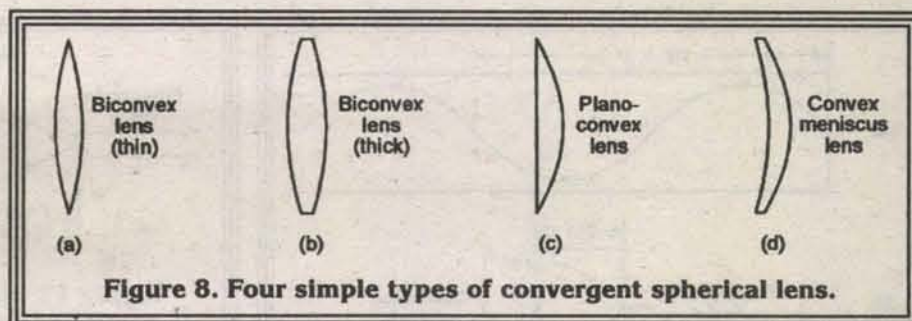


Figure 8. Four simple types of convergent spherical lens.

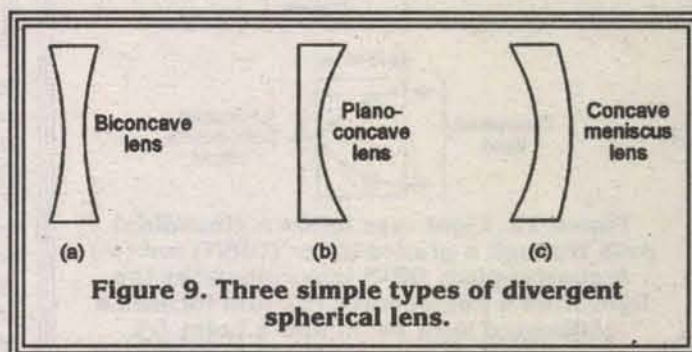


Figure 9. Three simple types of divergent spherical lens.

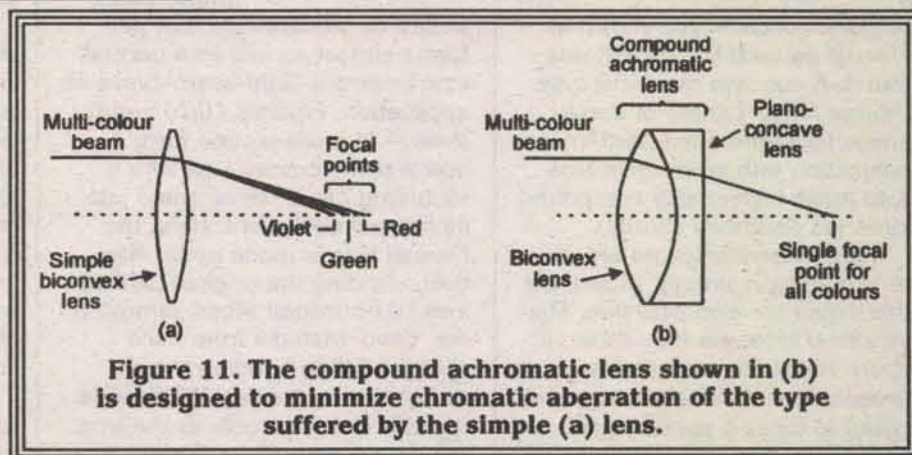


Figure 11. The compound achromatic lens shown in (b) is designed to minimize chromatic aberration of the type suffered by the simple (a) lens.


is the type used in most spectacles and contact lenses.

Figure 9 shows three simple

types of divergent spherical lens. The biconcave lens shown in (a) can be used either way around, but

PCB LAYOUT Software For Win95 - FREE

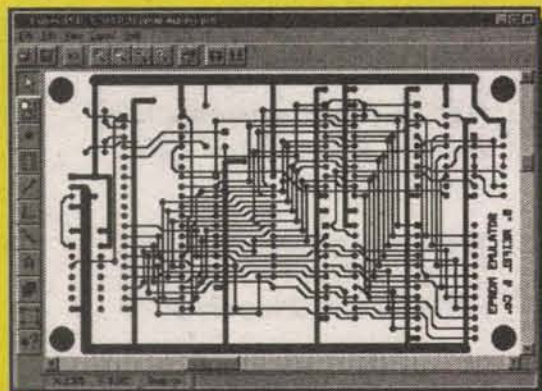- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



www.expresspcb.com

PIC'n Books

LEARN ABOUT PIC MICROCONTROLLERS

EASY PIC'n - Beginner \$29.95

PIC'n Up The Pace - Intermediate \$34.95

NEW!

PIC'n Techniques - Intermediate \$34.95

- 8-pin PICs
- Timer 1, timer 2 and the capture/compare/PWM (CCP) module
- Talking to a PIC with a PC using a terminal program
- Test equipment and data logger experiments

See Table Of Contents: <http://www.sq-1.com>
Secure Online Ordering is Available

+ \$4 s/h in US for 1 book, \$5 for 2 books, \$6 for 3 books

VISA, MC, AMEX, MO, Check

CA residents please add 7.25% CA sales tax

PIC and MPLAB are trademarks of Microchip Technology Inc.

SQUARE 1 ELECTRONICS

P.O. Box 501, Kelseyville, CA 95451
Voice (707) 279-8881 FAX (707) 279-8883
<http://www.sq-1.com>
E-Mail sqone@pacific.net

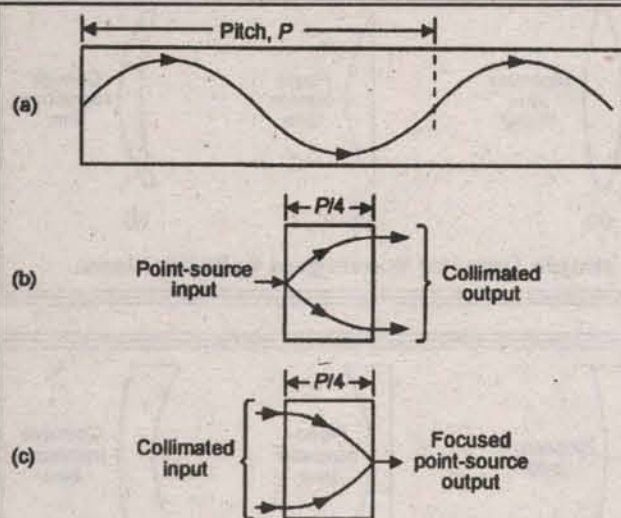


Figure 12. Light rays follow a sinusoidal path through a graded-index (GRIN) rod (a). A quarter-pitch GRIN lens collimates the light from a point-source (b), and focuses a collimated light beam into a point (c).

the plano-concave type shown in (b) must be used the correct way around. A concave meniscus type is shown in (c). Lenses of these various types are often used in conjunction with convergent lenses, to make high-quality compound lenses (as described shortly).

Most spherical lenses are of the simple type already shown, but other types are also available. The cylindrical biconvex lens shown in Figure 10(a), for example, is curved in one dimension only, and is used to focus a parallel light beam into a thin line, rather than a spot, or to convert a thin line of light into a collimated beam.

In most normal lenses, much of the sub-surface glass or plastic

weight or low-cost lens that performs almost as well as a normal lens in simple 'light-beam' types of application. Figures 10(b) and (c) show — in cross-section form — how a plano-convex lens with a mounting rim is transformed into its Fresnel equivalent. Here, the Fresnel lens is made up by effectively dividing the original (b) lens into 10 horizontal slices, removing the 'dead' material from each slice, and then bonding the remainder onto a base of identical material that also acts as the lens rim. In practice, most Fresnel lenses are molded, in plastic or glass.

The focused images generated by simple spherical lenses suffer from spherical and chromatic

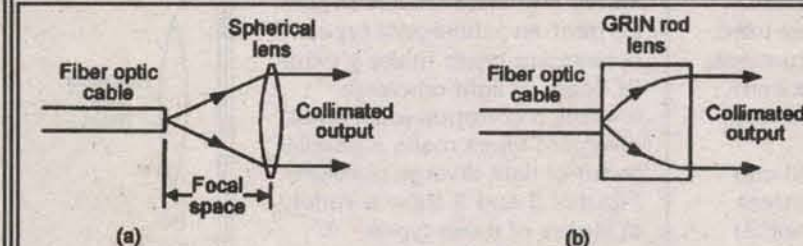


Figure 13. Method of collimating the light output from a fiber optic cable using (a) a spherical lens and (b) a GRIN rod lens.

lens material performs no useful function. A Fresnel lens is one in which most of the non-useful lens material is removed, to make a light-

defects or aberrations. *Spherical aberration* makes a straight line appear curved in the focused image; if you wear spectacles, you can see a demonstration of this effect by standing in front of a set of library shelves and noting how the shelves above and below your eye level appear curved when you have your glasses on, but not when they are off.

In simple lenses, *chromatic aberration* makes faint colored fringes appear around focused white or multi-colored images. The effect occurs because the refractive index of the lens material (and thus the focal length of the lens) varies with the color of light, as shown in Figure 11(a), making it possible to sharply focus only a small slice of the color spectrum; the rest of the spectrum is out of focus, producing the 'fringe' effect.

This problem can be overcome by using a compound lens made of one converging and one diverging lens, each with a different refractive index value, as shown in Figure 11(b). Such a lens can be made to give all colors

the same overall focal length, and is known as an *achromatic* or *antispectroscopic* lens.

The strangest and most recently developed lens is the *graded-index* (GRIN) rod lens, which is used in modern fiber optic applications and operates in a dif-

ferent way to a normal lens. A GRIN rod is a glass or fiber rod that has a refractive index that decreases progressively with distance from the rod axis. This index variation causes light rays to follow a sinusoidal path as they travel along the rod, as shown in Figure 9(a). The length of one complete sinusoidal cycle in the rod is called the *pitch* (P) of the rod; the P value is determined mainly by the rod's diameter and refractive index profile; the value is typically about 20mm.

A GRIN rod lens is simply a slice of GRIN rod with a length less than a single pitch-length, so that its optical output signal is out of phase with the optical input signal. The most interesting and widely used GRIN rod lens has a quarter pitch (giving it a length of about 5mm) and has the interesting properties illustrated in Figures 12(b) and (c).

Note in (b) that the light from a point source in contact with the center of the left face of the lens emerges from the right face in fully collimated form and, in (c), that a collimated light beam entering the left face leaves the right face as a focused spot. The GRIN rod lens thus has some properties of a conventional lens, but has a very short focal length.

GRIN rod lenses are widely used in modern fiber optic and laser module applications. Figure 13 shows an example that illustrates the advantages of a GRIN rod lens over a spherical lens in a simple fiber optic application in which the fiber optic cable's point-source 'light' output needs to be collimated when fed into the outside world.

In the case shown in (a), the light is collimated by a conventional lens, which must be placed a precise fixed distance from the end of the cable, to which it is coupled by an air gap. In the case shown in (b), the GRIN rod lens is simply bonded directly to the polished end of the cable, and no carefully spaced air gap is required.

More information on fiber optic and GRIN (graded index) operating principles will be given in next month's episode of this series, which will give an in-depth explanation of fiber optic principles and practice. **NV**

When Visiting Disney World And Sea World...
Come To The World Of Electronic Surplus!

SKYCRAFT

PARTS & SURPLUS, INC.
ORLANDO, FLORIDA

Located At The Intersection Of I-4
And Fairbanks Avenue.

Self-Service Retail Outlet Featuring Commercial
And Government Electronic Surplus Including:

- | | |
|--------------------|-----------------------|
| ★ WIRE | ★ COAX |
| ★ SWITCHES | ★ RELAYS |
| ★ RESISTORS | ★ HARDWARE |
| ★ TRANSISTORS | ★ CAPACITORS |
| ★ TRANSFORMERS | ★ PANEL METERS |
| ★ TEST EQUIPMENT | ★ CIRCUIT BOARDS |
| ★ NI-CAD BATTERIES | ★ INTEGRATED CIRCUITS |

★ ★ ★ ★ ★ ★ ★ ★

**We Buy Surplus
Electronic Parts —
FAX your list.**

FAX 407/647-4831

PH 407/628-5634

P.O. BOX 536186

ORLANDO, FLA. 32853-6186

HOURS:

Monday - Friday 8:30-6:00

Saturday 8:30-5:00



EXPLOSIVE DEALS!

CABLE CONVERTERS

Our converters are designed for
your specific need.

***85 Ch Plain Converter Ch-3,**
AFT/MFT, PG Lock, HRC/STD and
Sleep Timer

***125 Ch Plain Converter Ch-3**
AFT/MFT, PG Lock, HRC/STD
and Sleep Timer

***Volume Control, 135Ch,**
Ch-3/4, AFT/MFT, P/G Lock,
HRC/STD and Sleep Timer

UNBEATABLE PRICES
FREE BROCHURE

CALL (310)515-5085
CALL FOR DEALER PRICE

PCW CO

FAX (310)538-3636

Newsbytes

CALL FOR PAPERS CENTRAL STATES VHF SOCIETY CONFERENCE AND PROCEEDINGS

The CSVHF Conference will be held July 22-25 in Cedar Rapids, IA. Authors wishing to submit a paper and/or make a presentation at the conference are encouraged to contact Barry Buelow WA0RJT.

Papers will be accepted in technical areas related to VHF and UHF equipment design, antennas, and related topics. Operating procedures and reports of band openings are also welcome.

**The closing date for submitting a paper is
May 15, 1999.**

The CSVHF Society maintains a webpage at <http://www.csvhfs.org>.

Authors should contact Barry Buelow at: 4110 Emerson Ave. N.E., Cedar Rapids, IA 52411-6716; E-Mail to: bjbuelow@plutonium.net.

SIX STUDENTS WIN FIRST AND SECOND PLACE PRIZES IN DURACELL COMPETITION

100 Student Inventors Receive from \$20,000.00 to \$500.00 Savings Bonds

From a teaching tool that moves continents to an electronic pop-top opener, from a laptop security gadget to a color reader for the blind, from a new fire-fighting safety tool to an outdoor strobe thermometer, the bright ideas of six students were rewarded with first and second place honors in the 1999 Duracell/NSTA Scholarship Competition.

Duracell and the National Science Teachers Association announced first through fifth place winners who were recipients of \$160,000 in savings bonds during the 17th annual competition.

Over 1,900 students submitted photos and plans for 1,432 prototype entries in the 1999 Duracell; 100 were selected as finalists. These finalists were awarded savings bonds ranging in value from \$20,000.00 to \$500.00. The six first and second place winners, accompanied by their sponsoring teachers and parents, were honored in Boston March 24 and 25 during the annual convention of the National Science Teachers Association (NSTA).



FIRST PLACE WINNERS

First place winner in the 10th through 12th grade category was **Tom Kennedy**, 17, a senior at Randolph High School and a resident of Randolph, NJ. He received a \$20,000.00 savings bond for the **Cojack Laptop Computer Anti-Theft System**.

Cojack is a small, convenient anti-theft system. Its design could also be applied to protecting other valuables such as golf clubs, musical instruments, and portable stereos. An important feature is that it turns itself on so the owner does not need to remember to arm it. Kennedy's sponsoring teacher is George Collett.

The first place \$20,000.00 savings bond winner in the 6th through 9th grade category was **Ilana Jaatmaa**, 13, an 8th grader at Walkersville Middle School who lives in Frederick, MD. Jaatmaa's battery-operated invention is **Pangaea, A World in Motion** — a moving map and educational tool for children.

A World in Motion shows the changes of Earth's continents, from how they are today to a single large landmass, as Earth was 170 million years ago. "During this project, I learned a lot about gear ratios, levers, and serial electrical circuits in addition to continental drift," Jaatmaa says. Her sponsoring teacher is Owen Davis.

Sponsored by Duracell, Inc., and administered by the National Science Teachers Association, the Duracell/NSTA Scholarship Competition has awarded over \$990,000.00 in scholarships, savings bonds, and cash awards to over 875 students since 1983. Student inventors retain all rights to their devices.

SURPLUS TEST EQUIPMENT

HEWLETT PACKARD

11729B, Carrier Noise Test Set	\$3500
11975A, Amplifier, 2-8GHz	\$2000
16500A, Logic Analyzer Mainframe	\$950
3312A, Function Generator, 1Hz-13MHz	\$700
3325A, Synthesizer/Function Generator	\$1000
3325A/01/02, Synthesizer/Function Generator	\$1500
3335A, Frequency Synthesizer, 200Hz-81MHz w/Opt. 01	\$5500
339A, Distortion Analyzer	\$1000
3456A, Digital Multimeter, 6.5 Digits	\$800
3478A, Digital Multimeter	\$700
3488A, Switch Control	\$600
3551A, Transmission Test Set	\$600
3560A, Signal Analyzer	\$6000
3575A, Phase Gain Meter 1Hz-13MHz	\$1000
3577A, Network Analyzer w/35677A Test Set	\$10,500
3580A, Spectrum Analyzer, 5Hz-50KHz, Opt. 2 & 3	\$1000
3581C, Selective Voltmeter	\$800
3585A, Spectrum Analyzer, 20Hz-40.1MHz	\$5500
4192A, LF Impedance Analyzer w/16097A Kit	\$10,000
4342A, Q-Meter	\$1800
435B, Power Meter	\$500
436A, Power Meter w/Opt. 022	\$1000
4935A, Transmission Impairment Test Set w/Opt. 003	\$1100
5314A/01/02, Universal Counter	\$225
5316B, Universal Counter	\$1000
5328B, Universal Counter	\$1000
5335A, Frequency Counter, Opt. 10/20	\$850
5340A, Frequency Counter w/Opt. 01/02/011	\$1000
5342A, Microwave Frequency Counter, 10Hz-18GHz	\$900
5355A, Frequency Converter	\$1000
5386A, Frequency Counter, 10Hz-3GHz	\$2000
54100A, Digitizing Oscilloscope	\$2500
54100D, 1GHz Digital Oscilloscope	\$2700
54110D, 1GHz Color Digitizing Oscilloscope	\$2500
54120A, Digitizing Oscilloscope Mainframe	\$5750
54201D, Digitizing Oscilloscope	\$2650
6011A, Autotracking Power Supply, 20V/120A, 1000 Watt	\$1200
6274B, DC Power Supply, 0-60V, 0-15A	\$1250
6632A, DC Power Supply, 0-20V, 0-5A, 100 Watt	\$1000
8013B, Pulse Generator	\$750
8082A, Dual Pulse Generator, 250MHz	\$1200
8112A, 50MHz Pulse Generator	\$4000
8116A, 50MHz Pulse/Function Generator, Opt. 001	\$4000
8160A, Programmable Pulse Generator, 50MHz	\$2000
8165A/002, Programmable Signal Source w/AM	\$2200
8347A, RF Amplifier, 100KHz-3GHz	\$3000
8350A, Sweep Oscillator Mainframe	\$1000
8350B, Sweep Oscillator Mainframe	\$1500
83522A, Sweeper Plug-in, .01-2.4GHz, w/Opt. 02	\$4500
83540A, RF Plug-in, 2.0-8.4GHz	\$2000
83540A/002, RF Plug-in, 2-8.4GHz	\$2500
83545A, Oscillator Plug-in, 5.9-12.4GHz	\$1750
8411A/018, Frequency Converter, .11 to 18GHz	\$500
8494H, Programmable Attenuator (unused)	\$800
8495H, Programmable Attenuator (unused)	\$600
8501A, Storage Normalizer	\$1000
8505A, Network Analyzer w/8501A & 8503A	\$4000
8510A, Network Analyzer w/Opt. 010	\$7500
8510B, Network Analyzer w/Opt. 010	\$14,000
8554B, RF Spectrum Analyzer Plug-in, 500KHz-1250MHz	\$800
8559A, Spectrum Analyzer Plug-in, .01-21GHz	\$2650
8566A/B, Spectrum Analyzer, 100Hz-22GHz	\$17,000
8569B, Spectrum Analyzer, 10MHz-22GHz	\$7000
86222B, Sweep Oscillator Plug-in w/8620C Mntm	\$1250
8640A, Signal Generator, 0.5-512MHz	\$700
8640B, Signal Generator, Opt. 002, .5-1024MHz	\$2100
8640B, Signal Generator, Opt. 1, 2	\$2200
8654A, Signal Generator, 10-520MHz	\$450
8656A, Signal Generator, 100KHz-990MHz	\$1700
8656B, Signal Source, .01-2500MHz	\$2500
8660D, Synthesized Signal Generator	\$4500
8672A, Synth. Signal Gen., 2.0-18.0GHz	\$5500
8748A, S-Parameter Test Set w/Opt. 026	\$1350
8756A, Scalar Network Analyzer	\$1500
8757A, Scalar Network Analyzer, 10MHz-60GHz	\$4000
8901A, Modulation Analyzer w/Opt. 10	\$700
8901A, Modulation Analyzer w/Opt. 02 & 10	\$900
8903A, Audio Analyzer w/Opt. 001	\$800
8970A, Noise Figure Meter	\$4500
K382A, Variable Attenuator	\$2300

TEKTRONIX

1503, TDR Cable Tester w/Opt. 04 Recorder	\$1550
2215, 60MHz Oscilloscope	\$500
2236, 100MHz Oscilloscope w/Counter/Timer/DMM	\$1000
2246, 100MHz Oscilloscope	\$1600

2247A, 100MHz Oscilloscope w/Counter/Timer/Volmeter	\$2500
2337, 100MHz Oscilloscope w/DMM	\$1650
2430A, 150MHz Digital Oscilloscope	\$2850
2432A, 300MHz Digital Storage Oscilloscope	\$3000
2445, Four Channel 150MHz Oscilloscope	\$1500
2445A, 150MHz Four Trace Oscilloscope	\$1850
2465, Four Channel 300MHz Oscilloscope	\$2500
2754P, 10KHz-21GHz Spectrum Analyzer	\$8000
465B, 100MHz Oscilloscope	\$450
466, 100MHz Storage Oscilloscope w/DMM4	\$800
475, 200MHz Oscilloscope	\$650
475A, 250MHz Oscilloscope	\$800
576, Curve Tracer	\$2750
577/02, Curve Tracer, Non-storage w/177 Fixture	\$1750
7D20, Programmable Digitizer	\$400
7L5L3, Spectrum Analyzer, 20Hz-5MHz, w/Opt. 025 Tracking Generator	\$1850
7L12, Spectrum Analyzer, 100KHz-1.8GHz	\$1500
7L18, Spectrum Analyzer Plug-in, 1.5-18GHz Capable of 60GHz with Mixers	\$2500
7S12, TDR/Sampler	\$450
AFG5101, Arbitrary Function Generator	\$1500
CG5001, Programmable Calibration Generator	\$4000
DSA602, Digitizing Signal Analyzer	\$7500
PG506, Calibration Generator Plug-in	\$600
TM5003, Three Slot Power Mainframe	\$450
TM5006, Six Slot Power Mainframe	\$550

VISIT OUR WEBPAGE AT
WWW.RSSURPLUS.COM

MISCELLANEOUS

Acme Elect. PS2L1000, Electronic Load	\$850
Anritsu MS710-C, Spectrum Analyzer, 10KHz-23GHz	\$11,500
California Inst. 4500L/M3, AC Power Source	\$4000
California Inst. 4503L, AC Power Source	\$4000
Datron 1061A, 6.5 Digit Autocal Multimeter, DC Only	\$700
Datron 1062, 6.5 Digit Autocal Multimeter, DC/AC/Ohms	\$900
EIP 545A, Microwave Frequency Counter	\$800
EIP 548A, Frequency Counter, 10Hz-26.5GHz	\$2000
EIP 548B, Frequency Counter, 10Hz-26.5GHz	\$3250
EIP 578, Source Locking Frequency Counter	\$2500
ENI 325LA, Power Amplifier, 250KHz-150MHz 25 Watts	\$1850
Fluke 5100B/03/05, Multifunction Calibrator	\$3000
Fluke 5101B/03, Calibrator	\$3000
Fluke 5200A, AC Voltage Calibrator	\$2000
Fluke 8010A, Digital Multimeter	\$175
Fluke 8012A, Digital Multimeter	\$175
Fluke 8050A, Digital Multimeter	\$250
Fluke 8502A, Digital Multimeter, DC Only	\$225
Fluke 8520A, Digital Multimeter	\$350
Fluke 8600A, Digital Multimeter	\$85
Fluke 8810A, Digital Multimeter	\$250
Gigatronix 910, Frequency Syn., .05-26GHz	\$7000
Keithley 195A, Digital Multimeter	\$700
Kikusui PAB18-1, DC Power Supply, 18V/1A	\$100
Kikusui PAB18-3, DC Power Supply, 18V/3A	\$125
Kikusui PAB18-3A, DC Power Supply, 18V/3A	\$145
Kikusui PAB32-2A, DC Power Supply, 32V/2A	\$175
Kikusui PAD16-10L, Power Supply, 16V, 10A	\$300
Krohn-Hite 3202/R3202, Tunable Filter/Rack Version	\$500/\$350
LeCroy 9424, 350MHz Oscilloscope	\$3500
Marconi 2019A, Signal Gen., 80KHz-1040MHz	\$2200
Polarad 1105E-F, Signal Generator, 0.8-2.4GHz	\$400
Sorensen DCS40-25, DC Power Supply, 40V/25A	\$750
Trans. Devices DLR400 15 3500A, Dynamic Load	\$1500
Trans. Devices DLP 50-60-1000A, Electronic Load	\$800
Trans. Devices DLVP 130-110-1000 Electronic Load	\$950
Trans. Devices DLVP 50-120-1000 Electronic Load	\$1000
Valhalla 2703, AC Voltage Standard	\$2350
W & G DA-30, Protocol Analyzer	\$3000
W & G SNA5, 50Hz-3.2GHz Spectrum Analyzer	\$5000
Wavetek 178, Automatic Synthesizer	\$1850
Wavetek 650, Precision 2MHz Variable Phase Synthesizer	\$1700
Wavetek 2001A, Sweep Generator, 1-1400MHz	\$450
Wavetek 3000-200, Signal Generator	\$900
Wavetek 8003, Precision Scalar Analyzer, 10MHz-40GHz	\$2000
Wavetek 8501, Peak Power Meter	\$2000
Wiltron 560-7550, RF Detector, 10MHz-18.5GHz	\$300
Wiltron 560-7550, RF Detector, 10MHz-26.5GHz, Opt. 2	\$400
Wiltron 560-97N50, SWR Autotester, 10MHz-18GHz	\$600
Wiltron 560-97S50, SWR Autotester, 10MHz-18GHz	\$600
Wiltron 561, Scalar Network Analyzer	\$2500



R & S Surplus

1050 E. CYPRESS STREET, COVINA, CA 91724

(626) 967-0846 • FAX (626) 967-1999



PRECISE, KENSINGTON LABS, XY STAGE.

Model 8500-6X, 6"x6" of high performance travel. One of the best linear stages available. Highly repeatable, ultra-precise. Precision ground surfaces result in unmatched laboratory-grade performance. Linear glass scale, internally attached to the table, eliminates all drivetrain errors not measurable when an encoder is attached to the motor. System provides up to 0.025µm res. over 100 mm. Built from stress relieved 7075 aluminum. Crossed-roller bearings for excellent stiffness, load capacity and lifetime. Combined with a very low friction preloaded leadscrew and DC servo motor drive provides 20,000 hour MTBF. 100 mm/sec maximum speed and >50kg load capacity. Size: 15"L x 9"W x 2.75"H. Regular price > \$4K. X&Y stage with motors no drivers. USED, Very good condition. **8500-6, XY LINEAR STAGE.....\$1795**

350MHz, TEKTRONIX 485,

A superior performing O'scope, Dual Trace, Delayed sweep 1 nS/div Sweep rate, 5mV Vert. sensitivity. Switchable input imped., 50 ohm /1meg. Package includes 2 probes, cover and operation manual. Six month warranty. Excellent condition. **ORIG., \$9100ea.**

SPECIAL.....\$795

ULTRA MINI and WEATHERPROOF, "LIPSTICK" CAMERA

Sleek black anodized, alum. housing, O-Ring sealed & RAINPROOF. Adj. tilting mount. 1/3" CCD, 380 Lines, 0.3 Lux, AGC, Auto Shutter. 9-12VDC @100mA, 4mm, f1.8, 78° FOV real glass lens, NTSC video. <1ounce! IR SENSITIVE. 23mm d. x 50mm, 36" cable with BNC video & DC barrel jack. **GM-200K-STD.....\$119**
PINHOLE Model. So tiny you can install it directly into a door. Only a 0.9" diameter hole! Specs as above. 90° FOV Pinhole lens. 1/2 ounce! Size only 23mm d. x 35mm long. Think of the places you could put this little jewel. **GM-200K-PH lens.....\$119**

NEW! 0.008lux, COLOR NIGHT VISION CAMERA! UNBELIEVABLE LOW LIGHT PERFORMANCE. Our GMV-2K, DOES it in COLOR TOO!

For covert, military and scientific applications that must be color, this is it. Performance is enhanced through low speed electronic shuttering and digital frame memory. With an auto iris lens, 24 hour monitoring is possible. Auto sensitivity mode starts as it becomes dark. Eight Gain/Shutter modes are user selectable. Normal, X4, X8, X16, X24, X32, X64, X128. These provide frame rates of 60, 15, 8, 4, 3, 2, 1, and 0.5 frames per second. Auto/Manual white balance. Aluminum housing with dual 1/4x20 mounts. Specs: 1/3" CCD, with 291K pixels, 320 Lines, <1 Lux std. mode sens., 12VDC @200mA, Std. video out on BNC. Size: 54mmx50mmx94mm long. With pwr. adapter. All functions can be externally controlled via an 8 pin mini DIN. Uses std. c-mount lens not included.

Special Item, GMV2K.....\$589ea.

4mm, f1.4 A/I lens with custom cable.....\$99ea.

**Please fax us your list of
unique surplus material.**

NEW! DAYLIGHT to LOW LIGHT MINI CAM, w A/I LENS

For those applications that must work from dawn 'till dusk, this is it. Rugged aluminum housing with dual mounting sockets. Specs: 1/3" CCD, 420 lines resolution, 0.1 Lux sens., AGC, Auto shutter. 12VDC @120mA. Take full advantage of camera sensitivity with the super, 4mm, f1.4, 78° FOV Auto Iris lens included. Video out on BNC. Size: 50mm sq. X 65mm long. Power adapter included. Ready to go!

SPECIAL this MONTH, GM-510-A/I.....\$199ea. or 2 for \$369

CHECK THIS! ULTRA MINI, WEATHERPROOF & COLOR!

NEW "COLOR LIPSTICK" camera. For those applications that must be color, this is it. Black anodized, aluminum, housing is O-Ring sealed & RAINPROOF. Adjustable tilting mount included. Specs: 1/3" CCD, 400 Lines resolution, <1 Lux sensitivity, AGC, Auto Shutter. 12VDC @180mA, 4.3mm, 78° FOV lens, A real glass lens. Std. video out. Size: 32mm diam. X 65mm long. 24" leads with RCA jack and DC jack. With pwr. adapter. Ready to go!

SPECIAL this MONTH, GM-400K.....\$239ea.

NOW YOU CAN SEE WHAT THE "FISHES ARE DOIN' GO UNDERWATER (down to 60 ft.)

Waterproof B&W CAMERA with INTERNAL, INFRARED ILLUMINATOR!

Sleek black anodized, BRASS, housing is O-Ring sealed & WATERPROOF. Adjustable mount included. Specs: 1/3" CCD, 400 Lines resolution, 0.05 Lux sensitivity, AGC, Auto Shutter. Operates on 12VDC @225mA, 4mm, 78° FOV lens, A real glass lens. NTSC video out. Superior construction. SENSITIVE to IR. Ultra small Size only: 1.25" diam. X 2" long. With 60 ft. cable. Great for general outdoor use also. **REG. \$299, GM-300KIR.....\$219**

DOVER AIR BEARING X/Y TABLES, ULTRA PRECISE,

Like New, The ultimate in precision motion control. These are leadscrew operated air bearing tables with 1-20 Microns typical repeatability. Straightness, less than 1 micron each axis, angular error, less than 1 arc/sec. Squareness, less than 5 arc/sec. Three models available. Model "A" has 6"x6" travel with 2 type 238LS-021-02, 4.85A 24V Rapidsyn stepper/encoders. Type "B" is as above without motors. Type "C" has 4"x5" travel with two Compumotor LE57-51-MTR steppers. No controllers. **TYPE "A".....\$1200, TYPE "B".....\$949, TYPE "C".....\$849**

TINY, PRECISE, PORTESCAP SWISS, GEARMOTORS.

State of the art "Ironless" type, mini motors. Mod. A (left): 1219E-012-G-400 has 1044:1 Planetary gearbox. Size: 12mm d. x 44mm L. Model B (right): M11-210-54-0 with approx. 40:1 spur gearbox. Size: 16mm d. x 43mm L. Both have 2mm d. x 6mm L. flatted shaft, solder terminals.

VIN INL RPM

A: 6V 5mA 68

12V 5mA 145

B: 6V 8mA 141

12V 12mA 290

LIMITED QUANTITY

TYPE A: \$19ea. or 2 for \$34

TYPE B: \$15ea. or 2 for \$27

PIEZO ELECTRIC, 2-AXIS, TRANSLATOR

Physik Instrumente, P267 Like New, The ultimate in precision motion control. Includes two P178.37, 1/2" diameter PZT mounts. Each providing up to 40 microns of ultra precise movement. Motion can be controlled from the front panel or via an external control voltage. Rack mountable. **SPECIAL.....\$849**

COMPUMOTOR SX series, MOTION CONTROL

The SX is a bipolar, microstepping drive with built-in indexing. Drives two-phase permanent magnet step motors. MOSFET technology gives high performance in a small package while providing protection against short-circuit, brownout and over-temp. Built-in power supply. Indexer can store 99 multiple move motion programs in battery backed RAM. Programs can be selected via BCD inputs, programmable controllers or a computer via RS-232C Interface. The SX also provides the following features:

- 16 selectable resolutions (200 - 50,800 steps/rev)
- Smooth microprocessor controlled, wide range microstepping.
- Closed-loop positioning interfaces to incremental or absolute encoder.
- Motion profiling allows distance based velocity change without stopping.
- 90VAC - 132VAC, 50/60Hz power input. MANY more features too numerous to include here. Used, excellent condition. User manual.

SX model \$199 or 2 for \$349 also S model \$189 or 2 for \$329

TEKTRONIX 2465ADM, 4 Channels and 300MHz, O'Scope

on screen waveform

stats, DMM readout.

One of the most popular & powerful scopes available at a reasonable cost. Features: 500ps/Div sweep, 2mV/Div. vertical sensitivity, 1Mohm / 50-ohm input, 500MHz trigger bandwidth, four channels. On-screen waveform cursors provide vert. & horiz. scale factors, trigger level, voltage, time, freq., phase, ratio values and mode indication. Plus complete DMM! Complete with 2 probes, pouch, and manual. Mint condition, 90 day warranty. **\$2695.**

END FIELD of VIEW GUESSWORK!

3.5 to 8mm VARI-FOCAL LENS

Brand New, super f1.8 lens allows you to smoothly adjust from a 97° FOV @ 3.5mm to a 44° FOV @ 8mm. Now you can frame your area of interest just the way you want it! Standard C-Mount with adjustable focus and iris. **SPECIAL.....\$99ea. or 2 for \$189**

IS ANYBODY OUT THERE?

RESOURCES UN-LTD.

VISA, MC, AMEX, DISCOVER, COD.

ORDER: 800-810-4070 TECH: 603-668-2499

FAX: 603-644-7825 E-MAIL unlt4u@tnc.net

300 BEDFORD STREET, MANCHESTER, NH 03101

NEW, "STEALTH CAM", MICRO, with AUDIO!

The sleek aluminum housing fits like a glove! Removeable mounting bracket and a 1.3M cable with BNC vid., RCA aud., (internal mic) & DC barrel jack for, no sweat hook up. Why fool around with an open P.C. board? Now you can have the "STEALTH CAM". 1/3" CCD, 410 Lines, 0.3 Lux, AGC, Auto Shutter. Pwr. from 9 to 12VDC @110mA, 250K pixels, Std. model, 4mm, 78° FOV lens, Pinhole model, 90° FOV. A real glass lens. Focus from 10mm to infinity. NTSC video out. Only 1.7 ounce! SENSITIVE to IR. Size Std: 30mm sq. x 29mm d. PH is 16mm d. **WARNING:** Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS.

GM-2000S-STD, w/aud.\$79.00

GM-2000S-PH, w/aud.\$79.00

VICTOREEN 10,000Volt, 100Megohm Resistor!

A must have for serious high voltage work. New, non inductive, 5% tol., low tempco. Mini size only: 1" x .27" x .06" Hard to find. **10 for \$6 or 50/\$24**

**SLIM MOX
104 100M 5%**

Brand New, Video Motion Sensor. Model VM10. Attach

to any standard video signal and you've got an electronic "watchman" diligently watching the entire scene. Or any adjustable sized area within the scene. Such as a doorway or even a drawer or cabinet. A state of the art security aid. The unit will close a contact when it senses a change. Use it to turn on a VCR or call the hounds. Auto or manual reset. Compact, ac powered. Adjustable sensitivity. Video loop through jack. **NEW VM-10.....\$189.**

Low cost MICRO CAMERA, w/audio

1/3" CCD, 410 Lines Res., 0.3 Lux sens., AGC, Auto Shutter. Pwr. from 9 to 12VDC @100mA, 250K PIXELS, Std. model, 4mm, 78° FOV lens, Pinhole, 90° FOV. A real glass lens. Both focus from 10mm to infinity. Std. NTSC video out. 1/2 ounce! SENSITIVE to IR. Size Std: 1.25" sq. x 1" d. PH is 0.6" d. 1.6M long wiring harness with connectors included. **WARNING:** Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS. Six different models.

GM-1000A-STD.....\$60 GM-1000A-STD/Aud.....\$65

GM-1000A-PH.....\$60 GM-1000A-PH/Aud.....\$65

GM-1000A-CMNT.....\$60 GM-1000A-CMNT/Aud.....\$65

Micro Lenses for GM1000 series

2.5mm, 150°.....\$22 8.0mm, f2.0.....\$22
4.3mm, 78° f1.8.....\$22 12.0mm, f2.0.....\$22
6.0mm, f2.0.....\$22 5mm, 70°PH.....\$22

C-MOUNT LENSES

LOW LIGHT 16mm, f1.6, 15° FOV.....\$39 4mm, 80° FOV.....\$24
8mm, f1.3, 40° FOV.....\$49 8mm, 40° FOV.....\$24
4mm, f1.4, 78° FOV.....\$49 12mm, 28° FOV.....\$24

6V@12AH SEALED, RECHARGEABLE, BATTERY

New Panasonic, LCR6V12PI. Tough to get at a discount. Very compact. Two top mounted 1/4" faston connectors. Perfect for high drain projects. Size: 5.9"L x 3.7"H x 1.9"D **2 for \$20, or 10 for \$89**

NEW, 2.4GHz VIDEO + STEREO AUDIO TRANSMITTER with SONY, CCM-PC5 COLOR CAMERA.

Originally sold for \$500! Now available for a fraction of that price. Great looking styling. Camera has a very stable, adjustable tilting base, front panel LED pwr. indicator and sensitive built in electret mic, providing excellent audio and video performance from one compact package. Simply connect camera to the completely self contained 2.4GHz transmitter. All cables supplied. You can transmit up to 700 feet clear line of sight! Companion matching receiver works with any TV or VCR. Internal patch antennas. Camera has adjustable focus 6mm lens. (1" to infinity, macro capable) Auto power off when the privacy shutter is closed. Power is 7-13VDC. (all pwr. adapters and cables included) 1/3" CCD, 330Lines res. 35% better than standard VHS! Can also be used to transmit VCR output to another TV for remote viewing.

SPECIAL, 2.4GHz SONY-ASTROVIEW.....\$189ea. or 2 for \$339

addtl. 2.4GHz TRANSMITTER/RCVR. less Camera...\$129ea.

MOTORIZED ZOOM LENS SPECIAL, 6X mag. and auto iris!

New, fabulous hi-res. optics with std. C-Mount. Superior Fujinon and Vicon lenses. Normally cost from \$600 to \$1500. There is no substitute for a good lens! All drive motors will operate from 6-12VDC. The Auto Iris has a built in amp which works with any cameras video output for control.

Type B-6, 12.5 to 75mm, 6X, f1.2 \$189 or 2 for \$349

ZOOM LENS CONTROLLER, NEW \$169

10V @ 2.5 AH SEALED, LEAD ACID, PACK

Each pack consists of five, 2 Volt cells. Each cell the size of a std. 'D' battery. They are arranged as 1X5 cells. Enclosed in an ABS outer shell. (removed for photo) Mint condition. Perfect for robotics and other high drain applications. Buy several, make custom packs of any rating. Size: 7.5"L x 2.8"H x 1.5"D **5-five packs for \$20, 30 for \$99**

TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

QUESTIONS

I would like to build an adjustable thermal switch circuit to turn a 120-volt fan on/off. The circuit will be used with my home stereo receiver to turn on/off at set temperature of receiver temperature. The thermal sensor will be located on the outside of the receiver cabinet.

The fan is 120 volts and impedance protected. The circuit could also be used to operate a brushless 12-volt DC fan as well.

4991 Brad King
Winter Haven, FL

I am the proud owner of a military surplus PU-286 generator. The machine was made in 1958. While the generator is in fairly good shape, it could stand an overhaul.

Where can I obtain repair parts for the engine and the alternator. Operating supplies such as oil filters and exciter brushes are also needed.

4992 Bob Feeney
Atlanta, GA

I have a 1 MHz oscillator. Can anyone come up with a circuit that will provide outputs at 100 KC, 200 KC, and 500 KC.

I have 7490 and 4017 ICs on hand. The 1 MHz output is about 4-1/2 V PTP squarewave.

4993 Roger W. Hamel
Cedarville, MI

I have a Caller ID compatible modem that I would like to read the Caller ID information from the modem with Visual Basic 4.0 or 5.0.

Any suggestions on where to begin?

4994 Dan Hockey
via Internet

At my office we have a problem with telephone extensions ringing in adjacent cubicals causing confusion with exactly who's extension is ringing. If you are standing more than a few feet away from your phone, you never know if it's your phone or not.

Is there some type of visual indicator (preferably LED) that can detect a ring and flash? This device must not be electrically connected to the phone system, i.e., it must use the sound of the ring or something of that nature to do its ring detection.

The type of phone we use is the

Lucent Technologies 825 (nice phone — lousy ringer).

I work at a government agency, and I cannot connect anything to the phone. I would like to run this up to the top of the cubical to give me a visual queue to my ringing extension.

4995 R. S.
Baton Rouge, LA

In regards to the Alphastar satellite system: Is there a way to change the S/R (symbol rate, Astar's is 23.000) and the FEC (freq. error correction, Astar's is 2/3) to a different setting that would allow one to use this receiver to view MPEG 1 or 2 digital? This system was manufactured by Tee-Comm, Inc.

Would this be a firmware change/mod?

4996 Chief
via Internet

I am looking for an inexpensive way for a young ham operator to build a direct conversion receiver to listen to W/AW, either 80 or 40 meter.

This receiver should be where we could wind coils on a photo container. All the parts should be available at RadioShack.

4997 Virgil Gochee
Shabbona, IL

In cannibalizing a computer, I thought I had a good power supply (Power Tronic TK 4230DC). However, it trips off in less than one second, perhaps because one output (the "power good") is unused.

How do I hook up the "power good" lead so that the power supply will operate?

4998 Scott Duink
Los Gatos, CA

I have two UPS with similar problems. They both work except they shut down after they switch and start generating their own power.

They act as if the battery is low, but they are both good (fully charged). One will operate fine on low-line voltage, but shuts off when the line voltage goes below about 50 volts. The other shuts off after 0.1 to 2 seconds after power loss and also works on low-line voltage.

One is an ABI International

model Probackup 5000, the other is a Deltac model PRB 300. Why are they so complicated to do a relatively simple job?

4999 Gordon Simkin
Bellevue, FL

I need to locate a product that was made years ago in Sharon, PA. The name was "SAL-MET FLUX" solders all metals. It was a soldering flux that you could use with regular solder and you could solder aluminum, stainless, etc.

The company was a small operation, Hascol Enterprises and then sold to Henry Manufacturing in Westville, IL and now I cannot find any information on it.

49910 Ron Wineland
Meadville, PA

I understand that the military has been using a "cigarette pack size" electronic device to remove sulfation from car batteries, with up to five times the original lifespan of the batteries. I am looking for the circuit.

49911 Paul Isvolt, Jr.
Brantwood, WI

My VCR has channel 3 and 4 output. I would like to feed this into something that I can build or modify to have channel 3 or 4 in (one or the other not both), with channel 2 out, and have adjustable fine-tuning, and pass stereo audio.

49912 Lane Dixon
Haysville, KS

How do I interpret the error codes that pop up on the screen when a computer boots up with a problem? (Example: Screen reads bad fault in MS DOS extender).

49913 Larry Amati
Smithton, PA

I have several old King two-way radios: model LPA 5141 FCC ID ASY7BL LT 2001 made in Lawrence, KS.

The units have a rotary switch providing up to 14 different frequencies. Some are set from 144 to 163 MHz and some are blank, but make a squelching noise when squeezing the transmit button.

Where can I get a schematic or find someone who is familiar with

ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed.
- In most cases, only one answer per question will be printed.
- Your name, city, state, and E-Mail address, (if submitted by E-Mail), will be printed in the magazine, unless you notify us otherwise with your submission.
- Due to space limitations, we can not reprint the original questions with the answer. The question number and the issue it appeared in are printed above the answer.
- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

QUESTION INFO

TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

these radios, and how can one change frequency settings?

How much power are they putting out with a fully charged 10-volt battery? What distance can I reach?

49914 Pierre Hoyt
W. Bethesda, MD

I have an old IBM 3270 PC, model 16 with 640 KB, 5-1/4 disk drive that uses double density, double sided floppies.

Since I have no need of the newer, faster PCs on the market, I

TOOLS

**TWEEZERS, FORCEPS,
SCISSORS, DREMEL
TOOLS, OPTICAL AIDS,
PLIERS, SCREWDRIVERS,
WHOLESALE & RETAIL**

LASER POINTERS



Using high quality laser optics and microelectronics you can cast a 1/4" diameter dot as far as 1600-1800 ft away. Great for professional demonstrations, teachers, and even for amusing your dog or cat. Comes with 3 replaceable LR44 batteries; these are like watch type batteries. Has a wavelength of 630-680nm.
#LS2133 Unit 1 \$10.00

3 LENS HEAD MAGNIFYING GLASS

That's right! Not 1 lens but 3 lenses. This magnifier has many features and its easy operation as follows:
1. Light weight (approx. 110g only). You can get a clear, solid view in wide sight through the double lens two square glass.
2. Velcro head adjustable band to fit your head.
3. Convenient use. There's no need for the users to take off his glasses, and his hands will be free moving.
4. With one touch design, the magnifier is with a 1.8 power to a 2.3 power in just one touch. Then you can change the magnifying time from a 3.7 power to a 4.8 power.



#HM 213 Unit 1 \$19.00

**VISIT US AT
WWW.UTOPIATools.COM**

**UTOPIA
TOOLS**
CALL FOR FREE CATALOG
TOLL FREE 1-888-UTOPIA-2



The RF Connection
213 North Frederick Ave.
Suite 11NV
Gaithersburg, MD USA
20877

<http://www.therfc.com/>

**Complete Selection of MIL-Spec Coax, RF
Connectors and Relays**

UG-21B/U N Male for RG-213/214.....\$5.00
UG-21D/U N Male for RG-213/214.....\$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913.....\$6.00 Pins Only.....\$1.50
UG-21D/9913.....\$4.00 Extra Gasket......75

Amphenol 83-1SP-1050 PL-259.....\$0.90
UG-176/U Reducer RG-59/8X .25 or 5/16.....\$1.00
UG-175/U Reducer RG-58/58A .25 or 5/16.....\$1.00
Silver Teflon PL-259/Gold Pin.....\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F. 9913 with High Density PE Foam dielectric, stranded center cond. and Duobond III Jacket.....80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket Intro Price.....\$23.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom, Kenwood, and Yaesu

8 Pin Mike Female.....\$2.50
8 Pin Mike Male Panel.....\$2.50
13 Pin DIN for Kenwood.....\$2.75
8 Pin DIN for Icom.....\$1.00
8 Pin DIN for Kenwood.....\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666
Info 301/840-5477
FAX 301/869-3680

TECH FORUM

am reluctant to go out and buy a new PC.

My problem is that I would like to use several software programs that are on 3.5" 144 KB disks.

Would it be possible to add a 3.5" disk drive to this unit? What would I need in the way of hardware if it can be done?

**49915 Pete Bartholomey
Chattanooga, TN**

I need a solution to interface TV audio output to a strip of 10-20 headset jacks used in a dorm environment day room as a noise preventive. On the newer TVs, the output device overloads.

**49916 D. B.
Lansing, KS**

I hope to construct a series (61 total) of very narrowly selective band-pass filters (ideal less than 2% BW) to be used with live and recorded outputs of music synthesizers.

The outputs of these filters, rectified and likely buffered, would be used to selectively 'gate' the outputs of 61 selectively 'tuned' gravity-wave (per Gregory Hodowanec's work) sensor-oscillators.

With so many (61) filters needed, simplicity of construction and lowest costs are a prime consideration. Also, for the sake of flexibility and portability, this 'filter bank' should not be computer technique dependent.

**49917 Bill Ramsay
Grand Junction, CO**

I have a GBC look-out video camera, model LC2001. I need the pin out of the plug on the camera or a schematic.

**49918 Frank Bowen
Fresno, CA**

I drive a turbo diesel and the engine compartment suffers from very high temperatures in the summer. This has resulted in several premature failures of my alternator mounted voltage regulator (cracked).

Can you provide a design utilizing heatsinks and high-quality components so I can build and remote mount a regulator?

The regulator now on the alternator is about 3/4" square, and 1/4" thick with three connections: one to ground, one each to two brushes. I will modify the brush plate and provide connectors.

**49919 Roger Simon
Orlando, FL**

ANSWERS

ANSWER TO #3997 - MAR. 1999

Whenever you get a "Blue Screen of Death" (BSOD) in Windows, it means that a program did something bad, usually trying to access an illegal memory address or

performing an illegal function (i.e., divide by zero). Since you didn't give any more detailed information, I can only assume that one or more software modules used by Explorer is corrupted.

Question: Does the BSOD happen with any other program either before or after you use Explorer? If so, that program might be the culprit. Reinstall it and see if that fixes

the problem.

Next, I suggest you disable any/all programs you loaded at boot-up (i.e., "empty" the "Startup" folder) and see if Explorer still gives the BSOD. If it does, then you need to "refresh" the Explorer software by running SETUP on your Windows install CD/floppy and choosing "Restore damaged/missing pro-

Continued on page 54

ANSWER TO #39910 - MAR. 1999

A friend of mine bought a Spectracom WWVB VLF receiver/comparator without its active antenna. The manual didn't provide any schematics for the antenna, but the receiver input section supplied 12 VDC through a few kilohms and wanted a 50-ohm AC input.

We found many WWVB antenna designs on the web, but the designs did not meet the 50-ohm requirement or had other problems, so we built our own antennas.

The first was a ferrite loopstick 0.5 x 3 inches that had trouble locking [WWVB signal strength is about 100 microvolts per meter here]. The second was a small loop antenna of an 8 inch diameter, and it worked okay. The third was a 20 inch diameter loop that produced a signal big enough that I could see it on my [very sensitive] scope, but it was never connected to the Spectracom.

The output transformer has a tap with a 1:7 turns ratio. That raises the 50-ohm load impedance to about 2500 ohms. For a Q of about 100, the transformer reactance should be 25 ohms ($X_L = 2 \pi f L$, or $L = 25 / (2 \pi f) = 66$ microhenries). I used an MPP toroid (Arnold A051027) at 27nH/square turn, so $N = \sqrt{66 \mu H / 27 nH} = 49$ turns. I put the tap at seven turns.

If you use a different core, then calculate the proper number of turns and make sure the core has reasonably low loss at 60 KHz. Use thick wire to improve the Q. The resonant capacitor is $C = 1 / (L (2 \pi f)^2) = 106 nF$, but the value is not exact and must be tuned. I used a signal generator (with the loop antenna disconnected) and two paralleled capacitors to tune the output tank.

Use a large capacitor to get close and then use a smaller capacitor to fine tune the tank. You can also adjust the number of turns, but one turn changes the inductance by about four percent. You must tune to 0.5 percent or better.

Wind the 20 inch antenna loop as 11 turns of number 12 solid insulated wire (the kind electricians use); that's about 60 feet of wire. I taped the wire in a few spots so it would keep its shape. This loop must also be tuned, so I inductively coupled the signal generator to the loop and adjusted the input capacitors to maximize the response. I needed about 60nF ($X_C = 44$ ohms), but your results will vary because a scramble wound antenna loop is not well characterized. The loop must be very low impedance, so make solid connections between the loop antenna and the resonating capacitors.


The transistor is targeted for 1mA of collector current. The voltage gain to the collector should be about 80, and the gain to the tap about 11.

The input impedance of the amplifier should be about 3K, and it limits the antenna Q to about 70 (3K/44). You can check the literature for info about adding an electrostatic shield without imposing a shorted turn. We saw a lot of power line impulse noise, but it was magnetic.

Antenna orientation is important. The plane of the loop should be perpendicular to the ground, and the plane should include Fort Collins, CO.

Computer monitors throw out a lot of trash around 60 KHz, so locate the antenna far away from them (and turn them off if you have trouble locking).

**Gerald Roylance
Mountain View, CA**

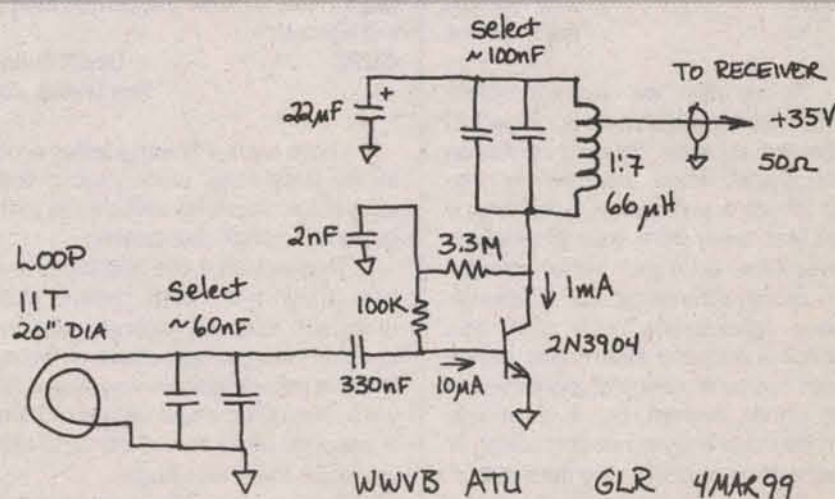


HAM GEAR FOR SALE

WANTED: ROCKWELL-Collins HF-80 equipment, 851S-1, 237B-3 log periodic, Collins literature. Jim Stitzinger 805-259-2011, 805-259-3830 (fax), bfl-jfs@smartlink.net

HAM EQUIPMENT repair or overhaul Collins, Drake, Swan, Astro, Yaesu, Kenwood, etc. 20 years experience with former Slep Electronics Co. Same excellent service, same reasonable rates, satisfaction guaranteed. Brooks Electronics, 828-349-3503. E-Mail: rwbrooks@dnet.net

LML RADIO & electronic: UHF Syntor 16 ch. prg. 45 watt \$50; 2 meter amp 60W \$30. GE, Midland, and more test equipment & other surplus. Free catalog 909-873-1319. Fax on demand 24 hr. 909-820-1885. Web catalog <http://members.aol.com/hrh6> Write 424 E. Shamrock, Rialto, CA 92376.

NEW PRODUCTS FROM S & S: UPGRADE YOUR OLD RIGS! Digital dial (counter) has 10Hz resolution HF, 100Hz VHF and frequency range 50KHz to 230MHz; kit \$99.95; assembled \$149.95. **NEW Digital VFO** with 1Hz resolution to 54MHz; kit \$169.95; assembled \$219.95. S&H \$7 (Continental US). **GUARANTEED TO WORK.** For info send SASE. Call/write to order: S & S Engineering, 14102 Brown Rd., Smithsburg, MD 21783. 301-416-0661, E-Mail: N3SAD@aol.com or see <http://www.xmetric.com/sseng>

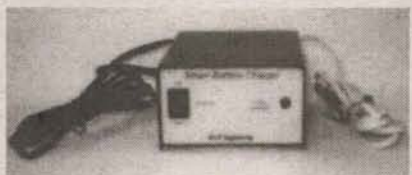

THE SMART BATTERY CHARGER for lead acid or gel cell batteries. Can be left connected to the battery **INDEFINITELY**, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MC/VISA accepted. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280.



MIKEMASTER: A microphone preamplifier with noise gating & compression. Created by Marv Gonsior W6FR, March 1998 QST. Got noise get MikeMaster! For kit order #210-KIT at \$69.95. Assembled & tested (specify Kenwood, ICOM, or Yaesu wiring) order #210-ASY at \$89.95. Shipping for US & Canada is \$6.50, others add 15%. CA residents add 7.75% sales tax. For info send legal size SASE to A&A Engineering, 2521 W. LaPalma #K, Anaheim, CA 92801. P 714-952-2114, Fax 714-952-3280.

KENWOOD TS-430S, PS-430, SP-820, AT-250, MC-42S, Shure-444-D, antenna, coax, and much more. Call 510-222-4445 or olfarter@aol.com

NEW 1999 catalog: Inductors, toroids, TC ceramic and Mica capacitors, semiconductors, wire and cable, hardware, more. Two stamps please. Johnson Shop Products, Box 2843, Cupertino, CA 95015.

Subscribe to Nuts & Volts!
Call 1-800-783-4624

Oldest Personal Computer Show in the World! Super NEW show location!

TRENTON COMPUTER FESTIVAL



24th Year!

MAY 1 - 2, 1999

TCFTM 99

AT THE NJ CONVENTION CENTER - EDISON, NJ

Indoor Vendors - 100 Speakers & Seminars - Ham Radio Testing
Internet Cafe - Hi Tech Job Fair - 1,000 Spot Outdoor Fleamarket
Saturday Night Banquet - National Vendors - New Expanded Location!

(Located at Exit 10 of the New Jersey Turnpike - Edison, New Jersey)

SHOW INFO CALL: (800) 631-0062

Check our Web Sites: www.tcf99.com (Vendor info)

www.tcf-nj.org (Attendees/Speaker Program/Directions)

Fax: (732) 422-0076

Managed by KGP Productions, Inc.

(c) 1999, Trenton Computer Festival, Inc.

HAM GEAR WANTED

CB - SCANNERS

KONNEX DISTRIBUTING. Call 1-888-777-7874. PO Box 451372, Los Angeles, CA 90045. CBs, antennas, meters, transistors. Best prices. Credit card acceptable.

SALES, SERVICE: CB equipment, radios, modifications, power mice, echo-reverb boxes, kits, meters, filters, antennas, noise toys, mounts, hard-to-find items. Partial list \$1, complete list \$4. D&R Electronics, 10 Park St., Thomaston, CT 06787. 860-283-9492.

HOW TO LOCATE HARD-TO-FIND CB (EXPORT, LINEARS, MODIFICATIONS, KITS, TECHNICAL BOOKS AND ACCESSORIES). THE RADIO HOBBYIST DEALERS DIRECTORY over 200 dealers, distributors, and manufacturers worldwide. Only \$19.95 send to Lord/Wyatt Communications, Dept. HDA, 147 Halsey St., Brooklyn, NY 11216-2103. 718-789-7329 ext. 16.

SCANNING USA: monthly magazine 100% scanning. All the news and product reviews from the writers you trust. Get more from your scanner. Subscriptions \$24.95, samples \$3. Call 1-800-651-0922 your Visa or MasterCard, or write 2054 Hawthorne, Joliet, IL 60435

ANTTRON 101 CB 10 METER base station antenna with isolation network, no bleedover, no splatter, no TVI tuning sleeve technology 3 piece fiberglass \$69.99. **Twin-Tronics, Inc.** PO Box 2571, Youngstown, OH 44507-0571. Send \$1 for literature, refundable. Ph 330-788-9693. Fax 330-788-7709.

ELECTRONIX EXPRESS

WELLER SOLDERING STATION - MODEL WLC 100

- Variable power control (5 to 40 watts)
- Replaceable heating element
- Quality light-weight pencil iron

\$36⁹⁵



DUAL-TRACE OSCILLOSCOPE


W/HIGH RESOLUTION, BLUE CRT
INCLUDES PROBES, POWER CORD
2 YEAR WARRANTY
Goldstar 5020
20MHZ \$349⁰⁰



INSTEK FUNCTION GEN.

WITH INT/EXT
FREQ. COUNTER

MODEL 8016 \$215⁰⁰

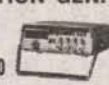

SCOPE PROBE 60 MHZ

SWITCHABLE X1, X10 \$12⁹⁵

ALLIGATOR LEADS

SET OF 10 \$2¹⁰



DIGITAL MULTIMETER

WITH CAP/FREQUENCY/
TRANSISTOR TESTER
Model DM645 \$34⁹⁵



SWITCHES

8 POS DIP 60¢ ea.
Mini Toggle SPDT 50¢ ea.



PAD-234

DIGITAL/ANALOG TRAINER

Complete portable workstation. Variable and fixed power supplies, function generator, digital I/O, rugged design, high impact case.



Assembled

\$150⁰⁰

Kit

\$110⁰⁰

HIGH QUALITY TOOLS

With Cushion Grips and Return Spring

Needle Nose Pliers \$2⁹⁵ Wire Stripper \$1⁵⁰ Diagonal Cutter \$2⁹⁵

POWER SUPPLIES

0-30 VDC, 0-3 Amp. Built-in current limiting, overload protected, constant voltage and current operation.

01PSGP4303A Analog Display \$165.00
01PSGP4303D Digital Display 189.00



SOLDERLESS BREADBOARD

830 tie points. MB102PLT model features 3 binding posts and aluminum backplate.

Part No. 1-9 10+
MB102 5.95 5.00
MB102PLT 8.95 8.00



HELPING

HAND

WITH

MAGNIFIER

#060836



RESISTOR KIT

1/4W 5% film. 5 pieces each of 73 values. 365 pieces total.

\$3⁹⁵

MOTION DETECTOR

\$2 ea. - 10 For \$15

LM555 10 Min. 22¢ ea.
LM741 10 Min. 27¢ ea.
74LS00 10 Min. 18¢ ea.
7805 Regulator 10 Min. 30¢ ea.
2N3904 10 Min. 6¢ ea.
PN2222 10 Min. 6¢ ea.
Red LED T 1 1/4 10 Min. 6¢ ea.
Green LED T 1 1/4 10 Min. 7¢ ea.
Yellow LED T 1 1/4 10 Min. 8¢ ea.
Photo Cell 10 Min. 65¢ ea.
100K Pot., 1" Shaft PC ML 10 Min. 15¢ ea.

SOLDERING IRON 3-WIRE

HIGH PERFORMANCE \$5²⁵

#060501

SOLDERING IRON STAND

W/SPONGE \$3⁵⁰

#060842

1 LB. 60/40 Solder Roll .031"

\$5⁹⁵

DESOLDER PUMP W/TIP

\$3⁵⁰

#060820

15 TURN POT

69¢ ea.

Bourns 3006P series. All standard values available.

7 SEG. DISPLAY

60¢ ea.

MAN72 C.A Red 0.3" MAN74 C.C Red 0.3"

FREE CATALOG

MORE Low-Priced Items In Our FREE 216-Page Catalog



TERMS: Min. \$20 + shipping. School Purchase Orders, VISA/MC, Money Order, Prepaid. NO PERSONAL CHECKS, NO COD. NJ Residents: Add 6% Sales Tax.

In NJ: 732-381-8020

FAX: 732-381-1572

365 Blair Road • Avenel, NJ 07001-2293

800-972-2225

<http://www.elepx.com>

email: electron@elepx.com

FREE CATALOG: hobby radio books; frequencies, modifications, repairs, upgrades, maintenance & more! Largest source of monitoring books available in one catalog! CRB, PO Box 56-NV, Commack, NY US 11725. Phone: 516-543-9169, 9-3, M-F. Fax: 516-543-7486. E-Mail: catalog@crbbooks.com

240+ CHANNEL CB/HAM/COMMER- CIAL radios: AM/FM/SSB/CW export/domestic: RCI, Motorola, Uniden, Cobra, Alinco, Kenwood. Mics, antennas, linears, meters, books, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244.



ULTIMATE MODIFICATION BIBLE Vol. 9. Mind boggling is the only way to describe this 232 page book. Modification of CBs, channels, power, sliders, talk back and more. 10 meter radios, HAM radio, scanners, toys, meters, and more. Only \$29.95 + \$4 shipping. Phone orders 1-800-256-9895 (MC-Disc-Visa) No CODs.

CB MODIFICATIONS! Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBI, Box 1898NV, Monterey, CA 93942. www.cbintl.com

MESSENGER, RED Devil, Shooting Star, Palomar, Superstar, Uniden, CB radios, microphones, exports, Galaxy, etc., more!! 5 page picture price sheets \$1 (refundable) scanners too!! Galaxy, Box 1202, Akron, OH 44309. Over 15 yrs. in business!

**Closing Date For
Next Issue - April 5th!**

IFR T-1200SR scanning receiver, combination spectrum analyzer, oscilloscope, frequency error meter, modulation meter, signal strength meter. 100KHz-1GHz in 100Hz increments. \$3,450, 90 day warranty. Ph 561-747-3647, fax 561-575-4635.


MUSIC & ACCESSORIES

WANTED: OLD guitars/tube amps. Fender, Gibson Vox, Gretsch, Rickenbacker, Martin, etc. 405-737-3312 fax 405-737-3355. E-Mail: SonnySound@aol.com

COMPUTER HARDWARE

WE CARRY a variety of cables, switch boxes, accessories, and adapters to connect PCs, printers, Mac's, networks, telecommunications, and audio/video equipment. We offer: custom cables, free catalogs, and same day shipping on most orders. Visit our website at www.rogerssystems.com or call 1-800-366-0579.

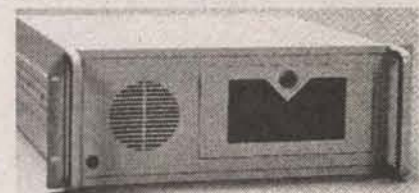CRTs CHEAP. Buy direct from the manufacturer. Save money. Mfg. all CRT types since 1950. 3 year warranty. Reg-Res 19" tubes \$75; 25" \$100; hi-res 13" tubes from \$80. We specialize in hi-resolution video/computer CRTs. T.M.C. 215-226-0749/215-223-0388.



19" RACKMOUNT PC chassis: Heavy duty, 4U, for standard 7 slots ATX motherboard. Optional 8, 12, 14 slots back panels available. Four (three hidden) 3.5"/two 5.25" drive bays, 4.625" front panel fan, power supply not included, \$169 with this ad! Monitor chassis \$229, keyboard chassis \$129. 8255-8253 I/O card with prototyping area \$69, 12-bit ADDA card \$89. Computronics Technology, 972-242-8087.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

EVERYTHING NEW w/warranty! MII 333MHz \$165, 15"/17" SVGA monitors \$145/225. Pentium systems from \$350. Also multimedia kits, hard drives, scanners, printers, SCSI adapters \$45. Memory, cases, etc. Call for monthly specials. CCI 714-778-0450. E-Mail: cci@net999.com

MII 333MHz multimedia systems liquidation \$395. Monitors \$100, laser printers \$175, color inkjets \$95, notebooks \$350, 486DX motherboards + VGA \$30. Closeout prices on software. Call 714-778-0450.

HARD DRIVE liquidation 85 megabytes \$25. 420 megabytes \$45. 8.4 gigabyte \$155. Mouse \$1.95, SVGA monitors \$135, flatbed scanners \$45, 56K modems \$35, 386SX40 \$25, 1.2 floppy \$15, Adaptec SCSI controllers \$45, memory 1.25/megabyte. 714-778-0450.

4 MB, 72 pin SIMMs \$4 ea. P-100 CPU \$25 ea., 400 VA UPS \$30 ea. Pikul & Assoc. 314-937-0335.

VIEW SONIC 21" P815 monitor, xfer warranty, like new, \$600. 314-937-0335.

OCEAN STATE ELECTRONICS

CALL, WRITE OR FAX FOR OUR FREE 104 PAGE CATALOG 1-800-866-6626

Step back into the past and build a Vintage tube type receiver or transmitter. Each kit comes with all the necessary components to get you on the air vintage radio style. A great opportunity to learn to build, troubleshoot and operate vintage tube type equipment.

THE CAKEPANION RECEIVER KIT 2 TUBES GENERAL COVERAGE REGEN



- Receives Am, SSB, and CW
- Regenerative Receiver Design
- Uses two 6AQ5 Tubes
- Continuous coverage 500 KC - 10MHz using pre-wound plug in coils as in old fashioned regenerative receivers (Coils sold below)
- Smooth Vernier Dial Tuning (No Logging Scale)
- J fet front end isolates the antenna and adds RF gain
- Solid frequency stability
- Ultra sensitive reception
- Hi Fi quality audio into 8 ohms. Enough to drive a small speaker (not included)
- Headphone Jack
- Audio clipper circuit eliminates key clicks and heavy static.
- Solid state power supply
- Complete punched and drilled chassis (tuning caps and solder lugs are pre-installed)
- Well written detailed assembly instructions include color pictorials. Manual included.
- Assembly time approx. 6 hours
- Measures 9" Wide x 9" Deep x 2" High • Weight approx. 5 lbs.

ASSEMBLE A COMPLETE QRP STATION: THE CAKEPANION RECEIVER MATES PERFECTLY WITH OUR CPCW-5 TUBE TRANSMITTER

Part No.	Description	Price
CPR-1	2 Tube Receiver Kit	\$119.95
CPR-B	Broadcast Band Coil 500KHz-1800KHz	\$14.95
CPR-160	160 Meter Coil 1.5 MHz-3.0MHz	\$9.95
CPR-80	80 Meter Coil 2.9MHz-7.5MHz	\$9.95
CPR-40	40 Meter Coil 4.0MHz-10MHz	\$7.75

DIGITAL LCR METER — ALSO MEASURES VOLTS, AMPS & FREQUENCY

At Last! An LCR meter that everyone can afford. Now you can measure coils, transformers, chokes from 1µH to 40H. Capacitors from 1 pfd to 400 mfd and resistors from 1 ohm to 40 meg ohms. DCV to 1000 V. ACV to 750V. Freq. 1Hz to 4MHz. Great price for this instrument.

LCM-1950..... \$79.95

VARIABLE CAPACITORS BROADCAST TYPE — 1/4" SHAFT

1 GANG 14-365PF.....	\$10.95
2 GANG 10-400/10-400/PF.....	19.95
3 GANG 15-500PF/SEC.....	12.95

Many more types available from small air trimmers to large 4KV tuner types.

6146W POWER TUBE

Regulated version of popular 6146B used in many transmitters. MFG. GE

\$17.95 EA. or \$37.00 MP

12BY7A Driver \$15.95

CALL US FOR ALL YOUR TUBE NEEDS.

LEARN COMPUTER THEORY BY BUILDING THIS KIT

DIGITAL TRAINER MODEL MM-8000

Starting from scratch you build a complete computer system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 micro-processor. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 EPROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language. Upon completion of this course you will be proficient in computer technology.

- Uses the 8085 Microprocessor
- Uses the 2816 EPROM, electrically erasable programmable ROM
- Uses the 8156C, 2048 Bit static MOS-RAM with I/O ports and timer
- Memory expandable option
- Built in 5V power supply
- 28 key keyboard
- Complete with lesson manual, instructions and experiments

All this for only \$79.95

QRP CW TRANSMITTER KIT 2 TUBES, 3 BANDS



- 3 Band CW Coverage — 160, 80, 40, meters using prewound plug in coils (sold below)
- Crystal Control
- 5 Watts Output Into 50 OHMS
- Single Antenna operation with built in TR Switch
- LED Output Power Indicator
- Cathode Keying Circuit
- Solid State Power Supply
- Tube Line Up 6CA Crystal OSC, 6AQ5 Final
- Complete with Pre Wound 80 Meter Coil Included
- Complete Instruction and Color Pictorials
- Use with any Receiver or Transceiver
- Includes 2 Crystals for 80 Meters — 3.64MHz & 3.70MHz
- Complete Punched and Drilled Chassis
- Measures 9"V x 9"D. Weight approx. 5 lbs.
- Assembly time approx. 6 hours

BE UNIQUE! GO QRP VINTAGE RADIO STYLE!

Part No.	Description	Price
CPCW-5	2 Tube Transmitter	\$109.95
CPC-160	160 Meter Coil	\$9.95
CPC-80	80 Meter Coil (included)	\$9.95
CPC-40	40 Meter Coil	\$7.95
CY1812	160 Meter Crystal 1.812MHz	\$9.65
CY3560	80 Meter Crystal 3.560MHz	\$9.65
CY7040	40 Meter Crystal 7.040MHz	\$9.65

OTHER CRYSTAL FREQUENCIES IN STOCK. PLEASE INQUIRE.

DELUX CODE KEY

Adjustable, heavy duty brass base with ball bearing pivots. Designed for hard usage. 3/16" plated contacts.

\$16.95

CODE PRACTICE OSCILLATOR & MONITOR

3" Speaker, Headphone Terminal, Volume & Tone Controls. Uses 1 9V Battery. Kit \$19.95
Wired \$24.95

SIGNAL INJECTOR/ TRACER

This handy tester is both a signal generator and receiver. As a generator use it to check out an amplifier, stage by stage. Also tests AM radio IF and RF stages. As a receiver you can pin point where a defective part exists. Will transmit and receive simultaneously.

Kit \$18.95
Assembled \$24.95

NEW! PCDATAK™ SOFTWARE

FOR MAKING PRINTED CIRCUIT BOARDS ON ANY WINDOWS 95 OR MS-DOS IBM COMPATIBLE PC!

- Make single or double sided PC Board artwork, up to 30" x 30"
- Print your artwork on any PostScript™ Laser Printer.
- Produces a 1X positive, ready to use with pre-coated board. No other artwork required.
- Produce industry standard solder mask and component layout for silkscreen art.

PCDATAK™ is supplied on one 3.5" diskette with a quick start manual. The full user's manual is larger and must be printed by the user (dot matrix printer ok); approximately 75 pages in length.

The NEW PCDATAK™ software lets you create PC boards ranging from prototypes to hobby projects, and on a par with the pro's. You may do the complete printed circuit board layout artwork on your own PC; at a fraction of the cost of other programs. Print the layout on any PostScript™ compatible printer, either on regular paper to be photographed for a positive or negative, or on clear film to be used directly as a positive with other DataK products.

ALL THIS FOR ONLY \$29.95

TO ORDER CALL

1-800-866-6626

Ocean State Electronics

P.O. Box 1458 6 Industrial Drive
Westerly, RI 02891
Phone: 401-596-3080 Fax: 401-596-3590

Mail in orders please include \$5.00 shipping.

CANADA \$10.50 OVERSEAS \$16.00

Minimum order \$10.00 (before shipping)

R.I. Residents add 7% Sales Tax

VISA & MASTERCARD ACCEPTED



VERNIER DIALS

- 1-1/2" Diameter 0-10 Marking \$11.95
- 1-1/2" Diameter 0-100 Marking \$12.95
- 2" Diameter 0-100 Marking \$13.25



VERNIER DRIVE

American made 6:1 vernier drive. Has dual plate mounting flange with two tapped holes (2-56) for dial mounting. Input & output mate with 1/4" shaft.

\$9.95



SIGNETICS NE602AN

Balanced Mixer/OSC. Popular IC among experimenters for building DC and super-het receivers.

\$2.49



MINI-CIRCUITS SBL-1

DIODE RING MIXER

Double Balance Mixer
LO/RF — 1-500 MHz
RF DC — 500 MHz
\$7.95

OTHER MINI-CIRCUIT PRODUCTS IN STOCK



AM RADIO

RECEIVER on a CHIP

(TYPE ZN414)



In a tiny (TO-92) transistor size case, a ten transistor tuned RF circuit that requires no setup or alignment. Nearly a complete circuit, add battery (1.1 to 1.6 volts), tuning coil and capacitor and crystal earphone. Data sheets with circuit examples included.

ZN414 \$7.95



FERRITE "LOOP-STIK" ANTENNA

Hard to find Loop-Stik Antenna. NOW IN STOCK! For radio receivers. Tunes the broadcast band. 540KHz-1600KHz.



Measures 1/2" Dia. x 3 1/2" Long. Includes mounting bracket. Q=25, L=788µH.

LA-540 \$2.25



PLUG IN COIL FORMS

Wind your own coils with these plug in coil forms. Made from Grade XX Phenolic. Equipped with rim, making it easy to insert and pull out. Coils measure 1 1/4" Dia. by 2 1/4" H. Exclusive of the pins. These are like the coil forms used in all the early receivers and transmitters. Hard to find item. Will mount in a 4, 5 or 6 pin tube socket.



Part No. PINS PRICE



CF-4 4 \$6.90
CF-5 5 \$6.90
CF-6 6 \$6.90



MAGNET WIRE

Enamel coated solid copper. For winding coils, transformers and toroids. Prices for 1/4 lb. spools.



#14 \$4.00 #24 \$4.25 #34 \$6.25
#16 4.00 #26 4.25 #36 6.45
#18 4.00 #28 4.85 #38 6.95
#20 4.00 #30 4.85 #40 7.85
#22 4.25 #32 4.85



TOROIDS



IRON



FERRITE



T-25-2 \$.40 FT37-43 \$.70
T-25-640 FT37-6170
T-37-255 FT37-7770
T-37-655 FT50-4385
T-50-265 FT50-6185
T-50-365 FT50-7785
T50-665 FT82-43 1.30
T68-090 FT82-67 1.30
T68-290 FT82-68 1.30
T68-690 FT114-61 2.30
T80-2 1.20 FT140-43 3.50
T200-2 6.00 FT240-61 8.75



WE STOCK A COMPLETE LINE OF TOROIDS AND BEADS.



FM RADIO IC

TDA 7000



Ideal for small mono FM receivers. Features an RF input stage, mixer LO, IF amplifier stage, phase demodulator and muting circuitry. Also useful in LAN, data and SCA receivers. Data Sheet Included.

TDA7000 \$9.95

SONY/AMIGA/MAC/IND. MULTISCANS
CPD-1302/1390 TTL/analog sync/gen.
Refurb. 6 mo. warr. \$175. Pikul & Assoc.
314-937-0335.

PANASONIC CF-V21P active color notebook computers, 486DX4 75MHz, 12 meg RAM, 200 meg I/D, sound, PCMCIA slot with 14.4 fax modem card, 3.5" floppy and mini CD-ROM, 2 spare batteries, manual, and AC adapter \$225. John 201-488-2652. E-Mail: durbeck@erols.com

SOCKET 7 MOTHERBOARD, PC100 operation, 1MB cache, on-board sound and 8MB AGP video, 2 ISA/3 PCI, \$96.
CPUs: Celeron 128K 300/333/366/400 @ \$85/95/119/149. Pentium II 350/400/450 @ \$199/349/549. Pentium III 450/500/569/759. **IBM/Cyrix** 300/333 \$59/66. **AMD K6 MMX** with 3D now 266/300/350/400 @ 69/89/109/189. 40X **CD-ROM**, audio button \$45, 32/64MB SDRAM 10ns DIMM \$49/99, 64/128MB PC-100 DIMM \$99/199. S3 Trio 3D 4MB (SGRAM) AGP video card \$34. Call for current pricing, other parts and illustrated catalog, faxback catalog pages, 1-year warranty or better. tech-specialties, Inc., 5703 Heffernan, Houston, TX 77087-4113, 1-800-864-5391 for orders and tech support, fax: 713-307-0314, Internet: www.ts.nu

WANT: BUYERS, telecommunications suppliers. Seller of used Tadiran sys. Coral I, II, III, Tadex, 60/124, 1A Z key eq. ITT, AT&T, GTE. Parts: USB, hubs, category 5 product 110 blocks & connectors, adaptors, cable, assemblies network, modular, cable tester, computer printer cable, video, accessories, wallplates, ITT, multiline phones, Western Electric IA 2 phones 2500 w/tap M/W. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711. 330-456-8177.

FOR SALE: All items list 9U computer, telephone, card, gauge, assembly, telephone, back plane assembly compact PCI, applications telephones, desktop #25 M/W cost ea. \$45 digital PC product line 3U hot swap back plane assemblies, 6U computer telephone assembly, I/O, connectors I/O cable assemblies, telecommunications, training, resources, self-study programs, manuals, video tapes, CBT disks, training courses. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711.

WHOLESALE DISTRIBUTOR of printers, fax & multipass machines. Dealers & public welcome. www.samelectronics.com Dealers bundle a printer with your PC sales and make \$\$. 336-545-7720. Also selling new & used PC parts. E-Mail us for a special's sheet: samsales@aol.com

USED STUFF: Sun Workstations, Cisco router, two-way radios, electronic test equipment, cellphones, broadcast equipment. <http://www.mbay.net/~thor>

Y2K RTC! Is your older PC Y2K compliant? We have software to check and hardware to fix. The millennium Y2K RTC board installs in an ISA slot and intercepts/replaces the PC BIOS clock. \$79 + S&H, qty. 1. Potts Technologies Company, 831-662-2293 fax 831-662-1877 or www.pottstech.com

HARD DRIVES tape drives 5.25" full height Seagate ST41200N, \$25; Micropolis 1936-3GB, \$45, 1991-9GB, \$105; Exabyte 8200, \$95, 8500 \$185, 8500C \$325; Maxoptix Tahiti2 \$65, Tahiti3 \$325, HP 1716 \$375. **GET ON OUR FAX/E-MAIL LIST! Weekly specials!** www.durabyte.com T: 1-800-474-8399.

HUGE WAREHOUSE sale April 10th: HP laser heads w/controller and optics, XYZ tables, test gear, POS printers, Exabyte tape drives, Colorado Travan, SCSI controllers, cables, hard drives, 17" and 20" monitors. Sun Sparc 5, 10 and 20 w/20" monitors. Mac Quadras, power macs. Thousands of items. For faxback list, call 1-800-474-8399.

COMPUTER BASED data acquisition gauge scopes, emulation, network cards, network sniffers, ISDN pods, ATM pods, cables, accessories, etc. **GET ON OUR FAX/E-MAIL LIST! Weekly specials!** Campbell Technical, T: 1-800-474-8399. www.durabyte.com

FOR MACS! Radius video vision telecast w/studiocard, cables, manual. Campbell Technical, T: 1-800-474-8399. www.durabyte.com

EXTERNAL SCSI Cases: 5.25 FH \$25, 5.25 HH \$20, 3.5 \$25. Campbell Technical, T: 1-800-474-8399, www.durabyte.com

COMPUTER SOFTWARE

FREE IBM DISK CATALOG of quality Shareware and CD-ROMs. **MOM 'N' POP'S SOFTWARE <ASP>**, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. momnpop@gate.net

CAM & MOTION SW/HW: Z-trace, PCB toolpath. Plotcam motion control, step drivers. cmheater@juno.com MSG/FAX 407-452-7197, 407-459-2729. www.megabits.net/ddt

LINUX & FREEBSD & LINUX & FREEBSD Linux and FreeBSD distributions on CD-ROM for as low as \$1.99. See our full range of Linux products and books at incredible prices. Use our secured shopping cart system at www.cheapbytes.com Visa and MasterCard gladly accepted. E-Mail: sales@cheapbytes.com fax: 209-367-8518. CheapBytes, PO Box 2714, Lodi, CA 95241.

LIQUIDATION WIN 95/98, Office97, WindowsNT, 10 PACK CDs 1,000 games \$25, DOS \$25, Lotus SmartSuite \$10, Wordperfect Suite \$35. Antivirus \$5. Call 714-778-0450.

Check us out on the web: www.nutsvolts.com

27pc•kit

\$12.95

K2637

MINIATURE AUDIO AMPLIFIER KIT
Big sound from a small unit!
Small PCB with both pre- and power amp
Short circuit protected
Input sensitivity: 20mV
Max. output power: 2.5W
Power supply: 4.5 to 15VDC

28pc•kit

K1771

FM OSCILLATOR KIT
Use for home broadcasts, baby monitoring, security
Frequency range: 100-108MHz
Microphone input
No coils to wind
Power supply: 9-12VDC

17pc•kit

\$9.95

K1803

UNIVERSAL MONO PRE-AMPLIFIER KIT
Boost any audio signal up to 40dB (x100)
Max input signal: 40mV
Frequency range: 20Hz to 20KHz
Power supply: 10-30VDC/10mA

19pc•kit

\$19.95

K5300

STROBOSCOPE KIT
Stage effects at home
Adjustable flash rate: 2-20 flashes/second
Powerful flash tube
Supply voltage: 110-125V AC

36pc•kit

\$18.95

K4304

10 LED VU METER KIT
Visualise any audio level
Line or speaker inputs
DOT or BAR mode. Range: -20 to +3dB
Front panel included. Vertical or horizontal mounting. Power supply: 10-15VDC

27pc•kit

\$24.95

K5002

HALOGEN LAMP DIMMER KIT
Light control at the touch of a button
Suitable for loads up to 3A
Can control small motors with brushes
Push button operation
Add any number of buttons
Power supply: 110-125V AC

16pc•kit

\$14.95

K6708

IR REMOTE CONTROL KEY CHAIN TRANSMITTER For K6709 Kit
Range: Up to 24 feet
LED operation indicator
8748 different code settings
Power supply: 12V battery

66pc•kit

\$24.95

K6709

IR REMOTE RECEIVER
For K6708 Kit
The easy way to add a remote control
10A relay with norm. or pulse changeover contact
Allows control of alarm systems, garage doors, outdoor lighting, garden pumps, etc
LED reception indicator
Accepts multiple transmitters K6708
Power supply 2x9VAC or 12 to 16VDC

12pc•kit

\$12.95

K1823

1 AMP POWER SUPPLY
Just add a transformer
Adjustable output voltage 1.5V to 35V/1A max.
Short circuit and thermal protection
Max input voltage: 37VDC
Max dissipation: 15W

18pc•kit

\$14.95

K6700

2-WIRE REMOTE CONTROL TRANSMITTER
Transmitter For K6701 Kit
Control up to 16 devices*, with only 2 wires! Remotely control 8 (*16 with 2 units) devices up to 160 feet away. Transmitter is powered over the data wires. Simple operation by means of switches (not included)
Transmitter can drive multiple receivers

46pc•kit

\$24.95

K6701

2-WIRE REMOTE CONTROL RECEIVER For K6700 Kit
8 open collector outputs (max 200mA)
LED output status indication
Daisy chain 2 units for 16 outputs
Power supply: 6-16V DC

18pc•kit

\$14.95

K2579

UNIVERSAL START STOP TIMER KIT
0-15 Minutes Adjustable Delay
3A changeover relay contact
Start and Stop button included
LED function indicator
Can be modified for longer delays.
Power supply: 12V/55mA

velleman

7415 Whitehall Street Suite 119
Fort Worth, TX 76118
(817) 284-7785 F: (817) 284-7712
www.velleman.be email: velleman@earthlink.net

Questions? Contact us for a list of US distributors or to get your FREE catalogue



COMPUTER PROGRAMMING: C, BASIC Stamp, 80486, Pentium, Windows 95. Applications: Robotics, monitor & control, user interfaces, web-pages. Let me help with your prototype or production design. <http://home.att.net/~kdelahou/robot.html>

WINDOWS NT 4.0 workstation full version, unopened, \$95.
btrim@teleport.com or 1-888-634-3526.

COMPUTER EQUIPMENT WANTED

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

HP CALCULATORS wanted: models 10, 70, calculator watch, others for private collection. Cash paid. Bob Morrow, 765-855-2348, rkmorrow@aol.com

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

WANTED: MAXTOR XT 1085, 1140, 2190 Hitachi 514-38, any 40MB 3.5" MFM drives, Fujitsu 2249E or S. Mountain 40MB tape drives. **GET ON OUR WEEKLY FAX LIST.** You will profit from it! Campbell Technical, T: 1-800-474-8399.

WANTED: TERMINALS + PRINTERS: DEC, Wyse, IBM, ADDS, Okidata, Data South, Epson, C.I.T.O.H., etc. Call for quote on any surplus computer equipment. Call Jeremy, 603-673-8077.

HOBBYIST SEEKS Altair 680, 8800, or Imsai 8080 computer. Call Shawn, 650-846-8208. maxweb@pacbell.net

TEST EQUIPMENT

FEITEK PROVIDES repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at WWW.FEITEK.COM 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

KENTRONIX TEST EQUIPMENT SPECIALS. Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to buy test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3229 or FAX 732-681-3312. E-Mail: brian@kentronix.com

EQUIPMENT MANUALS we have 1000's of service and operators manuals for all types of test and measurement equipment from 1950 to present. All test equipment manufacturers are represented. Call, write, or fax your want list. Please include mfg.'s manual P/N unit serial numbers if known. **Manuals Plus**, Box 549, TAD #601, Tooele, UT 84074. 435-882-7188, FAX 435-882-7195.


AFFORDABLE HP power sensor repair! Most 8481As repaired for \$255 or less. We also handle 478As and many others. Call or fax for more information. Willamette RF, Inc., 541-754-7226, FAX 541-753-4629.

BRUEL & KJAER BUY, SELL, BEST PRICES. EXCALIBUR ENGINEERING, 3198-C AIRPORT LOOP DRIVE, COSTA MESA, CA 92626. 714-540-0169, FAX 714-540-5417.

SPECTRUM ANALYZER in a probe. \$249. View thru your inexpensive scope. WWW.spectrumprobe.com

WANTED: RADIO service monitors, IFR, Motorola, HP, Marconi, also late model HP equipment. 716-763-9104 or FAX 716-763-0371. <http://www.amtronix.com>

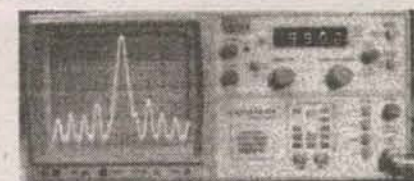POOR MAN'S Spectrum Analyzer/Monitor Receiver Kit. 2 to 1,700 MHz. Basic kit only \$78. Now available with switched resolution filters, tracking generator and direct digital frequency readout. Works with ANY scope or IBM compatible computer. Send stamped envelope for details. Science Workshop, Box 310B, Bethpage, NY 11714. <http://www.science-workshop.com>



ENGINEER TESTED: Spectrum analyzers, frequency counters, frequency standards, meters, scopes, generators, curve tracers. Books. Temperature, time, weight, light, sound, distance, etc., measurement instruments. **VISA, MASTER-CARD, AMEX.** "Performance tested." NIST calibrated. Warranted. **New & used.** Gary N6ZD. <http://TECH-SERVICES.COM> 831-385-7519.

TEST EQUIPMENT repair or overhaul Tektronix, HP, Wavetek, Boonton, etc. 20 years experience with former Slep Electronics Co., same excellent service same reasonable rates, satisfaction guaranteed. Brooks Electronics 828-349-3503. E-Mail: rwbrooks@dnet.net



EDLIE THE KIT KING

Presents New-Do-It Yourself Kits from Datak



Each Kit comes complete with an educational explanation of the circuit.

Build these useful kits and have! Fun Too! Each kit comes with its own PC Board

Voice Changer (80-1051)

Your voice can be changed to add a vibrato, like those used to disguise secret witnesses. Or you may change your voice upward or downward: women sound like men and vice versa. Includes a very ROBOT voice as well. A microphone and speaker are included on the PC board; all that you need to add is a 9V transistor battery. This is a very novel and entertaining circuit. **\$12.95**

FM Telephone Transmitter Kit.

(80-2801) Miniature transmitter attaches to your telephone line, transmits the conversation over 200 yards to an FM receiver. (much closer if your FM receiver is close to a related telephone wire). Tunable to clear spot in the FM band. Uses the phone line as an antenna & power source. Parasite. Not intended for illegal use. **\$7.50**

Two Stage FM Transmitter (80-320)

This is an extremely sensitive & Powerful FM bug; transmits to upper part of FM band. A 2 stage, 3 transistor FM transmitter. It operates on a 9-volt battery. The most sensitive & powerful you can legally buy. The circuit employs an electret mike for added sensitivity. Unit can run on 6V, greatest output at 12V. but use 9V and the short antenna wire included to stay legal in U. S. The Printed circuit bd is 3/4" W. x 2 3/4" L. **\$12.95**

Variable Power Supply (80-6801)

This is a basic adjustable voltage power supply with a range of about 1.5VDC to 35VDC set by a potentiometer. It is capable of 2 Amps if you add a simple heat sink. Circuit includes short circuit protection. **\$13.95**

4 Train Sound Effects (80-9101)

This Cob project will produce 4 very realistic user selectable sound effects that are ideal for model railroad. Throw any of switches to produce a train whistle blowing 3 times, a train chugging along, a level crossing bell & the "clickety clack" of a train crossing a bridge. Kit includes all parts including speaker Easy to assemble. operates on 2.4 to 6VDC. **\$7.95**

Stereo Preamplifier (80-1041)

Amplify any tiny audio signals about 50 times & deliver them to a power amplifier cleanly and undistorted. An AGC control eliminates pops or distortion. This circuit will be useful in boosting the output from tape heads, microphones or a magnetic cartridge etc. For input to an audio amplifier. Requires a 12VDC power supply at about 100mA peak **\$9.50**

Infrared Toggle Switch

(80-5801) Control just about any device using the remote control from just about any TV set. The circuit switches an on-board SPDT relay; Turn it on with the remote, and turn it off with another signal. The relay contacts are rated 1A at 125 V.A.C. The circuit operates any DC supply from 8 to 15v; use as an old calculator supply etc. This circuit can have some very practical Applications, such as turning on a light by an invalid. Your imagination is the limit. **\$15.95**

AM Radio Kit (AM-550) Learn AM radio Theory by building

This kit. 10.5 x 3.5 blue PC board, with schematic printed on surface. Comes complete with battery, solder and 28 page manual. Five lessons Covering RF, IF, Oscillator, detector and audio circuits. Easy - to read & understand. No previous knowledge of electronics necessary. Ideal for school or home projects **\$19.95**

Also Available in AM-FM MODEL (AM-FM108) **\$29.95**

Light Alarm (80-0801)

Detects very small amounts of light and sounds a piezo alarm. Put in your cash box or cupboard. Uses Darlington photo transistor MEL2 & 14011 I.C. A very educational kit. **\$8.50**

2 Stage FM Transmitter

This is an extremely sensitive and powerful FM bug; transmits to upper part of FM band. A two stage, three transistors FM transmitter. It operates on a 9V battery. The most sensitive & powerful that you can legally buy. The circuit employs an Electret microphone for added sensitivity. Unit can run on 6 volts, greatest output at 12V use. Use 9 volts and the short antenna wire included staying legal in U.S (80-3201) **\$9.50**

Photo Sensor with Control

Relay (80-1031) The most popular usage for this kit is to make your own night light. But you could switch just about any appliance either on or off with either darkness or daylight. Light sensitivity is adjustable over quite a range. The relay can handle up to 10 Amp A.C.. You need to add a 9-Volt transistor battery or a 9V. 25mA supply **\$8.95**

Buy These helpful tools to build the kits you buy

- 1- A 30Watt UL Approved Soldering Iron **\$4.25**
- 2- A Soldering Stand with sponge for cleaning **\$3.50**
- 3- A small Spool of rosin core solder **75¢**
- 4- A good quality Long Nose Plier **\$3.50**

Just arrived in time for this ad - 10' Parallel Cable Bi-Directional, IEEE1284 Compliant. This is the Preferred Printer Cable for Computer Buffs. It results in clean data transmission at faster speeds \$4.95ea. 3 for \$13.95



Call or Write for a
Free

76 page Catalog
800-516-645-4722
Outside the US Please send
\$3.00

Mail your orders to
Edlie Electronics Inc
2700 Hempstead Tpke.
Levittown, N.Y. 11756
Order Toll Free
800-516-645-4722
IN NYS 516-735-3330


Checks, or Money orders are Accepted by mail No C.O.D. Shipping & handling charge \$5 For the continental United States For all Others Including Canada, Hawaii, Alaska, & P.R. must pay full shipping charges

We accept MC, Visa, & AE

To order by Fax Call 516-731-5125
For Info Call 516-735-3330

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dilog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

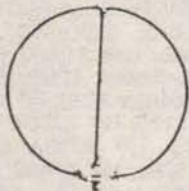HP 4815A Z-meter: Sandford Associates. **TOTAL** service specialist. Repairs warranted to HP/QA factory specs. Former HP tech/supv with expertise, parts, and tooling. Tel/fax: 908-852-7989, E-Mail: GeoSA4815@compuserve.com



WANTED: LOOP ANTENNA 10509A from Hewlett Packard 117A any condition. Call-Tim after 7pm EST 516-888-0275.

WE BUY electrical power systems test equipment. This includes the following manufacturers: **Multi-Amp** (now AVO Multi-Amp), **Biddle** or James G. Biddle (now AVO Biddle), **Megger** (now AVO Megger), **Associated Research**, **AEMC**, **EIL**, **Programma** or any other test equipment used for testing high voltage equipment and components. The test equipment that we are looking for is used for testing high voltage transformers, circuit breakers, cables, and protective relays. FAX 972-564-9139 or phone 1-800-261-9139 for quote. **Phase-3 Power Test Equipment.**

APRIL SPECIALS: HP 3488A mainframe \$550 (cards available); HP 4140B pA meter, DC voltage source with HP 16055A fixture \$2,300; HP 436A/022 RF power meter with cable \$975; HP 5343A/1,6,11 26.5 GHz microwave frequency counter \$3,500; HP 8112A 50MHz pulse generator \$3,900; HP 8116A/001 50MHz pulse/function generator with burst, logarithmic sweep \$3,700; HP 8161A/020 100MHz dual channel pulse generator \$2,500; HP 83522A .01 to 2.4GHz 8350B plug-in \$3,300; HP 83570A 18-26.5GHz 8350B plug-in \$3,900; HP 8410C, 8410B network analyzer mainframes \$595, 425; HP 8411A/018, 8411A harmonic frequency converters \$395, 250; HP 8743B/018, test set \$495; **Audio Precision SWR-122F** balanced switcher \$650. All with warranty, in excellent condition. **Pepper Systems** (<http://home.earthlink.net/~peppersys>) 214-353-0257 (Fax 214-902-9511). E-Mail: peppersys@earthlink.net

ANRITSU MS420K network-spectrum analyzer 10Hz-30MHz w/manual, \$3,500; HP 8672A 2-18GHz synth., \$4,950; HP 8350B w/8395A opt. 2 .01-20GHz sweep gen., \$10,900; HP 8559A/853A .01-20GHz S/A, \$3,000; HP 5342A 18 GHz freq. counter, \$950; Tek 492 opt. 2 S/A, \$3,200; Tek 11302 w/2 ea. 11A34 plug-ins GPIB scope 500MHz BW, \$2,900; HP 141T/8555A/552B/8445B S/A w/automatic preselector, \$1,300; HP 140T/8553B/8552A/8445A 110MHz S/A w/tracking generator/counter, \$600; HP 8443A w/cable and manual, \$275; HP 435B/8484A w/inst. case opt., \$750; HP 436A w/cables, \$950; Tek 1502 TDR w/chart rec., \$750. Many other items in stock too numerous to list. Please call with your test and measurement requirements. We accept Visa and MasterCard. **Parker Test Equipment**, 530-622-7007 fax: 530-642-8868 E-Mail: parkrtst@jps.net

LARGE ASSORTMENT of used test equipment for sale. Request catalog or visit our website. **Stevenson Equipment Company**, 609-888-2846, Fax: 609-888-2847. Website: <http://www.stevensonlabs.com>

ELECTRONIC EQUIPMENT over 85 instruments including: Fluke 332B, 750A, 845A, 721A, 335A, 540A, 382, 343A; HP 745A, 746A, 8640B, 3336B, 8690A, 8707A, 735A, 3555C/D/E, 8620A, 3400A, 419A, 3455A, 5328A, 5245L, 5255A, 5328A, 432A, 415E, 8410B, 8743A, 8660C, 5254A, 3490A; Ballentine 393; PM 1045; Tek 7603, 7403N, PG-502, 2901A; GR 1615B, 1232A, 1683; Epply 121, 125. Plus standard resistors, capacitors, inductors, fixtures, couplers, mixers, etc. Estate sale for us — unique opportunity for you. **SOLICITING REASONABLE BIDS.** Don't miss this chance to get what you need at a GOOD price. **HURRY** before it's gone. Call, write, or E-Mail for list. Ten day right-to-return. Contact: E-Mail: RgrGd@concentric.net **ELECTRONIC INSTRUMENTS**, 4702 W. LAZY C DRIVE, TUCSON, AZ 85745. 520-886-8488 or 520-743-0376.

IFR T-1200SR scanning receiver, combination spectrum analyzer, oscilloscope, frequency error meter, modulation meter, signal strength meter. 100KHz-1GHz in 100Hz increments. \$3,450, 90 day warranty. Ph 561-747-3647, fax 561-575-4635.

TEST EQUIPMENT for sale/wanted: RF, Microwave, video and fiber optic. Cable TV, Broadcast TV, satellite and related industries. Wavetek, Tektronix, Hewlett Packard and other manufacturers. Spectrum analyzers, signal level meters, sweep systems, TDRs, OTDRs, and much more. **PTL Test Equipment, Inc.** Phone 561-747-3647 FAX 561-575-4635.

ON-LINE AUCTION of 100+ lots of test & measurement equipment over 3 days. Descriptions & pictures will be available on-line. Auction will be on 20-22 April @ www.auction.net/sold Register to be on our E-Mailing list today. Surplus Asset Management, 336-545-7720.

GOOD DEALS: Tek PG501 \$75; 7A15A \$40; 7A24 \$90; 7D20 \$250; DAS 9100 logic analyzer complete, \$325; 91A08, 91A32 cards, \$40; HP 8445A preselector \$150; Boonton 4200 with 4E sensor, \$400; Fluke/Phillips PM3350 oscilloscope, \$300. Call Jeff at 508-533-5944.

POWER SUPPLIES (six) Topward 6306D digital triple tracking 30V/6A, new in box. List \$879, sacrifice \$475. Days 805-486-4827.

LOWEST COST LCD'S ON EARTH

 <p>VIDEO LCD 4 Inch Video NTSC \$150 Sharp P/N 4LU4E Composite NTSC & RGB Input 12:00 OR 6:00 Viewing Angle Integrated Backlight & Inverter Extended Temp: -10 to +60 C Brightness: 260 nits Power Consumption: 4.3 Watts Contrast: 50 to 1</p>	 <p>CHARACTER LCD OPTREX DMF-5005SN-EW 240 x 64 Graphic EL Backlit STN \$30 OPTREX DMF-5005N 240 x 64 Graphic Reflective STN \$30 SANYO DM2023-7G1 2 x 20 Character Reflective STN \$8 SHARP LM20A21 2 x 20 Character Reflective STN \$8 VIKAY 2035TNLD NOTW-D 2 X 16 Character LED Backlit STN \$8</p>	 <p>LCD MONITOR 10.4" DSTN or 12.1" TFT Analog SVGA Input Autosync Auto Sizing Automatic Expansion of VGA images to SVGA (On 12.1") Very Aggressive Pricing Starting under \$500!</p>
 <p>TOUCH MONITOR EarthVue 10.4 10.4" VGA TFT Analog VGA Input 105 Nit Brightness RS-232 Touch Screen Option Only 9.9"W x 7.7"H x 1.5"D Ideal For Factory Automation Fully Articulating Ball Mount Only \$1095 With Touch</p>	 <p>LCD DISPLAYS 6.3" Mono STN \$60 9.4" Mono Reflective \$60 8.4" TFT \$250 9.4" DSTN \$150 10.4" TFT \$350 10.4" DSTN \$240 NoteBook Screens 340 Models in Stock Obsolete Screens Stocked Hard To Find LCD? Call!</p>	 <p>CONTROLLERS ISA PCI PC/104 NTSC Analog VGA Complete LCD Kits with LCD, Controller & Cable Starting under \$200</p>



EARTH

Computer Technologies

"The World Leader In LCD Recycling"

Ph: (949) 361-2333 Fax: (949) 361-2121

<http://www.flat-panel.com>

Write In 35 on Reader Service Card.

Use your PC as a scope and datalogger!

Parallel Port Scope
spectrum analyzer, and digital multimeter



\$79 - \$799

Environmental Logging
record temperature, humidity, etc.



\$129 - \$645

osziFOX
20MS/s handheld scope



\$129

ADC Virtual Instruments turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 1.2MS/s 12-bit or 333kS/s versions. Great for schools, test depts, etc. Input to Excell LabView/NT drivers included.

ENVIROMON - temperature (thermistor), humidity & light sensors, door position, etc. Record for 365/24 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use **TC-08** for most thermocouples.

osziFOX - handheld storage scope and DVM - stand-alone or plugs into your PC for display, store-to-disk, printing in color. Inputs to 100V, trigger, backlit LCD.

Download FREE demo software. Sales only: 1-888-7SAELIG

www.saelig.com 716-425-3753 • -3835 (fax) saelig@aol.com

Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITlink 2-wire networks, RS232/422/485, frame grabbers, etc. See www.saelig.com for Product of the Month!

pico
Technology Limited

DIGITAL MULTIMETERS at dealer prices. Visit www.CrowRiver.com for details. Mention Nuts & Volts with order and deduct 30% from normal list price.

PULSE GENERATORS: Data pulse 102, \$50; E-H Research 131, \$50, 132, \$60; Eldorado 650DTY, \$75; GD A31300-004, \$60; HP 214A, \$60; 8005B, \$90; Lavoie LA-593, \$50; Systron Donner 114A, \$60; 218, \$75; Tek PG501, \$150. Telecomm testers: Automatic Electric H886867-1, \$50; HP 353A-C15, \$50; 3551A, \$150; 4904A, \$50; 4912F-001, \$40; Halcyon 500B/520B2, \$175; Murphy SBR-5, \$40; SBT-5, \$40; Stromberg-Carlson P84731-00, \$40; Western Electric KS14103L6, \$135. G&G 210-674-8771, fax: 210-674-8775.

SORENSEN DCS-40-25 power supplies new in box, dig read out 0-40V 0-25A CCCV, \$500 ea.; Ailtech/Eaton, NM 17/27A, field intensity receiver .1-30MHz, \$1,000, Ailtech/Eaton, NM 37/57A 30-1000MHz receiver, \$1,000; Tektronix TM5006 frame, \$500; Tektronix FG5010, 20MHz programmable function gen., \$600; DM5010 programmable volt-meter, \$600; DC5010, 35MHz programmable counter, \$750; A-COMM ELECTRONICS, 303-341-2283.

MANUALS: TEST equipment manuals bought and sold. See our list on the web: www.usimperio.com Call 410-685-1991 with your inquiries or for-sale list or fax to 410-685-7701. CONSOLIDATED SURPLUS.

TEK SCOPES: we have most 2200, 2400 series in stock. Metrowest Technologies, PH 508-478-7613, fax 508-634-3806. www.metrowesttech.com

TEK SCOPE Special: 2465B 400MHz with probes, \$4,000. Metrowest Technologies, PH 508-478-7613, fax 508-634-3806. www.metrowesttech.com

TEK SPECTRUM analyzers: special: 492/01/02/03, \$4,000. Metrowest Technologies, PH 508-478-7613, fax 508-634-3806. www.metrowesttech.com

TEK PLUGINS: We have many on the shelf. Metrowest Technologies, PH 508-478-7613, fax 508-634-3806. www.metrowesttech.com

TEK PLUG-IN SUPER SALE! ALL 7000 AND 500 SERIES PLUG-INS REDUCED! OVER 5,000 TEK PLUG-INS IN STOCK. 7A12/7A15/7A15A/7A16/7A16A/7A16P/7A18/7A18A/7B70/7B71/7D13 AND MANY OTHERS ONLY \$65 EACH. 7A11/7A13/7A14/7A19/7B80/7B85/7D11/7D12/7D14/7D15/7M11/7M13 AND MANY OTHERS, NOW ONLY \$95 EACH. CALL FOR SALE PRICING ON OTHER PLUG-INS NOW! LIMITED TIME OFFER. 1-888-216-7159.

TEST EQUIPMENT FOR SALE: [HTTP://WWW.A-COMM.COM](http://WWW.A-COMM.COM)

MISC. EQUIPMENT SALE! GENERAL RADIO 1689M Precision RLC digibridge \$1,200; FLUKE 5200 AC calibrator w/5215A power amp \$1,600; HP 5005B signature multimeter \$250; HP 5180A waveform recorder \$225; HP 410C \$45; HP 3400A \$125; HP 8740A \$225; HP 8742A \$375; HP 8743A \$225; HP 8743A/018 \$300; HP 8743B \$450; HP 8745A \$525; 8411A \$225; HP 8411A/018 \$350; HP 3488A switch control unit \$425; HP 3490A 5.5 digit DVM \$175; HP 3406A RF voltmeter \$175. MANY MORE ITEMS ON SALE NOW! CALL 1-888-216-7159. LIMITED TIME OFFER.

HP SPECTRUM analyzer: special: 8590A 1.5GHz, \$4,800. Metrowest Technologies, PH 508-478-7613, fax 508-634-3806. www.metrowesttech.com

FULL SPECTRUM of reconditioned test equipment for sale. Please E-Mail, fax or call to request our fax listings of equipment specials. Parker Test Equipment, E-Mail: parkrtst@jps.net Fax: 530-642-8868, PH: 530-622-7007.

GENERATOR SALE! HP 3325A synthesized 1uHz-21MHz \$950; HP 8165A programmable signal source 1MHz-50MHz \$900; HP 8660C opt. 1 (oven) w/86601A/86603A/86632B .01-2600MHz \$2,100; HP 8620C w/86290A 2-18GHz \$1,400; HP 8620C frame w/scales \$400; HP 8350A sweep oscillator frame \$950; HP 86222B RF plug-in \$750; Fluke 6060A synthesized 10KHz-1050MHz \$1,600; Boonton 102D AM/FM .45-520MHz phase locked 6 digit \$750. MANY OTHER GENERATORS/OSCILLATORS ON SALE NOW. LIMITED TIME OFFER. Call NOW! 1-888-216-7159.

HP SPECTRUM analyzers: 8555A, 8558, 8559, others. Performance guaranteed. Metrowest Technologies, PH 508-478-7613, fax 508-634-3806. www.metrowesttech.com

SCOPE SALE! TEK 2465 300MHz 4 channel \$1,400, TEK 2445 150MHz 4 channel \$950; TEK 2445A 150MHz 4 channel \$1,200; TEK 2247A 100MHz w/counter/timer/voltmeter/probes/manual (NICE) \$1,800; TEK 2335 100MHz \$625; TEK 2336 100MHz \$500; TEK T922 15MHz (VERY NICE) \$175; TEK 7104 w/7A29/7A24/7B10/7B15 SPECIAL \$2,400. BRAND NEW AMERICAN MADE SCOPE PROBES ON SALE NOW! CALL FOR PRICING. MANY MORE SCOPES ON SALE NOW. Call NOW! 1-888-216-7159.

ANALYZER SALE! TEK 492 opt 2 50KHz-21GHz \$2,800; HP 141T frame \$425; HP 141T w/8552B/8553B 1KHz-110MHz \$975; HP 141T w/8552B/8555A 10MHz-18GHz \$1,400; TEK 7L13 100KHz-1.8GHz \$1,200; TEK 7L5/L3 20Hz-5MHz \$750; HP 8901A modulation analyzer \$800. ALL EQUIPMENT HAS BEEN RUN THROUGH OUR LAB AND COMES WITH A 10 DAY RIGHT OF RETURN AND A 60 DAY WARRANTY. LIMITED TIME OFFER! 1-888-216-7159.

COUNTER/TIMER SALE! HP 5335A opt 010/040 oven/HPIB 200MHz \$550; HP 5334A opt 010 oven 100MHz \$275; HP 5340A 18GHz Nixie \$450. MANY OTHER COUNTERS ON SALE! CALL NOW FOR PRICE QUOTE. 1-888-216-7159.




**Great for
cruising
the net!**

Designer Netmouse 3-button PS/2
L/R click & netscroll button on side.
Complete in retail box w/ drivers!

TM-290-NET

\$5⁰⁰

Roger's Systems

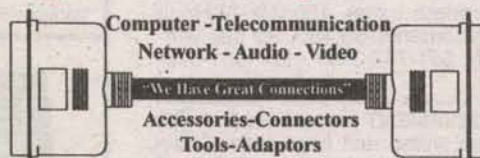

Specialist

www.rogerssystems.com



7ft. Cat. 5 Crossover
Patch Cable

TE-068-L5X

\$1⁰⁰



**Heavy Duty
Power Packs!**

TM-313 12VDC 1500ma AC Adapter \$5⁰⁰
TM-307 1.5VDC -12VDC 500ma AC \$3⁰⁰



Clip/Stick-on Lapel
Microphone

TM-MIC-2

\$1⁰⁰



Slim Multi-Media
Mic w/ Stand

TM-MIC-3


\$2⁰⁰



**Great Deals on
Famous Maker
Headphones!**

TM-165 Stereo Headphone w/ Mic \$6⁰⁰
TM-162 Digital Headphones/Leather Pads \$10⁰⁰
TM-170 Koss KX-3 Digital Headphones \$3⁰⁰

SCSI Cables

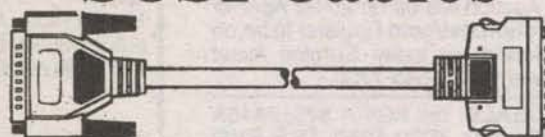


CC-669 3ft. DB25-Cent. 50 \$4⁰⁰
CC-671-6 6ft. DB25-SCSI2 (M) \$5⁰⁰
CC-671 3ft. DB25-SCSI2 (M) \$4⁰⁰
CC-679 3ft. SCSI2-SCSI (M/M) \$17⁰⁰
CC-687-6TS 6ft. SCSI3-SCSI w/ Thumb QCA \$19⁰⁰

Ultra SCSI-3 for Laptops!

CC-698 6ft. Micro Cent.68-HD68 \$22⁰⁰

Ask About Quantity Discounts!

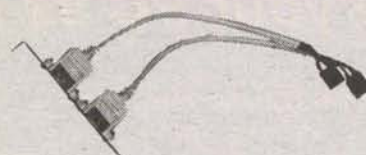

USB Cables

CC-USB-6 6ft. USB "A" to "A" M/M \$5⁰⁰
CC-USB-8 USB (2) to 2x8 pin w/ Bracket \$5⁰⁰
CC-USB-9 USB (2) to 2x5 pin w/ Bracket \$5⁰⁰
CC-USB-AB6 6ft. USB "A" to "B" M/M \$5⁰⁰
CC-USB-PP 6ft. USB to IEEE Printer Cable \$39⁰⁰
CC-USB-6 6ft. USB "A" to "A" M/F \$5⁰⁰

USB Accessories

USB-PCI USB x2 PCI Add on Card \$27⁰⁰
USB-KB-104 USB 104-Key Kybrd Win98/PS2 \$39⁰⁰
USB-CAM C-IT USB Cam w/ Software \$109⁰⁰

1-800-366-0579

24895 Ave. Rockefeller, Valencia, CA 91355

Local 661-295-5577

FAX 661-295-8777

\$20.00 minimum order required • Add \$4.50 shipping for prepaid orders • Prices subject to change without notice. All major credit cards accepted. • Special offers only valid on items in stock. California residents add 8.25% tax • eMail sales@rogerssystems.com. Call for quantity discounts • No out of state checks accepted • Most orders shipped same day! • Not responsible for errors in typesetting. Trademarks are the property of their respective companies. All photographs are for illustration purposes only and may not be a true representation of actual products.

SHOPPING FOR equipment: Metrowest Technologies, Bostons Equipment Supersource. Call for a quote on your next purchase. Metrowest Technologies, PH 508-478-7613, fax 508-634-3806. www.metrowesttech.com

BIG SALE: HP 8660B 1.3GHz \$750; HP 3325A HV \$1,000; M100 rubidium \$425; Austron 2110 quartz standard \$600; Commodore SX-64 \$125; HP 1720A \$325; HP 1720A and 1722A for parts, take both \$200; Graphtec WR7200 chart recorder \$200; 16 channel distribution amplifier \$400; LM299AH RFE \$15; MWA 120 and 130 RFE \$3; unused HP assemblies 08552-60149 \$75; 08552-60191 \$75; 8660-60043 \$150; 3406 probe replacement \$75. Corby Dawson, 805-736-0288.

SECURITY

ALARM PANELS, motion detectors, contacts, CCTV, and more. Equipment that only the professionals can buy. Visit www.heselectronics.com or E-Mail alarms@heselectronics.com



COUNTER-SURVEILLANCE=\$250 HR! Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.




FACTORY SALE! CNL100, CNP101: 1/3" CCD, 430 line horiz., 12V/100mA, lens and pin hole types, lens 3.6mm/F2.0, 0.08 LUX, 1.27" (W) x 1.27" (L) x 1/2"-1" (H). \$49 @ 5 pcs., \$44 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: sales@mat-co.com Web site www.mat-co.com



SALE! IC 113: PIR motion detector with audio! W/ NO/NC alarm output. CCD camera with audio can be turned on by detector. 5-1/4" (L) x 2-3/4" (W) x 2" (D). \$89 @ 5 pcs., \$82 @ 10 pcs. Matco, Inc. 1-800-719-9605 Fax: 630-350-9546. E-Mail: sales@mat-co.com Web site www.mat-co.com



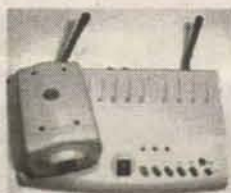SALE! QVS 104: Quad video system. Near real-time. 8.5" (W) x 2" (H) x 5.5" (L). \$169 @ 5 pcs., \$149 @ 10 pcs. Also available: 8-2 video auto-switcher, \$65 @ 5 pcs., \$59 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: sales@mat-co.com Web site www.mat-co.com



SALE! AS-1000, 2.4GHz transmitter & receiver with audio! Capable handling total of 3 wireless cameras, range: >300'. Built-in camera, 400 TV line. \$189 @ 5 pcs., \$179 @ 10 pcs. Additional camera \$119 @ 10 pcs. Matco, Inc. 1-800-719-9605 Fax: 630-350-9546. E-Mail: sales@mat-co.com Web site www.mat-co.com



SALE! PS 102: Built-in pin hole CCD, lens size: 3.6mm. 5-1/2" (D) x 1.7" (H). \$79 @ 5 pcs., \$72 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: sales@mat-co.com Web site www.mat-co.com

SURVEILLANCE-COUNTERSURVEILLANCE: I buy and sell used equipment. Steve 410-879-4035.

RAMSEY



World's Smallest TV Transmitters

We call them the 'Cubes'.... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies—that's a nickel in the picture!



Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency drift with performance that equals law enforcement models that cost hundreds more! Basic 20 mW model transmits up to 300' while the high power 100 mW unit goes up to 1/4 mile. Audio units include sound using a sensitive built-in mike that will hear a whisper 15 feet away! Units run on 9 volts and hook-up to most any CCD camera. Any of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air!

- C-2000, Basic Video Transmitter Cube.....\$89.95
- C-3000, Basic Video and Audio Transmitter Cube.....\$149.95
- C-2001, High Power Video Transmitter Cube.....\$179.95
- C-3001, High Power Video and Audio Transmitter Cube.....\$229.95

Super Pro FM Stereo Radio Transmitter



A truly professional frequency synthesized FM Stereo transmitter station in one easy to use, handsome cabinet. Most radio stations require

a whole equipment rack to hold all the features we've packed into the FM-100. Set frequency easily with the Up/Down freq buttons and the big LED digital display. Plus there's input low pass filtering that gives great sound no matter what the source (no more squeals or swishing sounds from cheap CD player inputs!) Peak limiters for maximum 'punch' in your audio - without over modulation, LED bargraph meters for easy setting of audio levels and a built-in mixer with mike and line level inputs. Churches, drive-ins, schools and colleges find the FM-100 to be the answer to their transmitting needs, you will too. No one offers all these features at this price! Kit includes cabinet, whip antenna and 120 VAC supply. We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.

- FM-100, Professional FM Stereo Transmitter Kit.....\$299.95
- FM-100WT, Fully Wired High Power FM Transmitter.....\$429.95

AM Band Radio Transmitter



Ramsey AM radio transmitters operate in the standard AM broadcast band and are easily set to any clear channel in your area. Our AM-25, 'pro' version, fully synthesized transmitter features easy frequency setting DIP switches for stable, no-drift frequency control, while being jumper settable for higher power output where regulations allow. The entry-level AM-1 uses a tunable transmit oscillator and runs the maximum 100 milliwatts of power. No FCC license is required, expected range is up to 1/4 mile depending upon antenna and conditions. Transmitters accept standard line-level inputs from tape decks, CD players or mike mixers, and run on 12 volts DC. The Pro AM-25 comes complete with AC power adapter, matching case set and bottom loaded wire antenna. Our entry-level AM-1 has an available matching case and knob set for a finished, professional look.

- AM-25, Professional AM Transmitter Kit.....\$129.95
- AM-1, Entry level AM Radio Transmitter Kit.....\$29.95
- CAM, Matching Case Set for AM-1.....\$14.95

CCD Video Cameras



If you're looking for a good quality CCD board camera, stop right here! Our cameras use top quality Japanese Class 'A' CCD arrays with over 440 line line resolution, not the off-spec arrays that are found on many other cameras. You see, the Japanese suppliers grade the CCDs at manufacture and some manufacturers end up with the off-grade chips due to either cost constraints or lack of buying 'clout'. Also, a new strain of CMOS single chip cameras are entering the market, those units have about 1/2 the resolution and draw over twice the current that these cameras do - don't be fooled! Our cameras have nice clean fields and excellent light sensitivity, you'll really see the difference, and if you want to see in the dark, the black & white models are super IR (Infra-Red) sensitive. Our IR-1 Illuminator kit is invisible to the human eye, but lights the scene like a flashlight at night! Color camera has Auto White Balance, Auto Gain, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. They run on 9 VDC and produce standard 1 volt p-p video. Add one of our transmitter units for wireless transmission to any TV set, or add our IB-1 Interface board for audio sound pick-up and super easy direct wire hook-up connection to any Video monitor, VCR or TV with video/audio input jacks. Cameras fully assembled, including pre-wired connector.

- CCDWA-2, B&W CCD Camera, wide-angle lens.....\$99.95
- CCDPH-2, B&W CCD Camera, slim fit pin-hole lens.....\$99.95
- CCDPH-2, Color CCD Camera, wide-angle lens.....\$149.95
- IR-1, IR Illuminator Kit for B&W cameras.....\$24.95
- IB-1, Interface Board Kit.....\$24.95

FM Stereo Radio Transmitters



Microprocessor controlled for easy frequency programming using DIP switches, no drift, your signal is rock solid all the time - just like the commercial stations. Audio quality is excellent, connect to the line output of any CD player, tape deck or mike mixer and you're on-the-air. Foreign buyers will appreciate the high power output capability of the FM-25: many Caribbean folks use a single FM-25 to cover the whole island! New, improved, clean and hum-free runs on either 12 VDC or 120 VAC. Kit comes complete with case set, whip antenna, 120 VAC power adapter - easy one evening assembly.

- FM-25, Synthesized FM Stereo Transmitter Kit.....\$129.95

A lower cost alternative to our high performance transmitters. Offers great value, tunable over the 88-108 MHz FM broadcast band, plenty of power and our manual goes into great detail outlining aspects of antennas, transmitting range and the FCC rules and regulations. Connects to any cassette deck, CD player or mixer and you're on-the-air, you'll be amazed at the exceptional audio quality! Runs on internal 9V battery or external power from 5 to 15 VDC. Add our matching case and whip antenna set for a nice finished look.

- FM-10A, Tunable FM Stereo Transmitter Kit.....\$34.95
- CFM, Matching Case and Antenna Set.....\$14.95
- AC12-5, 12 Volt DC Wall Plug Adapter.....\$9.95

RF Power Booster

Add some serious muscle to your signal, boost power up to 1 watt over a frequency range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM Stereo transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat, professionally finished look, add the optional matching case set.

- LPA-1, Power Booster Amplifier Kit.....\$39.95
- CLPA, Matching Case Set for LPA-1 Kit.....\$14.95
- LPA-1WT, Fully Wired LPA-1 with Case.....\$99.95

SATELLITE EQUIPMENT



BEST PRICING on 18" satellite TV systems for home and RV. DSS, DISH Network programming, multi-room viewing options, accessories. www.skyvision.com Call 1-800-543-3025.

Treasure Finder Kit



Search for buried treasure at the beach, backyard or park. This professional quality kit can detect metal at a depth of up to 6 inches. Easy to use, just listen for the change in tone as you 'sweep' the unit across the surface - the larger the tone change - the larger the object.

Has built-in speaker or earphone connection, runs on standard 9 volt battery. Complete kit includes handsome case, rugged PVC handle assembly that 'breaks down' for easy transportation and shielded Faraday search coil. Easy one evening assembly. This nifty kit will literally pay for itself! That guy in the picture looks like he found something - what do you think it is - gold, silver, Rogaine, Viagra? You'll have fun with this kit.

- TF-1, Treasure Finder Kit.....\$39.95

Binocular Special

We came across these nice binoculars in an importers close-out deal. Not some cheap in-line lens jobs, these beauties have roof prisms, a super nice rubber armored housing over light weight aluminum. 10 x 25 power with fully coated optics. Includes lens cleaner cloth, neck lanyard and nice carry case. For extra demanding use in bright sun, choose the EX module with ruby coated Objective lens. First quality at a close-out price! We've seen the exact same units with the 'Bushnell' name on them being sold for \$30 more!

- BNO-1, Binoculars and case.....\$24.95
- BNO-1EX, Ruby Coated Lens Binoculars and case.....\$29.95

Speech Descrambler

Decode all that gibberish! This is the popular descrambler / scrambler that you've read about in all the Scanner and Electronic magazines. Speech inversion technology is used, which is compatible with most cordless phones and many police department systems, hook it up to your scanner speaker terminals and you're in business. Easily configured for any use: mike, line level and speaker output/inputs are provided. Also communicate in total privacy over telephone or radio, full duplex operation - scramble and unscramble at the same time. Easy to build, all complex circuitry contained in new custom ASIC chip for clear, clean audio. Runs on 9 to 15VDC. Our matching case set adds a professional look to your kit.

- SS-70A, Speech Descrambler/Scrambler Kit.....\$39.95
- CSS, Custom Matching Case and Knob Set.....\$14.95
- SS-70AWT, Fully Wired SS-70A with Case.....\$79.95
- AC12-5, 12 Volt DC Wall Plug Adapter.....\$9.95

Call for our Free Catalog!

See our complete catalog and order on-line with our secure server at: www.ramseyelectronics.com


RAMSEY ELECTRONICS, INC.
793 Canning Parkway Victor, NY 14564

Order Toll-free: 800-446-2295

Sorry, no tech info, order status at this number

Technical Info, Order Status
Call Factory direct: 716-924-4560

Fax: 716-924-4555

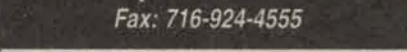

ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.

FREE SATELLITE TV CATALOG. Tech books, installation videos, analysis software
1-800-843-2425 or
www.baylin.com



FREE BIG dish catalog. Low prices! Systems, upgrades, parts, and "4DTV" Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56537. www.skyvision.com
Call 1-800-543-3025.

FREE FLYER on DBS files, hacking, hardware info. Bill 1-800-879-9657.

SATELLITE RADIO BOOK AND GUIDE. New book covers all Audio Services, SCPC, Subcarriers, FM Squared, Facsimile, Press Services, Weather Services. Simple how-to-receive instructions. \$16.95 plus \$3 Priority Mail. UNIVERSAL ELECTRONICS, 4555 GROVES ROAD, #12, COLUMBUS, OH 43232. 614-866-4605.

SATELLITE EQUIPMENT available: Receivers \$25 and up; 20-25 LNB \$30; C-KU feed horns \$65. Call 757-599-4408.

DSS TEST CARD information. Call toll free, 1-888-416-7296.

1999 DSS SOFTWARE COOKBOOK 700+ CD-ROM COLLECTION: CLONING, REVERSE-ENGINEERING, PPV, ADULT, EMULATORS, DIAGRAMS, SCHEMATICS, PATCHES, PLANS, MUCH MORE. (SPECIAL: 1ST 500 ORDERS GET 500+ ADDITIONAL PROGRAMS!) WHOLESALE ONLY \$22 (BUY 2, GET 1 FREE!!!). DSS TEST-CARD INFO SOURCE MANUAL \$10. VISA/MC/AMEX/COD/CHECKS/MO. BRINKER ENGINEERING LABS, USA. CALL NOW 352-429-5496.

Sell Nuts & Volts
in your store and earn \$\$\$!
Contact us for details. 909-371-8497
E-Mail distributors@nutsvolts.com

MILITARY SURPLUS ELECTRONICS

AUDIO - VIDEO - LASERS



ANTIQUE VIDEO TRANSFER SERVICE: transfer of any 2" quadruplex video tapes. Quad TV spots, features, medical, corporate, military, government, and university tape libraries TRANSFERRED TO VHS. Affordable. Phone/fax 415-821-7500. If no answer call 415-821-3359 or pager 415-245-8700.

FREE LASER CATALOG. Helium-Neon, Argon, ruby, visible laser diode modules, lightshows, holography, laser pointers. Lowest prices. Midwest Laser Products, PO Box 262, Frankfort, IL 60423. 815-464-0085 www.midwest-laser.com

WANTED: PRO video equipment, VCRs, switchers, cameras, etc. Advanced Media 702-874-1911.

ATV 2.2GHz to 2.7GHz wireless video data link module tuner & transmitter 100mW. Picotronic, web: http://members.aol.com/picotronic/atv.htm

BROADCAST VIDEO equipment wanted: all types, new or old. Please call, Jon with info. 1-800-539-2859.

CREATE 3-D video images with the Visual Eyes Video system. Phone or fax 918-479-6451 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352.

SYNC-A-LINK UNIVERSAL VIDEO SYNC GENERATOR restores all horizontal & vertical sync lines, DC level, compensates for inverted video, color phase, from standard or distorted analogue video-type formats. Comes complete with operations manual & 90-day warranty. \$160. 918-479-6451 or write to Sync-A-link Communications, PO Box 4, Locust Grove, OK 74352.

CABLE TV

UNMODIFIED JERROLD 212 converter \$50. 97.5, 106.5, 108.5, AB filters \$12 ea. 100dB deep. Digital 125 ch PRO converter \$150. Call for the best you can buy! Toll free 1-888-561-4796 M-F 10-6pm. http://bbctech.hypermart.net

WANTED: TEKNIKA 6510 cable converter boxes/parts. 415-221-5940.

NEW! CABLE converter electronic service equipment and supplies for most cable converter boxes. Highest service, lowest prices. Call Ken Erny Electronics. 24 hr. order and information hot line 516-389-3536.

ADEAL4U WHOLESALES BIG SAVINGS \$\$\$ BEST QUALITY - NO CHEAP CLONES 888-387-1248 www.adeal4u.com

JERROLD UNMODIFIED CONVERTERS FOR SALE. CALL FOR BEST PRICES. NO DESCRAMBLER SALES. CALL BRD ELECTRONICS 1-800-322-6316.

GENUINE UNMODIFIED JERROLD DPBB 7312. 1-800-804-8655. E-MAIL: CLEWIS7298@AOL.COM

RAINBOW KITS



FAN CONTROLLER

Use this kit to control cooling fans, or any device that is temperature activated. Output is 100mA. For a 3 Amp application use the Relay kit RP-1 or the new Micro-controlled Relay PRC-1 kit. Temperature probe included. Operating voltage: 7.5 to 18v DC. Size: 1.5" x 1.2"

FC-1 KIT \$14.95

WIDE BAND PRE-AMP


Uses PCB and surface mount technology for better performance. Use this for scanners, HT's, Frequency counters, Satellite Receivers. It amplifies low-level (weak) signals. If the signal is extremely low, two amplifiers can be used in a series.

- 1MHz to 2.5 GHz 2.8dB NF
- 1dB compression=0dBm
- Gain: 1MHz-20dB to 2.5GHz-6dB
- Power requirement: 12v @ 6Ma

WBA-6 KIT \$19.95

TV NOTCH FILTERS

FOR CHANNELS
2 thru 22
ONLY

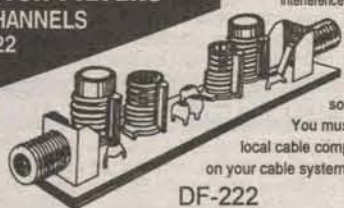


DF-222

KIT \$14.95

FM STEREO TRANSMITTER

Have your own FM radio station. Any stereo signal you plug into the FMST-100 transmitter kit will be transmitted to any FM radio tuneable from 76 to 108MHz FM. Plug in your CD player, tape deck and have a wireless link to any FM radio, within 200 ft. Listen to your CD while mowing the lawn. Transmit from your car to your camper, or through an auditorium. Transmit music on one channel sing on the other. Compatible with any audio system. Clarity is excellent, approx. 40dB stereo separation. Length of antenna determines distance of transmission. Comes complete with left & right input level control as well as a crystal for left & right stereo separation. ANTENNA NOT INCLUDED 9v Battery operation.

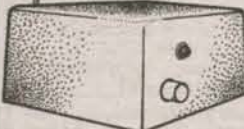

FMST-100
Cabinet

SIZE: 1.5" x 1.6" KIT \$29.95
SIZE: 1.5" x 2.5" x 3" \$8.95

RAINBOW MINI-LIGHT Super Bright Flashlight


- LED's don't burn out!
- Battery lasts for years!
- If you have your keys, you'll have a flashlight.
- Rechargeable battery!
- Better buy 2, your wife is going to take yours!

Lights up a complete bedroom at night

Red MLR \$9.95 each
Yellow MLY \$9.95 each
Blue MLB \$12.95 each
White MLW \$12.95 each
Infrared MLI \$12.95 each



SHOWN ACTUAL SIZE

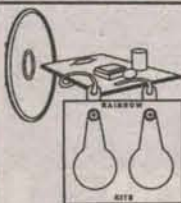

LIE DETECTOR

This kit can be great fun at parties. When you lie, generally your hands will sweat and the more you sweat the louder the tone. This kit allows you to measure these changes, only a slight amount of change will cause the tone to increase in frequency. Power requirement 6 to 12v DC. SIZE: .8" x 1.2"

LD-1 KIT \$9.95




BUSY PHONE LIGHT

Add this little kit to any or all of your telephones. When one phone is used a red LED will light on the other extension.

This lets everyone know when your computer modem is in use. Power requirement 9v DC. SIZE: 1.1" x .6"

TEL-LITE KIT \$9.95

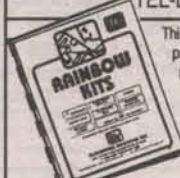

This Manual contains schematics, parts lists & P.C. board layouts for many of the Rainbow Kits. Use your own parts to construct our kits.

KIT BOOK \$14.95



SUPER SNOOPER BIG EAR

Listen through walls, hear conversations across the room. Add a parabolic reflector and hear blocks away. The BIG EAR can be hidden about anywhere. Makes an ultra sensitive intercom. Can be used as a 1.5W AMP. We supply a mini-electret mike in the kit. Power requirement 6 to 12v DC. SIZE: 1.75" x 1"

AA-1 BUILT \$29.95 KIT \$10.95



STROBE LIGHT

Do you need an attention getter, warning light, or flashing light for model airplanes? Then this kit is for you. Use it as an emergency light for your auto, radio tower, even use it on your bicycle. Has a variable flash rate. Power requirement 6 or 12v DC. Size 3.5" x 1.9"

ST-1 KIT \$11.95



AUDIO PREAMP

Boost your microphones output up to line level! Plug your mic into our AP-1 and drive your amp, to full capacity. Connect an AP-1 to a pair of amplified speakers, plug your mic in and you have an instant PA system. Requires 6 to 12v DC. Size: 1.75" x 1"

AP-1 KIT \$9.95



Sweet 16
TONE
DECODER

Sweet 16 tone decoder operates great over phone lines, radios or scanners.

- 16 TTL Level Outputs
- DTMF Decoder Decodes 16 different touch tones using the phone, radios, or scanners.
- One relay & driver circuit on board.
- 9v battery powered. Size: 2 3/4" x 2 1/8"


TT-16 KIT \$34.95



WIRELESS FM MICROPHONE

Small but mighty this little jewel will out perform most units many times its price. It really stomps out a signal. The WM-2 kit is a buffered wireless mike that operates from 80MHz to 120MHz FM, the frequency of any broadcast FM radio. Includes a mini-electret mike. 6 to 12v DC. SIZE: 1.25" x 1"

WM-2 KIT \$14.95

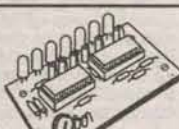

DC VOLTAGE MONITOR

If battery status is important, you need this kit. This kit uses 7 LEDs to monitor 12v DC in 1v, 1/2v, or 1/4v steps. Monitor 8v or 5v in 1/4v steps. Great for boats, motor homes, model planes or race car ni-cads. All parts and instructions are included. SIZE: 1.3" x 2.7". If you want to switch more power see our Triac (TP-1).

VM-1 KIT \$7.95

For 110 AC VM110 KIT \$10.95




INDUCTANCE METER

This is the kit everyone has been asking for. Turn your digital volt ohm meter into an inductance meter. It will read inductors 3uH to 7MH. Power requirement 9v DC. SIZE: 1.75" x 2.5"

IA-1 KIT \$14.95




IA-1 CABINET \$8.95

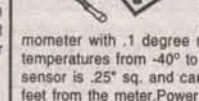

DIGITAL THERMOMETER

The DT-3 kit will turn your digital volt ohm meter into an accurate digital thermometer with .1 degree resolution. Measure temperatures from -40° to 250F° The remote sensor is .25" sq. and can be mounted many feet from the meter. Power requirement 9V DC. SIZE: 2" x 1.35"

DT-3 KIT \$8.95

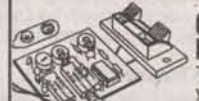

CAPACITANCE METER

This kit will turn your digital volt meter into a capacitance meter. Turn that junk box of unmarked capacitors into a fortune of usable parts. Measure capacitors from <2.2pF to 2.2uF. Power requirement 9v DC. SIZE: 1.80" x 2"

CA-1 KIT \$12.95



VOICE ACTIVATED SWITCH

This VOX circuit can be used to operate a tape recorder, ham radio, CB radio, or turn on an alarm. The VOX-1 kit has 100mA of output that operates a relay, light, motor, ? What could you do with a sound activated switch? Power requirement 7.5 to 18v DC. SIZE: 1.5" x 1.3"

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

VOX-1 KIT \$6.95



PHONE RECORDING SWITCH

This phone line powered switch is small enough to be installed anywhere. Every time the phone is picked up the recorder will record both sides of the conversation automatically. Use it in your office to record all phone calls so you don't lose important information. SIZE: 1" x .6"

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

TEL-SW1 KIT \$12.95



WATER ALARM


Don't ever get stuck with a flooded basement or over fill your water bucket. When the liquid level reaches the sensor it automatically turns the pump on or off. The Water Alarm supplies you with 100 mA of output that activates a relay (that you supply). This relay can turn on a sump pump, or in applications where you are filling a area with liquid it turns off the pump. Sensor included. Size 1.4" x 2"

WA-2 KIT \$17.95



Please add sufficient postage First lb \$5.50. Canada \$7.50. Additional LB. Add \$1.00 US FUNDS ONLY We will accept telephone orders for Visa or Mastercard
Electronic Rainbow Ind., Inc.
6227 Coffman Rd. Indianapolis, IN 46268
CALL 317-291-7262 FAX 317-291-7269
INTERNET: www.rainbowkits.com

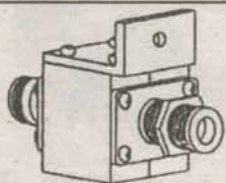DISCOUNT CABLE converters, bullet snoopers, all makes and models: Genuine unmodified General Instrument, Jerrold, Tocom, Scientific Atlanta, Zenith, Pioneer, Panasonic and more. Best warranty. Free catalog 1-800-243-0962.



EXPLOSIVE CABLE TV GRAB! BRINKER ZAPPER/SNOOPER STOPPER combo module all in one! Buy wholesale factory-direct, no middleman. Let others get fined + zapped instead. 100% COMPATIBLE. Your order shipped NATIONWIDE immediately! LIFETIME GUARANTEE! VISA/MC/AMEX/COD/MO/CHECKS. ONLY \$10 (SPECIAL: 3/\$20 plus FREE DESCRAMBLER PLANS!). SUPER ZAPPER MODULES ONLY \$16! (3/\$33)! Use SUPER ZAPPERS if you have COX, TC, WARNER in: CA, TX, FL, NY, PA, MI. DESCRAMBLER PLANS (4=\$5, 20=\$15) 130+ DESCRAMBLER SOURCES (\$5). FREE SHIPPING. OPEN 24 HOURS! 352-429-5496. BRINKER ENGINEERING LABS, USA.

CABLE HACKER'S SECRETS COMPLETELY EXPLAINED! FREE DETAILS! Write: Sierra Publishing, 909 E. Yorba Linda Blvd., Suite H-181, Dept. B1, Placentia, CA 92870.

UNMODIFIED CABLE CONVERTERS. Zenith ST1600, ST1086, ST300, Panasonic 175, 145 vol. & non-vol. Regal RR-92 & RC 83, DP5, DP7, DRZ, 5503 VIP, SA 8580. Guaranteed low prices. Please call for more converters 405-631-1856.

CBTV REPAIR. We specialize in all converters, including Zenith. Give us a call: 405-634-1535.

ONE STOP shop. We carry a full line of CBTV equipment for all your cable needs. Also a wide variety of converter parts and accessories. Call for free catalog: 405-631-5153, FAX: 405-631-4788.

TUNERS TOCOM 5503 tested \$4.75 ea., bargain, 10 lot min. Call 706-657-4445.

UNMODIFIED, POWER-UP, Pioneer BA: 6110, \$75; 5135 \$45; 5125 \$25; Jerrold DP5, channel 2: \$19, DPBB 7312, \$95; S/A 8590-7S7 (11 button) \$95. Minimum 10-lot. 405-631-5153.

CABLE TV. Panasonic TZPC 175DG2, brand new, \$80 w/volume, 1 year warranty, minimum 10 pcs. any qty., plus all major brands available. Lowest price new/field pulls. E-Mail: OCALA@BELL SOUTH.NET phone: 1-800-929-1549 fax: 305-220-9396

UNBELIEVABLE PRICES. We carry a full line of cable tools and equipment for all your cable needs. Also a wide variety of electronic parts & accessories, tools, diagrams, converters, step-by-step instructions, no raw parts. Full technical support. 12pm-7:30pm EST. 1-800-562-8442.

ATTN. DEALERS: Are you a current dealer or just getting started? Buy factory direct & save \$. New 181 and 125 channel converters, major brand name cable converters & all other accessories not listed, no more delayed shipments. All products 6 month warranty, 30 day money back. A & S Wholesale, 1-800-370-0801.

BOARD R US, for all your cable needs or computer software, programming service available. 4 MHz resonators 3 pins as low as 34¢. For info call 909-948-3736 or visit us at our web site <http://members.aol.com/BoardRUS>

CABLE PARTS! Computer parts. Call for great prices or visit us on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

ATTENTION: YOU'VE tried the rest, now go with the best. **UNICORN ELECTRONICS** where our valued customers ALWAYS come first. **CABLE CONVERTERS AND ACCESSORIES.** We will beat all competitors prices GUARANTEED. All UNITS in STOCK FOR IMMEDIATE SHIPMENT. FREE batteries and coax cable. FREE bullet protection with every unit purchased. FREE shipping with a \$500 purchase or more. NO COD charges. ALL products come with a 1 year warranty and a 30 day money back guarantee. Please give us a call TOLL FREE 1-888-738-8181 9am to 6:30pm EST. VISA, M/CARD, DISCOVER, COD. UNICORN Electronics does not advocate unauthorized use or theft of cable services.

TOCOM UNMODIFIED 5503 CABLE CONVERTERS UNTOUCHED. \$6 EACH. 10 LOT MIN. CALL 706-657-4445.

EXPERT CABLE box repairs. All makes and models. Call 877-581-8014.

Tiny FBasic Computer



(Shown 85% Actual Size - 40 pin DIP)

The TICkit 62 module is like a Parallax Basic Stamp II, but has 4 times the program space installed (expandable to 64K). It also has 4 times the variable space (96 bytes), and uses a modern structured language similar to BASIC only more powerful.

- Only tool you need is a PC
- Inexpensive \$45/module, \$16/IC
- Development Kit only \$45
- Huge library of I/O function
- Structured FBasic Language
- Easy to learn and use
- Powerful enough for large projects

ASK ABOUT OUR STAMP COMPATIBLE PERIPHERAL COMPONENTS

VersaTech

Electronics

PHONE: (303) 828-9156, FAX: (303) 828-9316

e-mail: versatech@csn.net

Web: <http://www.csn.net/versatech>

11170 Flatiron Drive, Lafayette, CO 80026


Basic Stamp is a registered trademark of Parallax, Inc.

TOCOM UNMODIFIED 5503 CABLE CONVERTERS UNTOUCHED. \$6 EACH. 10 LOT MIN. CALL 706-657-4445.

CABLE CONVERTERS. Original equipment with remote. Like new, ready to go. Lowest prices guaranteed. Limited models. Tele-Pix Electronics, 412-833-0773.

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

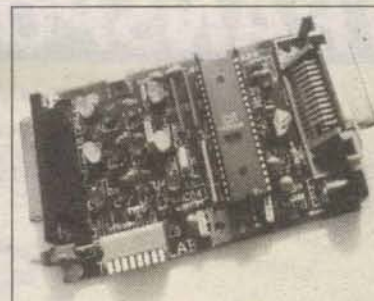Techno Lab: PROCON-1 IEEE to Centronics Converter



more products: TECHNO-LAB.com

For IEEE sources:

- Logic Analyzer
- Spectrum Analyzer
- Oscilloscope and more

Print your measurement results on your PC Printer with never seen quality! Enjoy possibilities you have with your PC printer now also for your measurement print-outs! Use up to 50 feet long cable or print on plastic sheets! See status messages about data transmission: DAV/NRFD/NDAC and STROBE/ACK/PE.

Don't waste money on special IEEE high price printers! No special cables needed, no installation- just plug and print!

only \$99.00

TECHNO LAB DIGITAL SYSTEMS

1628 E Amar Rd Ste. L

West Covina, CA 91792

Phone: 626 964 1122

Fax: 626 964 7962

Write in 40 on Reader Service Card.

ATTN: CABLE brokers, dealers & operators. We broker all types of cable-related equipment, most brands of converters, filters, and remotes. All converters are field pulls in raw factory condition. We also sell parts such as ICs 16C54, 56 and 57. Plain JAIN converters, new, starting at \$39.95 10 lot. No decoder sale. For orders: 1-800-318-2795. Questions: 818-776-0692.

CABLE BOX COVERS TOCOM 5503, good condition \$3.75 ea. 20 lot min. Call 706-657-4445.

Any waveform you want!

● Synthesized Signal Generator

Clean sinewaves DC-21.5 MHz with .001% accuracy! .01 Hz steps. DC Offset. RS232 remote control.

● Arbitrary Waveform Generator

40 Megasamples/Second. 32,768 points. 12 bit DAC

● Function Generator

Ramps, Triangles, Exponentials, Noise & more. 0 to 2 MHz in 1 Hz steps. Continuous or Triggered.

● Pulse Generator


Digital waveforms with adjustable duty cycle




Telulex Inc. model SG-100A

New Features:

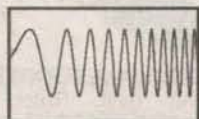
- ✓ 21.5 MHz
- ✓ .01 Hz steps
- ✓ multi-unit phaselock




DC to 21.5 MHz linear and log sweeps

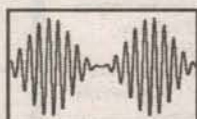


Int/Ext AM, SSB, Dualtone Gen.

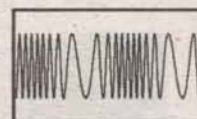

Int/Ext FM, PM, BPSK, Burst

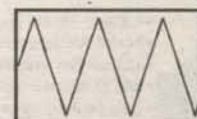


Ramps, Triangles, Exponentials

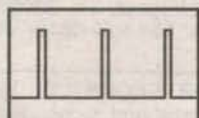


Pulse Generator



Noise

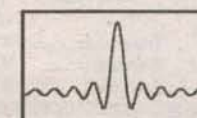

Arbitrary Waveforms

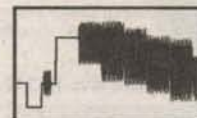

Unlimited Possibilities!

Telulex Inc.

2455 Old Middlefield Way S

Mountain View, CA 94043

Tel (650) 938-0240

Fax (650) 938-0241

<http://www.Telulex.com>

Email: sales@Telulex.com

Control High Security Access with a Unique TRANSPONDER KEY



Easy, Safe, Secure, Convenient, & Cost Effective

The ideal security solution for an infinite number of applications

The proximity technology employed by our unique transponder kit permits the transfer of data between the keyfob and the transmitter/receiver when the key is within range, up to 70mm. The list of applications for which the kit may be used is literally endless.

How does it work?

The user receives a master key in a sealed container. The master key provides the user with the ability to program new keys (and to erase lost or stolen keys). The coding of new keys to the system is very easy - it is done within a few seconds. The system "learns" the new key code automatically by using the master key. There is no need for programming or similar manual entry. Up to 20 keys may be added. The transponder key fob contains no moving parts or batteries - it is completely weatherproof and waterproof. When the key is brought within range of the matching transmitter/receiver, the system activates by performing the pre-set task - setting off or deactivating an alarm, opening a door, gate, calling an elevator, etc.

- Security Authorization
- Home or Office Security Entrance
- Gate Access Control
- Private Parking
- Entrance to restricted areas
- Restricted elevator call
- Alarm Systems
- Etc.

AS LOW AS
\$9.00
PER UNIT*

*10,000 UNITS
One (Sample) \$25
50+ units \$18 each
100+ units \$16 each
500+ units \$15 each
1000+ units \$12 each
10,000+ units \$9 each
- Plus S&H -

Includes simple schematic diagrams for connecting a pulse relay and 'on' switch to enable activation of - for example - an alarm system and door opener

SPECIFICATIONS: Circuitry housing: Black plastic 4 1/8" x 2 1/8" x 1". Sensor: Extends 19" from housing, size 2 1/8" x 5/8" x 1/4". Detects key up to 2.75" through wood, glass, or plastic. Keys: Comes with 2 keys. Waterproof, crush resistant. Power: 12VDC. Standby mode 21mA, Detection Mode 48mA

TO ORDER - CALL OR FAX
Tel. 914-352-5053 • Fax 914-426-5374

A.S. Electronics • P.O. Box 601 • Monsey, NY 10952 914-352-5053

Write in 41 on Reader Service Card.

RF Data Modules



AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current: 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 \$12.10

AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery. CMOS
- Low current. 2.4mA typical
- 2kHz data rate. CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx \$10.95

FM TRANSCIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F \$87.36

RS232 TRANSCIVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- μ Controller with user EEPROM
- RS232 interface protected to $\pm 15kV$
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 \$139.30



70 x 65 x 15mm

Transceiver.....
Transmitter.....
Receiver.....

- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair (RTcomTX & RTcomRx)
- 7.5V-15Vdc operation

RTcom-4xx..... \$247.90
RTcomTx-4xx..... \$ 87.15
RTcomRx-4xx..... \$105.52

CABLE CONVERTERS, DBS, remotes, schematics, etc., free flyer. Jake 419-385-3100.

CABLE BOX repairs and upgrade. Most models, warranty lowest prices. Call 214-695-5982.

PLANS: DESCRAMBLE CABLE FOR UNDER \$12. PLUS TWO FREE BONUS. TOLL FREE 1-888-588-3715.

TOCOM UNMODIFIED 5503 CABLE CONVERTERS UNTOUCHED. \$6 EACH. 10 LOT MIN. CALL 706-657-4445.

DTV & DISH NETWORK INFORMATION (33 PAGES) only \$15. Mainline Electronic, Inc. Free cable information included. Playstation & Nintendo 64 games at wholesale prices. Visa & MasterCard accepted. Call toll-free 1-877-539-9896.

TELEPHONE/FAX

TELEPHONE CATALOG 160 pages including office automation, voice mail, and all phone accessories. Send \$10 to HES Electronics, POB 183, Brick, NJ 08723. A 10% off certificate will be included! Visit www.heselectronics.com

PHONE SYSTEMS WANTED!!! We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.,** 937-847-2300 or FAX 937-847-2350.

CELLULAR CLONING COLLECTION. 1999 CELLULAR CLONING INFO BIBLE \$22, 1999 CELLULAR CLONING SOFTWARE COLLECTION \$33, 1999 CELLULAR SECRETS & PROGRAMMING MANUAL \$11. ALL 3 FOR \$44, WOW!! (SAVE \$22). FOR EDUCATIONAL/TECHNICIAN TESTING USE ONLY. (VISA/MC/AMEX/COD). OPEN 24 HOURS! 352-429-5496. **BRINKER ENGINEERING LABS, USA.**

COMPONENTS

PHOTOMULTIPLIER TUBES, radiosondes, electro-luminescent panels, electronic parts, test equipment. www.lonemtn.com

RF TRANSISTORS, TUBES, 2SC2879, SD1446, MRF455, MRF454, 3SC1969, 2SC2166, 2SB754, TA7222AP, 2SC1419, 2SC1947, 2SB688, 2SD880, MRF422, MRF448, MRF247, MRF317, SAV7, SAV17, 3-500ZG 4CX250B, 572B, 3CX3000A7, 4CX400A silver mica caps, resistors, electrolytics, etc. Westgate 1-800-213-4563.



AMAZING! 35¢ ALL TOGGLE SWITCHES. Brand new. Rated 6A/125V. Hardware included. 1/4" panel hole. SPDT or DPDT on-on, or on-off-on. Minimum 100pcs./package. Add \$6 freight. Gateway Products Corporation, PO Box 936397, Margate, FL 33093, 954-974-6864, Fax: 954-974-6818, VISA/MC, no COD.

RESISTOR SACRIFICE: 10,000 quarter-watt metal and carbon film. One, two, and five %. 1 ohm to 22 megohms. **FIFTY** each of **TWO HUNDRED** different values. \$45 (less than one-half cent each). Hyatt Surplus, 371 N. Johnson Ave., El Cajon, CA 92020. Tel: 619-444-2434 fax: 619-444-1987.

NEW 1999 catalog: Inductors, toroids, TC ceramic and Mica capacitors, semi-conductors, wire and cable, hardware, more. Two stamps please. Johnson Shop Products, Box 2843, Cupertino, CA 95015.



FACTORY SALE! CNL100, CNP101: 1/3" CCD, 430 line horiz., 12V/100mA, lens and pin hole types, lens 3.6mm/F2.0, 0.08 LUX, 1.27" (W) x 1.27" (L) x 1/2"-1" (H). \$49 @ 5 pcs., \$44 @ 10 pcs. Distributors welcome. Matco, Inc., 1-800-719-9605 Fax: 630-350-9546. E-Mail: sales@matco.com Web site www.matco.com

SEE OUR ad on 4-channel 2.4GHz wireless system in the admart section on page 81. Matco, Inc.

GOLD, SILVER, platinum content of over 200,000 defense supply system items. 3 CD set, \$145. 334-889-4637. <http://down.town.ala.net/~myoung/fedcd.html>

CUT AND formed resistors, for one penny! Yes! One penny! Get all the details at www.CrowRiver.com

MICROCONTROLLERS



PIC MICROCONTROLLER PROGRAMMER KIT. Super value at \$19.95 + \$4.95 shipping. See our web site for the complete range of PICs that can be programmed. Includes PCB, parts and instructions. P16PRO shareware must be downloaded from the web. Amazon Electronics, tel 1-888-549-3749. Lots of other products. www.electronics123.com

MPLC MICROCONTROLLER! Basic programmable EEPROM via RS232. 16 user configurable I/O. Supports I2C bus and 1 wire devices. Direct drive LCDs. Starting under \$100. Developers kits available. Potts Technologies Company, 831-662-2293 fax 831-662-1877 or www.pottstech.com

68HC11, 80C552 and 8031 microcontroller boards. Uploader, assembler and compiler software included. See our products at: www.tecel.com

ANTIQUE ELECTRONICS

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

ANTIQUE RADIO CLASSIFIED. Free sample copy! Antique radio's largest-circulation monthly magazine. Old radios, TVs, ham equip., 40s & 50s radios, telegraph, books & more. Ads & articles. Free 20-word ad monthly. Subscribe today. Six-month trial: \$19.95. Yearly rates: \$39.49 (\$57.95 by 1st Class). Foreign: write. ARC, PO Box 802-G23A, Carlisle, MA 01741. Phone: 978-371-0512; Fax: 978-371-7129; Web: www.antique-radio.com

WESTERN ELECTRIC WANTED: 1920's-1960's. Amplifiers, mixers, preamps, speakers, tubes, etc. **FREE OFFER** 1-800-251-5454.



ABACOM TECHNOLOGIES



Tel: (416)236-3858
Fax: (416)236-8866
www.abacom-tech.com
abacomtech@compuserve.com

RADIO TUBES and phono. needles. 870-347-2281.

CRYSTAL SETS. Parts, plans, books, kits. Largest source in the world. Catalog \$2. MIDCO, PO Box 222288, Hollywood, FL 33022.

ANTIQUE COMPUTERS: Buy/sell. E-Mail: teamwithus@aol.com or 319-358-5911 for complete listings and my wish list!

AVIATION ELECTRONICS

BUY, SELL, trade, avionics equipment, Collins, King, Sperry: test equipment, IFR, Litton LTN series INUs. 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

PUBLICATIONS

UNDERGROUND, HACKING, SNEAKY 1999 BRINKER MASTER CATALOG! 1,200+ PRODUCTS FOUND NO-WHERE ELSE! 95% OF PRODUCTS ARE \$3!! CATALOG (30+PAGES) \$10 (FIRST 500 CALLERS: FREE \$25 GIFT CERTIFICATE!!) OPEN 24 HOURS! 352-429-5496. BRINKER ENGINEERING LABS, USA.

COMPUTER TELEPHONY. You've heard the term, now learn the details by ordering our 35 page publication packed with facts. Only \$9.95! Harmony Products, PO Box 91, Netcong, NJ 07857.

WEBBOOKS OFFERS discount prices on technical/engineering books plus free assistance to authors. Please visit us at <http://webbooks.net>

NEW SURVIVAL COMMUNICATIONS BOOK. How to build complete home communications systems. Covers all needs: shortwave radio, amateur radio, citizens band, scanners, federal, weather, alternate news, satellite radio, equipment sources. How to build and use alternate emergency power sources, solar, generators, backup batteries. 200 pages. \$24 Fast delivery Priority Mail. MC or Visa. Call Universal Electronics 1-800-241-8171.

ROBOTICS

ROBOT BOOKS.COM visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! www.robotbooks.com

ARobot KIT from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/arobot>

H-BRIDGE MOTOR controllers, 12VDC, 35A average, 50A peak PWM out. Forward, reverse, ramp-up and ramp-down on acceleration/deceleration. Current foldback when hot, reverse polarity protected, conformal coated, regenerative braking, compact, approx. 3.75"x5.5". \$25 & S&H. 717-735-5053. <http://members.tripod.com/~divelec>

68HC11, 80C552 and 8031 microcontroller boards. Uploader, assembler and compiler software included. See our products at: www.tecel.com

GET STARTED in robotics with an ARBE-ONE kit (the "Model T" of mobile bases), a TCOMP tiny computer (68HC11 controller on a board optimized for robotics). On-line ordering: <http://www.BecTec.com>

100 WATT P A AMP

GROMMES-PRECISION ST100E AUDIO AMPLIFIER, solid state 100 watt public address amp; response 35 to 20000 Hz 4 ohm output, 0.3% distortion. Volume controls for MIC-1 & -2, AUX input, MUSIC and MASTER plus BASS and TREBLE controls. Also slide switches: Loudness and Lo Filter plus Peak Power/Over-load indicator. Back page, two Lo or Hi Z mic select, uses discrete transistors, and two XLR 3-pin male mic connections, with instructions and schematic. 4.3x15x12.8, 25 lbs sh. NEW, \$199.50

1950's CAR TESTER

HEYER MODEL 337 TACH / VOLTMETER with 4.5" chrome-rimmed meter. ranges 0-1000 & 0-5000 RPM and +/- 0-18 VDC. Amplifier button plus socket for timing light. With tubes 0A2 & 2D21; 6 or 12 VDC use. Nice addition to a car collector's display! 13x5x5, 9 lbs sh. UNUSED, not tested, \$24.95

1 to 1400 MHz Sweeper

WAVETEK 2001A SWEEP GENERATOR, covers 1 to 1400 MHz sweep and CW in bands 1-500, 450-950, and 950-1400 MHz. Sweep width 50 KHz to 500 MHz. Sweep time: 100 to 0.01 S in 4 decade steps. Markers at 0.2, 1.5 and 20 MHz harmonics and single frequencies 63 MHz, +/-0.35 and +/-0.9 MHz. Marker width 15-400 KHz in 4 steps. RF output continuously adjustable +9 to -81 dBm into 50 ohms. Requires 115/230 VAC 50-60 Hz; 5.3x 11x14.2, 25 lbs sh. USED-repairable w/book, \$395.00

30 FT ANTENNA MAST

AB-1244/GRC MAST KIT, twelve aluminum alloy on steel sections form sturdy, yet lightweight 30 foot 1.7" dia mast. Kit includes five each lower and upper sections, one ea lower and upper adapter sections, gin pole swivel base, four ea 36 and 42 ft guy ropes, four guy stakes, two guy rings plus a 2.5 pound sledge hammer. Part of OE-254/GRC antenna set; 30 lbs. NEW, \$139.50

Prices F.O.B. Lima, Ohio. VISA, MASTERCARD accepted.

Allow for shipping charges. Write for latest Catalog.

Address Dept. NV + Phone 419/227-6573 + FAX 419/227-1313

E-mail: fairradio@wcoil.com Home Page: <http://www2.wcoil.com/~fairradio>

FAIR RADIO SALES CO.

1016 E. Eureka + Box 1105 + Lima, Ohio 45802

Write in 43 on Reader Service Card.

MICRO VIDEO CAMERAS



MB-650PA - \$139.95
2.8mm Pinhole Lens.



MB-650UA - \$129.95
4.3mm Micro. Lens




MB-750P - \$129.95
2.8mm Pinhole Lens.




MB-750U - \$119.95
4.3mm Micro. Lens

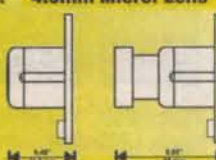MB-650a Series
• Built-In Audio
• 1.18" sq.
• 380 TV Line



MB-750 Series
• 1.25" sq.
• 420 TV Line

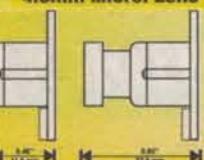

The Best, Smallest, Micro Cameras on the Market Today!
Call and Compare! We Match or Beat All Prices!

Panasonic Color Camera Sale

Ask for the **Quick-Start KIT** Accessory

MB-45cB - \$99.95
Size: 1.25 x 1.25 sq. w/ Footprint

Micro Color MB-45cB: \$99.95

- Wide Voltage Range, 5-14 Volts!
- Small Footprint!
- Self contained ultra small package design for various applications.
- MCM PCB design for minimizing the size and improve durability.

Specifications: MB-45cB Color Camera

Pick-up device	1/4" Interline transfer
Effective Pixels	512 (H) x 496 (V)
Scanning System	2:1 Interlace
	525 lines - 60 fields
Frame per second	30 frames
Synchronization	Internal
Video output	VBS. 1vpp 75 Ohms
Horizontal Res.	More than 330 lines
AGC	On fixed
White Balance	ATW fixed
Operating Temperature	32°F to 104°F
Ambient conditions	Indoors
Lens	F2.8 Hor. Angle 45° - Ver. Angle 34°

WIRELESS VIDEO



Compatible with AC or Battery
Wireless 4-Channel BW & COLOR Cameras Available!

Wireless Observation System's
GFS-1001 (900MHz) - \$499.95
GFS-1001c (900MHz) - \$599.95
(900, 1.2 & 2.4 Ghz systems available.)

GFT-1001 \$189.95
Gives any camera the ability to be Wireless.



Visit **Polaris Ind.** Web Site at: <http://www.polarisusa.com>

1-800-752-3571

Polaris Industries 470 Armour Drive NE • Atlanta GA 30324 • Tech Info: 404-872-0722 • FAX 404-872-1038

Our Smallest Video Camera

CMOS Camera
CM-550u - \$69.95

Pin Hole Camera:
CM-550p - \$69.95

LIPSTICK CAMERAS

These cameras are supplied with a PCM-1 Video/Power cable. The BNC connection is for standard video connection to a Monitor or VCR.

LP-850p
\$139.95

Length: 1.37"
Diameter: .87"

LP-850i
\$129.95

Length: 1.9"
Diameter: .91"

Write in 42 on Reader Service Card.

Nuts & Volts Magazine/April 1999 49

IndustroLogic™

Fast, friendly project development!



**SBC-1 80C51
Single Board
Computer**
\$179

Menu based monitor and BASIC in ROM. 50 I/O, A/D, RTC, serial, I/O rack interface, up&download to EEPROM. Includes software.



**SMD-12 Stored
Message Display**
\$179

Display & enter messages with switch closure or serial port. 12 messages of up to 32 characters. 6"W x 3"H x 6"D Steel case.



**SIO-1000 RS-232
Data Acquisition
Interface Board**
\$179

8 TTL in, 8 TTL out, dual 12 bit A/D & D/A channels. counter in, frequency out, WINDOWS/DOS software, cable, case & supply. 4.25" x 6.5" x 1.5" high. 12 oz.

Industrologic, Inc.
3201 Highgate Lane
St. Charles, MO 63301
(314) 707-8818
9AM-5PM Central

Full technical info on the Web!

www.industrologic.com

Write in 44 on Reader Service Card.

Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

with the AES learning system/
embedded control system.
Extensive manuals guide
you through your
development project.
All programming
and hardware details
explained. Complete schematics.
Learn to program the LCD, keypad
digital, analog, and serial I/O, for
your applications.



**THREE MODELS AVAILABLE.
Choose from an Intel 8051,
Intel 8088, or Motorola 68HC11
based system.
All models come with:**

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts, timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly, BASIC, and C programming (varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals: cover all details (over 300 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

Everything you need. From \$279
Money Back Guarantee

Call for Free Info Pack, or see

WEB at <http://www.aesmicro.com>


714-550-8094, FAX 714-550-9941

Call 1-800-730-3232



AES 575 ANTON BLVD., SUITE 300, COSTA MESA, CA 92626, USA

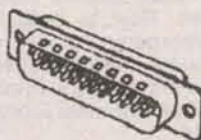ROBOTS, ROBOT kits, 68HC11 micro-
controllers, tutorials, software, spy cam-
eras. Different level kits. <http://www.mrrobot.com> 804-272-5752, 1-888-Mr-Robot.



MICROPROCESSOR CONTROLLED
RS-232 to RS-485 converter 2 and 4
wire models all baud rates, all word
structures. Easy to adjust using rotary
switches. Also available RS-232 to fiber
and RS-485 I/O modules. Visit web site:
pages.infinet.net/cec CEC, Inc., 514-830-7215.

www.futurerobots.com **ROBOTS** are
coming soon to our homes. Most of the
technology is now here, as well as the
need. Read technical papers and con-
struction articles for active security sys-
tems.

PLANS — KITS — SCHEMATICS

HOBBY CATALOG: Broadcasting and
microbroadcasting transmitters, ampli-
fiers, antennas. **Start your own radio
station books.** Audio, TV, ham, CB, sur-
veillance, science projects, and more.
PAN-COM International, Box 130-V,
Paradise, CA 95967. www.panaxis.com

BUILD THE MENDOCINO MOTOR. This
fascinating device is a solar powered,
magnetically levitated motor. It will
delight and amaze you and your friends.
The 27 page plans book includes a list of
parts suppliers. The motor uses readily
available parts. Plans are \$15 plus \$2.50
S&H. Write to: St. Elmo's Fire, PO Box
141, Stow, MA 01775. E-Mail: tcv@genrad.com

ELECTRIC POWER METER STOPPER
MAKES METER RUN SLOWER, STOP,
OR EVEN REVERSE! COMPLETE
PLANS \$15, SOLD FOR EDUCATION-
AL PURPOSES ONLY.
(VISA/MC/AMEX/COD) OPEN 24
HOURS! 352-429-5496 BRINKER
ENGINEERING LABS, USA.

200+ ELECTRONICS PROJECTS. Build
for pleasure or make 100% (or more)
profits reselling printed plans. \$1 (refund-
able) for catalog & dealer info. **MATCO-**
A5, PO Box 509, ROSEVILLE, MI
48066-0509.




SOLDERLESS BREADBOARD SB-
147: 3260 tie points, 4 binding posts.
\$29.95 plus \$2.60 (2% of subtotal plus
\$2) UPS ground delivery. Call 972-242-
8087 for 10+ prices. Mail check to: **CTI**,
1301 West Beltline #105, Carrollton, TX
75006.


HOVERBOARDS, JETPACKS, LIGHT-
SABERS. Plans, schematics, and kits for
over 100 incredible devices. \$3 for cata-
log. Future Horizons, PO Box 125,
Marquette, MI 49855. www.futurehorizons.net



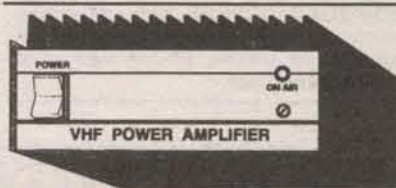CIRCUIT BOARDS. Low-cost, precision-
made PC boards from your CAD pro-
gram files (no photoplots required).
Single and double-sided with contour
routing. Ideal for RF/analog/digital pro-
totypes. Full details at <http://www.pcbmilling.com> E-Mail: feedback@pcbmilling.com FAX: 703-818-0071.



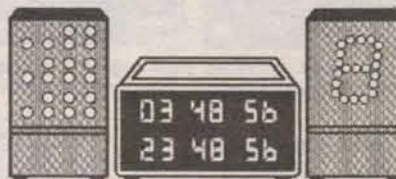BROADCAST FARTHER! 75-110MHz
amplifier connects to stereo transmitters.
Produces 2-15 watts. Requires 50-
150mW drive. Complete plans with part
source and antenna information only \$14
+ \$2 S&H. **Progressive Concepts**, PO
Box 586, Streamwood, IL 60107. 630-
736-9822.



TERRIFIC TIMEPIECES! LED binary
clock. LED digital clocks, other kits! Free
catalog! **WPC**, 805-339-0702.
www.west.net/~wpc

FOR SALE: manufacture schematic dia-
gram cover, color TV camcorder and
VCR. Contact Asa Davis 606 253-4016.

VOICE CHANGER: PCB with all board
mounted components plus speaker.
(Watch for our N&V article.) New price
\$9.95 postpaid in US. MicroMethods, PO
Box 909, Warrenton, OR 97146. 503-
861-1765 jdennon@seasurf.com

NEED LARGE, precision wound coils for
vehicle detectors, alarms, loop antennas,
proximity detectors, metal locators, direc-
tion finders, security gates or other pro-
jects? We also sell tubes and AM radio
signal boosters which improve reception.
Send \$2 for details (refundable with pur-
chase). Fala Electronics-V, POB 1376,
Milwaukee, WI 53201.

AWESOME KITS: voice changers, levi-
tators, lasers, solar robots, and more!
Catalog \$1. **LNS Technologies**, PO Box
67243, Scotts Valley, CA 95067.
www.ncal.verio.com/~lnstech

YOU WIN!

Subscribe today!!

and be automatically entered each month
in our Prize Drawing (see ad on page 85).

WE'LL MEET OR BEAT ANY COMPETITOR'S PRICE!

ALL PRODUCTS
1 Year Warranty



BRAND NEW
Wavemaster 99 Channel
• Sleep Timer • Std./HRC Switch • Parental Control
AS LOW AS \$45⁰⁰ COMPLETE
CHECK US OUT!



Formerly JES, Inc.

BEST PRICES!
FAST SERVICE
SAME DAY SHIPPING



Panasonic I45 & I75's
WE STOCK
EVERY MODEL USED.
CALL NOW FOR
WHOLESALE PRICING

TOLL FREE: 800-322-9690



FAX: 516-246-5634

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401
(612)332-2378 FAX (612)332-8481 E-MAILSURPI@VISI.COM
WE BUY TEST EQUIPMENT AND COMPONENTS.
VISIT US ON THE WEB AT WWW.ABCTEST.COM

HP 54301A 100MHZ DIGITIZING SCOPE	\$1300.00	HP 4935A TRANSIMPAIRMENT TEST SET	\$900.00
HP 54201D 300MHZ DIGITIZING SCOPE	\$1000.00	HP 5008A SIGNATURE ANALYZER	\$150.00
HP 54201A 300MHZ DIGITIZING SCOPE	\$1000.00	HP 86602B 1MHZ-1300MHZ RF PLUG	\$400.00
HP 54200A 50MHZ SCOPE/WAVEFORM ANALYZER	\$700.00	EIP 575 MICROWAVE COUNTER	\$1500.00
HP 3312A 13MHZ FUNCTION GENERATOR	\$250.00	FLUKE 95 50MHZ SCOPEMETER	\$550.00
HP 3370A 100MHZ U.T.I. COUNTER	\$400.00	LECROY 7200 400MHZ O-SCOPE	\$1000.00
HP 3586C LEVEL METER	\$750.00	TEK 475 200MHZ O-SCOPE	\$500.00
HP 436A POWER METER W/O SENSOR&CABLE	\$500.00	TEK 465 100MHZ O-SCOPE	\$400.00
HP 8350B SWEEP OSCILLATOR MAINFRAME	\$2000.00	TEK 496P 1KHZ-1.8GHZ SPEC. ANALYZER	\$3500.00
HP 3437A 3.5DIGIT SYSTEM VOLT METER	\$250.00	TEK 1240 LOGIC ANALYZER	\$750.00
HP 3455A DIGITAL MULTIMETER	\$250.00	TEK TDS320 100MHZ DIGITAL O-SCOPE	\$1400.00
HP 3456A DIGITAL MULTIMETER	\$400.00	TEK 11401A 500MHZ PROG.O-SCOPE FRAME	\$750.00
HP 3336C SYNTHESIZER/LEVEL GENERATOR	\$800.00	TEK 7834 400MHZ OSCILLOSCOPE FRAME	\$500.00
HP 3325A SYNTHESIZER/FUNCTION GENERATOR	\$1000.00	TEK 7904 400MHZ OSCILLOSCOPE FRAME	\$250.00
HP 5335A 200MHZ COUNTER	\$600.00	TEK 7A26 200MHZ VERTICAL PLUG	\$75.00
HP 8165A PROGRAMMABLE SIGNAL SOURCE	\$1100.00	TEK 7A24 400MHZ VERTICAL PLUG	\$150.00
HP 8558B/181 100K-1500MHZ SPECTRUM ANALYZER	\$1000.00	TEK 7B80 400MHZ TIME BASE	\$75.00
HP 8559B/183 10MHZ-21GHZ SPECTRUM ANALYZER	\$3000.00	TEK 7B92A 500MHZ DUAL TIME BASE	\$125.00
HP 1790A 100MHZ OSCILLOSCOPE	\$250.00	TEK 7S12 SAMPLING PLUG	\$250.00
HP 6034A 60VDC-10A POWER SUPPLY	\$750.00	TEK 7L14 10KHZ-1.8GHZ SPEC. ANALYZER	\$1000.00
HP 6269B 40VDC-50A POWER SUPPLY	\$800.00	TEK AMS03 CURRENT PROBE AMPLIFIER	\$250.00
HP 6553A 40VDC-12.5A POWER SUPPLY OPT.J01	\$1200.00	WAVETEK 145 20MHZ PULSE/FUNCTION GEN.	\$400.00
HP 6632A 20VDC-5A POWER SUPPLY	\$500.00	WAVETEK 182A 4MHZ FUNCTION GEN.	\$150.00
HP 6643A 45VDC-4.3A POWER SUPPLY OPT.J03	\$750.00	WAVETEK 955 7.5-12.4GHZ MICROSOURCE	\$1100.00

Write in 46 on Reader Service Card.

HEATHKIT COMPANY is selling photocopies of most Heathkit manuals. Only authorized source for copyright manuals. Phone: 616-925-5899, 8-4 ET.

WIRELESS DOORBELLS! Battery-operated transmitter and receiver. 200ft range. Plans for interfacing to external electronics. Experiment with RF. Add remote control to projects. \$26.95 + \$3 S&H. Volume discount. Pine Valley Technologies, Inc., W4117 Pine Valley Rd., Belleville, WI 53508. 608-424-3836.

EXOTIC PATENT list, free energy, Tesla, anti-gravity, high mileage carbs. Free information. Conti, Box 1014V, Carmel, NY 10512.

MANUALS - SCHEMATICS WANTED

MANUALS: TEST equipment manuals bought and sold. See our list on the web: www.usimperio.com Call 410-685-1991 with your inquiries or for-sale list or fax to 410-685-7701. CONSOLIDATED SURPLUS.

WANTED: INSTRUCTIONS manuals, computer AST Bravo LC 4/50D, computer Wang PC 240-3. Derabertis, 18 Cammann Road, Coram, NY 11727.

WANTED: MANUAL and/or schematic for Daven type 170 electronic voltmeter. This reads AC volts logarithmically and decibels. Photocopy ok. Cecil Grace, Box 5127, Asheville, NC 28813.

MISCELLANEOUS ELECTRONICS FOR SALE

CALL FOR a free electronics catalog or visit our web site at www.bgmicro.com B.G. Micro, PO Box 280298, Dallas, TX 75228. Order line 1-800-276-2206.



SOLAR-POWERED FAN HAT. Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.

HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE. European and American screwdrivers, nut-drivers, pliers, hex-keys, balldrivers, and more! Wiha, Bondhus, and Knipex. Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 6437V, Fair Haven, NJ 07704. Telephone or fax 732-758-8388. E-Mail: w2tv@csi.com



ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. Wire cut & strip to specs. If interested, please call 1-800-626-7540, FAX: 714-771-5043. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anaheimwire.com> OR E-Mail: info@anaheimwire.com

NUCLEAR ELECTRONICS (NIM, CAMAC), PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Ph: 505-583-2482, Fax: 505-583-9190, E-Mail: oetech@newmexico.com <http://www.oetech.com>

NEW, USED, and "as is" Radio Shack items. Software, printers, computers, books, parts for R/C cars, etc. Free list. B and B Enterprises, 208 S. Pulaski St., Baltimore, MD 21223. 410-566-5388.


NEW ITEMS: Telephone-coupling transformers for interconnecting data/voice modem terminals to telephone lines meet FCC. Part 68 modular plugs, modular jacks, shielded modular plugs and jacks. SMT jacks with Sof-Lok post, Harmonica jacks, cable ready jacks, compu shield plugs, compu shield jacks, die sets and modular plugs. New products and cable assemblies. Power application tooling and cable tester. Send for schematic and connection diagrams, phone and fax mach. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711-8802.

"FIX ANY PC ... quick!" With the new ICDPOST diagnostic card, fully plug 'n play flash technology. Hoeft-Designs, POB 50054, Reno, NV 89513. 775-334-6935. www.greatbasin.com/~4mtech/post

Digital Storage Oscilloscopes

From \$189?

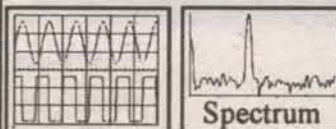ATC modules connect to your PC printer port and transform it into a full-function DSO, spectrum analyzer, logger, & DVM. Units DC to 25MHz



Captured Waveforms
Pico Tech
ADC-200 in
Windows

O-Scope II
in DOS



ATC proudly announces the addition of Pico Technology Ltd. products to our product line. Pico is based in Britain and offers a variety of data logging and virtual instrument modules.

O-Scope Ip (ST 50KHz).....\$189
O-Scope II (DT 500KHz).....\$349
ADC-100 (DT 12bit 50KHz)..... \$449
ADC-200/20 (DT 10MHz)..... **CALL**
ADC-200/50 (DT 25MHz)..... **CALL**
Loggers 1-22 ch. (8-16 bit) from \$99
Shipping UPS \$7.50 grnd, \$11.50 (2 day)

800-980-9806
Allison Technology Corporation
2006 Finney Valley Rd., Rosenberg, TX 77471
Fax: 281-239-8006 Technical: 281-239-8500
E-Mail: atc@accesscomm.net
<http://www.atcweb.com>

SUPERCIRCUITS

America's #1 Microvideo Source

AMAZING!
MICRO VIDEO TOP 10
OVER 120 NEW VIDEO PRODUCTS!

1. World's Smallest Video Camera* 1 lux, 3oz, \$59.95
2. Pinhole Video Camera 410 lines, 0.5 lux, Sharp chip \$39.95
3. Color Video Camera 350 lines, 2 lux, Remote head \$89.95
4. Live Aerial Video R/C Videotape How to & more \$24.95
5. Wireless Covert Tape Cam 300' range, FCC OK \$349.95
6. Super Tiny Color Pinhole 350 lines, less than 1" sq. \$99.95
7. Micro Video Transmitter 1000' range, ATV band \$159.95
8. Complete Wireless ATV Video Set 3 Miles Range \$419.95
9. World's Smallest Wireless Video Cam Please Call
10. Video Goggles Dual hi-res LCD's, 3D capable \$599.95

Buy your microvideo equipment where NASA, The Air Force, JPL, Lawrence Livermore Labs and the FBI does. Call us today.

For the best in high performance microvideo equipment, call the experts at Supercircuits. We've grown to be America's microvideo leader by consistently offering the best equipment at the lowest prices, with unbeatable service...compare our plug 'n play ease of use, warranties and return policies. Of course, Supercircuits microvideo is used by some of the biggest names in science, industry and national defense. But with prices starting at under \$40 for tiny high resolution video cameras, it is technology that is as affordable as it is amazing. Call us today, and get our free 72 page Microvideo Catalog, loaded with photos, specs and more.

1-800-335-9777 ext NV

Or fax us at 512-260-0444
One Supercircuits Plaza Leander, TX 78641
www.supercircuits.com

*Supercircuits PC-21XP and PC-51XS are listed as world's smallest pinhole and spy video cameras

Listed In
Guinness Book
of Records*

FREE FLYER on DBS, cable TV, phones, credit cards, schematics, health items. Bill 1-800-879-9657.

RESISTOR SACRIFICE: 10,000 quarter-watt metal and carbon film. One, two, and five %. 1 ohm to 22 megohms. **FIFTY** each of **TWO HUNDRED** different values. \$45 (less than one-half cent each). Hyatt Surplus, 371 N. Johnson Ave., El Cajon, CA 92020. Tel: 619-444-2434 fax: 619-444-1987.

POWER SUPPLIES, dual regulated, + -12 to 15VDC out, 105-132VAC in. 3-3/16 x 3-5/16 x 5", 3lb. Lambda: LXD-3-152-R. New \$20. Ithanji Ideas, 615-244-4444.

MISCELLANEOUS ELECTRONICS WANTED

WANTED: TUBES, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyneess Company, 709B Delair Road, Cranbury, NJ 08512-4212. Phone: 609-395-1116, FAX 609-395-1117.

WANT USED or surplus DC motor controls or adjustable frequency AC drives, 1/2 HP and up. DC motors fractional to 3 HP. C. Woodruff, 5507 55th Ave. S., Seattle, WA 98118. Voice/Fax 206-723-8487.

RADAR/MICROWAVE equip: Aviation, marine, fire control. Like TPS 21, APS 10, 42 APG 30. Parts, TM's, etc. Radar, Box 10215, Pittsburgh, PA 15232.

WANTED: BALANCING machines & vibration analyzing equipment manufactured by the following: Spectral Dynamics, Hofmann, Bentley Nevada, Schenck, IRD Mechanalysis, Gishott. Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

WESTERN ELECTRIC WANTED: 1920's-1960's. Amplifiers, mixers, preamps, speakers, tubes, etc. **FREE OFFER** 1-800-251-5454.

WANTED: CIRCUIT design for Stun Gun 400,000 volts. Reward \$100. Fax 302-762-5039.

WANTED: AVIONICS test equipment, IFR, 600A, 401L, others, Collins, King, Sperry, North Atlantic, Litton INUs LTN series, rate and tilt tables, air data test sets, 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.



WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL LA PALMA SEMICONDUCTOR, 714-523-8892 FAX 714-523-8898.

HIGHEST PRICES PAID: I will pay the following prices for Western Electric tubes: 211A/D/E new \$300, used \$175; 212A/D/E new \$750, used \$275; 274A/B (engraved base) new \$250, used \$200; 300B (engraved base) used \$550; 422A new \$50, used \$25; 437A new \$50, used \$25; and many more. Also buying Western Electric, and other audio tube and equipment literature. Call or send us your list. Toll free tel/fax: 1-888-715-8823. Don Singerhouse/Singerhouse Sound, LLC, PO Box 321, New Richmond, WI 54017. E-Mail: singtube@frontiernet.net

WANTED: GENRAD 1633A inductance bridge, 1608A amplifier oscillator, 1265A power supply, and 1633-P1 range extension. 610-932-4019.

WANTED: 8749H microcontroller ICs. Must be reprogrammable. Also HP 1630D operator manual, Tektronix T922 service manual. 561-388-3991, fix circ@win.bright.net

Tired of Expensive Inkjet Cartridges ?

Save 90% on Inkjet Inks !

Printer	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP 500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP 600 Series, Officejet 500, 570, 600	7	14	4.71	3.21	32.95	44.95
HP 800 Series, 1000C, 1150C, Copier 120, 210	6	10	6.67	4.00	39.95	39.95
HP 720C, 722C, 890C, 1120C	6	10	6.67	4.50	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple SWriter 1200, 1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	60	60	0.50	0.67	29.95	39.95
Apple StyleWriter 2400, 2500						
Canon BJC-600, 610, 620 Apple SWriter Pro	20	13	1.50	3.07	29.95	39.95
Epson Stylus Color, Color Pro, Pro XL	12	12	2.50	3.33	29.95	39.95
Epson Stylus Color II, IIs	15	15	2.00	2.66	29.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, Photo	20	17	1.50	2.65	29.95	44.95
Lexmark JP 1000, 1020, 1100, ExecJet II, IIC, Medley 4C	10	17	3.00	2.35	29.95	39.95
Lexmark JetPrinter 5700, 5000, 7000, 7200	10	17	4.00	2.35	39.95	39.95
Xerox Home Center 450C, XJ6C Inkjet	22	12	1.36	3.33	29.95	39.95

SAVE 30 - 50% on New Compatible Cartridges!

Printer	BLACK	COLOR
	CARTRIDGE	CARTRIDGE
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	\$5.50	\$12.95
Apple StyleWriter 2400, 2500	\$5.50	\$12.95
Canon BJC-600, 610, 620 Apple StyleWriter Pro	\$4.95 (9cc)	\$4.95 @ (9cc)
Hi-Capacity Canon BJC-600, 610, 620	\$5.95 (15cc)	\$5.95 @ (12cc)
Canon BJC-70, BJC-80	\$9.95 (3-pak)	\$14.95 (3-pak)
Epson Stylus Color, Color Pro, Pro XL	\$12.00	\$19.00
Epson Stylus Color II, IIs	\$14.00	\$19.00
Epson Stylus Color 500, 200	\$14.00	\$19.00
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	\$14.00	\$19.00

- **BULK Inks, Refill Accessories**
- **Glossy card stock & Coated Paper**
- **School & Government PO's Welcome**
- **2 - 3 Day Shipping**

Quality Inks for:
HP • Epson • Lexmark
Canon • Apple • DEC

Call or see us online!

Monday - Friday
7:30 - 4:30 PST 10:30 - 7:30 EST

Inkjet

Southwest



www.inkjetsw.com

(602) 668-7334 Fax

1-800-447-3469

(602) 668-0959

BBS & ONLINE SERVICES

EDUCATION

BUSINESS OPPORTUNITIES



COUNTER-SURVEILLANCE=\$250 HRI
Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For **FREE** catalog call: 1-800-732-5000.

COMPUTER TECHNICIANS needed for Year 2000 compatibility testing in your community. Excellent hourly rate. Software supplied. 319-338-7313, Teamwithus@aol.com

REPAIRS — SERVICES

ENGINEERING CONSULTING. Product development from conceptual to manufacturing stages. Digital, analog, and RF expertise. Microcontroller designs for HC05xx, HC11xx, and PIC families. Software design for IBM PC, XILINX and Altera FPGA design. In-house schematic capture and PWB. Hicks Electronic Design, PO Box 7366, Loveland, CO 80537-0366. Toll Free 1-888-849-6792 E-Mail: steve@hicksengineering.com website: www.hicksengineering.com

PINBALL MACHINES! Books, Magazines, Manuals, Diagrams, Supplies, Parts. \$2 catalog. Marco Specialties, 5290-N Platt Springs Rd., Lexington, SC 29073-9252. 803-957-5500. FAX 803-957-6974. E-Mail: tilt@ix.netcom.com <http://pinballmachine.com>

(E)EPROM PROGRAMMING done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

PC BOARDS REPAIRED. Prices start at \$5. Minimum 5 of one type. Network Sales, 616-683-0500.


CABLE CONVERTER REPAIR: Quality repair service for all name brands. If you're tired of the runaround you're getting from the company you purchased it from, or they're out of business. Give us a call for fast and courteous service. Have model and problem ready. Sorry no box, chip, or IL repairs. **Highview Engineering 815-245-3735** or E-Mail: HIGHENG1@AOL.COM ask for George.

WELD ALUMINUM WITH PROPANE! EZ, INEXPENSIVE, STRONG. DETAILS: WEEKS, 36 CAROLINA ST., TAYLORS, SC 29687. 1-800-547-WELD(9353) FAX 864-244-6349. <http://www.dura-fix.com>

PRINTED CIRCUIT design by professional with 30+ years: conventional, multilayer, downhole, fine line. Prototype and production fabrication. Reverse engineer existing 2-layer board. www.circuit-applied-tech.com call toll free 877-236-3223.

PCB SERVICES: Graphic design from schematic, thru hole and SMT. In-house prototype fabrication, assembly, turn key or kit. Small quantity specialist. In business 16 years. Midland Technologies, 34374 E. Frontage Rd., Bozeman, MT 59715. 1-800-726-8871.

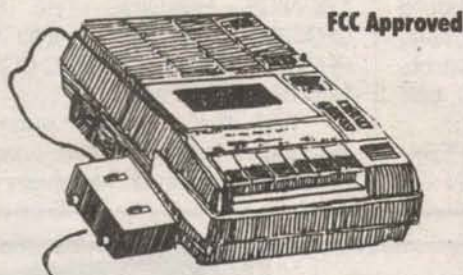TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER



Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.

For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00

Call 407-725-1000

USI CORP

P.O. Box N2052 Melbourne, FL 32902
COD'S OK

Write In 50 on Reader Service Card.

PRINTED CIRCUIT BOARDS

DELIVERY ON TIME WITH QUALITY

- Prototype through production
- UL approved
- Single and double side
- Multilayers
- SMOBC
- LPI mask
- Through hole or SMT
- Nickel & gold plating
- Scoring and routing
- Electrical testing
- Artwork or CAD data
- Quick quotes

**CALL FOR
SPECIAL
OFFERS!**

SKY ELECTRONICS, INC.

10235 PACIFIC AVE., FRANKLIN PARK, IL 60131

PHONE: (847) 671-0786 • FAX: (847) 671-0791

MODEM: (847) 671-0770 • E-MAIL: SKY_EL@yahoo.com

WEB: <http://www.hotyellow98.com/thesky>

Write In 49 on Reader Service Card.

FOR THE BEST PRICES ON PROFESSIONAL TOOLS, CALL ELECTRO-TOOL



platt — Case — Deluxe Polypropylene. Chemical Resistant. Tools by CooperTools and others. 800T Case, complete with tools ... \$419.95
800T Case Only ... \$121.80




platt — Case — Cordura Exterior. Two exterior pockets & one literature pocket. 660ZT Case, complete with tools ... \$223.00
660ZT Case Only ... \$59.45
Optional Sperry meter #DM6510 as shown ... \$65.00



Weller WCC100 — Electronically controlled station, temperature adjustable from 350°F-850°F. Zero voltage circuit-safe for sensitive components, 40 Watt pencil ... \$97.90

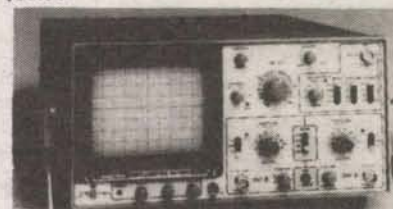OptiVISOR — Superior magnification, Optical Glass Prismatic lenses (not plastic). Select any one of (6) magnifications ... \$24.00



GoldStar — 20 MHz Dual Trace Oscilloscope OS-9020A—Large 6" rectangular, high sensitivity: 1mV/div, high accuracy: ±3%, stable, low-drift design, 8 divisions of displayed dynamic range and accurate, distortion-free waveform measurements ... \$372.00


Electro Tool, Inc.

9103 Gillman, Livonia, MI 48150
Customer Service: (734) 422-1221
ORDERS ONLY: 1 (800) 772-3455
FAX: (734) 422-3432

"Tools American Made."



<http://www.nutsvolts.com>

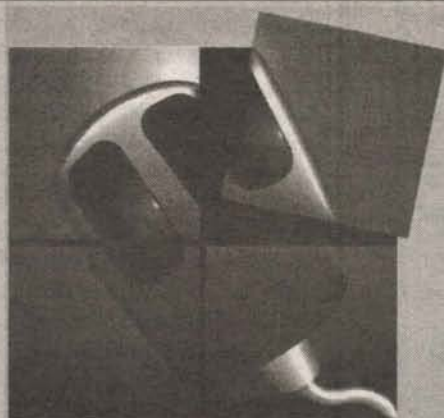

You're just a click away!!

We now have hot links to all our display advertiser's websites so you can find the products you need **fast.**

gram modules" (or something similar).

If Explorer does not give a BSOD, restore your StartUp programs back to the "StartUp" folder one at a time, rebooting after each program is "restored," until Explorer gives the BSOD. Note: The last program you restored in the "StartUp" folder — that's the one causing the problem. It might be corrupted (reinstall it) or it needs an update (go to the web site

of the program author/distributor).

If, after these tests, you still get a BSOD with Explorer, you will have to re-install "the whole smack" of Windows software. If that doesn't solve the problem, your motherboard or expansion card(s) may be at fault. Either a loose IC or a "thermal" problem (i.e., dust accumulation, bad power supply fan) may be at fault.

NOTE: THE FOLLOWING OPERATIONS REQUIRE YOU TO OPEN UP

THE COMPUTER! TAKE APPROPRIATE PRECAUTIONS AGAINST ELECTRICAL SHOCK (turn power off!) AND ELECTROSTATIC DISCHARGE DAMAGE (ESD) TO THE COMPUTER ELECTRONICS. HOLDING THE BARE CHASSIS WITH ONE HAND WILL PROTECT THE ELECTRONIC COMPONENTS FROM ESD!

With the computer open and plugged-in but turned-off, carefully press down on each and every sock-

eted IC on the motherboard and all installed cards, listening for a "crunch" and feeling for chip re-seating in the sockets.

Also examine the CPU to ensure it's securely installed in its socket. Blow out any accumulated DUST that's in the case, on the CPU fan/heatsink, and "clogging" the power supply vent slots. Re-assemble the system and turn it back on. Note whether the power supply fan is operating at this time. If it isn't, replace the supply as soon as possible (or, if you're electronically handy, replace the supply's fan, they're 12VDC, brushless types).

Let the system reboot and play with it awhile. If you're fortunate, your Explorer BSOD problem may be gone. If it's still there, then I can't think of anything else to try short of replacing the motherboard.

Ken Simmons
Auburn, WA

ALL ELECTRONICS CORPORATION

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX
or E-MAIL For A
Free 96 Page
CATALOG.
Outside the U.S.A.
send \$3.00 postage.

Koss Digital STEREO HEADSET

Koss MAC-5
Made for the Ford Motor Company for use in

Windstar and Aerostar Vans. These lightweight, adjustable headsets have great sound quality with great bass response for home or studio use. Supra-Aural foam ear cushions for hear-through sound and comfort. The 8' rubberized cords are terminated. Frequency response: 20-20,000 HZ. 1/4" stereo phone plug.

\$12.50 each CAT # HP-7

3000 MCD ULTRA-BRIGHT RED LED

Everlight # 383URC-2/TR1-C(R) Red, "Ultra-bright" T 1 3/4 LEDs now at our lowest price ever. Due to a special purchase of "tape-and-reel" parts we are able to offer these LEDs at an incredibly low price when purchased on the reel. These are 5 mm diameter water-clear LEDs that light bright red at 20 ma.

CAT# LED-50
2 for \$1.00
100 for \$35.00
1000 for \$250.00
(25¢ each)

S-VHS Tape (Used)

Super VHS tape users! Save a bundle on name-brand S-VHS, T-120 tapes. These tapes were used for a brief period, then bulk erased. The record-protect tabs have been broken out, so you will have to cover the notch with a piece of tape, but they work great and cost a fraction of the "new" price.

CAT #S-VHS **\$3.00 each**
10 for \$28.00 • 100 for \$250.00

30 Minute Timer Board

Timer circuit board will operate 120 or 240 Vac devices. Originally designed to run a vibrating motor in a massage chair, the circuit automatically shuts-off a motor, lamp or other device after approximately 30 minutes. Shut-off time can be varied by replacing one of the resistors on the board with a pot or resistor of different value. Hook-up instructions included with the board explain how to make this modification. 1.9" x 2.5".

CAT# TMR-5 **\$3.50 each**

10 CD Storage Book

Small padded, refillable binder contains plastic sleeves for protection and storage of 10 CDs. Great for music or computer software. Inside cover has an index page for referencing contents. Velcro flap keeps binder closed in transit. Ideal for car or home. 6.5" x 5.8" x 1.2".

CAT# CDB-1425 **\$4.25 each**

10 for \$37.50 100 for \$300.00

INCREDIBLY CHEAP!! Switching Power Supply

Voltek Corp # SPEC7188B
Input: 100 - 240 Vac
Outputs: +5 Vdc @ 3.70 A,
+12 Vdc @ 0.60 A,
-5 Vdc @ 0.05 A,
+5 Vdc Trickle @ 0.1 A
Metal encased switching supply. Standard three-prong IEC socket power input. 7 conductor, Molex-type connector output. 9" x 2.1" x 1.36". UL recognized. Removed from new equipment.

CAT # PS-27 **\$3.50 each**

20 Character X 4 Line LCD

Optrix # DMC 20434-CEM (PWB 20434-CEM)
5 x 8 dot format.
3" x 1" viewing area.
3.88" x 2.38" module.
Removed from new equipment. May have felt padding on metal bezel. 14 pin single row header is pre-attached. Spec/hook-up sheet included.

CAT# LCD-46 **\$7.00 each**
10 for \$60.00

3 BUTTON Serial MOUSE

Windows compatible three button serial mouse. Includes 3.5" floppy disk with drivers.

\$3.50 each

CAT #MSE-3

10 for \$30.00

100 Meg IDE Hard Drive

Assorted Brands
100 to 120 MB IDE hard drive.
Removed from working equipment.
5.77" x 4.02" x 1".



CAT #HD-100U **\$9.50 each**
10 for \$80.00

"Hi-8" Video Cassette

SONY HI-8 Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box.



CAT # VCU-8 **\$3.00 each**
10 for \$28.00 • 100 for \$250.00

ORDER TOLL FREE

1-800-826-5432

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
INTERNET <http://www.allcorp.com/>
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

ANSWER TO #29911 - FEB. 1999

Amperite Co., Inc., 600 Palisade Ave., Union City, NJ 07087, telephone 1-800-752-2329, makes the relay you are seeking. It is their VPR series voltage protection relay.

For the specified voltage window, their part number is 120A100-130VPR.

This is a double pole double throw relay that plugs into a standard octal socket and it will close only when the input voltage is between 100 and 130 volts. If the voltage falls out of that window, the relay opens. The relay can also be special ordered with the required 100-second delay.

Alternatively, a standard DPDT time delay relay, also supplied by Amperite, can be connected to the VPR relay to provide the 100-second delay.

The voltage protection relay is available with any desired custom voltage window. Amperite parts can be ordered from such suppliers as Newark Electronics and Allied Electronics.

A. Caristi
Waldwick, NJ

ANSWER TO #29912 - FEB. 1999

A simple IR repeater circuit can be built with an inexpensive IR receiver module such as RadioShack part #276-0137, a 555 timer, an IR LED attached to a short two-wire cable, and several "glue" components.

The basic idea behind such a repeater circuit, is that the IR module receives the IR signal from the remote, which is riding on a 40KHz carrier. The IR module removes the carrier and sends the signal to the 555, which is set up as a 40KHz oscillator. The output from the 555 is then fed to the base of a transistor which is used to drive the IR LED attached to the end of the cable.

Assuming you have access to the Internet, a repeater circuit which

TECH FORUM

makes use of these parts is shown at <http://www.nysaes.cornell.edu/cc/staff/pool/electronics/irrepeat.htm>. (Just scroll down about half-way on the page to see the diagram.)

If you need more distance, you might want to look into the IR repeater sold by RadioShack, catalog #15-1959. This device uses RF rather than a cable to send the signal to the remote IR emitter. At around \$50.00, it's much more expensive than the do-it-yourself approach, but it might be worth it if the extended range (up to 100') is an issue.

Mark Winters
Drem, UT

ANSWERS TO #3993 - MAR. 1999

The website you're looking for is <http://www.dzn.com/w5es/electro.htm>

The "ElectraSlide Antenna" is based on an original design by Don Johnson W6AAQ, called the DK3. Some additional contact information:

Clay Emert K5TRW
cemert@dzn.com
2100 San Diego Ave.
El Paso, TX 79930
915-859-5502

Mike Nalbene
Trenton, NJ

ANSWERS TO #3993 - MAR. 1999

I have used a screwdriver antenna for about two years now. You can contact the manufacturer at T.J. Antenna Co./Nott Ltd., 3801-4001 La Plata Hwy., Farmington, NM 87401; 1-800-443-0966, E-Mail: judy@tjantenna.com. They call it the "Broadband BB3."

As for the operation, I would be happy to answer any questions about its operation via E-Mail.

Charlie E. Zalenski
via Internet

ANSWER TO #3996 - MAR. 1999


A "Non-Polarized Electrolytic" capacitor is just what it says: an electrolytic capacitor WITH NO POLARITY! Their "plates" are made in the same way as "regular" electrolytics except when they're put together, they are usually constructed with two "positive" plates.

Their use is typically in AC motors as "starting" capacitors, and other high-voltage "AC-intensive" applications.

If you cannot find an "exact" replacement NPO, or can find one with the right capacitance but not rated high enough (i.e., 200V instead of 300V), you can make your own NPOs using two regular high-voltage electrolytics wired IN SERIES, joining both NEGATIVE (-) leads together.

In other words, to create a 5uF, 300V (or higher voltage: you can always use a larger voltage cap as a substitute!) NPO, simply join a pair of 10uF 150V (or higher voltage) in series. (Remember: capacitance decreases in series circuits and work-

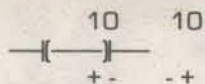ing voltage increases — just add-up the individual cap voltages) like this:



Carefully insulate the joined leads and you have an "instant" non-polarized electrolytic.

For a source of NPOs, I would try Digi-Key Electronics www.digikey.com

or MCM Electronics www.mcmelectronics.com. Even if you can't find the NPOs, these firms do carry high-voltage electrolytics that you can make into "NPOs."

Ken Simmons
Auburn, WA

ANSWER TO #12985 - DEC. 1998

The TCM3105 Bell 202 modem IC is available from JDR Microdevices, 1850 S. 10th St., San

Jose, CA 95112-4018. They can be reached at 1-800-538-5000 [orders] or at www.jdr.com

In catalog #67C, it was priced at \$14.99 each in quantities of under 25 pieces.

It was also listed in a recent flyer from Debco Electronics, Inc., 4025 Edwards Rd., Cincinnati, OH 45209 for \$11.99 each. They can be reached at 1-800-423-4499

Continued on page 71



LEVITRON

"The Amazing Anti-Gravity Top"

This spinning top floats in mid air, supported by opposing magnetic forces. Includes floating top, levitron magnetic base, assortment of adjustment weights, lifter plate, levelling shims, and instructions. It takes some practice and a lot of patience to keep the top afloat, but the results are truly amazing! Levitron Floating Top \$39.95

mini keyboard

\$10.00

A very small computer keyboard (measures less than 5-3/4" x 9-3/4") that takes up minimal desk space. Uses a PS2 connector, and keyboard enclosure is black. Great for applications requiring a complete keyboard in a limited space, and an ideal solution for those wanting something lightweight and compact for transporting.

Great for home or work applications!



optional keyboard adapter:
PS2 to 5 pin DIN \$3.95



Solar Panel
12v 100mA
\$19.95

Perfect for charging batteries, powering projects, light-duty emergency back-up, and other solar fun applications. These panels are framed and feature red and black alligator clip leads for easy attachment of most applications. approximate dimensions: 5.5" x 12.25" x 0.75"

PHOTON II MICROLIGHT

The popular photon microlight has been improved. These super-bright (better than 8 candellas!) LED lights are visible over a mile away. The LED is secured in a tough ABS case and offers a squeeze button for quick use, and a constant on slide switch for prolonged lighting needs. The lithium batteries last a very long time (10 year shelf life!) and are included. The light won't burn out because it is an LED! Specify your choice of five incredible bright colors. Great for home or office use, popular with fire and rescue professionals, pyrotechnicians, stage performers, and dimly lit restaurant patrons. PHOTON II microlights include a keyring and come in ruby red (\$13.50), amber yellow (\$13.50), orange (\$13.50), sapphire blue (\$17.50), turquoise (\$17.50), diamond white (\$17.50), and emerald green (\$17.50). Includes two replaceable 2016 lithium batteries.



127 THERMOCOUPLES PELTIER JUNCTIONS

The peltier junction is a solid-state thermoelectric device. Current applied to the device will produce heat on one side of the device and a cold surface on the other side.

Water placed on the surface will freeze or boil depending on polarity of applied voltage.

Ideal for applications from 3-12 VDC -- grab a battery and let your imagination run wild!

DOCUMENTATION INCLUDED!!!

Small Peltier Junction \$20.00 (approximately 1.17"x1.17"x.12")
Large Peltier Junction \$29.50 (approximately 1.56"x1.56"x.15")



8123 PAGE BLVD. * ST. LOUIS, MO 63130 * (314)427-6116
9222 CHESAPEAKE DR. * SAN DIEGO, CA 92123 * (619)279-6802
2525 FEDERAL BLVD. * DENVER, CO 80211 * (303)458-5444
MAIL ORDERS CALL TOLL-FREE 1-800-669-5810
FAX ORDERS (314)427-3147

Geophone vibration sensing kit

Detect a fly stomping across the desk! Well maybe not that sensitive, but almost.

These vibration sensors made by Geosensor® were used in oil exploration to determine geological statistics. They are made with a magnet suspended in a coil and are very sensitive to vibration. Compact size, the unit measures approx. 1.6" high and 1.2" dia. The kit includes a geophone vibration sensor along with parts to build a basic detector that will light an LED. In addition we include a schematic that will show you how to operate a relay. The sensitivity is adjustable, so you can set it to detect elephants and other small creatures. Similar units were used by our armed forces to detect enemy troop movements...the perfect device to alert you to the pitter patter of little Leroy's feet! Unit sensitivity can be set high enough to detect a business card dropped on a table, and we've made it work with vibrations up to 40 feet away! Earthquake or Aunt Agatha...you decide! It's a fun gadget with many uses. COMPLETE GEOSENSOR KIT.....\$ 9.95

GEOSENSOR UNIT ONLY.....\$7.95



Power Up

Wireless Antenna Booster

A small square circuit (approx 1.5" x 1.5") that affixes to the back of your analog or digital cellular phone. It works with a patented design and white gold properties...This is not a miracle device, if the service is not there, this unit won't help. But, it does help reduce unwanted noise, dropped calls, and interference that may be experienced in office buildings, cars, parking structures, and weak electrical fields. Power Up may not be effective in some rural areas. \$19.95


VOICE CHANGER KIT

Change your voice with this really cool kit! Using DSP (Digital Signal Processing), you can make a man sound like a woman, make a woman sound like a man, create scary monster sounds (just in time for halloween!), and have lots of fun. Use the special echo and vibrato modes for additional special effects. Kit features clip-on electret mic, removable speaker with metal case, sound effects selector switch, adjustable volume control, up/down pitch shifts, and step-by-step instructions. 3.5mm jacks for the microphone and speaker make it easy to connect to other audio equipment. Requires 4 AA batteries (not included.) \$49.50

TV TRANSMITTER KIT \$27.95

Tired of logging the VCR to another room to see a movie while Aunt Martha watches reruns of the Julia Child special on PBS? Sick of stringing wires through the house so Junior can watch the latest Power Ranger movie in the comfort of his room? Never fear, we've got the solution! This kit allows you to send any audio and video source, like a VCR or TV camera, to any TV set for up to 300 feet. With this little kit, you're the producer and the programming director of your own TV station. Tunable to any TV channel 2-6, runs on 12 VDC, and accepts standard audio and video signals. Optional matching case set, \$14.95

THE FINE PRINT: PRICES SUBJECT TO CHANGE WITHOUT NOTICE * GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS * MASTERCARD, VISA AND DISCOVER ACCEPTED * YES, WE'LL TAKE YOUR CHECK -- SORRY, NO C.O.D.s * \$10 MERCHANDISE MINIMUM ON MAIL ORDERS * SUPPLY OF SOME ITEMS IS LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. IF KNEES WERE BACKWARDS, WHAT WOULD CHAIRS LOOK LIKE?

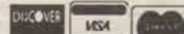

Events

CALENDAR

APRIL 1999

APRIL 2-3

OK - MOORELAND - Hamfest. Tri-State AR Group, Duane Henderson KC5NID, 580-994-2223. E-Mail: kc5nid@pdl.net

APRIL 2-3-4

GA - AUGUSTA - Hamfest. Radisson Hotel & Conference Center, 2 10th St. Garden City Channel Masters CB Club, Inc., Moses 706-793-7828

APRIL 3

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

CO - LONGMONT - Hamfest. Longmont ARC, Fred Pilz KB0JUD, 303-817-5526. Web: <http://www.qsl.net/larc>

APRIL 9-10

GA - ATLANTA - Southeastern VHF Conference. Southeastern VHF Society, Dick Hanson K5AND, 770-844-7002. E-Mail: k5and@prestique.net Web: <http://www.svhfs.org.svhfs>

APRIL 9-10-11

CA - FRESNO - Int'l DX Convention. Gordon Gorton W6NW. E-Mail: gordon@svpa.org E-Mail: w6nw@amateur-radio.org Web: <http://www.amateur-radio.org/ncdxc.org>

APRIL 10

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

MN - ROCHESTER - Hamfest. Rochester ARC, John Scott N0HZN, 507-285-6522. E-Mail: n0hzn@aol.com

Web: <http://members.aol.com/rarchams/>

NC - MORGANTON - Hamfest & Computer Fair. Burke County Fairgrounds, Hwy. 181N (Exit 100 Eastbound, Exit 105 Westbound I-40). 8am-5pm. Talk-in: 147.15 (KAVLY repeater). Catawba Valley, Tom Taylor, 704-433-6205. E-Mail: kc4qpr@vistatech.net

NH - TWIN MOUNTAIN - Hamfest. Town Hall. 8am-2pm. VE Exams. Talk-in: 147.345. North Country ARC and LARK, Richard Force WB1ASL, 603-788-4428. E-Mail: bhabooks@together.net

TX - BRENHAM - Hamfest. Brenham ARC, Dan N5JUN, 409-836-8739. Bob KA5BOB, E-Mail: angdenis@tca.net

WA - SPOKANE - Hamfest. Spokane Community College, 1810 N. Greene St. 9am-5pm. VE Exams. Talk-in: 146.52 simplex, 147.32 repeater. Lilac City ARC, Warren Kelsey KJ7BB, 509-534-8443

APRIL 11

CT - BRISTOL - Hamfest. Insurance City Repeater Club, Jack McLaughlin WK1S, 860-621-6623. E-Mail: wk1s@aol.com Web: <http://www.connix.com/~pcb/icrc-file.htm>

IA - DELOIT - Hamfest. Denison Repeater Association, John Amdor III KD6MXL, 712-388-8042. E-Mail: johnmxl@radix.net Web: <http://www.radix.net/~johnmxl/deloit.html>

MA - FRAMINGHAM - Hamfest. Framingham ARA, Beverly Lees N1LOO, 508-626-2012

NC - RALEIGH - RARSfest. State Fairgrounds, Jim Graham Bldg. 8am-4pm. Raleigh ARS, Wilbur Goss WD4RDT, 919-266-9883. E-Mail: k4hf@juno.com

NY - MONTGOMERY - Hamfest. Valley Central High School, 1175 St. Rt. 17K. 8am-2pm. VE Exams. Talk-in: 146.160 in, 147.760 out 100 Hz PL tone. Orange County ARC, Edward J. Moskowicz N2XJI, 914-534-3492 eves. E-Mail: n2xji@banet.net

WI - MADISON - Hamfest. Madison Area Repeater Assn., Paul Toussaint N9VWH, 608-245-8890. E-Mail: n9vwh@hotmail.com

APRIL 17

AL - ALBERTVILLE - Hamfest. Marshall County ARC, Buddy Smith KC4URL, 256-593-2516. E-Mail: kc4url@airnet.net

AZ - PHOENIX - Hamfest. Arizona ARC, George Cooney KQ7C, 602-274-6212. E-Mail: george@aztec.asu.edu

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

Web: <http://www.srv.net/~w4vrv/hamfest.htm>

CANADA - TORONTO - Durham Region Hamfest. Ian Smith VE3ITG, 905-427-4873. E-Mail: ve3itg@rac.ca

Web: <http://www.globalserve.net/~ismith>

FL - MIAMI - Hamfest. Flamingo, Univ. of Miami ARC UM Campus, Physics Parking Lot. Talk-in: 146.865 (-). Walt W4DWN, 305-895-0398

56 April 1999/Nuts & Volts Magazine

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

Nuts & Volts Magazine

Events Calendar

430 Princland Court

Corona, CA 91719

Phone 909-371-8497

Fax 909-371-3052

E-mail events@nutsvolts.com

COMPUTER SHOWS

AGI Shows, 317-299-8827.

E-Mail: info@agishows.com

<http://www.agishows.com>

Blue Star Productions

612-788-1901

<http://www.supercomputersale.com>

Computers And You, 734-283-1754.

www.al-supercomputersales.com

Computer Central Shows

847-412-1900 & 1-888-296-6066.

E-Mail: compcent@magsinet.net

www.computercentralshows.com

Five Star Productions

810-890-0988 E-Mail: jeff@fivestar

www.fivestars.com

Georgia Mountain Productions

706-838-4827.

E-Mail: gamtpro@blrg.tds.net

www.georgiamountain.com

Gibraltar Trade Center, Inc.

734-287-2000. Taylor, MI.

Gibraltar Trade Center, Inc.
810-465-6440. Mt. Clemens, MI.

KGP Productions

1-800-631-0062, 732-297-2526.

E-Mail: kgp@mail.com

MarketPro, Inc., 201-825-2229

<http://www.marketpro.com>

MarketPro, Inc., 301-984-0880.

E-Mail: md@marketpro.com

<http://marketpro.com>

Narisaam Computer Show

770-663-0983.

E-Mail: narisaam@aol.com

Web: <http://www.showsale.com>

Northern Computer Shows

978-744-8440

E-Mail: inquiries@ncshows.com

Web: ncshows.com

Peter Trapp Computer Shows, 603-

272-5008. Web: www.petertrapp.com

Web: <http://www.seorf.ohiou.edu/~xx017/hamfest.html>

OH - CANFIELD - Hamfest. Twenty Over Nine RC, Don Stoddard N8LNE, 330-793-7072

APRIL 30-May 1

LA - BATON ROUGE - LA Section Convention. Baton Rouge ARC, Herb Ramey W5LSU, 504-654-6087. E-Mail: daveramey@worldnet.att.net Web: <http://www.brarc.org>

MAY 1999

MAY 1

AL - MOULTON - Hamfest. Bankhead ARC, Rex Free KN4CI, 256-905-0822. Ed Weatherford K4EKW, 256-974-0436.

Web: <http://www.symmetric-inc.com/N4IDX>

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

CANADA - ONTARIO - OTTAWA - Hamfest.

John Barnhardt VE3ZOV, 613-521-8910

CO - MONUMENT - Hamfest. Pikes Peak RAA,

Robert Ryals K1QGF, 719-265-9950. E-Mail:

rryals@pcisys.net Web:

<http://www.qsl.net/ppraa/swapfest.html>

KY - FALLSBURG - Hamfest. Big Sandy ARC,

Fred Jones WA4SWF, 606-638-9049

MD - GRAYSONVILLE - Hamfest. Kent Island &

Anne Arundel ARCs, Tony Young WA3YLO, 301-

262-1917. E-Mail: tony@juno.com Web:

<http://home.att.net/~n3szw/aarc.html>

MI - CADILLAC - Swapmeet. Cadillac Middle

School. 8am-1pm. VE Exams. Talk-in: 146.98.

Wexauke ARC, Dan KE8KU, 616-775-0998.

E-Mail: ke8kudan@juno.com

SC - WINDSOR - Hamfest. Salkehatchie ARS, Bill

Chapman N3WCM, 803-641-0666

TN - NASHVILLE - Hamfest. Vaughn Bldg., TN

State Fairgrounds. Nashville ARC, Bob Malone

WB5ZDS, 615-865-6225. E-Mail:

WB5ZDS@juno.com

WI - CEDARBURG - Hamfest. Ozaukee RC, Joe

Holly AA9HR, 414-377-2137. E-Mail:

561-641-8244

NJ - HARMONY - Hamfest. Warren County Farmers Fairgrounds, Rt. 519 N. 8am-2pm. VE Exams. Talk-in: 147.375+ 146.730. Cherryville RA II, Inc., Randy Vance N2MQZ, 908-788-4080 or 908-454-4370. E-Mail: n2mqz@aol.com Web: <mailto://w2cra@qsl.net>

NM - ALBUQUERQUE - Hamfest. Albuquerque ARC & AR Caravan Club, Chuck Opdyke KC5GA, 505-858-0306. E-Mail: n5oqi@worldnet.att.net

VA - CHESAPEAKE - Hamfest. Chesapeake AR Service, Jim Cannon KF4RQQ, 757-382-0193. Web: <http://www.qsl.net/cars>

WA - VANCOUVER - Hamfest. Salmon Creek American Legion Post 176. 8am-2pm. VE Exams. Clark County ARC, Luther Brisky KC7KVL, 360-896-8909 or 360-254-5082. E-Mail: lwayne@e-z.net Web: <http://www.w7aia.org>

APRIL 25

DE - NEW CASTLE - State Convention. Nur Temple, Rt. 13 N. 9am-2pm. VE Exams. Talk-in: 147.225+ or 224.220/R. Penn-Del ARC, Hal Frantz KA3TWG, 302-793-1080. E-Mail: hfrantz@snip.net Web: <http://www.magpage.com/pennndel>

FL - GAINESVILLE - Hamfest. Gainesville ARS, H. Walter Johnston W4TKE. E-Mail: w4tke@juno.com E-Mail: w4tke@gator.net

IL - ARTHUR - Hamfest. Moultrie/Douglas County Fairgrounds. 8am-1pm. Talk-in: 146.055/146.655 & 449.275/444.275. Moultrie ARK, Ralph Zancha WC9V, 217-873-5287 or 217-543-2178. E-Mail: rzancha@one-eleven.net Web: <http://home.stinet.com/~jhudson/hamfest.html>

IL - GALVA - Hamfest. National Guard Armory. 8am-2pm. VE Exams. Talk-in: 145.4900 88.5 PL, 146.460 simplex. AARO, Bill Anderson WB9TEW, 309-932-3023. E-Mail: bill@inw.net

NY - Poughkeepsie - Convention. Mt. Beacon ARC, Ken Akasofu KL7JQC, 914-485-9617. E-Mail: k7jrc@iname.com Web: <http://www.mhv.net/~fritzing>

OH - ATHENS - Hamfest. City Recreation Center. 8am-3pm. Talk-in: 145.15 MHz (-600 offset). Athens County ARA, Drew McDaniel W8MHV, 740-592-2106. E-Mail: dmcDaniell@ohiou.edu

ID - IDAHO FALLS - Hamfest. Elks Lodge, 640 E. Elva St. VE Exams. Talk-in: 443.00 MHz + QHF, 147.15 MHz + VHF. Eastern Idaho UHF Society, Jay Greenburg WA4VRV, 208-524-1388. E-Mail: w4vrv@srv.net

KY - MURRAY - Hamfest. Murray State University ARC, Pat Compton KF4FMZ, 502-762-6433. E-Mail: patrick.compton@murraystate.edu Web: <http://mursuky.edu/clubs/msuarc/hamfest.htm>

MN - BLAINE - Hamfest. National Sports Center, 35W, Exit #32. 7:30am-3pm. Jerry Dorf N0FWG, or Harriet Johanson 612-537-1722. E-Mail: jerryd@skypoint.com

MO - JOPLIN - Hamfest. Joplin ARC, Ray Brown KB0STN, 417-781-4967. E-Mail: raybrown@ipa.net Web: <http://www.joplin-arc.org>

OK - LAWTON - Hamfest. Lawton Ft. Sill ARC, Bob Morford KA5YED, 580-355-6120 or 580-353-8074

TN - DAYTON - Hamfest. Rhea County ARS, Bob Jordan KN4VY, 423-775-3225. E-Mail: kn4vy@volstate.net Web: <http://webcube.volstate.net/~ko4sy/>

TX - BELTON - Hamfest. Bell County Expo Center. Talk-in: 146.820, PL 123.0. Temple ARC, Mike LeFan WA5EQQ, 254-773-3590. E-Mail: hamexpo@tarc.org Web: <http://www.tarc.org>

APRIL 18

CT - HARTFORD - 1999 Trinity College Fire-Fighting Home Robot Contest. Trinity College campus. Jake Mendelsohn, 190 Mohegan Dr., West Hartford, CT 06117. E-Mail: JMENDEL141@AOL.COM Web: <http://www.trincoll.edu/~robot>

MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: <http://web.mit.edu/w1mx/www/swapfest.html>

MN - SHAKOPEE - Hamfest. Canterbury Park. 12pm-5pm. VE Exams. Talk-in: 147.165+.

SMARTS, Helen Haynes WBOHOX, 612-556-0077. E-Mail: smarts@maven.mn.org Web: http://www.wavefront.com/~tim_fogarty/

PA - MONROEVILLE - Hamfest. Two Rivers ARC, Michael Kowalcheck, Jr. KV3L, 412-751-9657. E-Mail: w3oc@nb.net

APRIL 23-24

AR - LITTLE ROCK - Hamfest. Expo Center, Exit 126, I-30 SW. Fri: 4pm-9pm, Sat: 8am-4pm. Jim Blackmon K5VZ, 870-246-7833 H, 870-246-6734 W. E-Mail: lrhamfest@usa.net Web: <http://www.aristotle.net/~ares/hamfest/>

FL - GAINESVILLE - Hamfest. Alachua County Fairgrounds, SR 222. VE Exams. Talk-in: 146.820. Steve King KC6WCH, 352-375-8023 eves. only. E-Mail: gars@afn.org

APRIL 24

AR - BENTONVILLE - Hamfest. Benton County Radio Operators, Betty Weiberg N0XWQ, 417-435-2332

CA - ARMONA - Hamfest. Hanford Fraternal Hall, 10th Ave. @ Florida. Talk-in: 145.11, 147.33, 224.44 or 441.900. The Kings ARC, Rick WB6VFZ, 209-945-2266. Doug KC6BGQ, 209-582-0949 or 209-584-5414

CA - SONOMA - Hamfest. Sonoma Valley Veteran's Memorial Bldg., 126 1st St. W. 8am-12pm. VE Exams. Talk-in: 145.35, -600 PL 88.5. VOMARC, Darrell Jones WD6BOR, 707-996-4494

IA - DES MOINES - Hamfest. Des Moines RAA, Duane Bower WB0UCV, 515-287-6542

FL - LANTANA - Flea Market. Next to Pizza Hut, 6170 S. Congress Ave. 7am-12pm. Talk-in: 146.67. The Major Armstrong FM Assn., Jeff Beals WA4AW, 561-586-5120. Al West W4SDC,

LASERS & ACCESSORIES

HELIUM NEON LASERS

- Complete Systems
- Plasma Tubes
- Power Supplies

ACCESSORIES

- Optics
- Electro-Optics
- IR Viewers
- Books & More



MEREDITH
INSTRUMENTS

Phone: 602-934-9387 • Fax: 602-934-9482

DIODE LASERS

- Visible / IR
- Complete Modules
- Collimating Optics
- Drive Circuits

FREE CATALOG

WEB SITE:
www.mi-lasers.com

Write in 111 on Reader Service Card.

Events CALENDAR

aa9hr@execpc.com

WI - SUPERIOR - Hamfest. Arrowhead RAC, Jeff Daniels N0VQF, 218-485-8131

MAY 1-2

AL - BIRMINGHAM - Convention. Zamora Temple, off I-459 E. Birmingham ARC, Glenn Glass, 205-681-5019. Dan Morgan KB4MDI, 205-822-5242, E-Mail: kb4mdi@scott.net Web: <http://bro.net/barc/fest.html>

IL - ELGIN - CoCoFest. Elgin Plaza Hotel, 345 W. River Rd. The Glenside Color Computer Club, Tony Podraza, 847-428-3576.

E-Mail: tonypodraza@juno.com

Web: <http://members.aol.com/clubbbs/glenside>

NJ - EDISON - Trenton Computer Festival. NJ Convention Center, Raritan Center. Sat: 9am-5pm, Sun: 9am-4pm. KGP Productions, Inc., Marin Light, 1-800-631-0062. E-Mail: kgp@mail.com

Web: www.tcf-nj.org
TX - ABILENE - West Texas Section Convention. Key City ARC, Peggy Richard KA4UPA, 915-672-8889. E-Mail: jlmr@swconnect.net Web: <http://www.westex.net/kcarc/hamfest.html>

MAY 2

IL - DECATUR - Hamfest. Cenois ARC, Tracy Ruble N9VIM, 217-423-0314. E-Mail: n9vim@springnet1.com

IL - SANDWICH - Hamfest. Kishwaukee ARC, Bob Yurs W9ICU, 815-895-3219. E-Mail: w9icu@tbcnet.com Web: <http://tbcnet.com/~jleopard/hamfest.htm>

HAGERSTOWN - Hamfest. Community College, Athletic and Recreation Bldg. 8am-3pm. Talk-in: 147.090+. The Antietam Radio Assn., Tina Jones KB8ZQM, 304-728-7769.

E-Mail: kb8zqm@intrepid.net

Web: <http://www.erols.com/rjlong61/ara>

NY - YONKERS - Flea Market. Lincoln High School, Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network, Otto Supliski WB2SLQ, 914-969-1053

PA - WRIGHTSTOWN - Hamfest. Warminster ARC, Tony Simek N3YNH, 215-674-5218. E-Mail: tsimek@aol.com

WV - RIPLEY - Hamfest. Jackson County ARC, Gary Casto AG8RY, 304-372-2849

MAY 7-8

NH - ROCHESTER - Hamfest. Hosstraders, Joe Demaso K1RQG, 207-659-3492

MAY 8

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

KY - DAWSON SPRINGS - Hamfest. Curt Beshear KE4UZE, 502-797-9117. E-Mail: ke4uze@juno.com

OK - MCALISTER - Lake Eufaula Hamfest. John Petersen KM5ES, 918-452-2279. E-Mail: km5es@cwis.net

SC - ANDERSON - Hamfest. Anderson County Fairgrounds, Hwy. 29 Business. Talk-in: 146.610. Blue Ridge ARS, Robert G. Watson W4RGW, E-Mail: w4rgw@backroads.net

Web: <http://www.brars.org>
TX - CHICOTA - Hamfest. Red River Valley ARC & ARES of Lamar County, Kevin "Mort" Winslow N3YNL, 214-894-3088.

E-Mail: 4n3ynl@uniconp.net
WI - MANITOWOC - Hamfest. County Expo Center, County Hwy. R. 8am-12pm. VE Exams. Talk-in: 146.01/61. Mancorad RC, Red 920-684-3733, Fred 920-682-9312

MAY 10

MA - GREENFIELD - Hamfest. Franklin County ARC, Richard Strycharz KD1XP, 413-665-2211. E-Mail: kd1xp@arrl.net

MAY 14-15-16

OH - DAYTON - Hamfest. Dayton ARA, Dick Miller N8CBU, 937-427-3109. E-Mail: chair@hamvention.org

Web: <http://www.hamvention.org>

MAY 15

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-In, 619-561-0052

CANADA - ONTARIO - ETOBICOKE - Hamfest. Skywide ARC, Murray Smith VA3KTL, 416-621-1233. E-Mail: murray.smith3@sympatico.ca

GA - STATESBORO - Hamfest. Statesboro ARS, Martin Holzman WB4MOG, 912-764-5959. E-Mail: mart@bulloch.com Web: <http://www.cs.gasou.edu/stars/>

ID - CALDWELL - Hamfest. Snake River ARC, Don Ingram KB7UKP, 208-459-2459. E-Mail: ingramde@cyberhighway.net

NC - GREENVILLE - Hamfest. East Carolina Antique Radio Club, Herman Schnur K4CTG, 252-752-2264

TN - CLARKSVILLE - Hamfest. Clarksville Amateur Transmitting Society, Hank Koebler N3ORX, 931-645-5206. E-Mail: n3orx@arrl.net

Continued on page 86

BLOWOUT SPECIALS

SUPER SAVING UPGRADE KIT

MBOARDS WITH CPU, 8MB AGP & SOUND:

K6-2 300 MHz MMX	\$199
K6-2 333 MHz MMX	\$229
K6-2 350 MHz MMX	\$249
Pentium II Celeron 300 w 128Kcache	\$199
Pentium II Celeron 333 w 128Kcache	\$219
Pentium II 333 MMX	\$289
Pentium II 350 MMX	\$299
Pentium II 400 MMX	\$445
Pentium II 450 MMX	\$675

CASES WITH POWER SUPPLIES

MED TOWER CASE PREMIUM.....	\$29
ATX MED TOWER CASE PREMI.....	\$49



40X CDROM...\$49

Orders & Price

Tel: (800) 899 6430

36X Bundle

\$69

36X Speed CD

16 Bit Sound Card

with Wavetable.

Amplified Speakers 80W

For ALL kinds of Drives, Sound Cards

Speakers and CD Titles: \$Call

HARD DRIVES SPECIALS

4.3GB..\$136	6.4GB..\$155	8.4GB..\$185	10GB..\$219
13.5GB..\$245	16GB..\$375	21GB..\$555	any other CAL

IBM 6X86

333 MMX

Motherboard
CPU, 8MB AGP
VGA & SOUND

\$199

Simm Memory

LOW \$\$\$

Will beat any price

Resellers

Dealers

Welcome

AMD K6-2

350 MMX

Motherboard
CPU, 8MB AGP
VGA & SOUND

\$249

All Systems carry

3 years Parts &

5 years Labor

Warranty.

Lifetime Tech

Support

CREDIT CARDS OK

Govt.P.O. C.C.O.D.

us out

No Minimum Charge No Hidden Charge.

Prices subject to change without notice.

15% Restocking fee for Non Defective Items.

Orders of \$950 or more, ground shipping free,

except for Cases, Monitors, Keyboards and FDrives.

EVERYDAY LOW PRICES

www.bisme.com

BISME COMPUTERS OUTLET 906 N Carpenter Rd, Suite A, Modesto, CA 95351

Write in 112 on Reader Service Card.

ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT



DMM

DMM-899 (\$179.00): true rms, AC/DC (V,A), Ω , bar graph, freq, capac, dBm, logic, diode
DMM-23T (\$99.95): 4 1/2 digit, true rms, high resol. (10uV, 10nA, 10m Ω), hFE, diode, contin.
DMM-20 (\$74.95): AC/DC (V,A), Freq, cont., Capac, Induct, Ω , hFE, diode, duty cycle
DMM-122 (\$59.95): DC/AC (V,A), Ω , hFE, diode, capacitance, freq, logic, continuity
DMM-123 (\$44.95): DMM + capacitance, DC/AC (V,A), Ω , hFE, diode, continuity
DMM-10 (\$19.95): 3 1/2 digit, DC/AC V, Ω , hFE, diode, signal output (+3V, -0.5Vsq, 50% duty)



Single Output DC Power Supplies

- Constant current, constant voltage mode
- Short Circuit and overload protected

Triple Output

- Independence or Tracking operation
- Parallel to double current output (PS-8102 & PS-8103 only)

DC POWER SUPPLIES

- PS-303 (\$159.00) 30V/3A
- PS-305 (\$219.95) 30V/5A
- PS-8102 (\$399.95) 30V/3A/30V/3A
- PS-8103 (\$489.95) 30V/5A/30V/5A
- PS-1610 (\$289.00) 16V/10A
- PS-8107 (\$399.95) 30V/10A
- PS-8200 (\$179.95) 30V/3A
- PS-8201 (\$239.95) 30V/5A
- PS-8300 (\$199.95) 30V/3A
- PS-8301 (\$299.95) 30V/5A

FUNCTION GENERATOR

- RF Generator • SC-4160 (\$124.95) 100kHz-150MHz sine waves in 8 ranges
- SC-4162AD (\$229.95) with 6 digit counter
- Audio Generator • AG-2601 (\$124.95) 10Hz-1MHz, 0.8Vpp sine, 0-10Vpp square wave
- AG-2603AD (\$229.95) with 6 digit counter
- Function Generator • FG-2100A (\$154.95) 0.2Hz-2MHz, 5mV-20V_{pp}
- FG-2103 (\$329.95) Sweep 0.5Hz-5MHz

AUDIO/RF/FUNCT. GEN.

- DM-8034 (\$179.95) 3 1/2 digit
- AC/DC (V,A), C, Ω , diode
- DM-8040 (\$339.95) 3 1/2 digit
- ACV to 50kHz, true rms
- DM-8055C (\$889.95) 5 1/2 digit
- 0.006% accuracy, GPIB
- dBm, auto, REL, min/max

GW/INSTEK

- OS-620 \$324.95
- Most economical scope
- Dual CH/X-Y operation
- 1 mV/div sensitivity
- Z-axis input, CH1 output
- TV syn, ALT trigger
- 2 probes (x1, x10)

- OS-626G \$599.95
- Readout & Cursor meas
- Dual CH / Delay sweep
- Built-in delay line
- ALT trigger, Hold-Off
- Z-axis input, CH1 output
- 2 probes (x1, x10)

- 2 variable out 0-30V, 0-3A
- One fixed 5V, 3A output
- Auto track, serial, parallel
- Const. volt, current mode
- 4 analog or 2 digital display
- PC-3030 (\$499.95)
- PC-3030D (\$549.95) digital

- Const voltage, current mod
- Voltage regulation <0.01%
- Current regulation <0.2%
- PS-1830 (\$198.95) 18V/3A
- PS-1850 (\$214.95) 18V/5A
- PS-1830D (\$214.95) 18V/3A
- PS-1850D (\$244.95) 18V/5A

- Auto serial/parall (PPT ser)
- Auto track (PPT series), IEEE-488.2 and SCPI compatible command set
- PS-1860G (\$1,149.95) 18V/6A
- PS-3635G (\$1,149.95) 36V/5A
- PPT-1830G (\$1,499.95) 18V/3A
- PPT-3635G (\$1,499.95) 36V/5A

- FC-8020G (\$209.95)
- 0.02Hz-2MHz w/counter
- Sine/Sqr/Tripulse/Ramp
- FC-8026G (\$209.95)
- 0.02Hz-2MHz w/counter
- FC-8050 (\$449.95) Sweep
- 0.05Hz-5MHz w/counter
- INT/EXT AM/PM mod

- DM-8034 (\$179.95) 3 1/2 digit
- AC/DC (V,A), C, Ω , diode
- DM-8040 (\$339.95) 3 1/2 digit
- ACV to 50kHz, true rms
- DM-8055C (\$889.95) 5 1/2 digit
- 0.006% accuracy, GPIB
- dBm, auto, REL, min/max

- OS-620 \$324.95
- Most economical scope
- Dual CH/X-Y operation
- 1 mV/div sensitivity
- Z-axis input, CH1 output
- TV syn, ALT trigger
- 2 probes (x1, x10)

- OS-626G \$599.95
- Readout & Cursor meas
- Dual CH / Delay sweep
- Built-in delay line
- ALT trigger, Hold-Off
- Z-axis input, CH1 output
- 2 probes (x1, x10)

- 2 variable out 0-30V, 0-3A
- One fixed 5V, 3A output
- Auto track, serial, parallel
- Const. volt, current mode
- 4 analog or 2 digital display
- PC-3030 (\$499.95)
- PC-3030D (\$549.95) digital

- Const voltage, current mod
- Voltage regulation <0.01%
- Current regulation <0.2%
- PS-1830 (\$198.95) 18V/3A
- PS-1850 (\$214.95) 18V/5A
- PS-1830D (\$214.95) 18V/3A
- PS-1850D (\$244.95) 18V/5A

- Auto serial/parall (PPT ser)
- Auto track (PPT series), IEEE-488.2 and SCPI compatible command set
- PS-1860G (\$1,149.95) 18V/6A
- PS-3635G (\$1,149.95) 36V/5A
- PPT-1830G (\$1,499.95) 18V/3A
- PPT-3635G (\$1,499.95) 36V/5A

- FC-8020G (\$209.95)
- 0.02Hz-2MHz w/counter
- Sine/Sqr/Tripulse/Ramp
- FC-8026G (\$209.95)
- 0.02Hz-2MHz w/counter
- FC-8050 (\$449.95) Sweep
- 0.05Hz-5MHz w/counter
- INT/EXT AM/PM mod

- DM-8034 (\$179.95) 3 1/2 digit
- AC/DC (V,A), C, Ω , diode
- DM-8040 (\$339.95) 3 1/2 digit
- ACV to 50kHz, true rms
- DM-8055C (\$889.95) 5 1/2 digit
- 0.006% accuracy, GPIB
- dBm, auto, REL, min/max

- OS-620 \$324.95
- Most economical scope
- Dual CH/X-Y operation
- 1 mV/div sensitivity
- Z-axis input, CH1 output
- TV syn, ALT trigger
- 2 probes (x1, x10)

- OS-626G \$599.95
- Readout & Cursor meas
- Dual CH / Delay sweep
- Built-in delay line
- ALT trigger, Hold-Off
- Z-axis input, CH1 output
- 2 probes (x1, x10)

- 2 variable out 0-30V, 0-3A
- One fixed 5V, 3A output
- Auto track, serial, parallel
- Const. volt, current mode
- 4 analog or 2 digital display
- PC-3030 (\$499.95)
- PC-3030D (\$549.95) digital

- Const voltage, current mod
- Voltage regulation <0.01%
- Current regulation <0.2%
- PS-1830 (\$198.95) 18V/3A
- PS-1850 (\$214.95) 18V/5A
- PS-1830D (\$214.95) 18V/3A
- PS-1850D (\$244.95) 18V/5A

- Auto serial/parall (PPT ser)
- Auto track (PPT series), IEEE-488.2 and SCPI compatible command set
- PS-1860G (\$1,149.95) 18V/6A
- PS-3635G (\$1,149.95) 36V/5A
- PPT-1830G (\$1,499.95) 18V/3A
- PPT-3635G (\$1,499.95) 36V/5A

- FC-8020G (\$209.95)
- 0.02Hz-2MHz w/counter
- Sine/Sqr/Tripulse/Ramp
- FC-8026G (\$209.95)
- 0.02Hz-2MHz w/counter
- FC-8050 (\$449.95) Sweep
- 0.05Hz-5MHz w/counter
- INT/EXT AM/PM mod

- DM-8034 (\$179.95) 3 1/2 digit
- AC/DC (V,A), C, Ω , diode
- DM-8040 (\$339.95) 3 1/2 digit
- ACV to 50kHz, true rms
- DM-8055C (\$889.95) 5 1/2 digit
- 0.006% accuracy, GPIB
- dBm, auto, REL, min/max

ALFA ELECTRONICS
P.O. BOX 8089
PRINCETON, NJ 08543-8089

TEL: (800) 526-2532 / (609) 897-1135
F

will be large enough to hold the rest of the parts. Cut out the front-panel hole for the meter, but mount it last. A suggested layout would be to follow the layout in Photo D from Part 1. Drill the holes for the ON/OFF switch and the photo cell. Photo A shows mounting details for the photo transistor. Photo B gives that

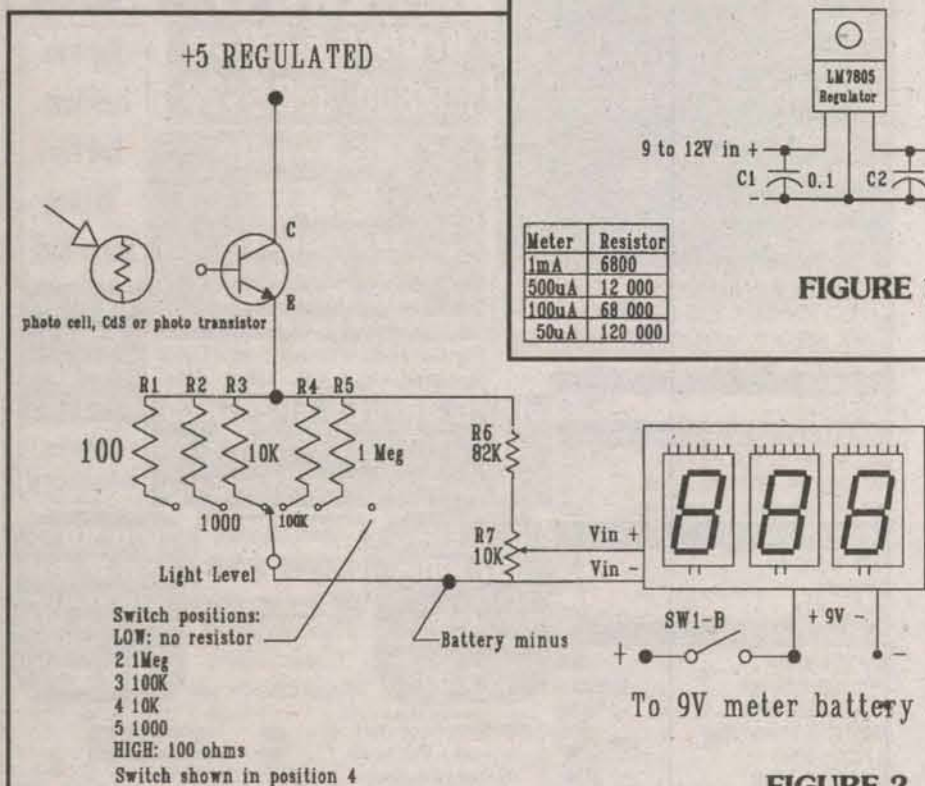


FIGURE 1.

For details of SW1-A and the regulator, see Figure 4.

information for the CdS cell.


The back of the DPM has easy-to-read markings telling where to connect the battery and the signal. The signal connects to the Vin and the G terminals. The battery plus goes to the terminals marked 9V and battery minus. Check the instructions that come with your meter.

Testing It

Once you have the parts installed in the box, doublecheck to see that the batteries go to the proper places. Then, turn on the POWER switch.

Table below shows suggested values for scaling resistor R3, with common meters.

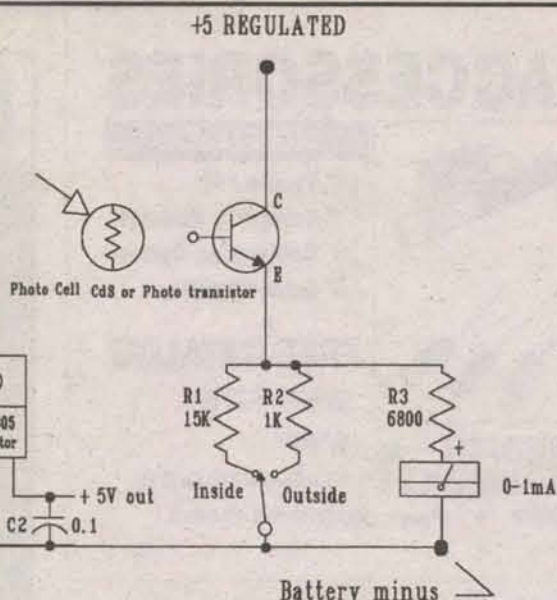Simplified drawing of light meter with analog readout. Instead of the photo transistor, a CdS photo cell may be used. One is shown to the left of the photo transistor.



recheck the wiring to and from the regulator, as well as the wires from the RANGE switch. While you are at it, when you have the battery connected to the regulator, take a voltmeter and make sure that the regulator puts out five volts.

Calibrating It

When you get readings that seem to follow the RANGE switch, you can "calibrate" it. This is strictly an arbitrary calibration. I took my meter outside and set the RANGE switch for the HIGH position. Then, with the diffuser on and the

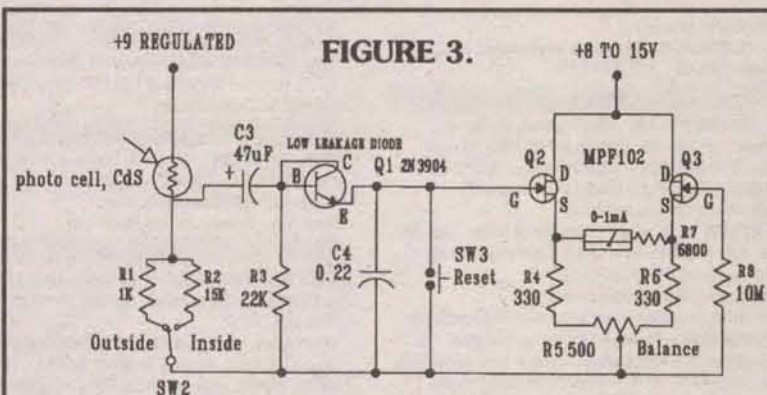


FIGURE 3.

SW1, ON/OFF, connects the battery to the regulator. C1 and C2 go on the regulator, see Figure 5. Q1, a 2N3904, is connected as a diode. Analog display with CdS sensor will work, but photo transistor gives better results. Typical values shown for working model: Photo C. Using 9V instead of 5V gives a bit more sensitivity. However, this requires a 12V battery; somewhat less inconvenient than a 9V battery. See Figure 5 for details of regulator.

unit pointing toward the sun, I set the sensitivity control — the 10 K pot — for an on-scale reading, somewhere around 1,900. Taking it into a shady area, the reading dropped until I could set the RANGE switch to a lower setting. Going inside, it was possible to put the switch on the LOWest setting. There, it would read the light in a dimly-lit room or the light on the TV screen.

The next step would be comparing those readings with a known meter. Lacking a

'CELLULAR ACCESSORIES'

FROM
M.F.M. COMMUNICATIONS.

No. 1

FOR ALL
YOUR CELLULAR NEEDS

WEB SITES:

English: <http://members.aol.com/mfmcom123/index.htm>
Spanish: <http://members.aol.com/mfmcom123/index2.htm>

EMAIL:

MFMCOM123@aol.com

TELEPHONE:

+44 - 1342 312403

57 Addison Road, Caterham, Surrey, CR3 5LU. UK.

**To Go Beyond 2000,
There's TECH 2000.**

- We are on the the cutting edge of cable T.V. technology.
- We offer the most advanced equipment available.

Call 1-888-201-2772

Monday through Friday 9 am to 6pm CST

30 day Money Back Guarantee

One Year Full Warranty

COD Available

- Se Habla Español -

**If You're Not Ready For 2000
Then Call TECH 2000.**

calibrated light meter, you could take a series of readings and write down the conditions. While doing that, take a series of pictures, possibly of your new light meter, and write down the f stops and the shutter speeds. Keep that information handy as that becomes your calibration chart. It tells you what readings you got for a certain set of lighting conditions and how you set your camera to get a good picture. Once you have that information, you can expect repeatable readings from the meter.

Strobe Meter with Analog Display

Figure 3 gives the circuit for the strobe meter with analog display. The parts can go on a piece of perf board as shown in Photo D. That would also serve as a suggested layout for


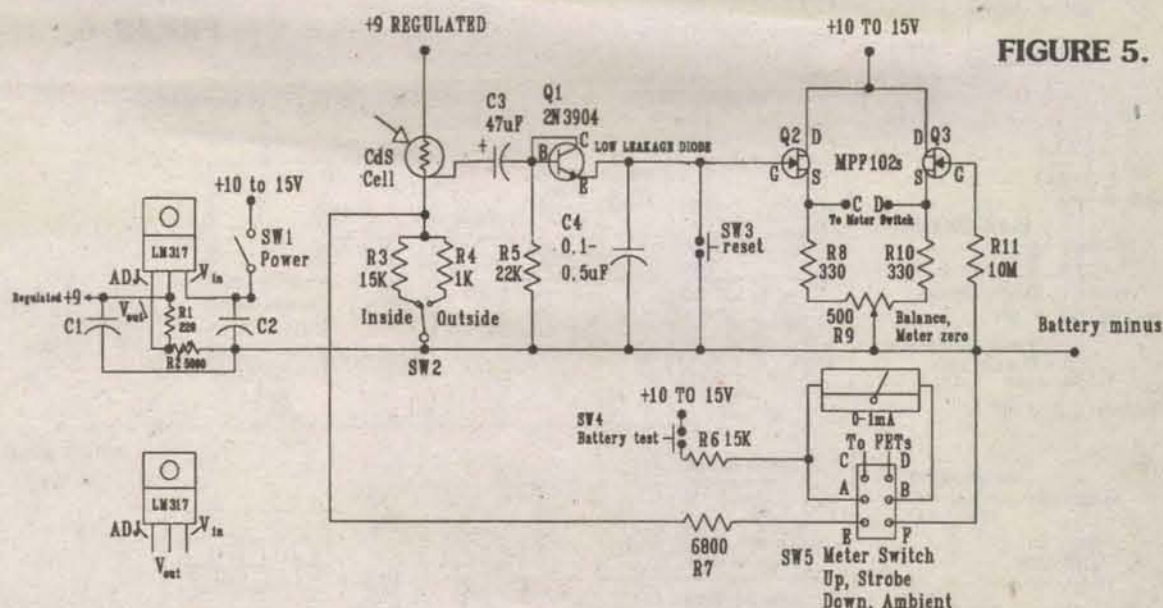


FIGURE 5.

FIGURE 4.

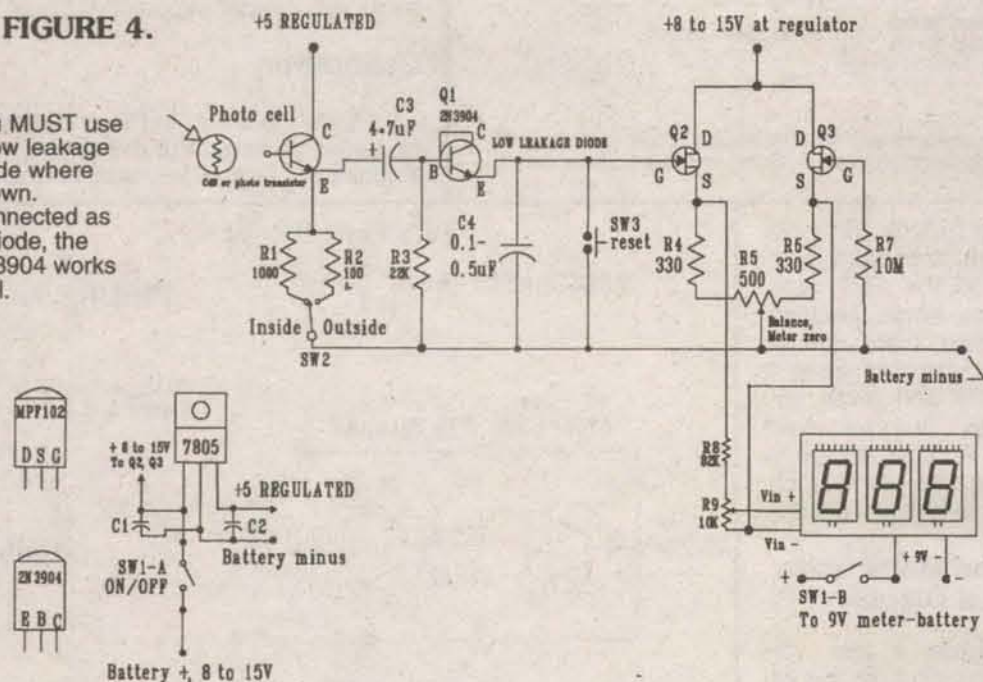You MUST use a low leakage diode where shown. Connected as a diode, the 2N3904 works well.



For Battery test: POWER switch off, STROBE/AMBIENT switch in AMBIENT position. Press TEST button, full scale = 15 volts. As an option, you could take the RESET circuit from Figure 7 (Part 2) and add it to this circuit.

that set for zero, release the RESET button (remove the clip). The meter should stay on zero. With the INSIDE/OUTSIDE switch set to INSIDE, point the unit at a strong light, cover the sensor, then suddenly uncover the sensor. The meter should jump upscale. Of course, if you have a strobe handy, put the switch on the OUTSIDE position and fire the strobe at it.

If you have an on-scale reading, the meter should hold that reading for several minutes; at least long enough for you to get a reading. Push the RESET button and try it again. Move the strobe about two-three times the distance and fire again or, just point the strobe away from it for the next test shot. Changing the light into the meter should give varying readings.

If the meter hits the pin for the conditions that you want to use — distance to the meter, high power strobe, etc. — then decrease the size of the 1 K resistor, increase the size of the Hold capacitor, or both. I derived the values shown here from a nominal 60 watt second

either the strobe, the analog, or the combined system. The difference amounts to about five parts and an external switch. So, for just the strobe meter, put the parts on a board and run wires to the switches, the battery, the photo cell, and the meter.

Watch the 47 uF capacitor. The plus side of it must connect to the emitter of the photo transistor, or the CdS photo cell, where that connects to the INSIDE/OUTSIDE switch.

As mentioned earlier, if you can not find a 500 ohm control, a 1,000 or even a 1,500-2,200 ohm control will work. Preset the Balance control to about the center of its range. Pay close attention to the wiring on the FETs. When you have it all wired, lean on the RESET button while turning on the Power switch. If all goes well, the meter will show some life.

Balance

With your finger on the RESET button, or an alligator clip across it, adjust the Balance control for zero on the meter. The control should let you move the meter a little distance either side of zero. Once you have

Miniature Transmitters and Receivers

2 Button / 3 Channel Transmitter



RF300T

1...\$22.95
5...\$19.95 ea
10...\$16.95 ea

RF300XT

1...\$25.95
5...\$22.95 ea
10...\$19.95 ea

- 300' (XT), 150' (T) Range
- Frequency: 318 MHz
- 59,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.8 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Slide Button Cover Included

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

- Magic Props
- Medical Alert
- Monitoring Systems

4 Button / 15 Channel Transmitter



RF304XT

1...\$27.95
5...\$24.95 ea
10...\$21.95 ea

- 250' Range
- Frequency: 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

- Industrial Controls
- Surveillance Control
- Motor Control

2-4 Data / 3-15 Channel Receivers



RF300RL
RF300RM

1...\$27.95
5...\$24.95 ea
10...\$22.95 ea

RF304RL
RF304RM

1...\$29.95
5...\$26.95 ea
10...\$23.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma. Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea.)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available

Visitect Inc.

(510) 651-1425 Fax: (510) 651-8454
P.O. Box 14156, Fremont, CA 94539

Email: Support@Visitect.Com
Visa / Mastercard, COD

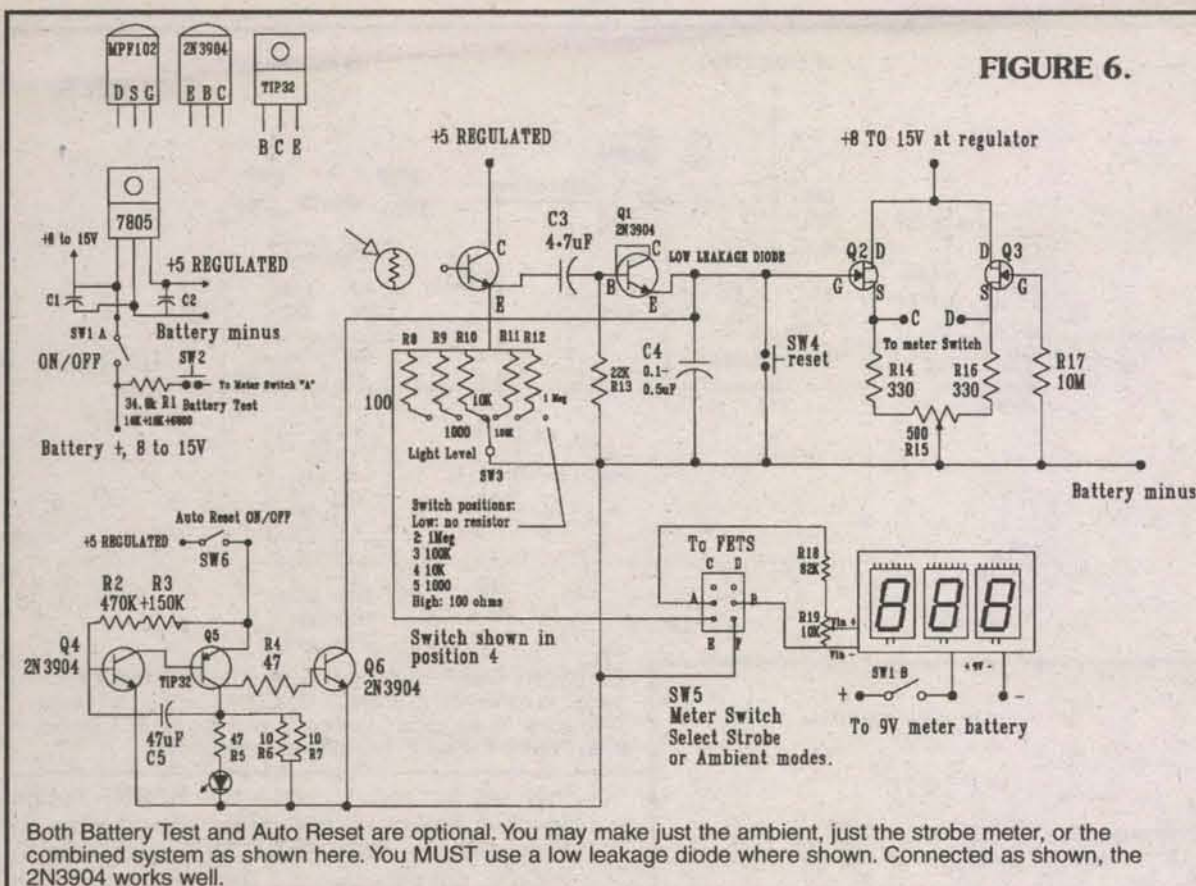


FIGURE 6.

resistor, and the 10 K pot. With the higher sensitivity DPM, we use a five-volt regulator.

Again, the parts may go on a piece of perf board. Check the photos, E for how to mount the photo transistor, or F for mounting the CdS cell. Add the external controls/switches, and the batteries. Check the wiring, hold down the RESET button, and turn on the power. The DPM should show some numbers. Adjust the 500-ohm Balance control for zero on the read-out.

If the zero adjust seems to have a lot of drift, recheck the wiring. If it seems to hold zero, let go of the RESET switch, then change the RANGE switch. That usually puts a pulse into the system. Otherwise, fire a strobe at it. Hit the RESET button and try it again. Point the strobe away from it and fire again. That should give a lower reading unless you are in one of the classic strobe test rooms: a small room with everything painted bright white.

Calibration

Place the meter in the area that you plan on taking pictures. Put the strobe, or strobes, in position. Fire a few test bursts. Note the

strobe at practical working distances; in my case, about 10 feet.

Keep in mind that the FET voltmeter as shown here can handle input voltages up to about four volts. After that, it saturates. Normally, this circuit would have a voltage divider across the front end, where the Hold cap is, to keep the input voltage to the FETs at the one-two volt level. As noted before, you can not put a voltage divider there since that would kill the 'sample and hold' feature.

Fine Tuning

You can trim the sensitivity by changing the value of the 6,800-ohm resistor that is in series with the meter. That is the resistor in the very top right side of Photo D. You may make it adjustable by putting a 10 K pot in series with it. That would cut the sensitivity of the metering circuit by more than half. Keep in mind that too much input voltage to the gate will overdrive the FET voltmeter, so that you do not chase yourself in circles wondering why the meter gives inconsistent readings. Worse yet, as happened to me with the digital version, it read the same for test shots from 5 to 15 feet.

I went to a less sensitive range. Trimming the 1 K resistor or increasing the size of the Hold

cap to reduce the input voltage, to prevent overdrive to the FET gate, may be better choices. As I said, more options than ... but that gives it flexibility and gives you choices, if you want them. Another choice is making the strobe-only meter with digital display.

Strobe Meter with Digital Display

Figure 4 lets you view the diagram for the strobe meter with digital display without having to sort out the circuit from the complete diagram, Figure 5.

Note that the main difference between Figures 3 and 4 is the metering circuit. Here, in Figure 4, we add the signal conditioning resistors for the DPM, the 82 K

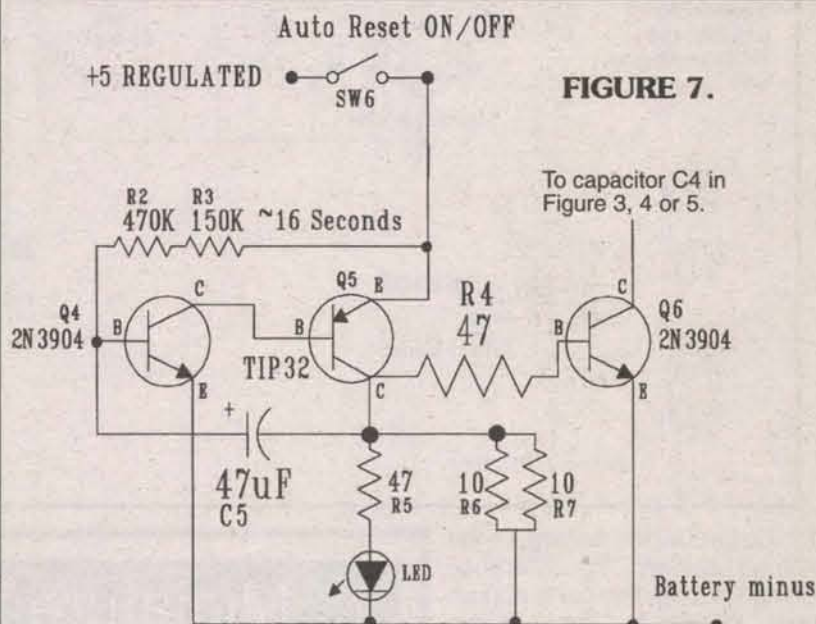


FIGURE 7.

When turned ON, this three-transistor circuit will reset the HOLD capacitor for you. The values shown give a reset pulse about once every 16 seconds. The LED gives a friendly wink to let you know that it has reset the capacitor, returning it and the display to zero, making the system ready to receive the next light burst from your strobe.

68HC11 & 68HC12 Modules

for Solderless Breadboards & Embedded Applications

- miniature interchangeable modules, from 1.7" by 2.6" small
- versatile connector options, including 'DIP-style' spacing, for use with solderless breadboard—great for educational use!
- all modules have reset circuit, pushbutton, & Load/Run switch
- RS-232 interface & 5V regulator are standard on all modules
- all I/O signals brought out to standardized connector pinout

One-piece price from \$63, depending on configuration...

68HC11 Starter Package comes with Adapt11 module for solderless breadboard, 68HC11E2 microcontroller with 2K EEPROM on-chip, PC serial cable for downloading code, Motorola Programming Reference Guide, Adapt11 Handbook, programming & downloading utilities, & demo program. (#AD11SP) \$74.95 + \$5 S&H. Students: ask for 15% discount.

EXPANSION ACCESSORIES:
• Backplanes, prototyping cards, applications cards, and memory expansion

Plug PLCCs, D-sub connectors, ribbon cables, and 1mm flex cables right into your Solderless Breadboard with our complete range of low-cost adapters!

NEW PRODUCT!

ADAPT-812DX

- 68HC812A4 expanded SBC
- 128K or 512K Flash
- 128K or 512K SRAM
- Real-time clock/calendar
- modular & stackable
- RS232 & RS485 interfaces
- 3.25" x 3.25" quality pcb

Starter Packages:
AD812DX128-SP \$189
AD812DX512-SP \$229

Terms: Credit Cards, Check, Money Order. School & Government P.O.s accepted. All prices in US dollars.

TECHNOLOGICAL ARTS

26 Scollard St., Toronto, Ontario, Canada M5R 1E9
Phone: (416) 963-8996 • Fax: (416) 963-9179
techart@interlog.com • www.interlog.com/~techart

\$\$\$ We Can Save You Money \$\$\$

Computers	PCB Manufacturing	PCB Assembly Services	Full Line Of Electronic Components
Custom Built PC's at the Lowest Prices	Single & Double Sided	Board Stuffing Wave Soldering Acquisition of Parts	IC's Semiconductors Capacitors Resistors Sockets Relays Transistors & More
Computer Accessories			

Call **Chaffin Electronics** Toll Free at **(800) 442-2330**

WE WANT YOUR BUSINESS!!! BIG OR SMALL

Phone	Fax	Email	Internet
(800) 442 2330	(740) 354-9462	ccinc@zoomnet.net	www.chaffinelectronics.com

Write in 54 on Reader Service Card.

TABLE II. AMBIENT LIGHT INSIDE

LM1	LM2 A	LM3 D
12K	1.6	738-L 712-2 450-3 86-4 1982-2
4800	4.5	

TABLE III. AMBIENT LIGHT OUTSIDE

LM1	LM2 A	LM3 D
175 Ohms	7-1/2 (outside)	350-H, 1900-5 Bright sun for ASA 200, f16@1/200
215 Ohms	6 (outside)/ 12 (inside)	92-H, 930-5 Refl. off light surface, without diffuser
600 Ohms	3 (outside)/ 9 (inside)	218-5, 1860-4 Shaded area, indicated settings: f5/6@1/125

This table shows readings for the three meters under the same outside lighting conditions.

TABLE IV. STROBE, 16WS

LM2 A	LM3 D
11.7	1128-5
8	1120-5
4	1095-5

Small, directional strobe. Readings on analog and digital light meters.

TABLE V. STROBE, 60WS

LM3 D	Indicated Settings ASA 200
600-H	10 FT Brn Hd
730-H	10 FT Blu Hd
600-H	12 FT Brn Hd
690-H	12 FT Blu Hd

60WS power pack and two different heads. The blue head has almost one stop more light.

TABLE VI. STROBE, 60WS GRY HD

LM2A	LM3 D	12 Feet
7-1/2	90-H	
7-1/2	1105	

Readings from unknown head. Compare with known head to get starting point.

TABLE VII. EXPOSURE VALUES

EXP VAL	f	1/T	ASA
13	16	25	25
14	16	50	50
15	16	125	100-125
16	16	200	200-250
17	16	400	400

TABLES SHOWING LIGHT VS. READINGS FOR VARYING SOURCES.

NOTES:

LM1 is the simple light meter.
LM2 A is the analog meter.
LM3 D is the digital light meter.
Numbers followed by a -2 or -H indicate the range on the digital light meter.
Numbers next to (outside) or (inside) indicate switch setting on the analog meter.
Table II show readings for room lighting. Note several scales on the digital meter. The last reading indicates increased light level.

Without a doubt, the meter(s) that you build will have different readings for similar conditions. That does not mean that these readings are right or wrong. These are the readings that I got and how they relate to one film speed. Readings for Tables IV-VI are average of several shots. Table VII gives some common exposure values. Some equipment uses these numbers instead of f/stops and shutter speeds.

to fit the pre-drilled holes. The board will accommodate larger pots, I just did not happen to get them. One other thing, the board calls for MPS102s that should read MPF102. Other than that, I found the board a real time saver.

Stuffing the Board

On printed circuit boards, I usually put on the resistors first, then the next taller parts, and so on. I would put the regulator on last as it is the most likely to get a broken lead if the board is turned over many times after you put the regulator on it. After stuffing the board, run the wires that go to the switches, controls, etc. CAREFULLY inspect the bottom (the solder-side) of the board for accidental connections. Sometimes a wire from a component may stick out and touch the run going to another part. Sometimes a bit of solder will bridge two circuit runs. Look for that and if you find it, fix it.

Board Contamination

While most of the circuits associated with these instruments are non-critical, the Hold cap used in the STROBE mode needs some consideration. The board must be clean. After putting the PCB version together, it did not want to hold the reading from the strobe. After a while, I traced it to 'leftovers' on the board.

With the power removed, the board got a good scrubbing with a stiff-bristled brush and rubbing alcohol, in a WELL ventilated area. After that, it held the charge.

readings, write them down. The Tables II-VI show some examples. Most likely, you already know what f stops go with a particular strobe and a given distance. Once you have established that, you can compare readings obtained with other strobes. At most, a short roll of film run through the processing lab should confirm your settings or, at worst, indicate which way to make adjustments.

Complete Analog System

So far, we have looked at simple light meters in 'bite-size' pieces. Relatively simple, easy-to-construct meters that will measure light and give us consistent readings. They have gotten progressively more complex. In exchange, they have done more for us. Now we will look at combined systems: light meters that will measure ambient or strobe light in one instrument. We will start with what I consider the simpler system, the analog unit.

Figure 5 shows the circuit for the entire system. Photos B and E give interior views. Photo C

from Part 1 showed the finished unit. In addition to the other features of the simpler system, it has a battery test and the meter switch. The meter switch connects the analog meter to one of two circuits.

In the Ambient position, it ties the meter to the cold side of the CdS photo cell (or to the emitter of the photo transistor) and to the battery return, circuit common. In the Strobe position, the switch connects the meter to the sources of the FETs. Both circuits remain active all of the time; you select which one you want.

Probably the most convenient way to put this one together would be to get one of the printed circuit boards from Fred at Far Circuits. They save a LOT of time. They have an easy-to-read silkscreen on the component side of the board. That lets you pick your parts and stick them on the board; quite a bit handier than the prototype version. Otherwise, you can just use the layouts, Figures 8-13, if you like to do your own boards.

A close look at this board, Photo E, shows that the controls need a bit of 'adjusting' in order

Lowest Dealer Price Available

	5+	10+	20+
Refurb. Panasonic 145	\$45	\$40	\$35
Regal w/Remote	\$38	\$35	\$30
BC4535 86 Channel	\$30	\$28	\$25
Oak Sigma 99 Channel	\$45	\$40	\$35
75 Channel Converter	\$18	\$18	\$18
Zenith ST1600 w/Remote	\$75	\$70	\$65
Panasonic Converters Model-175 (550MHz)	\$65	\$55	\$45

Six month's warranty on this model only

Call us today to satisfy all your cable equipment needs!

SAM'S ELECTRONICS
1-405-631-1856

All Cable Equipment is unmodified.

USB Relay Module

Model JSB-210

Controls 8 to 16 "form C" relays over the USB (Universal Serial Bus). Program the module with simple commands in any program language that supports USB Communications. Driver and sample code provided

J-Works, Inc

12328 Gladstone St., Unit 4
Sylmar, CA 91342
(818) 361-0787 Voice (818) 270-2413 Fax

Other Products

RS-485 Remote I/O
ISA Waveform Generator
RS-485 to DS-1820
RS-485 Temperature I/O
DS-1820 Probe

Visit our Web site for
Information on all our products
<http://www.j-works.com>
E-mail sales@j-works.com

PARTS LIST

Parts List Figure 2

Simple, Stand-Alone, Ohmmeter for measuring light
 R1 1000 ohm pot, or See Table in Figure 2
 R2 1000 ohms, or See Table in Figure 2
 R3 56-100 ohms
 Battery 1-1/2 volts and holder
 Photo Cell CdS 276-1657
 SWITCH Single Pole 3 Position
 Meter 22-410 (0-1mA) or see table
 Meter 910-0388 (0-1mA Tech America)

Parts List Figure 7

Ambient Light Meter with Analog Readout
 R1 15K C1 0.1uF/15V 272-1069 Photo Cell CdS or Photo transistor 276-1657 or 276-145
 R2 1K C2 0.1uF/15V 272-1069
 R3 6800 or See Table in Figure 7 Regulator LM7805, LM7806, LM7808 Pick one
 Meter 22-410 (0-1mA) Meter 910-0388 (0-1mA Tech America 1-800-877-0072)
 Diffuser/holder for photo cell 272-340

Parts List Figure 8

Ambient Light Meter with Digital Display
 R1 100 C1 0.1uF/15V 272-1069
 R2 1000 C2 0.1uF/15V 272-1069
 R3 10,000 Photo Cell CdS or Photo transistor 276-1657 or 276-145
 R4 100,000 Diffuser/holder for photo cell 272-340.
 R5 1,000,000 LCD Panel Meter PM-128 (Circuit Specialists 1-800-528-1417)
 R6 82K SW1 ON/OFF, DPDT Toggle switch 275-626
 R7 10K pot SW2 LIGHT LEVEL, 2P 6 position Rotary Switch 275-1386

Parts List Figure 9

Strobe Light, Analog Display
 R1 1000 C1 0.1uF/15V 272-1069
 R2 15K C2 0.1uF/15V 272-1069
 R3 22K C3 10-50uF/15V 272-1024, 1026 or 1027
 R4 330 C4 0.22uF/15V 272-1070
 R5 500 ohm pot, up to 2200 ohms ok. Q1 2N3904 276-1617 (Pkg of 15)
 R6 330 Q2 MPF102 276-2062
 R7 6800 Q3 MPF102 276-2062
 R8 10 Meg Diffuser/holder for photo cell 272-340.
 Photo Cell CdS or Photo transistor 276-1657 or 276-145
 Meter 22-410 (0-1mA) Meter 910-0388 (0-1mA Tech America 1-800-877-0072)
 SW1 ON/OFF, DPDT Toggle switch 275-626
 SW2 INSIDE/OUTSIDE, SPDT Toggle Switch 275-625, 635
 SW3 RESET, SPST Push Button Switch 275-1556

Parts List Figure 10

Two-Range Strobe Level with Digital Display
 R1 1000 C1 0.1uF/15V 272-1069
 R2 100 C2 0.1uF/15V 272-1069
 R3 22K C3 4.7-50uF/15V 272-1024, 1025 or 1026
 R4 330 C4 0.22uF/15V 272-1070
 R5 500 ohm pot, up to 2200 ohms ok.
 R6 330 SW1 ON/OFF, DPDT Toggle switch 275-626
 R7 10Meg SW2 HIGH/LOW SPDT Toggle Switch 275-625, 635
 R8 82K SW3 RESET, SPST Push Button Switch 275-1556
 R9 10K pot Diffuser/holder for photo cell 272-340.
 LCD Panel Meter PM-128 (Circuit Specialists 1-800-528-1417)
 Photo Cell CdS or Photo transistor 276-1657 or 276-145

Parts List Figure 11

Strobe/Ambient Light Meter with Analog Display
 R1 220 C1 0.1uF/15V 272-1069
 R2 5000 Pot C2 0.1uF/15V 272-1069
 R3 15K C3 4.7-50uF/15V 272-1024, 1025 or 1026
 R4 1000 C4 0.22uF/15V 272-1070
 R5 22K
 R6 15K Q1 2N3904 276-1617 (Pkg of 15)
 R7 6800 Q2 MPF102 276-2062
 R8 330 Q3 MPF102 276-2062
 R9 500 ohm pot, up to 2200 ohm ok.
 R10 330
 R11 10Meg
 SW1 ON/OFF, SPST Toggle Switch 275-612, 275-645, 275-634
 SW2 INSIDE/OUTSIDE, SPDT toggle 275-625, 635
 SW3 RESET, SPST Push Button 275-1556
 SW4 BATTERY TEST, SPST Push Button 275-1556
 SW5 Function Select, Meter Switch (STROBE/AMBIENT), DPDT Toggle 5-636, 275-663, 275-626
 Regulator LM317, Adjustable Diffuser/holder for photo cell 272-340.
 Photo Cell CdS or Photo transistor 276-1657 or 276-145

Parts List Figure 12

Strobe/Ambient Light Meter with Digital display
 R1 34.8K* R10 10,000 R19 10K pot
 R2 470KR11 100,000 C1 0.1uF/15V 272-1069
 R3 150KR12 1,000,000 C2 0.1uF/15V 272-1069
 R4 47 R13 22K C3 10-50uF/15V 272-1024, 1026 or 1027
 R5 47 R14 330 C4 0.22uF/15V 272-1070
 R6 10 R15 500 pot, up to 2200 ok.

Figure numbers referenced here are based on Part 1 figures.

R7 10 R16 330 C5 47uF/15V 272-1027
 R8 100 R17 10Meg
 R9 1000 R18 82K Diffuser/holder for photo cell 272-340.
 Photo Cell CdS or Photo transistor 276-1657 or 276-145
 LCD Panel Meter PM-128 (Circuit Specialists 1-800-528-1417)
 Q1 2N3904 276-1617 (Pkg of 15)
 Q2 MPF102 276-2062
 Q3 MPF102 276-2062
 Q4 2N3904 276-1617 (Pkg of 15)
 Q5 TIP32 or similar power transistor
 Q6 2N3904 276-1617 (Pkg of 15)
 SW1 ON/OFF, DPDT Toggle 275-636, 275-663, 275-626 (DPDT, but that is all they list)
 SW2 BATT TEST, SPST Push Button Switch 275-1556 SW4 RESET, SPST P B 275-1556
 SW3 LIGHT LEVEL, 2P 6 position Rotary Switch 275-1386 LED 276-069
 SW5 Function Select, Meter Switch (STROBE/AMBIENT), DPDT Toggle 275-636, 275-663, 275-626
 SW6 AUTO RESET ON/OFF, SPST Toggle Switch 275-612, 275-645, 275-634
 *R1 consists of 10K+18K+6800 connected in series. A 10K resistor plus a 25K pot would work

Parts List, Figure 13

Parts lifted directly from Figure 12.
 Auto-Reset option
 R2 470K Q4 2N3904 276-1617 (Pkg of 15)
 R3 150K Q5 TIP30, TIP32 (900-5168, 900-5170 Tech America)
 R4 47 Q6 2N3904 276-1617 (Pkg of 15)
 R5 47 LED 276-069
 R6 10 SW6 AUTO RESET ON/OFF, SPST Toggle Switch 275-612, 275-645 etc.
 R7 10 C5 47uF/15V 272-1027

Comments

Where to get the parts

As a convenience to those less familiar with this type of equipment, I have broken down the complete systems into smaller, easier-to-build units. That gives us a light meter for ambient-light with analog or with digital display: likewise, strobe-only, with analog or digital display. This way, if you do not want to build a complete, and somewhat more complex system, you may use the parts list for just what you want to build and not have to dig the pieces out of two or three other diagrams.

For the same reason, I have listed some of the part numbers from RadioShack. They are available in many parts of the country. That may save the trouble of getting the parts by mail order. In most cases, you will find equivalent parts from other sources, local distributors or if you have to, via mail-order. If you have to go mail-order, Circuit Specialists and Tech America look like good mail-order stores. Tech America has a wide variety of parts that the serious experimenter should like, and they seem to specialize in making it convenient to do mail-order.

Units with Digital display

The units with digital panel meters need a Double Pole ON/OFF switch. A DP Single Throw switch is ideal, but the RS catalog lists only DP Double Throw (DPDT). You pay a few cents more for the extra contacts, or get the switch somewhere else.

Transistors

The parts lists call for 2N3904s which come in single units, or packages of 10-15, depending upon where you get them. The 2N2222 should work in these instruments. At 10-15 cents each, they look like a good deal, especially since they lend themselves to other projects.

Boxes


The box for the Digital Light Meter, came from Circuit Specialists. It has a nice appearance, but cost a bit more than the easier to get, 'black box' used for the analog meter. That box came from RadioShack as did the box for the 'Instant' Light Meter, Photo A.

PC Boards

You may get the printed circuit boards for \$4.00 ea., from:

Far Circuits
 18 N. 640 Field Court
 Dundee, IL 60118

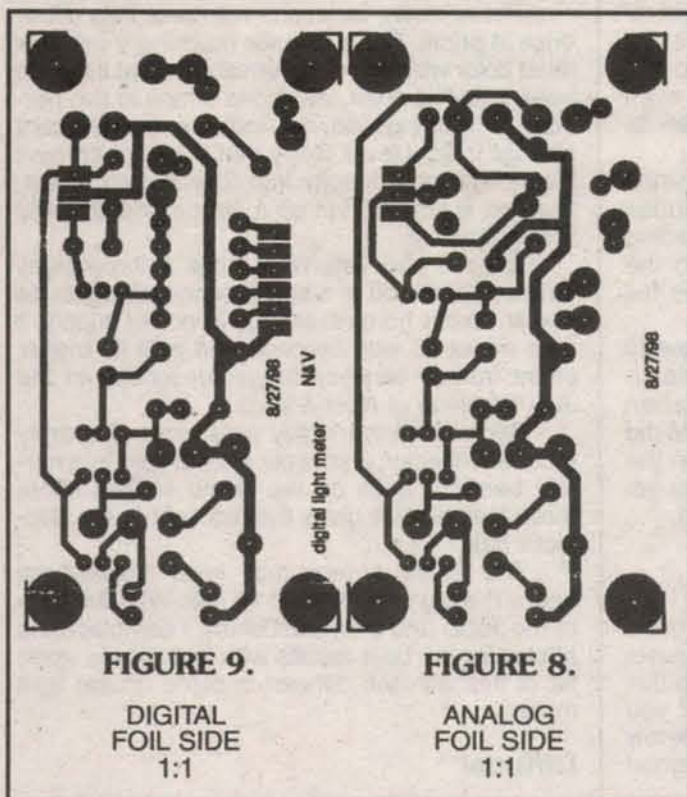Those are the complete strobe/ambient systems, either analog or digital display. Be sure to specify which board you want: digital or analog. These are some of the finest prefab boards that I have seen in years. Fred kindly supplied the layouts if you wish to make your own boards.



if you move around, the readings can change until you hold still. It is that sensitive. Turn the range LIGHT LEVEL switch up a range or two. The numbers should get smaller. On the highest ranges, "5" and HIGH, you will probably want to go outside or point it at a strong light. Outside, this one shows around 400-500 on HIGH and 1,900 to overrange on "5," when looking at a sunlit sky. Calibration will be done later, just check it out now.

To check the STROBE function, set the controls for STROBE, LIGHT LEVEL for "5" or HIGH. Turn it ON or, if it was on, it will probably show some reading. That should stabilize in a second or two. Changing ranges usually puts a reading on the meter.

If the reading drops off, decreases faster than one or two units per minute, go over the section on Board Contamination.

Otherwise, tap the RESET button. After a second or two, the reading should drop down to 000 or maybe as much as 007. If it reads more than that, then hold down the RESET button, or put a clip lead across it and rezero (balance) the FET volt-meter.

Check Photo F for the location of the BALANCE pot, R15 in Figure 6. Set the control for a reading of 000 or as close to that as you can. When done, remove the clip lead. The control should let you move the meter through zero. It should go from plus to minus. Normally the DPMs do not show a polarity sign when reading a positive voltage, but they do display the minus (-) sign when the input goes negative.

Battery Test

If you included the TEST BAT function, this would be a good time to set it. Set the controls

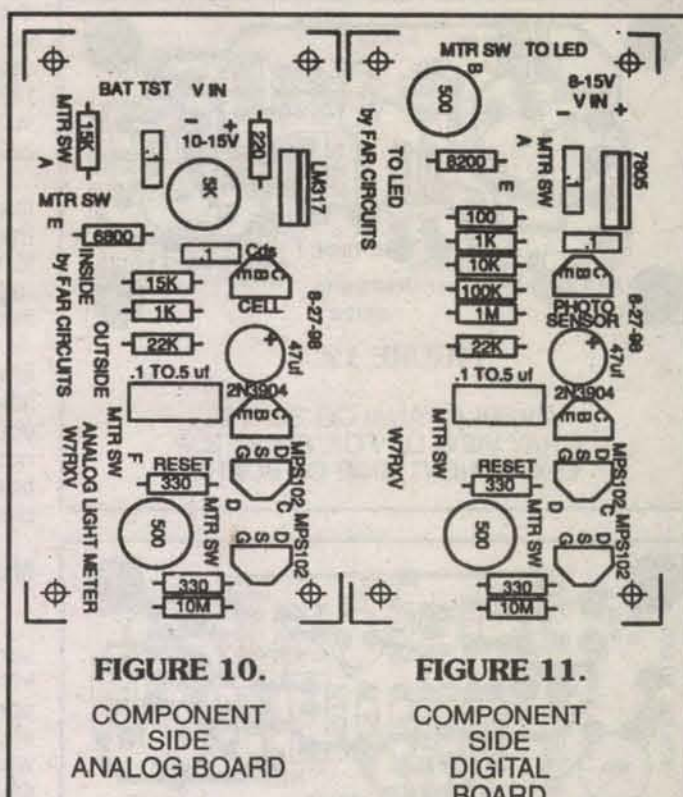


FIGURE 10.

COMPONENT
SIDE
ANALOG BOARD

FIGURE 11.

COMPONENT
SIDE
DIGITAL
BOARD

When you test your unit, If everything seems to work, but the readings from the strobe shots seem to drop off, clean the board. That can happen with either the analog or the digital board. Once you finish the board, lay out the box, and drill the holes for the controls. Mount the controls, then run wires from them to the board, the battery, etc. Before you turn it on, give it one more close look.

Complete Digital Version

As with the analog board, I would recommend putting the resistors on first, then the taller parts. Photo F gives a close-up view of the finished digital board. Lay out the box. Tape a piece of graph paper to the box. Use a pencil to mark the positions for the parts. That makes it easy to 'adjust' the layout. When you like the layout, mill and drill the box. You will probably find it most convenient to put on the labels before mounting the controls and other panel-mount parts. Mount the controls first, mount the digital panel meter last.

Run the wires from the board to the controls and the switches. Make sure that battery plus goes to the correct place, particularly the battery for the digital panel meter. Be sure to follow the instructions that come with your particular DPM.

Check Out Time

When you have everything wired, connect just the battery for the DPM and turn on the power (ON/OFF switch). The meter should show 000. If it does, turn it off and connect the other battery. Set the controls for LOW, AMBIENT, and POWER ON.

The meter should show some numbers, say anywhere from 100 to 1,900, depending upon how much light you have in your work area. After five to six seconds, the reading should stabilize, although

to AMBIENT, LIGHT LEVEL to "4", cover the photo cell. Press the TEST BAT button or put a clip across it. Measure the battery that feeds the main circuit. Adjust the 10 K pot, R19 in Figure 6, so that the DPM gives the same reading as the bench meter did on that battery. Remove the clip from the TEST BAT switch.

I admit that it is a bit crude, but I just could not see taking the thing apart just to check the battery. The AUTO RESET LED will give a bright wink if that battery is up, otherwise the circuit will reset the system but the LED will hardly give a visible light.


Reset

If you included the AUTO RESET, you may check it now. Get a reading on the meter with the switch in the STROBE position. Turn on the

ADDRESSABLE STEPPER MOTOR CONTROLLER

Part Number: JWP1X-1A

\$199.95

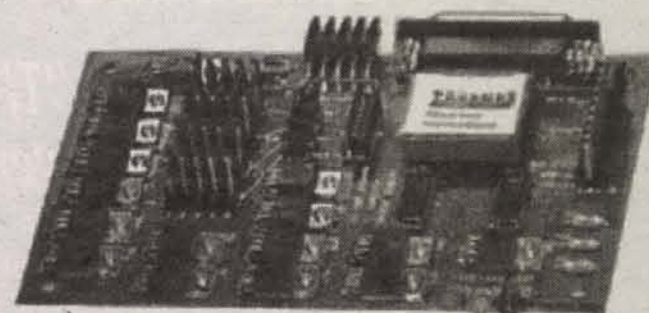

PARAMAX INC.
(800) 473-8080

Come and visit us on the internet at:
www.paramax.net

The PARAMAX stepper motor controller is a PC parallel port based addressable controller capable of simultaneous operation of 4 uni-polar stepper motors ranging in voltages from 5 to 12 volts at up to 2 amps per phase. The PARAMAX stepper motor controller includes 8 digital inputs with a data throughput rate of 500k bytes per second. Using the unique PARAMAX addressing method, up to 256 controllers can simultaneously function from a single parallel port. The programming package includes libraries that allow you to create applications both under Windows and DOS. Included libraries are: C++, Pascal, Delphi, Basic and utilities for DOS and Windows.

Also available at:
FORD ELECTRONICS, INC
(714) 521-8080

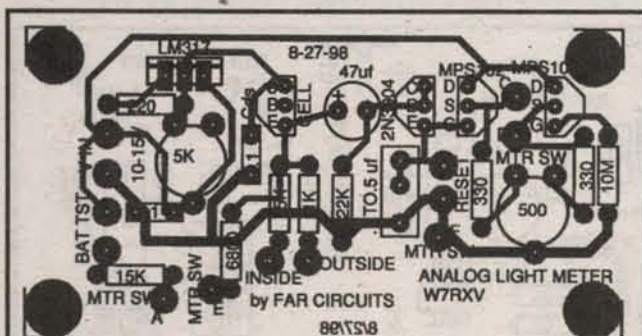


FIGURE 12.

OVERLAY ANALOG BOARD.
X-RAY VIEW OF FOIL FROM TOP
COMPONENT SIDE OF BOARD.

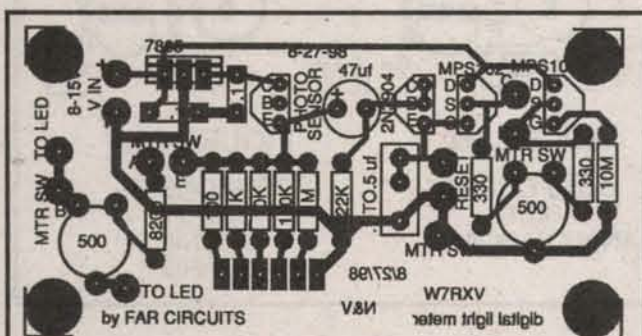


FIGURE 13.

OVERLAY DIGITAL BOARD.

AUTO RESET. After about 15 seconds, the LED should wink and the readout should reset to zero, 000. If it resets but the LED did not seem to wink, wait for it again and try not to blink.

If it looks like the LED does not work, try turning the wires around that go to the LED. If that still does not work, make sure that the battery is up to at least eight volts. As mentioned

earlier, the LED can serve as a form of battery indicator. Although the circuit will still reset the system, the voltage to the LED circuit must be above about eight volts in order to get the LED to give its bright wink.

At first that may seem strange since the AUTO RESET circuit, which includes the LED, has a five-volt regulator feeding it. What it means is the voltage into the regulator has fallen too low to get the full five volts out of it.

Therefore, the main battery needs attention. The battery for the DPM has so little drain on it that you may check it when you replace the main battery. The DPM did not seem to lose accuracy even when the battery for it got so low that the display got dim. Now, let's put the display to work.

Numbers vs. Light, Strobe

While these light meters have good sensitivity, they do not give you light levels in terms of f stops, shutter speed, and film speed. You have to determine that. If you start with a known light source and know what settings you use, that makes a good starting point.

For example, with my favorite strobe and film, I set the camera for f 7 with the strobe 10 feet away from the average subject. See Table II. That means set the lens for f 3.5 at 20 feet or close to f 16 at five feet. With a faster or a slower film, I have to make suitable changes in the f stop setting.

To get a set of numbers that I could relate to camera settings, I set up the strobe, measured the distance to the light meter, and started firing away at it. I took several readings at each distance and averaged them for Table II. They showed minor variations. However, whether the meter showed them or not, they were always there.

Those minor variations will make little difference in prints. The automatic machinery used for most color work will compensate for that if it even sees it. At this point, variations of one to two percent in readings do not indicate a significant change in light level. Sorry that I can not convert these readings directly into footcandles or lux. But that is why we set up a strobe and shoot at the light meter.

Table II also lists what I call a throw-away strobe. It came off of a small camera and gets its power from a home-built plug-in power supply. It runs about 16 watt seconds and gets its trigger pulse from a wireless trigger described in the July '94 issue of *Nuts & Volts*.

Because of the highly polished and sharply focused reflector, it puts out a lot of light in a narrow beam. It goes on top of the subject about three feet away. It gives the highlight to the subject's hair.

The Table shows that level somewhere below the big strobe at 10-12 feet. With the help of the Table and a few test shots, I can place the strobe for the best results with less guess work; all of this with the diffuser in place on the light meter.

Diffuser

The white diffuser screws into the top of the light meter. You want to use it when measuring incoming incident light. Without it, you point the light meter at the subject and measure reflected light. I will let the professional photographers argue over which one they like best, and why.

Without the diffuser, these meters get quite directional. With the diffuser in place, the analog meter reads about 4-5 in an average room. Without it, the meter went from 3-12, depending upon where it was pointed.

Numbers vs. Light, Ambient

This should be easier than you might think. The chart that comes with the film, say ASA 200, tells you that for bright sunlight and average subject, set the camera at 1/200-1/250 and f 16. For close-ups of back-lighted subjects, in shade, set the camera ... Okay, you get the picture. So, take the light meter and see what numbers it gives you in bright sunlight, in the shade, or wherever you may want to take pictures. Those first two settings — bright sunlight and open shade — should be easy to duplicate and make a rather good standard.

Do that and make some test pictures for comparison. That will give you a good idea of how to set the camera when you come across that beautiful meadow or woodland scene that you want to capture on film.

For indoor use, you will have to borrow a standard light meter or make a series of test shots while writing down the readings. Most likely you can draw on past shots to get an idea of where to set the camera until you get the prints or the transparencies back.

After a while, you will develop a series of readings versus lighting conditions that will let you get consistent pictures with the help of one or more of these (more or less) simple, practical light meters. **NV**

CABLE TV CONVERTERS

WILL NOT DECODE

The Best Prices and Service • In Business over 15 years!

Phone 218-346-6660 Fax 218-346-6664

TIMELESS PRODUCTS

New! "TP 125 V"
128 Channel Converter with Volume

Special Prices for
TP1550PC
Call for Details

Panasonic still available!

- REFURBISHED CONVERTERS ALSO AVAILABLE •
- QUALITY REPAIR DEPARTMENT FOR ALL YOUR TUNER REPAIRS •
- REMOTES AVAILABLE FOR MOST CABLE BOXES •

DEALERS ONLY • GREAT QUANTITY PRICES • NO DECODER SALES

We've Got It!

MCM Electronics®

Prices effective
March 19 through
April 30, 1999.

MCM is the leading supplier to the consumer electronics service industry. Additionally, hobbyists, educators and even manufacturers have looked to MCM for all of their component needs. Call today for your free catalog!

100W Subwoofer Amplifier Module

Ideal for anyone interested in making their own powerful subwoofer. Internally, this amplifier isolates, then sums the left and right inputs to give a single mono channel with 100W RMS output @ 4ohm, 85W RMS @ 8ohm. •Speaker level inputs •Satellite outputs •Line level inputs •Auto turn-on •12dB continuously variable 60Hz~160Hz crossover •Adjustable level control •0°/180° phase selector •Fully sealed rear housing •Requires 8" square opening •Call for quantity pricing



Order #
#50-6265
\$99.95

8" Rubber Surround Polypropylene Woofer

MCM AUDIO SELECT™

Popular woofer design is the foundation of many home and auto speaker systems. 70W/100W RMS/peak capacity, frequency response 30Hz~3.5KHz. 8ohm. Other sizes available. **Regular price \$13.50**



Order #
#55-1190
\$9.95

5" Stage Monitor Driver

MCM AUDIO SELECT™

Replaces Hot Spot, Bullfrog, Legend and Bose type stage monitors. Features a treated cloth surround and paper cone. Magnet weight: 17.7 oz. Voice coil: 8ohm Power handling: RMS/peak 50W/100W. Frequency response: 80Hz~15KHz. **Regular price \$10.25**



Order #
#55-1595
\$6.99

Hole Cutter With Adjustable Radius Blade

Great for speaker mounting. Cuts 1 1/2"~7 1/2" holes in plywood, plaster board and acrylic sheet up to 1 1/2" thick. Also cuts aluminum, brass and metal sheets up to .04" thick. Base keeps bit perpendicular to cutting surface and cowl collects debris when ceiling cutting. **Regular price \$103.00.**



Order #
#22-1825
\$84.95

RF Modulator

Outstanding price on this popular audio/video/surveillance accessory. Accepts standard A/V signal and places it on channel three or four, RCA type inputs, "F" type output. Requires 117VAC. **Regular price \$19.95.**



Order #
#33-1480
\$11.95

Solder Station

TENMA®

Perfect for most soldering applications including SMD. Overheat protection with closed loop temperature control provides precise heat. Includes replaceable iron clad conical 3/64" tip. Linear LED display shows operating temperature. **Regular price \$79.95.**



Order #
#21-147
\$49.95

Portable DMM

TENMA®

Affordable hand held meter features 3 1/2 digit LCD display, DC voltage measurement to 600V, transistor and battery test. Input impedance 10Mohm. Includes holster and test leads. **Regular price \$31.95**



Order #
#72-2055
\$24.95

BassBox Pro Ver. 6.0 Design Program

Design bandpass, vented, passive radiator and closed box speaker enclosures. Contains database of over 1,300 woofers including all MCM Audio Select models. Others can be added. Provides frequency plots from many popular measurement systems including IMP, LMS, MLSSA, and TFE-20. Requires MS Windows.



Order #
#81-2236
\$129.00

To take advantage of special pricing on the items listed, please provide this code: **NVM24**

Medium Size Prototype Board

This board was designed for medium sized circuits with room for several ICs and lots of components. The outside traces are all connected while the center was designed to accept multiple ICs with 45 traces available for multiple connections. Board dimensions are 5 1/2" x 1 1/2" x 1/16"



Order #	(1-9)	(10-up)
21-4580	\$1.29	\$0.99

30 Piece Security Tool Kit

Kit includes security torx bits, tri-wing bits, security hex bits, Nintendo type bits and more. Ideal when servicing Sega and Nintendo games, PS/2 monitors and more.



Order #
#22-1476
\$9.99

Multi-Voltage Power Supply

Fully regulated supply provides up to two amps, at the following selectable voltages: 3 • 4 • 6 • 7 • 9 • 12V • 15V • 18V • 24V • 30V • 36V • 48V • 60V • 75V • 90V • 100V • 120V • 150V • 180V • 200V • 220V • 240V • 250V • 260V • 12950V • 129

Build a SEPIC Regulator for Your Battery-Powered Digital Project

Portable electronics are everywhere. The trend itself is not new; what is new is the fact that these portable devices are becoming increasingly sophisticated, and many of them are incorporating some sort of microcontroller or other embedded digital circuits. This has been fueled by the increased availability, ease of use, and lower cost of development tools and the microcontrollers themselves.

Perhaps you have got a great idea for such a portable digital project, and you may have started to punch some code. As you debug the code and start laying out the project, a question looms deep in the background: How am I going to power the project? With batteries, of course. Simple question, simple answer, right?

The real answer is that there is more than meets the eye; that portable power is not a trivial consideration.

Beyond Linear Regulators

The old standby for most of the homebrew digital projects has been a 9 to 12 volt "wall-wart" DC supply, followed by a three-terminal linear regulator. The ubiquitous 7805-type regulator is extremely popular for the application. A simple and almost foolproof solution, it only

requires some decoupling caps here and there, and to use your finger as a temperature sensor to determine if a little heatsink is necessary.

The only problem with this scenario: efficiency. Half or more of the total power may be consumed as heat in the regulator. This in itself is no showstopper for a line-powered application. But as every cell phone user knows, high energy storage and utilization efficiencies are paramount to low weight and size while maximizing usage time.

Unfortunately, high energy capacity batteries and their associated chargers are not cheap, and usually beyond the budget of home projects. Thus, the only alternative left is to achieve high regulator efficiency.

High efficiency means, of course, either a low dropout linear or a switch-mode regulator. Low dropout linears are also a simple and attractive solution for many projects. However, battery considerations again may restrict the use of such a device. If our goal is to have simple, low-cost batteries and charging devices (if rechargeable operation is required), then this goal rules out lithium, NiMH, or other state-of-the-art chemistries. For portable devices, nothing beats four "AA" size NiCad or Alkaline batteries. They are affordable and ubiquitous, have an adequate ener-

**JUST ABOUT EVERYTHING YOU
NEED FOR FAXES & PRINTERS IS
AT ONE CONVENIENT ADDRESS:**

www.faxrepair.com

*For service, parts & sales, Cyber-Test is
America's Largest Fax Support Center.*

- **CIRCUIT BOARD REPAIR** Component level repair on boards and power supplies for all brands & all models.
- **ENTIRE MACHINE REPAIR** We fix any thermal, ink jet or laser fax. Low flat rates available!
- **PARTS** We have a huge inventory of new & refurbished fax and printer parts ready to ship. Easy ordering with no part number necessary. H-P laser parts available!
- **SALES** Great deals on commercial grade plain paper faxes.
- **SUPPLIES** Drums, toner & developer for laser faxes or printers. Lowest prices anywhere for Okidata, AT&T, DEX and Samsung!
- **SUPPORT** Why go anywhere else? Check our Web Site or call today!



800-881-3344

press "6" for repair & sales
448 Commerce Way - Bldg. 100 - Longwood, FL 32750

**CHECK CAPACITORS
IN-CIRCUIT WITH
100% ACCURACY**



CapAnalyzer 88 \$179

- Automatically discharges cap;
- Checks for low DCR and shorts;
- Checks high-frequency ESR and displays on 20-segment LED meter
- 3-color chart shows typical values.
- Includes gold-plated tweezer probe
- Portable... Batteries included!

**LOCATE ANY SHORTED
or LEAKY COMPONENT
TO THE EXACT SPOT**



LeakSeeker 82A \$179

Locates shorted & leaky parts to the exact spot on the PCB without cutting up the board or unsoldering any parts!

**• 60 DAY SATISFACTION
OR MONEY BACK
GUARANTEE**

**• AVAILABLE AT YOUR
FAVORITE DISTRIBUTOR**



ELECTRONIC DESIGN SPECIALISTS

4647 Appalachian St, Boca Raton, FL 33428 561-487-6103 www.eds-inc.com
we make test equipment designed to make you money.

Table 1. Typical Power Supply Ratings

Input voltage: 3.9 to 7.0 volt DC @ full load
3.5 to 7.0 volt DC under half load
Output voltage: 5 volt DC, $\pm 5\%$
Operating frequency: 100 KHz nominal.
Load current: 10 to 160 mA continuous rating.
Worst case ripple: 400 mV pk-pk @ full load and minimum input voltage.
Average ripple: 200 mV pk-pk.
Short circuit protection: current limited to ~700 mA.

gy storage capacity for their size and weight, and apparently battery vendors have standardized their retail practices to four-packs. Therefore, four cells should become our portable power target.

Let us analyze the conflict between the proposed four cells and a linear regulator. The end voltage of a depleted cell is about 0.9 to 1.0 volts, depending on the chemistry. On the other hand, most low voltage regulators require at least 0.4 volts above the regulated voltage. This means that to meet the minimum input voltage of 5.4 volts, at least six cells are required. This will not meet our four-cell criteria, and worse, with a fully charged alkaline, 45% of power would be wasted.

Thus, a low dropout regulator is ruled out. This leaves us with switch-mode regulators, of which there are many topologies. Some may be ruled out quite readily; a buck regulator, although simple and efficient, still requires more than four cells. A push-pull regulator is very efficient but complex, and their transformers require to be custom wound and may be too challenging for a novice builder.

The boost topology merits some consideration, as it would allow for even fewer cells. This topology is becoming very attractive for high-end portable devices employing lithium single cell solutions, however, the cost and availability of regulators which may operate in the two to three volt range is still beyond the reach of hobbyists.

The buck-boost would be an ideal candidate: This topology allows the input voltage to be above

or below the output voltage. This is particularly useful in our four-cell target, as the input range will fluctuate from six to below four volts. The fly in the ointment for this topology is that it inverts the polarity of the output voltage; voltages negative to ground are obtained.

Thus, the best solution would be the SEPIC regulator, which also allows input voltages to be above or below the regulated output voltage, while maintaining the polarity. The SEPIC topology provides an additional and very substantial advantage: There is no direct DC path between the input and the output, therefore shorting the output will not cause very high currents to flow, even if the controller IC itself fails. One of the reasons for the SEPIC topology not being very popular is that the feedback loop is more difficult to compensate, but the selected controller IC takes care of it.

Regulator Description

The heart of the switch mode regulator is a LM3578 device, which is part of National Semiconductor's family of Simple Switcher® devices. As its name implies, National has done a superb job of creating a product line which is full-featured, yet simple to use.

The LM3578 is a little more adaptive than other family members which are dedicated to a single topology. The device provides a very novel feedback scheme, which allows simple loop compensation for this topology, which is not particularly easy to stabilize for all voltage input/loading conditions.

This removes one of the

Table 2. Parts List

Designator	Description	Digi-Key p/n
R1a, b	0.33 1/4W 5% 1210 SMT resistor	P0.33SCT
R2	220K 1/8W 5% 1206 SMT resistor	P220KECT
R3	40.2K 1/8W 1% 1206 SMT resistor	P40.2KFCT
R4	10.0K 1/8W 1% 1206 SMT resistor	P10.0KFCT
R5	31.6K 1/8W 1% 1206 SMT resistor	P31.6KFCT
C1	2200 pF 10%, 1206 SMT ceramic capacitor	PCC222BCT
C2	20 pF 5%, 1206 SMT ceramic capacitor	PCC200CCT
C3	2200 pF 10%, 1206 SMT ceramic capacitor	PCC222BCT
C4	4.7 uF, 6.3V, size A Tantalum capacitor	PCS1475CT
C5a, b	4.7 uF, 6.3V, size A Tantalum capacitor	PCS1475CT
C6a, b	4.7 uF, 6.3V, size A Tantalum capacitor	PCS1475CT
L1	150 uH inductor Miniature Hi Current	M5820
L2	100 uH inductor Miniature Hi Current	M5818
D1	1N5817 Schottky diode	1N5817CT
IC1	LM3578 switch-mode controller, 8-DIP	LM3578AN

Miscellaneous Parts:

Four-cell AA battery holder, SPST switch, hookup wire, ferrite beads.
Contact the author at HYPERLINK E-Mail: garciaviesca@worldnet.att.net for board availability.

Unicorn Electronics


Components & More!

1142 State Route 18
Aliquippa, Pa. 15001

www.unicornelectronics.com

Celebrating our 17th Year Of Service !!

DIODE/TRANSISTOR TESTER KIT




This dynamic tester allows checking of transistors & diodes in circuit. Identifies NPN or PNP transistors. Checks all types, small or large power. Identifies anode or cathode of diodes.

STOCK#	1-9	10-24	25+
DT100K	24.99	23.74	21.37

STOCK#	1-9	10-24	25+
DT100K	24.99	23.74	21.37

SINGLE TURN TRIMPOT



- 1/2 Watt
- 10% Tolerance
- 3/8" Square
- TO-5 Grid
- Top Adjustment
- Bourns 3386P or equal

STOCK#	DESCRIPTION	1-24	25-99	100+
PO150	50 ?	.59	.56	.50
PO1100	100 ?	.59	.56	.50
PO1500	500 ?	.59	.56	.50
PO11K	1K ?	.59	.56	.50
PO12K	2K ?	.59	.56	.50
PO15K	5K ?	.59	.56	.50
PO110K	10K ?	.59	.56	.50
PO120K	20K ?	.59	.56	.50
PO150K	50K ?	.59	.56	.50
PO1100K	100K ?	.59	.56	.50
PO1200K	200K ?	.59	.56	.50
PO1500K	500K ?	.59	.56	.50
PO11M	1 Meg ?	.59	.56	.50

ANTI-STATIC FOAM CLEANER



A thick, foaming cleaner for use in static sensitive applications. Safe for plastics and fiberglass. Use on computer cases and all office equipment. Also cleans soft fabrics. 5 oz. aerosol can.

STOCK#	1-9	10-24	25+
SB1102	1.99	1.89	1.70

STOCK#	1-9	10-24	25+
SB1102	1.99	1.89	1.70

What Do We Have ?

- I.C.'s
- Oscillators
- Crystals
- Diodes
- Tools
- Laser Diodes
- Vises
- Resistors
- Capacitors
- Connectors
- Trimpots
- Kits
- Vises
- LED's
- Transistors
- And more!

TELEPHONE KIT




Build this high-tech, see-thru plastic telephone. Learn theory on how telephones work. Flashing neon lamps when phone rings. Redial system and wall mount included. Comes complete with manual.

STOCK#	1-9	10-24	25+
K30	15.99	15.19	13.67

STOCK#	1-9	10-24	25+
K30	15.99	15.19	13.67

FM MICROPHONE KIT

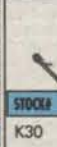

Transmit your voice on any FM radio. Range up to 1000'. Case included.

STOCK#	1-9	10-24	25+
K30	15.99	15.19	13.67

STOCK#	1-9	10-24	25+
K30	15.99	15.19	13.67

ANTI-STATIC CLEANER




General purpose cleaner for use in static sensitive applications. Safe for plastic and fiberglass. 1.75 oz. non-aerosol bottle.

STOCK#	1-9	10-24	25+
SB1101*	.99	.94	.85

STOCK#	1-9	10-24	25+
SB1101*	.99	.94	.85

HEAT SINK

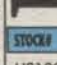


- Thermalloy # 6073
- TO-220 type
- .75" square x .375" high

STOCK#	1-24	25-99	100+
HS1001	.19	.18	.16

STOCK#	1-24	25-99	100+
HS1001	.19	.18	.16

PEAKING COIL

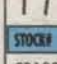

- TDK # H301CLR391
- 390 uH
- .375" diameter


STOCK#	1-24	25-99	100+
SB1037	.15	.14	.13

STOCK#	1-24	25-99	100+
SB1037	.15	.14	.13

ORDER TOLL FREE! - 1-800-824-2432 • FAX ORDERS - 724-495-7882

NO SHIPPING CHARGES !!!

41 WATT SWITCHING



- Input - 115/230V
- Outputs - +5V @ 3.75 Amps
- +12V @ 1.5 Amp
- -12V @ .4 Amp
- Size - 5.25" W x 7" L x 2.50" H

STOCK#	1-9	10-24	25+
PS1003	9.99	9.49	8.54

STOCK#	1-9	10-24	25+
PS1003	9.99	9.49	8.54

www.unicornelectronics.com

11 PIECE COMPUTER TOOL KIT




11 piece kit containing:

- 3/16" & 1/4" nut driver
- 3 prong parts retriever
- Tweezer
- 3/16", 1/4", #1 & #2 phillips reversible screwdriver
- T-10 & T-15 reversible screw driver
- 14-16 pin IC inserter
- 1/8" flat screwdriver
- Black vinyl zippered case

STOCK#	1-9	10-24	25+
TK1100	19.99	18.99	17.09

STOCK#	1-9	10-24	25+
TK1100	19.99	18.99	17.09

PROTOBOARD DESIGN STATION

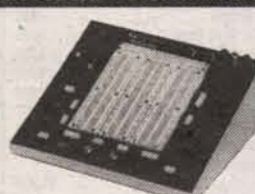


- The total design workstation including expanded instrumentation, breadboard and power supply
- Ideal for analog, digital and micro processor circuits
- 8 logic probe circuits
- Function generator with continuously variable sine, square, triangle wave forms, plus TTL pulses
- Triple power supply offers fixed 5 VDC supply plus 2 variable outputs - +5 - 15 VDC and -5 - 15 VDC
- 8 TTL comp. LED indicators, switches
- Pulsers
- Potentiometers
- Audio experimentation speaker
- Multiple features in one complete test instrument saves hundreds of dollars needed for individual units
- Unlimited lifetime guarantee on breadboard sockets

STOCK#	1-9	10-24	25+
PB503	299.99	284.99	256.49

STOCK#	1-9	10-24	25+
PB503	299.99	284.99	256.49

SLIDE DIP SWITCHES

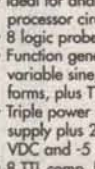

- SPST
- 50 VDC @ 100 ma
- Numbered switches
- .100" spacing

STOCK#	DESCRIPTION	1-24	25-99	100+
SW4S	4 Position	.59	.56	.50
SW5S	5 Position	.59	.56	.50
SW6S	6 Position	.59	.56	.50
SW7S	7 Position	.59	.56	.50
SW8S	8 Position	.59	.56	.50
SW10S	10 Position	.69	.66	.59
SW12S	12 Position	.69	.66	.59

STOCK#	DESCRIPTION	1-24	25-99	100+
SW4S	4 Position	.59	.56	.50
SW5S	5 Position	.59	.56	.50
SW6S	6 Position	.59	.56	.50
SW7S	7 Position	.59	.56	.50
SW8S	8 Position	.59	.56	.50
SW10S	10 Position	.69	.66	.59
SW12S	12 Position	.69	.66	.59

RCA JACK



- PC Mount
- Vertical or rt. angle
- Metal body

STOCK#	1-24	25-99	100+
CORCA	.19	.18	.16
CORCARA	.19	.18	.16

STOCK#	1-24	25-99	100+
CORCA	.19	.18	.16
CORCARA	.19	.18	.16

PADDLE SWITCH



- SPDT/off-on
- 3 amps @ 125 VAC
- Solder tail
- 9/16" x 7/8" mounting

STOCK#	1-24	25-99	100+
SW1004	.39	.37	.33

STOCK#	1-24	25-99	100+
SW1004	.39	.37	.33

PROTOLAB




A state of the art electronics lab for your PC. You can build & experiment with actual circuits, choosing from an unlimited number of components. Then, analyze your circuits with built-in high-tech instruments. This complete electronics lab simulates thousands of dollars worth of parts and instruments. Plus you get a unique experiment book. Easy to use, menu driven, mouse controlled circuits come alive on your screen. You can't blow up your 'lab' because it's fool-proof & safe on your PC!

STOCK#	1-9	10-24	25+
PROTOLAB	49.99	47.49	42.74

STOCK#	1-9	10-24	25+
PROTOLAB	49.99	47.49	42.74

PRINTER CLEANING KIT

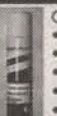

Contains:

- 100 ml safety solvent spray
- 10 G.P. wipes
- Static reducing cloth
- Disposable gloves
- Brush

STOCK#	1-9	10-24	25+
SB1108*	1.99	1.89	1.70

STOCK#	1-9	10-24	25+
SB1108*	1.99	1.89	1.70

INFRA-RED COLLIMATOR PEN



A low power collimator pen containing a GaAlAs laser diode. Pen delivers 2.5mW @ 820nm. Operating voltage of 2.2-2.5V @ 90-150mA is designed for lower power applications. The stainless steel case measures .11 mm in diameter and 27 mm long.


STOCK#	1-9	10-24	25+
SB1052	49.99	47.49	42.74

STOCK#	1-9	10-24	25+
SB1052	49.99	47.49	42.74

EPROMS

STOCK#	1-24	25-99	100+
2732A-20	5.49	5.22	4.70
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
27C64-15	2.99	2.84	2.56
27C64-15	4.79	4.55	4.10
27C256-15	2.99	2.84	2.56
27C512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	2.79	2.65	2.39
27C020-15	3.49	3.32	2.99
27C040-12	5.49	5.22	4.70
27C080-12	10.99	10.44	9.40

CHOKE

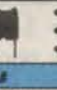

- Postage stamp type
- .375 W x .500 H
- 10 uH @ 0.5 A

STOCK#	1-24	25-99	100+
SB1070*	.12	.11	.10

STOCK#	1-24	25-99	100+
SB1070*	.12	.11	.10

ELECTRONIC TEST EQUIPMENT BOUGHT & SOLD

90 DAY WARRANTY PARTS & LABOR • 10 DAY RIGHT OF RETURN, OPEN ACCOUNTS


Altech 360D11, Frequency Syn., 0.1-2GHz	\$800	HP 8672A/01, Signal Generator, 2-18GHz	\$5,000
Altech 7615, Noise Source, 28VDC, 0.1-1.5GHz	\$250	HP 8697A, RF Plug-In, 26.5-40GHz	\$250
Altech Type 32, Precision Attenuator, 0-100dB	\$300	HP 8743A, Reflection Transmission Test Set	\$200
Argosystems AS210, Frequency Calibration System	\$2,000	HP 8743A/018, Reflection Transmission Test Set, 18GHz	\$300
Austron 2100R, Loran-C Frequency Monitor	\$500	HP 8750A, Storage Normalizer, Includes Cable	\$250
Austron 2110, Disciplined Frequency Standard	\$500	HP 8756A, Scalar Network Analyzer	\$1,500
Bird 4381, RF Power Analyser, Opt. 832	\$200	HP 8903B, Audio Analyzer, Opt. 001	\$2,500
Boonton 25A, Millivoltmeter Calibrator	\$100	HP 8970A, Noise Figure Meter	\$4,000
Boonton 82AD, Modulation Meter	\$650	HP E3617A, DC Power Supply, 0-40V, 1A	\$250
Boonton 92B0, Digital RF Millivolt Meter	\$250	HP K486A, Power Sensor, 18-26.5GHz	\$100
Boonton 102B, Signal Generator, 45-520MHz	\$500	HP P486A, Power Sensor, 12.4-18GHz	\$100
Boonton 518-A4, Q Standard	\$100	HP X486A, Power Sensor, 8.2-12.4GHz	\$100
Boonton 2500, DC Range Calibrator	\$250	Hughes 8010H, TWT Amplifier, 3-8GHz	\$1,000
Boonton 4200/4E, Power Meter with Sensor	\$200	Hunttron HTR 1005B, Tracker Component Tester	\$300
Boonton 4200/4G, Power Meter Sensor, 0.1-26.5GHz	\$200	Keithley 192, Programmable DMM, 6.5 Digits, HP/IB	\$600
Boonton 4220/51013, Power Meter with Sensor	\$600	Keithley 195A, Digital Multimeter	\$300
Boonton 4300, Power Meter, 2 Channel	\$1,200	Keithley 614, Electrometer	\$700
Brüel & Kjær 1612, Bandpass Filter	\$250	Krohn-Hite 3202, Filter, LP, HP, BP, Unused	\$350
Calif. Inst. 101T, AC Power Source	\$400	Leeds & North 1091, Capacitor Decade, .001uF-1uF	\$150
Eaton 380K11, Frequency Synthesizer, 1-2000MHz	\$2,000	Micronetics NSI-52640W, Noise Source, 26.5-40GHz	\$350
EIP 371, Source Locking Microwave Counter, 18GHz	\$1,000	Narda 5082, High Directivity Bridge, 2-18GHz	\$300
EIP 545A, Microwave Counter, Opt. 02, 05, 08	\$1,000	Narda 5292 Directional Coupler, 1-18GHz	\$200
EIP 931, Microwave Source, 0.1-18.6GHz, Opt. 9320	\$6,000	PMI 1018B, Peak Power Meter	\$200
ESI 296, Auto LCR Meter	\$800	Racal Dana 1515, Delay Pulse Generator	\$500
Fluke 515A, Portable Calibrator	\$800	Racal Dana 1992, Frequency Counter, High Stab.	\$500
Fluke 540B, Thermal Transfer Standard	\$500	Racal Dana 9082P, Signal Gen. 1.5-520MHz	\$400
Fluke 6010A, Frequency Synthesizer, 10Hz-11MHz	\$300	Racal Dana 9303, True RMS RF Level Meter	\$500
Fluke 6080A/AN Frequency Syn., 5-1024MHz	\$4,000	Racal Dana 9515, Universal Counter, HP/IB, Opt. 41	\$200
Fluke 8922A, True RMS Voltmeter	\$250	Sencore TF30, Super Cricket Transistor Tester	\$200
Fluke A55, Thermal Converter	\$200	Simco A300, Aerostat Anti-static	\$100
FTS 1150/001, Frequency Standard	\$400	Tek 11A72, Vertical Amp, 2 Channel, 1GHz	\$1,000
General Microwave 478A, Peak Power Meter	\$700	Tek 134, Probe Amplifier for P6021 & P6022	\$100
General Radio 1557, Vibration Calibrator	\$400	Tek 1420, NTSC Vectorscope	\$500
Gigatronics 600/8-12, Frequency Synthesizer	\$1,000	Tek 1470, NTSC Color Sync & Test Sig. Generator	\$500
Gigatronics 600/10-18, Frequency Synthesizer	\$1,500	Tek 1502, TDR, Opt. 4, Chart Recorder	\$1,000
Gigatronics 910, Frequency Synthesizer, .05-26GHz, Opt. 0306	\$8,000	Tek 1503/0105, TDR, Scale in Meters	\$1,000
Guideline 9154C, Transvolt Standard Cell	\$300	Tek 176, Pulsed High Current Fixture for 576	\$500
Guideline 9577, Precision DMM, 7.5 Digits	\$300	Tek 178, Linear IC Test Fixture, For 577	\$150
Hitachi V-212, Scope, 20MHz, Dual Trace	\$200	Tek 2336, Scope, 100MHz, Dual Trace	\$700
HP 11590A, Bias Network	\$250	Tek 2432, Scope, Digital, 300MHz, 4 Channel, HP/IB	\$2,000
HP 11604A, Universal Extension	\$100	Tek 2445B/10/12, Scope, 150MHz, 4 Trace, HP/IB	\$1,800
HP 11605A, Flexible Kit	\$100	Tek 2465, Scope, 300MHz, 4 Channel	\$1,800
HP 11638A, Calibration Kit, Type N	\$600	Tek 305DMM, Scope, 10MHz, Dual Trace, DMM, battery	\$500
HP 11665B, Modulator	\$250	Tek 4041, System Controller, GPIB	\$200
HP 11869A, Adapter for Plug-In 8350A/B	\$350	Tek 464, Scope, 100MHz Dual Trace, Storage	\$400
HP 11970A, Harmonic Mixer, 26.5-40GHz	\$800	Tek 465, Scope, 100MHz Dual Trace	\$400
HP 11970K, Harmonic Mixer, 18-26.5GHz	\$800	Tek 492, Spectrum Analyzer, Opt. 01/02	\$4,000
HP 11970Q, Harmonic Mixer, 33-50GHz	\$800	Tek 492/02, Spectrum Analyzer	\$3,500
HP 1600A, Logic Analyzer w/pods	\$400	Tek 492BP, Spectrum Analyzer	\$8,500
HP 1630D, Logic Analyzer w/pods	\$500	Tek 496P, Programmable Spectrum Analyzer	\$4,000
HP 1631D, Logic Analyzer, Digital Scope w/pods	\$700	Tek 5A13N, Differential Comparator	\$250
HP 16510B, Logic Analyzer Card, 16500A System	\$500	Tek 5A20N, Differential Amp	\$100
HP 16530A/16531A, Digital Scope Card, 16500A System	\$500	Tek 604, XY Monitor	\$100
HP 214B, Pulse Generator	\$1,000	Tek 7D20, Programmable Digitizer PI	\$600
HP 33102A, Microwave Switch, 100MHz-18GHz	\$100	Tek AA501, Distortion Analyzer	\$800
HP 3314A, Function Generator, Opt. 001	\$2,000	Tek DC503, Universal Counter Timer TM500	\$100
HP 3325A, Function Generator	\$1,000	Tek DC504, Counter/Timer TM500	\$100
HP 3325A/0102, Function Gen., Opt. 01/02	\$1,500	Tek DM502A, Autoranging DMM	\$150
HP 33322H, Programmable Attenuator, DC-18GHz	\$250	Tek FG501, Function Generator, 1MHz	\$100
HP 3400A, RMS Voltmeter, 10Hz-10MHz	\$200	Tek FG502, Function Generator, 1Hz-11MHz	\$250
HP 3403C, True RMS Voltmeter	\$200	Tek P6046, Differential Probe	\$300
HP 3455A, Digital Multimeter	\$300	Tek P6201, FET Probe Kit, 900MHz	\$400
HP 3456A, Digital Multimeter	\$600	Tek P6204, 1GHz FET Probe	\$300
HP 346A, Noise Source, 10MHz-18GHz	\$800	Tek P6430, Temperature Probe	\$100
HP 3468A, Multimeter, 5.5 Digits	\$400	Tek PG508, Pulse Generator, 50MHz	\$300
HP 3586C, Selective Level Meter, 50Hz-32MHz	\$600	Tek PS503A, Dual Power Supply	\$150
HP 4140B, Picammeter, DC Source	\$2,000	Tek SC502, Scope, 15MHz, Dual Trace	\$200
HP 4274A, Multi-frequency LCR Meter, Opt. 001, 002, HP/IB	\$3,000	Tek SC504, Scope, 80MHz, Dual Trace	\$500
HP 436A/022, Power Meter, HP/IB	\$500	Tek SG502, Sig. Gen. 5Hz-50KHz	\$200
HP 5005B, Signature Multimeter	\$350	Tek SG5010, Programmable Oscillator	\$800
HP 5006A, Signature Analyzer	\$300	Tek TDS410, Digitizing Oscilloscope, 150MHz	\$3,000
HP 5316A, Universal Counter, Opt. 004	\$200	Tek TG501, Time Mark Generator	\$200
HP 5334A/020, Universal Counter w/DMM	\$600	Tek TM503, 3 Slot Power Module	\$100
HP 5335A/010, Frequency Counter	\$600	Texscan SSG2000, Freq. Syn., 100KHz-2GHz, AM, FM	\$1,800
HP 5335A/030, Frequency Counter, 1300MHz	\$800	Ungar 4624, Solder, Desolder Station	\$250
HP 5340A, Frequency Counter, 18GHz	\$600	Vaihalli 2000, Auto Digital Watt-Ammeter	\$200
HP 5340A, Frequency Counter w/Opt. 01/02/011	\$1,000	Vu-Data 5110, Semiconductor Tester, In/out Circuit	\$150
HP 5342A, Microwave Counter	\$400	Wavetek 143, 20MHz Function Generator	\$200
HP 5345A, Frequency Counter, Opt. 012	\$400	Wavetek 166, Pulse Function Generator, 50MHz	\$500
HP 5350A/010/002, Microwave Frequency Counter	\$2,000	Wavetek 178, 50MHz Programmable Waveform Syn.	\$1,000
HP 54100D, Digital Scope, 1GHz	\$2,000	Wavetek 180, Sweep Function Generator	\$200
HP 54200A, Digital Storage Scope	\$800	Wavetek 185, Sweep Function Gen. .0001-5MHz	\$400
HP 6112A, Power Supply, 0-40V, 0.5A	\$200	Wavetek 186, 5MHz Phase Lock Generator	\$200
HP 8015A, Pulse Generator, 1Hz-50MHz, 30V	\$500	Wavetek 1084, Signal Gen. Sweeper, 3.5-4.5GHz	\$300
HP 8165A, Programmable Signal Source, .0001-50MHz	\$1,000	Wavetek 1910, XY Monitor, Dual Trace	\$400
HP 8165A, Programmable Signal Source, Opt. 02/03	\$1,200	Wavetek 452, Filter, Dual Hi/Low, 1Hz-10KHz	\$450
HP 8350B, Sweep Oscillator Mainframe	\$2,000	Wavetek 7530A, FFT Spectrum Analyzer 0-100KHz	\$500
HP 83540A, RF Plug-In, 2-8.4GHz	\$1,200	Wavetek 907, Signal Generator, 7-11GHz	\$600
HP 83545A, RF Plug-In, 5.9-12.4GHz	\$1,200	Wavetek 955, Micro Source, 7.5-12.4GHz, AM, FM, Sweep	\$1,000
HP 83592C, RF Plug-In, 0.1-20GHz	\$8,000	Wiltron 560A, Network Analyzer	\$800
HP 8410C/8412B, Network Analyzer	\$800	Wiltron 560-7K50, RF Detector, 10MHz-40GHz	\$400
HP 8411A, Frequency Converters	\$250	Wiltron 560-97A50, SWR Autotester, 0.1-18GHz	\$500
HP 8414A, Polar Display	\$300	Wiltron 610D, Sweeper Mainframe	\$250
HP 8445B, Spectrum Anyz., Automatic Pre-Selector	\$300	Wiltron 610D/6237D, Sweep Generator, 2-18GHz	\$800
HP 8505A, Network Anyz. w/8501A & 8503A, Opt. 05	\$4,000	Wiltron 6213D, RF Plug-In, 10MHz-4.2GHz	\$400
HP 85021B, Directional Bridge, 10MHz-26.5GHz	\$1,200	Wiltron 6219D, RF Plug-In, 2-8GHz	\$200
HP 85027B, Directional Bridge, 10MHz-26.5GHz	\$1,200	Wiltron 6223D, RF Plug-In, 4-12.4GHz	\$250
HP 8557A/180TR, Spectrum Analyzer, 0.1-350MHz	\$1,000	Wiltron 6229D, RF Plug-In, 7.9-18.5GHz	\$300
HP 8559A/182T, Spectrum Analyzer, 0.1-21GHz	\$2,500	Wiltron 62FF75, VSWR Bridge, 10-1000MHz	\$150
HP 8559A/853A, Spectrum Analyzer, Digital, .01-21GHz	\$3,500	Wiltron 6647A-20/02/03, Programmable Sweep Generator	\$4,000
HP 8565A, Spectrum Analyzer, 0.1-22GHz	\$3,500	Wiltron 6NF50, Autotester, 1-1500MHz, for 640	\$100
HP 8565A, Spectrum Analyzer, 0.1-22GHz, Opt. 100	\$4,000	Wiltron 7B50, Detector, 1-1500MHz, for 640	\$100
HP 8566A, Spectrum Analyzer	\$20,000		
HP 8569A, Spectrum Analyzer, 10MHz-22GHz	\$5,000		
HP 86241A, RF Plug-In, 3.2-6.5GHz	\$400		
HP 86260A, RF Plug-In, 12.4-18GHz	\$400		
HP 86290A, RF Plug-In, 2-18GHz	\$1,200		
HP 86290B, RF Plug-In, 2-18GHz	\$1,400		
HP 8643A, Synthesized Frequency Generator 26-1030MHz	\$8,000		
HP 8656B, Signal Generator, 1-990MHz, AM/FM	\$2,000		
HP 8660C, Freq Syn w/86603A & 86635A, 2.6GHz	\$2,500		
HP 86601A, RF Plug-In, 110MHz	\$200		
HP 86602A, RF Plug-In, 1300MHz	\$500		
HP 86603A, RF Plug-In, 2600MHz	\$1,000		
HP 86632A, Modulation Plug-In	\$200		

MONTHLY CLEARANCE SALE

➔ WILTRON 610D SWEEP GENERATOR MAINFRAME SALE PRICE \$100.00 — MANY PLUG-INS TO CHOOSE FROM ➔

HELPS INSTRUMENTS

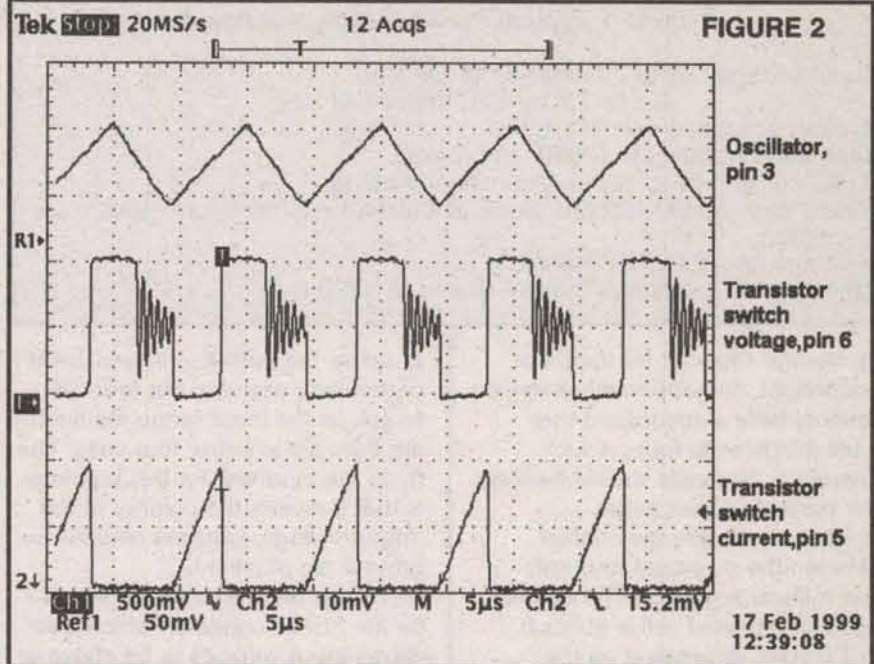2631 Hillside Ave., Norco, CA 91760
909-279-7347 • FAX 909-279-7347



Relevant waveforms at five-volt DC input and a load of 65 mA. These waveforms may change with different input voltages and/or load currents.

SEPIC's drawbacks. It also allows the frequency to be determined by an external capacitor, which is very useful in this project since the SEPIC topology requires two inductors, and choosing the highest allowable frequency will minimize their size. Provision for setting the current limit is performed by an external resistor.

Figure 1 shows the complete schematic of the supply. Attached to U1's pin 4, C1 is the timing capacitor, which sets the internal oscillator to run around 100 KHz, which clocks the pulse width modulator. This, in turn, drives the output transistor. In this topology, the transistor's collector switches to ground the node at L1 and C5, simultaneously allowing current to build up at L1 and for capacitor C5 to pump current into L2, with the charge previously stored at C5.

At this point of time, D1 is reverse biased, and the charge stored at C6 supplies current to the load. During the next phase, the transistor releases the node, and the current stored in L1 both recharges C5 and flows into diode D1, which becomes forward biased.

At the same time, the current stored in L2 starts flowing into the diode. The sum of both L1 and L2 currents supplies the load and replenishes the charge on filter capacitor C6. The cycle then repeats itself. Figure 2 shows some relevant scope waveforms.

Feedback stability compensation is achieved with R2, C2, and C3. Resistor R1 sets the transistor's current limit, and R4 provides feed-forward compensation for varying battery voltages.

You may have asked yourself by now how come R1, C5, and C6 are implemented with two paralleled devices instead of using a single device of the appropriate value. The reason is that through these components a fairly high current at high

frequency passes; to maximize efficiency, it is good practice to parallel devices, as it will reduce parasitic losses. Besides, the devices employed are surface mount, which usually come in multiples of 5 or 10 pieces.

Rather than discard the unused parts, it is better to employ them. Typical performance is summarized in Table 1. Since this is a hobbyist circuit and cannot control the assembly methods or the components used, the circuit performance is not guaranteed and should be taken as reference only.

Building the Circuit

As this project is intended for portable devices, compact size and low weight are important considerations. To meet these considerations, while reducing interference emissions and maximizing efficiency, surface mount components are strongly suggested. SMD's leadless components behave extremely well at high frequencies. And, to effectively use SMD components, a printed circuit board should be employed, as shown in Figure 3.

Some leaded components are also utilized in this project. The board is a mere 1.95" x 1.50" and is half the height of a battery pack, so it should fit comfortably in any handheld enclosure. A parts list is shown in Table 2.

Don't despair if you have not assembled SMD devices before. For ease of assembly, the SMD components chosen for the board are the largest available — the 1206 size. You'll have to solder them first before assembling the leaded components.

SMD assembly requires a fine point, low wattage iron, tweezers, and fine 63/37 solder. A small magnifying glass to check solder quality is very helpful. Assembling SMD devices presents some challenge

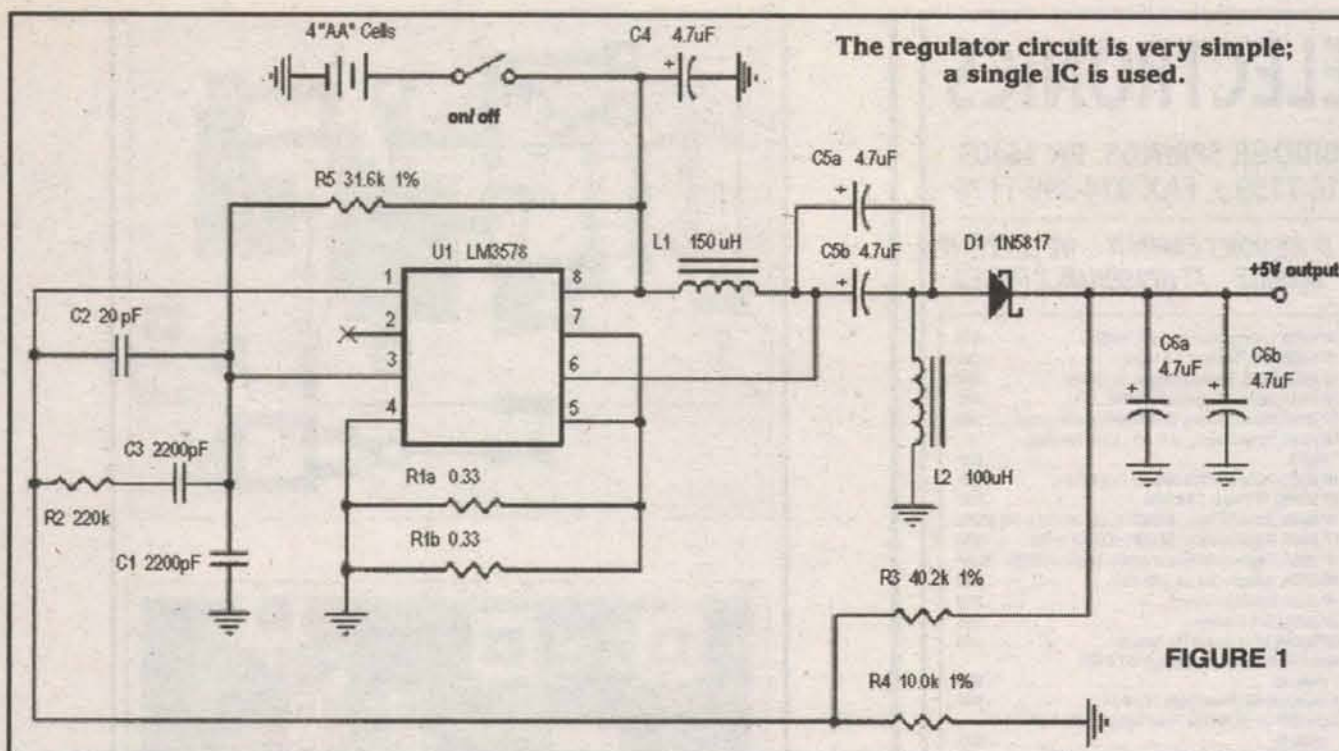


FIGURE 1

since they are not mechanically secure to the board as you try to solder them.

An easy way to solder them to the board is a three-step process: First, slightly wick with solder just one of the board pads and, while keeping the pad warm with the iron, attach the component. The component is secured now to the board, which frees one hand. Second, you solder the opposite side of the component. Lastly, you come back to

the first side — which may have a poor solder joint — to retouch it and to achieve a bright nice solder.

Tantalum capacitor polarity is particularly important, and it is marked with "+" signs on the board.

Leaded components are assembled next. Although the board has plated thru holes, for good assembly practice ensure that the devices are soldered to the component (top) side, as all signals run there. This recommendation extends to

the IC pads. You may need to retouch a few pads. The bottom layer is mostly used as a ground plane. The diode's polarity is marked with an arrow. The battery pack and the on/off switch are assembled outside the board.

After doublechecking your assembly, it is time to test the circuit prior to hooking it up to a digital circuit. Switch-mode power supplies always require a load to function properly so, for testing purposes,

attach a 68-ohm, one-watt resistor to the output. Power-up the supply using fresh alkaline or fully charged NiCad batteries. With a voltmeter, ensure that the output voltage is correct. Now you are ready to hook up a real load.

A note about switch-mode regulators: they produce high frequency ripple on the output. The capacitor values as shown in the schematic will produce about 400 mV ripple worst case, with full load and minimum input voltage. Supplemental capacitance may be added to the regulator or at the point of load to reduce ripple. The latter solution is preferable, as it will also provide some necessary decoupling to the load.

Although this project does not produce excessive EMI due to the tight layout and generous ground plane, if interference is detected, just slip a ferrite bead through both the output leads. And a last recommendation: Always doublecheck that batteries have not been installed backwards.

To avoid efficiency penalties due to the voltage drop of a series diode, reverse polarity protection has not been provided in this project. If you determine that the feature is essential, employ only a Schottky diode as it provides a lower forward voltage drop. **NV**

See PCB patterns on page 70.

Metric
Equipment Sales, Inc.

800-432-3424

Fax: 510-264-0886
www.metricsales.com

RENT • BUY • SELL
Yes, we will buy your surplus equipment!

Scopes, Meters, Analyzers, Power Supplies, Signal Generators, Counters, Recorders and more

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu, Wavetek, Keithley, and more

Test & Measurement Instruments

Over 7000 Models • 6-Month Warranty
Save 30-90% • 5-Day Free Trial

Write in 74 on Reader Service Card.



ALL CABLE NEEDS
SE HABLAN ESPAÑOL
CONVERTERS
ALL BRANDS WITH REMOTE

TOLL FREE ORDER LINE:
1-800-361-4586

ALSO

HOOK-UP HELP LINE:
1-847-233-0621

NO ILLINOIS SALES



ACQUED

COMPETITIVE PRICING

PARENTAL LOCKOUT AVAILABLE

HOURS: Mon. thru Fri. 9-6, Sat. 10-2
30-DAY MONEY BACK GUARANTEE
1 YEAR WARRANTY

KDE ELECTRONICS CORP.
P.O. BOX 1494, ADDISON, IL 60101

Write in 72 on Reader Service Card.

Nuts & Volts Magazine/April 1999 **69**

AST GLOBAL ELECTRONICS

24529 STATE HWY. 408, CAMBRIDGE SPRINGS, PA 16403
VOICE 814-398-8080 • 1-888-216-7159 • FAX 814-398-1176

VIEW COMPLETE LISTING AT:
<http://www.astglobal.com>

IF WE DON'T CARRY IT ... WE'LL FIND IT
QUICKLY ... AT REASONABLE PRICES.

B&K 3020, Sweep/Function Generator, 2MHz (Sine, Square, Triangle).....	\$175
EIP 545, Microwave Counter 18GHz.....	\$500
ESI DP1311, Variable Resistor, 100K max 1K/Step.....	\$75
Fluke 332B, DC Voltage Standard.....	\$350
Fluke 382A, Voltage/Current Calibrator.....	\$400
Fluke 540B, Transfer Standard w/AS-2 Voltage Plug-in.....	\$475
Fluke 845AB, Null Detector/Micro Voltmeter 1uV-1000VDC.....	\$375
Fluke 893A, AC/DC Differential Voltmeter 0 to 1100 Volts, AC/DC, 0.1%DC, 0.5%AC, 1uV Resolution.....	\$75
Fluke 3330B, Constant Current/Voltage Calibrator.....	\$325
Fluke 5100B, Multifunction Calibrator, Opt. 0305.....	\$2,800
Fluke 5100B, Multifunction Calibrator.....	\$2,700
Fluke 5200A, Programmable AC Calibrator.....	\$1,000
Fluke 5215A, Precision Power Amp.....	\$900
Fluke 6070A, Synthesized RF Signal Generator.....	\$1,400
200kHz-520MHz.....	\$1,400
Fluke 8000A, DMM 3-1/2 Digit.....	\$50
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145
Fluke 8050A, DMM 4-1/2 Digit w/o Battery Pack.....	\$145
Fluke 8520A, DMM 5-1/2 Digit.....	\$275
Fluke 8800A, DMM 4-1/2 Digit w/o Battery Pack.....	\$100
Fluke 8800A, DMM 5-1/2 Digit.....	\$125
Fluke 9010A, Micro System Troubleshooter.....	\$375
Gigatronix 6061A, Synthesized Signal Generator.....	\$2,200
10KHz-1050MHz.....	\$475
HP 141T, Spectrum Analyzer Mainframe.....	\$1,000
HP 141T, Spectrum Analyzer w/8552A/8553B, 1KHz-110MHz.....	\$1,200
HP 141T, Spectrum Analyzer w/8552B/8553B, 1KHz-110MHz.....	\$1,200
HP 141T, Spectrum Analyzer w/8552B/8556A, 20Hz-300KHz.....	\$1,100

INVENTORY REDUCTION SALE PRICES SLASHED UP TO 50%

HP 141T, Spectrum Analyzer w/8552B/8554B, 1KHz-1.2GHz.....	\$1,700
HP 141T, Spectrum Analyzer w/8552B/8555A, 10MHz-18GHz.....	\$1,900
HP 180TR, Scope Mainframe.....	\$250
HP 204B, Oscillator, 5Hz-1.2MHz, 5VRMS.....	\$100
HP 204C, Oscillator, 5Hz-1.2MHz, 5VRMS.....	\$125
HP 214A, Pulse Generator, 0.6V-100V.....	\$200
HP 334A, Distortion Analyzer.....	\$275
HP 339A, Distortion Analyzer w/Low Distortion Oscillator.....	\$950
HP 350D, Attenuator.....	\$75
HP 400EL, AC Voltmeter, 10Hz-10MHz.....	\$150
HP 400FL, RMS Voltmeter, 20Hz-4MHz, 100uV-300V.....	\$175
HP 415E, SWR Meter.....	\$100
HP 4276A, LCZ Meter.....	\$1,700
HP 432A, Power Meter w/Cable/47dB, .01-18GHz Sensor.....	\$350
HP 432A, Power Meter w/o Cable/Sensor.....	\$150
HP 435A, Power Meter w/o Sensor/Cable.....	\$100
HP 436A, Power Meter w/o Cable/Sensor.....	\$475
HP 651B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 652B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 654A, Oscillator, 10Hz-10MHz, 90dB Attenuator.....	\$195
HP 1630D, Logic Analyzer wipods.....	\$550
HP 3312A, Function Generator, 1Hz-13MHz.....	\$490
HP 3325A, Programmable Frequency Synthesizer 1Hz-32MHz.....	\$950
HP 3330B, Automatic Synthesizer, 20Hz-13MHz.....	\$295
HP 3400A, True RMS Voltmeter, 10Hz-10MHz, 1mV-300V.....	\$125
HP 3403C, True RMS Meter, AC/DC/KB 100MHz.....	\$275
HP 3406A, RF Voltmeter, 50uV-3V, 1.2GHz.....	\$200
HP 3455A, DMM 5-1/2 Digit.....	\$250
HP 3456A, DMM 6-1/2 Digit.....	\$525
HP 3466A, DMM 4-1/2 Digit, AC/Battery, 5 Function.....	\$175
HP 3478A, DMM 5-1/2 Digit.....	\$525
HP 3551A, Portable Transmission Test Set.....	\$550
HP 3575A, Digital Phase Gain Meter 1Hz-13MHz.....	\$500
HP 3580A, Spectrum Analyzer, 5Hz-50KHz, LED Readout.....	\$850
HP 3580A, Spectrum Analyzer, 5Hz-500KHz, Mechanical.....	\$500
HP 3581A, Wave Analyzer, 15Hz-50KHz.....	\$300
HP 3770A, Amplitude/Delay Distortion Analyzer.....	\$300
HP 3779B, Primary MPX Analyzer.....	\$500
HP 3781B, Pattern Generator.....	\$250
HP 5318A, Counter, 100MHz, HP1B.....	\$350
HP 5328A, Counter, 100MHz w/DVM/Opt. 021.....	\$200
HP 5328A, Counter, 500MHz.....	\$250
HP 5334A, Counter, 100MHz, Opt. 010 Oven.....	\$500
HP 5340A, Counter, 18GHz (niche).....	\$600
HP 5345A, Counter, 500MHz.....	\$450
HP 5345A, Counter, 500MHz, HP-1B.....	\$650
HP 59307A, VHF Switch.....	\$100
HP 6112A, Power Supply, 40V @ 5A (metered).....	\$150
HP 6202B, Power Supply, 40V @ 75A (metered).....	\$150
HP 6203B, Power Supply, 7.5V @ 3A (metered).....	\$150
HP 6205B, Power Supply (dual), 0-40V @ 3A, 0-20V @ 8A (metered).....	\$175
HP 6206B, Power Supply, 0-60V @ 1A (metered).....	\$200
HP 6208B, Power Supply, 10V @ 100A (metered).....	\$300
HP 6255B, Power Supply, 40V @ 3A (metered).....	\$200
HP 6256A, Power Supply, 40V @ 6A (metered).....	\$200
HP 6289A, Power Supply, 0-40V @ 1.5A (metered).....	\$175
HP 6294A, Power Supply, 0-60V @ 1A (metered).....	\$200
HP 8011A, Pulse Generator, 1Hz-20MHz.....	\$175
HP 8013B, Pulse Generator, 1Hz-50MHz.....	\$275
HP 8015A, Pulse Generator, 1Hz-50MHz 30V.....	\$400
HP 8091A, Rate Generator (1GHz) w/8092A Delay Generator (1GHz) w/8093A Output Amp w/15401A & 15400A.....	\$1,000
HP 8165A, Programmable Sig Source, 1mHz-50MHz.....	\$1,450
HP 8180A, Data Generator.....	\$350
HP 8350B, Sweep Oscillator Mainframe.....	\$1,550
HP 8410B, Network Analyzer Mainframe.....	\$200
HP 8411A, Frequency Converter, 11-18GHz.....	\$250
HP 8411A/D18, Frequency Converter, 11-18GHz.....	\$375
HP 8414A, Polar Display.....	\$225

HP 8443A, Tracking Generator, 1KHz-110MHz.....	\$275
HP 8445B, Auto Preset, 1.8-18GHz.....	\$350
HP 8557A/180TR, Spectrum Analyzer, .01-350MHz.....	\$850
HP 8601A, Sweep Generator, 1-110MHz.....	\$400
HP 8614A, Signal Generator, 800-2400MHz, AM/FM Leveled.....	\$300
HP 8618A, Signal Generator UHF, 1.8-4.5GHz, +10-126dB, AM/FM.....	\$300
HP 8620C, Frame w/8622B Sweeper .01-2.4GHz.....	\$1,150
HP 8624D, RF Plug-in, 5.9-9.0GHz.....	\$225
HP 8640B, Signal Generator, 5-1050MHz, Opt. 002/001 or 003.....	\$1,800
HP 8640B, Signal Generator, 5-512MHz, Opt 001 or 003.....	\$700
HP 8660C, Frequency Synthesizer w/86603A/86601A/86632B.....	\$2,500
HP 8743A, Reflection Test Set, 2-12.4GHz.....	\$200
HP 8901A, Modulation Analyzer.....	\$800
HP 59303A, D/A Converter.....	\$125
HP 59501A, HP-1B Isolated D/A Converter.....	\$100
Keeco ATE15-50M, Power Supply, 0-15V @ 50A (metered).....	\$500
Keeco ATE55-5M, Power Supply, 55V @ 5A.....	\$350
Keeco BVP100-4M, Bi-Polar Power Supply, 0-100V @ 4A (metered).....	\$375
Keeco JCE 36-15MVPT, Power Supply, 0-36 @ 15A (metered).....	\$275
Keeco JCE 36-3MVPT, Power Supply, 0-36 @ 3A (metered).....	\$175
Krohn-Hite 3202R, Dual Channel Tunable Filter, 20Hz-2MHz, High Pass, Low Pass Band Reject.....	\$200
PG506A, Calibration Generator Plug-in.....	\$500
Polarad SPNH, Signal Generator, 20Hz-20KHz.....	\$275
Polarad SPNL, Signal Generator, 1Hz-600KHz.....	\$200
Racal Dana 9303, True RMS RF Level Meter.....	\$200
Rockland 1022F, Dual Hi/Lo Filter.....	\$125
Rockland 5100, Synthesizer, DC-2MHz, .001 Hz Resolution.....	\$325
Sencore SC61, Scope (100MHz) w/New Probes, Dual Trace.....	\$750
Sencore SC61, Scope (100MHz) w/o Probes, Dual Trace.....	\$400
Sencore SC3100, Waveform Analyzer (like new).....	\$1,800
Sencore TVA92, TV Video Analyzer.....	\$1,100
Sencore VG91, Universal Video Generator.....	\$1,200
Sorenson DCR-80-5A, Power Supply, 80V @ 5A (metered).....	\$375
SRL 112B, PLO/PRF Synthesizer.....	\$75
Tek DC503, Plug-in Counter Universal, 100MHz.....	\$150
Tek DM501A, Plug-in DMM, 4-1/2 Digit.....	\$175
Tek DM502, Plug-in DMM, 4-1/2 Digit.....	\$150
Tek FG501, Plug-in Function Generator, .001Hz-1MHz.....	\$175
Tek PG501, Plug-in Pulse Generator, 5Hz-50MHz.....	\$175
Tek PS501-1, Plug-in Power Supply.....	\$150
Tek PS503A, Plug-in Power Supply Triple.....	\$175
Tek OIG-502, Plug-in Optical Impulse Generator (unused).....	\$500
Tek T922, Scope (15MHz), Dual Trace, nice.....	\$175
Tek TMS03, Power Module, 3 Slot.....	\$125
Tek TMS04, Power Module, 4 Slot.....	\$150
Tek TMS06, Power Module, 6 Slot.....	\$200
Tek 7A16A, Plug-in (225MHz), Single Trace Amp.....	\$75
Tek 7A18, Plug-in (75MHz), Dual Trace Amp.....	\$50
Tek 7A19, Plug-in (600MHz), Single Trace Amp.....	\$100
Tek 7A26, Plug-in (200MHz), Dual Trace Amp.....	\$100
Tek 7B50A, Plug-in (150MHz), Time Base.....	\$75
Tek 7B53A, Plug-in (100MHz), Dual Time Base.....	\$100
Tek 7B70, Plug-in (200MHz), Time Base.....	\$50
Tek 7B80, Plug-in (400MHz), Delayed Time Base.....	\$100
Tek 7B92A, Plug-in (500MHz), Dual Time Base.....	\$125
Tek 7D11, Plug-in Digital Delay.....	\$125
Tek 7D13, Plug-in DMM 3-1/2 Digit.....	\$100
Tek 7D15, Plug-in Counter/Timer, DC-225MHz.....	\$175
Tek 7L13, Spectrum Analyzer, 100KHz-1.8GHz.....	\$1,200
Tek 7S11, Plug-in Sampling Unit.....	\$125
Tek 134, Current Probe Amp.....	\$75
Tek 453, Scope (60MHz), Dual Trace.....	\$175
Tek 465, Scope (100MHz), Dual Trace.....	\$425
Tek 465B, Scope (100MHz), Dual Trace.....	\$475
Tek 466, Scope (100MHz storage), Dual Trace.....	\$575
Tek 475, Scope (200MHz), Dual Trace.....	\$475
Tek 475A, Scope (250MHz), Dual Trace.....	\$625
Tek 485, Scope (350MHz), Dual Trace.....	\$700
Tek 492, Opt. 2 Spectrum Analyzer 50KHz-21GHz.....	\$3,400
Tek 520A, NTSC Vectorscope.....	\$400
Tek 2213, Scope (60MHz), Dual Trace.....	\$375
Tek 2215, Scope (60MHz) Dual Trace.....	\$450
Tek 2235, Scope (100MHz) Dual Trace.....	\$650
Tek 2247A, Scope (100MHz) Dual Trace w/Counter/Timer/Voltmeter.....	\$1,550
Tek 2336, Scope (100MHz) Dual Trace.....	SPECIAL \$525
Tek 2445, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,100
Tek 2445A, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,400
Tek 2465, Scope (300MHz), 4-Channel Cursor Readout.....	\$1,600
Tek 7104, Scope (1GHz), Dual Trace.....	\$1,200
Tek 7603, Scope Mainframe (100MHz).....	\$150
Tek 7704A, Scope Mainframe (250MHz).....	\$150
Tek 7904, Scope Mainframe (500MHz).....	\$225
Wavelek 145, Pulse/Function Generator, .0001-20MHz.....	\$300
Wavelek 185, Lin Log Sweep Generator, .0001Hz-5MHz.....	\$300
Wavelek 288, Synthesized Function Generator, 20Hz-20MHz (unused).....	\$800
Wavelek FG3B, Sweep/Function Generator 2Hz-100KHz (unused).....	\$200


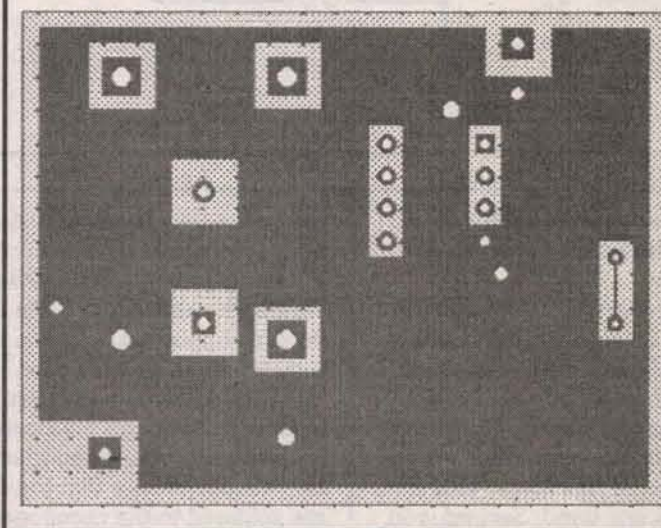
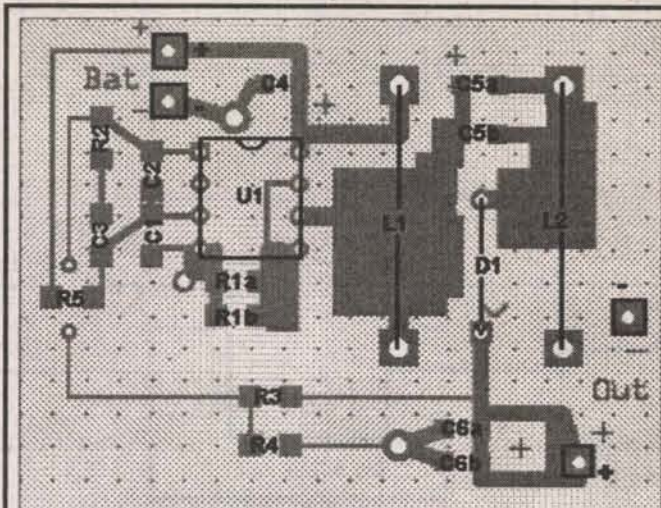
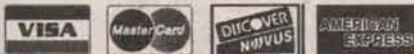
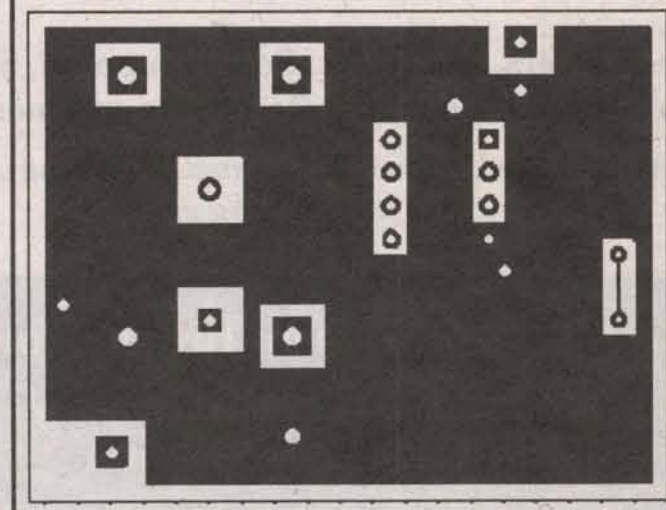


FIGURE 3. Suggested board layout. Components and most of the traces go on the top layer, the bottom layer is used mostly as ground plane.

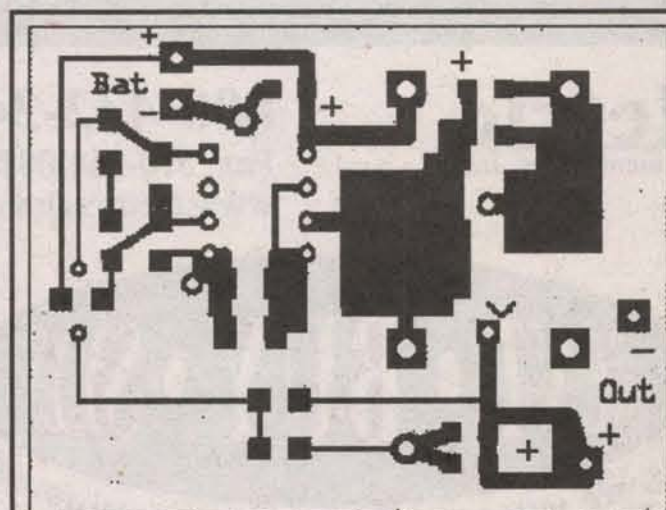

• 60-DAY WARRANTY
• 10-DAY RIGHT OF RETURN
• SATISFACTION GUARANTEED

TECH FORUM

Continued from page 55

ANSWER TO #29910 - FEB. 1999

Part 1: A quick and expensive solution would be to check AVTinc at www2.ari.net/avt-inc/. They have OBDII related adaptors for desktops and portable computers.

Look for a 19-pin D-type connector under the area of the steering wheel, under the dash if you see it, then your vehicle OBDII compatible. Once you have the software and hardware, you will be able to

read/erase fault codes and get a live sensor and actuator data with the engine running.


On vehicles with automatic transmissions, the same computer also runs the transmission such as Fords E4OD or GMs 4L80E that are used in the pickup trucks. Some Chrysler/Dodge products use a separate computer to run the transmission.

Part 2: If you are going to do it

yourself, you would still need the diagnostic equipment, plus another computer to watch the serial data and record the commands that are used to activate the vehicle's computer to send the fault codes or to send the live data from the sensors and actuators. Either way, it's going to be expensive.

Dan Hockey
via Internet

Identifying Data Link Terminals

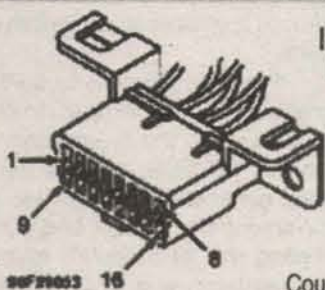

Courtesy of Chrysler Corp.

DATA LINK CONNECTOR TERMINAL IDENTIFICATION

Terminal	Wire Color	Function
3	Violet/Brown	CCD Bus (+)
4	Black/Light Green	Ground
5	Black/White	Ground
6	Light Green	SCI Receive
7	Pink	SCI Transmit
11	White/Black	CCD Bus(-)
14	Pink/Light Blue	BCI Receive (TCM)
16	Pink	Fused B+

ANSWERS TO #2994 - FEB. 1999

The ZN414 and ZN416 are obsolete, so buy them while you can.

They have been available recently from Nuts & Volts advertiser Halted Specialties:

Halted Specialties Co.

3500 Ryder St.

Santa Clara, CA 95051

408-732-1573

1-800-442-5833 orders

<http://www.halted.com/>

They also have a Sacramento location.

If Halted runs out, Oatley Electronics (Australia) sells an MK484 part which they claim is the same as a ZN414:

Oatley Electronics

P.O. Box 89

Oatley NSW 2223

Australia

oatley@world.net

Phone: +61-2-9584-3563

Fax: +61-2-9584-3561

<http://www.oatleyelectronics.com/>

David DiGiacomo
San Francisco, CA

ANSWERS TO #2994 - FEB. 1999

AM radio receiver chips ZN414 are available from Ocean State Electronics, 1-800-866-6626 for \$7.95.

They also carry FM Receiver ICs TDA7000 for \$9.95, and Signetics NE602AN mixer-oscillator for superhet receivers and ferrite antennas. Look at their ad in *Nuts & Volts Magazine* in the Feb. '99 on page 42.

Joe Kish
Clackamas, OR

[orders] or at 513-531-4499 (information).

Brian Piller
Baxter Springs, KS

ANSWERS TO #39912 - MAR. 1999

Although you could design and construct a suitable voltage step-up circuit (Maxim sells several DC-DC step-up controller ICs), it would be much easier to purchase a 12VDC to 115VAC inverter at one of the discount stores.

These are small electronic products that plug into the car's cigarette lighter and provide 115V/60 Hz main power for PCs, TVs, VCRs, or whatever. Be sure to get one that has a wattage rating that exceeds your worst case

load.

On a trip to Walmart, I found a 140-watt unit (more than enough power for a typical laptop PC) for \$39.00, but if you watch for a sale you can get low wattage units for as little as \$25.00.

Thomas Black
Folsom, CA

ANSWERS TO #39912 - MAR. 1999

Probably the safest way to secure 18 volt DC for your computer would be to purchase three small to mid-size six-volt lead-acid batteries from a supplier such as H&R, 1-800-848-8001 which start at \$8.00 each for the four-amp hour lead-acid

Y2K PLANNING? USING BATTERIES? GET AN E-METER™



From \$200

OEM's: Call for free applications assistance.

Fits 2" hole

Up to 1000 Amps
@500 Volts!

Here's why every Y2K battery bank needs an **E-Meter** - the world's most popular DC energy monitor. The multi-colored bar graph shows battery status at a glance. The bright digital display reports Volts, Amps, Amp-hours, Time Remaining, - even Kilowatt-hours. Reports historical information including battery Charge Efficiency, number of discharge cycles, deepest depth of discharge and average depth of discharge. The optional Low Battery contact can optimize your generator run times for charging and RS232 output is available for remote sites.

Don't be afraid of Y2K - be ready with an E-Meter!

Cruising Equipment

5245 Shilshole Ave. NW, Seattle, WA 98107

(206) 782-8100 Fax: (206) 782-4336

<http://www.cruisingequip.com>

Write in 119 on Reader Service Card.

Quality Computer Towers AT Style Cases (Not ATX)

Full (260 Watt)(11 bays) \$35.00

Mid Size (230 Watt)(7 bays) \$20.00

Mini Size (230 Watt)(6 bays) \$17.00



SCSI Hard Drives

New 2.1 Glg Seagate
\$80.00

New Micropolls 1.53 glg
\$50.00

IBM 4 Glg WIDE Differential
\$100.00 ea.



Dealer Special Designer Mouse

3 button Serial Mice

\$120.00 per case of 80



Lots of MicroWave Goodies in Stock

Brand New Wavetek 907AF Frequency Generators

Range 7-12.4 GHz \$900.00

HP Direct Reading Frequency Meter

#R532A 26.5-40 GHz New \$450.00



SMA Attenuators - Stepper Motors

Electro Mavin

800-421-2442 or FAX 310-632-9867

E-Mail john@mavin.com

Visit Our Web Site for More Info and Specials

<http://www.mavin.com/mavin.html>

WE BUY & SELL!

C and H

50 YEARS IN BUSINESS

SALES COMPANY

2176 E. Colorado Blvd.
Pasadena, CA 91107

Take advantage of our special purchase on TEST EQUIPMENT

HIGH PRECISION DIGITAL MULTIMETER

FLUKE, Model 8810A. LED readout. 5-1/2 digit auto-ranging multimeter. Has ohms converter and true rms options. Accuracy AC volts 0.1% to 0.5%, AC rms 0.2% to 0.4%, DC volts 0.01%, ohms 0.02% to 0.2%. Max input voltage 1000 VDC or peak AC. Input impedance to 1 to 1000 meg ohms depending on range. Power input voltage 115 VAC 50/60 Hz. Has built-in carrying handle that can be used as a tilting base. Dimensions: 9-1/4" wide x 14-1/2" deep (including carrying handle) x 3-1/4" high.

Stock #TE9805

\$295.00

3-1/2 DIGIT DIGITAL MULTIMETER

FLUKE, Model 8000A. LED readout. Classic digital multimeter. Ideal companion to our Stock #TE9800 counter. Measures AC/DC volts/milliamperes plus ohms. Input range 0-200 mV to 1200 volts, 0-200 uA to 2000 mA. 0 to 2000 K ohms. Portable unit with carrying handle which also can be used as a tilt stand. Input impedance 10 meg ohms. Max. input voltage 1200 VDC or rms. Accuracy DC volts 0.1% of input +1 digit. AC volts 0.5% of input +2 digits 45 Hz to 10 KHz. Input power 115 VAC 50 to 400 Hz 5 watts. Dimen.: 8-1/2" wide x 12" deep (including carrying handle) x 2-1/2" high.

Stock #TE9801

\$75.00

MILLIOMETER

HEWLETT PACKARD, Model 4328A. Designed to measure very low resistances. Measurement range 1m ohm to 100 ohms. Resolution 20 u ohms. Analog meter readout. Ideal for measuring contact resistance of switches or relays. This unit is also useful for measuring the resistivity of semiconductor devices. (Requires special 4 terminal probes which are not supplied, but probably are available from Hewlett Packard.) Power input: 115-230 VAC 48-66 Hz, 5 VA max. Dimensions: 5-1/8" wide x 11-1/2" deep x 6-1/2" high.

Stock #TE9812

\$200.00

200,000 COUNT DIGITAL MULTIMETER, FLUKE, Model 8800A.

LED readout. 6-digit, auto-ranging multimeter. Basic accuracy $\pm 0.05\%$. 15 ranges DC volts: ± 200 mV to ± 1200 V in 5 ranges accuracy $\pm 0.08\%$ or better. AC volts: 2 VAC to 1200 VAC in 4 ranges. Accuracy $\pm 1\%$ or better depending on frequency and range. Resistance 200 ohm to 20 meg ohms in 6 ranges. Accuracy $\pm 0.2\%$ or better. Input impedance: 1000 meg ohms or more on DC ranges, 2 meg ohms on AC ranges. Has complete overload protection and isolated inputs. Power input 110/230 VAC 50/60 Hz 8 watts. Built-in carrying handle that also acts as a tilt-up base. Dimensions: 3-1/2" high x 9" wide x 12-1/2" deep.

Stock #TE9815

\$100.00

3600 RPM DC MOTOR WITH OPTICAL ENCODER PACIFIC SCIENTIFIC, #4VM82-004-4. 30 volts nom. input voltage. Permanent magnet, reversible servo motor. Has Hewlett Packard optical encoder. Ball bearings. No load speed at 30 VDC input is 4600 rpm. No load current 0.75 amp at 60 oz-in load rpm is 3600, current is approx. 6.6 amps. Torque constant is 9.1 oz-in per amp. Rotor inertia 0.0007 oz-in-sec². Terminal resistance 0.89 ohm. Optical encoder is similar to "HEDS 6000" series. Encoder has 1024 counts per revolution, two channel quadrature output. Outputs are TTL compatible. Encoder requires 5 VDC input at less than 50 mA input current. Dual shafts: front shaft is 3/8" dia. x 3/4" long. This shaft is tapped on the end 8X32 tpi. Rear shaft is 1/4" dia. x 7/16" long. This shaft has dual flats that measure approx 3/16" across. Motor has four 8X32 tpi tapped mounting holes on front. A 3-3/16" dia. centering pilot is also provided on the front face. Dimensions: 4" dia. x 5-1/2" long (excluding shafts.)

Stock #DCME9850

\$79.50

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

TOLL FREE: 1-800-325-9465

Write in 120 on Reader Service Card.

TECH FORUM

battery and \$20.00 for the 10-amp battery.

You can charge these batteries individually from your generator, and then connect them in series for your computer. Using this method over the DC to DC converter means that there is a zero power loss due to switching or resistance, with a 99.99% safety factor over voltage fluctuations or parts failure.

The battery is a tried and true method of accomplishing a stable

platform for power especially if every watt is important to you due to your remote living status. Even the best DC to DC converter will waste some power in switching no matter how efficient they have become.

Ni-Cds can also be used and placed in a series/parallel configuration to accomplish both the current and voltage requirements that you seek, but they generally cost more.

Chris
Bieber, CA

ANSWERS TO #2991 - FEB. 1999

These garage door obstacle detectors typically use an infrared LED light source in the transmitter with a matched infrared receiver. The most effective arrangement (used in TV and VCR remotes) pulses the IR LED at around 40KHz. This helps to avoid interference from ambient light sources.

Several manufacturers make small receiver modules for around \$3.00 which are tuned to accept 40KHz pulsed IR signals, and reject other light sources. They typically run from a 5V supply, and have three pins: +5V, signal, and ground.

One such receiver is the GP1U52X, which is manufactured by Sharp, and is also sold by RadioShack as part #276-0137 or #276-137B. You can find a copy of the data sheet at http://support.tandy.com/support_supplies/17533.htm.

If you want to build transmitter and receiver circuits using this module, there is a lot of information available on the Internet. See <http://www.seattlerobotics.org/>

guide/infrared.html for an example of both transmitter and receiver circuits.

If you have access to a PIC programmer, a very simple circuit can be built using the inexpensive eight-pin PIC 12C508, which is used for both generating the 40KHz signal for driving the IR LED, and for interpreting the IR module's output on the receiving end to detect a valid signal.

A circuit schematic, PCB layout, and PIC source code can be found on the Internet at <http://www.verinet.com/~dlc/projects/botproj.htm>

Note that the circuit described above was originally intended for use as an obstacle detection device for a mobile robot, with both the IR LED and the IR detector module mounted to the PCB.

For your application, you should be able to simply attach the IR LED to the end of a two-wire cable, rather than to the PCB.

For the resistor which is in series with the IR LED, I would try experimenting with different values until you get the desired range.

Regardless of the circuit you choose, if you intend to use this outdoors you will want to ensure that you protect the IR receiver from ambient sunlight as much as possible, since sunlight contains enough IR energy to swamp the receiver, making the IR light coming from the LED virtually indistinguishable.

Under these conditions, you should consider shielding the receiver with a black tube that is opaque to IR light, and placing the LED emitter in such a way as to point into the open end of the tube. It also helps if this tube is threaded on the inside to reduce the amount of ambient light that is able reflect off the inside of the tube and make its way to the receiver. Placing lenses in front of the LED and/or receiver may also help.

For further background information on IR transmitters and receivers, check out <http://www.wirz.com/tutorial/IR/index.html>.

Another good source for IR circuits, in general, is <http://godot.tuniv.szczecin.pl/~mjaskula/tomi/opto.html>.

Mark Winters
Orem, UT

COMPUTER PARTS

www.lapazusa.com

MEMORY UPGRADES

1Mx9-70 SIMM\$10
4Mx9-70 SIMM\$19
1Mx32/36-70 72-pin SIMM (4MB) \$10/15
2Mx32/36-70 72-pin SIMM (8MB) \$19/25
4Mx32/36-70 72-pin SIMM (16MB) \$39/49
8Mx32/36-70 72-pin SIMM (32MB) \$79/89
64M(8x64) SDRAM / PC 100 \$89/92

VIDEO

1MB KIT(2-256x16)2CAS SOJ/ZIP...\$18/35
1MB KIT(2-256x16) 2WE SOJ/ZIP...\$19/36

CACHE

64Kx1-15ns 22-DIP.....\$5.50
32Kx8-25/20/15ns 28-DIP.....\$3/2/2.50
64Kx8-15ns 32-DIP.....\$6
128Kx8-15/20ns 32-DIP narrow. \$12 & up
128Kx8-15/20/25ns 32-DIP wide.\$12 & up

CPU

INTEL 486DX2-66 (5v) CPU.....\$30
INTEL 486DX4-100 (5v) kit CPU.....\$69
INTEL PENTIUM 83MHz OVERDRIVE.....\$85
INTEL PENTIUM 133/166 CPU.....\$54/65

MISC.

LBA CARD. Upgrade your hard drive beyond 540MB without the expense of a new Bios. \$29.95

486DX4 KIT. Upgrade your old 5V 486 CPU with this kit: AMD DX4-100 CPU+5v Adaptor+CPU Fan. \$65.00

MMX ADAPTOR. Allows 3v Pentium boards to accept MMX CPU. Adaptor for Intel or Cyrex CPU. \$30.00

PENTIUM MOTHERBOARD/SYSTEMS SPECIALS
Pentium M/B 133MHz Intel, 512K, 32MB RAM. \$195.00

Pentium II - Intel Celeron 300A, ATX M/B, 1.44 FDD, 2GB-HD, 8MB Video, 56K Fax Modem, 36X CD ROM, Mid tower ATX case. Best value! \$595.00
1-YEAR WARRANTY ON PARTS & LABOR

PACKARD BELL
486 to Pentium motherboards

PRICES SUBJECT TO CHANGE WITHOUT NOTICE - TERMS:
VISA/MC - MINIMUM ORDER \$20 - SHIPPING & HANDLING: \$7 MIN.
ORDER LINE: (800) 586-4199

LA PAZ ELECTRONICS INT'L
P.O. BOX 261095, San Diego CA 92196
TEL (619) 586-7610 FAX (619) 586-1482
e-mail: lapazusa@pobox.com

THIS IS THE ONE YOU HEARD ABOUT!!!

Price:
\$2,499.97

- Mini Mag Reader
- Lightweight (67g)
- Compact (approx. 3-3/8 x 1-1/4 x 1-1/4)
- Operates on CR2032 lithium batteries
- Stores 100 2-track ANSI mag swipes
- Easily downloads to DOS-based PCs
- Mini Reader comes complete w/PC cable, software, batteries & instructions
- Warranty included



To order call:
LIFELINE ELECTRONIX, INC.
(818) 994-1683
Or email us at:
lifelineelectronix@yahoo.com

TECH FORUM

ANSWERS TO #2991 - FEB. 1999

A beam breaking alarm can be fairly easily made with an Infrared (IR) receiver/demodulator module as used for IR remote controls. RadioShack sells an IR receiver module #276-137. It includes an application note with a circuit which will function just as you have described.

I have, in fact, built a garage door entrance alarm using a slightly modified version of this circuit. Referring to the figure, for continuous operation remove S1 and short the connections to it.

A +5 VDC power supply can be substituted for Bt 1, so the transmitter and receiver circuitry can use the same power source. If 5V is used, R1 should be changed from 150 to

50 ohms. The output of the LM567 tone decoder is an open collector (pin 8) and is turned on when the receiver is detecting the modulated IR beam from the transmitter. This means that the output goes high when the beam is broken.

A 4.7K resistor can be substituted for R2, LED 2 if a TTL compatible signal is desired from the tone decoder. Two IR LEDs can be connected in series (R1 is changed to 10 ohms) to get a wider beam pattern and more range between the transmitter and receiver.

In my application, the transmitter and receiver are separated by 20 feet!

Kevin Goodwin
Oceanside, CA


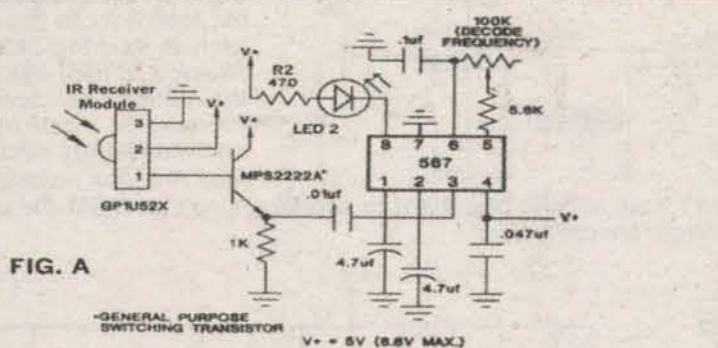


FIG. A

*GENERAL PURPOSE SWITCHING TRANSISTOR
V+ = 5V (6.8V MAX.)

RECEIVER

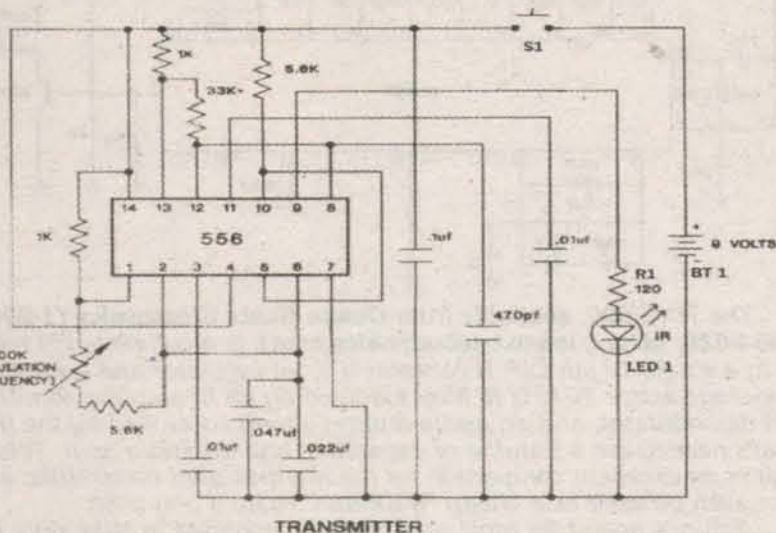

TRANSMITTER


*Ground Pin 6 and adjust to 40kHz +/- 2 kHz from pin 9 with parallel/series resistance

ANSWERS TO #2991 - FEB. 1999

I have used this circuit in a stop watch for the Pinewood Derby, I think it will meet your needs. The parts are all available from RadioShack.

If you need a switch closure, put a buffer and relay at the IR receiver output.

Russell Kincaid
Milford, NH

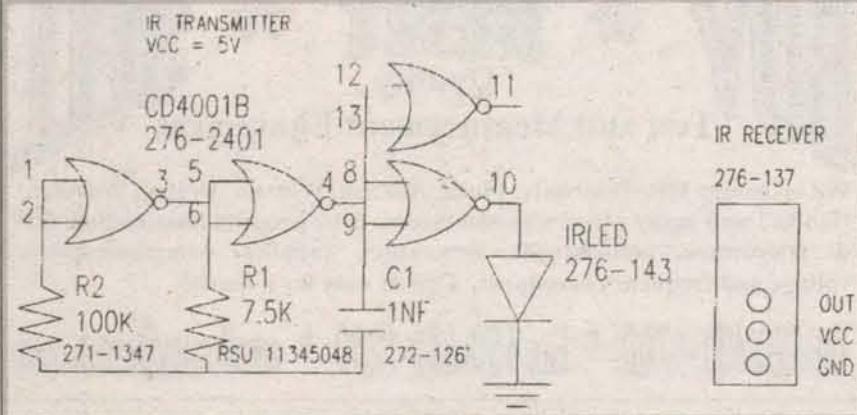

Go Wireless With Our Modules

SILRX/TXM

SILRX — \$26.00 ea.
TXM — \$15.50 ea.

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link-up to a distance of 200m over open ground.

Both units are supplied in space-saving single in-line packages and offer SAW controlled, wide band FM transmission/reception.

The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.



TX2/RX2

TX2 — \$19.50 ea.
RX2 — \$38.50 ea.

The TX2 and RX2 radio transmitter and receiver pair enable the simple implementation of a data link at up to 40kbit/s at distances up to 75m in-building and 300m open ground. Both modules combine full screening with extensive internal filtering to ensure EMC compliance by minimizing spurious radiations and susceptibilities. The TX2 and RX2 modules will suit one-to-one and multi-node wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking.

Because of their small size and low power requirements, both modules are ideal for use in portable, battery-powered applications such as hand-held terminals.



900 MHz
AVAILABLE JAN '99

RPC

RPC — \$99.00 ea.

The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor-intensive low-level packet formatting and recovery functionality, requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.



BiM

BiM — \$69.00 ea.

The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a low-cost solution to implementing a bi-directional short-range radio data link.



Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501

Phone (508) 798-5004 ♦ Fax (508) 798-4782

www.lemosint.com ♦ lemosint@ma.ultranet.com

All products available in either 418 or 433 MHz

Write in 123 on Reader Service Card.

Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

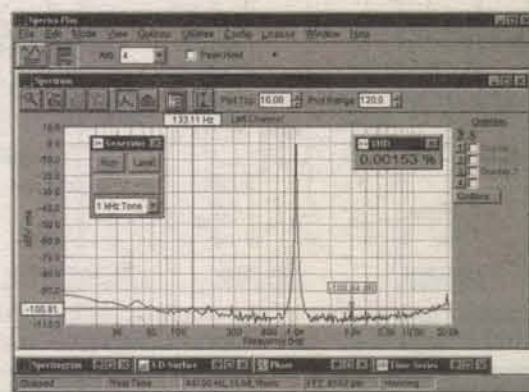- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



Priced from \$299

(U.S. sales only — not for export/resale)

DOWNLOAD FREE 30 DAY TRIAL!

www.spectraplus.com

PHS Pioneer Hill Software
24460 Mason Rd.
Poulsbo, WA 98370
a subsidiary of Sound Technology, Inc.

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

Spectra Plus
FFT Spectral Analysis System

Write in 124 on Reader Service Card.

Nuts & Volts Magazine/April 1999

73

Q & A

• • • • • With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware and software. This column doesn't replace the Tech Forum that you've grown to love and support. Instead, it will supplement it, so feel free to participate as always with your questions and answers. You can reach me at TJBYSERS@aol.com, TJBYSERS@juno.com or by snail mail at Nuts & Volts Magazine, 430 Princland Ct., Corona, CA 91719.

What's Up: Plenty of projects: FM transmitter with latching receiver for alarm applications, a 30-minute watchdog timer, battery-operated phone ring tester, and battery-powered event sequencer. More on hard-to-find parts and schematics, including video game schematics and pinouts. Reader feedback on propane generators.


Mailbox Monitor

Q. Do you know of anyone who builds a device that announces when the mail person has delivered, something similar to Kenton Chun's "Electronic Mail Is In-Dicator" that appeared in the Jan. '98 issue? It's for my Grandpa, who is 84 years old. Every day he walks to the mailbox, nearly 1,000 feet from the house, to check the mail — often more than once. I know the walk is good for him, but after four trips (when the mail is late) he grows weary. Grandpa and I are both experienced ham operators, and neither believe a doorbell transmitter like that described in the Jan. '98 issue can span this distance. Do you have a better solution? (P.S. I'd like to make it for him in time for Christmas, as a present.)

Mike Kirby KB7QWA
via Internet

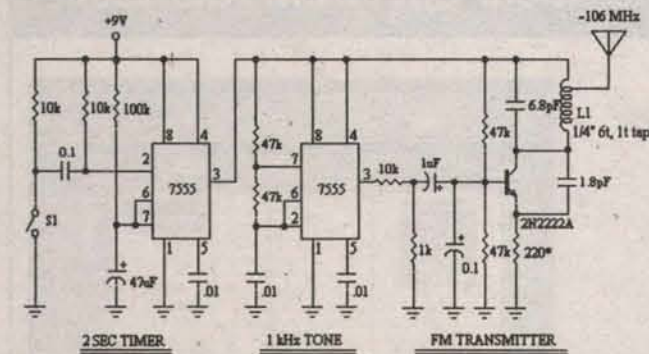
A. I know for a fact that the wireless doorbell chime won't cut it. I have one, and the signal grows weaker with each passing day – it's down to 30 feet now! I know you're under a time crunch, so I didn't have time to test the circuit below. Given the fact that you're a ham, I trust you can cut and try this transmitter without too much trouble.

It's an FM transmitter that should span the 1,000-foot distance; if not, reduce the 220-ohm resistor to 100 ohms to increase the output power. The antenna is a two-foot hank of insulated wire. S1 is a mercury switch




attached to the door of the mailbox. When the door is opened, the switch triggers the two-second timer, which applies power to the

audio and RF oscillators. (The first IC prevents the transmitter from continually sending should the mail carrier leave the door open.) The receiver can be any FM radio tuned to about 106 MHz. You can fine-tune the transmitter's frequency by expanding or compressing the windings of L1. If you're not in the room when the alarm goes off, though, you won't hear the beep. The solution is to add a latching indicator to the receiver. Simply plug the indicator circuit below into the earphone outlet, and adjust the volume control so it responds to the mail only, and not static. If you have a mute/squelch switch, turn it on.

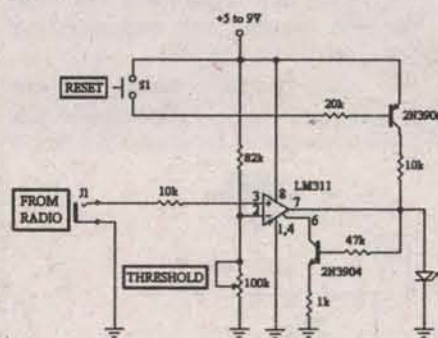

The latch is a simple LM311 comparator with a strobe input. When the comparator output goes high, indicating an alarm tone, it turns on the 2N3904 transistor, which locks the output high. A flashing LED (Radio Shack 276-036) lets you know the mailbox has been opened. Pressing S1 resets the LED and readies the circuit for the next mailbox invasion. If you

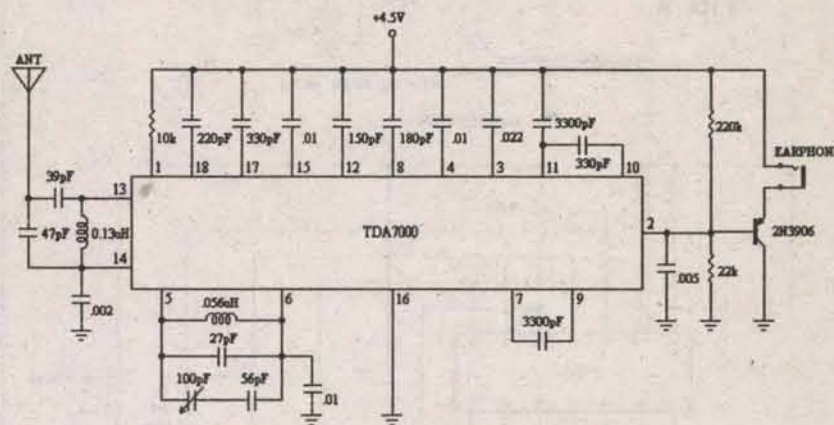don't have a radio you want to sacrifice, you can build the simple FM receiver shown below.



The TDA7000, available from **Ocean State Electronics (1-800-866-6626; <http://www.oselectronics.com>)**, is a complete FM receiver in a single 18-pin DIP. It contains a local oscillator and a mixer, a two-stage active 70-KHz IF filter followed by an IF amplifier/limiter, an FM demodulator, and an audio muting circuit controlled by the IF. All that's needed are a handful of capacitors and an audio amp. This circuit is an excellent companion for the mailbox alert transmitter, and can even be used as a cheap "Walkman" radio if you wish.

(Editor's note: Like most questions, I responded to Mike's via E-Mail. A few days later he mailed back to say that the transmitter works just fine, and that he had it working in time for Christmas.)

EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- www.m2l.com

Fast - Programs 27C010 in 23 seconds

Portable - Connects to PC Parallel Port

Versatile - Programs 2716-080 plus EE and flash (28, 29) to 32 pins

Inexpensive - Best for less than \$200

- Correct implementation of manufacturer specified algorithms for fast, reliable programming.

- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web.

- Full over current detection on all device power supplies protects against bad chips and reverse insertion.


- Broad support for additional devices using adapters listed below.

Available Adapters

EP-PIC1 (C55x61,82x71,84)	\$49.95
EP-PIC84 (16K62-5.72-4)	\$39.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751,C51)	\$39.95
EP-11E (68HC11,C51)	\$59.95
EP-11D (68HC71D13)	\$39.95
EP-16 (16bit EPROMs)	\$49.95
EP-Z8 (286E02,3,4,6,7,8)	\$39.95
EP-SEE2 (93x24x,25x,85x)	\$39.95
EP-750 (87C750,1,2)	\$59.95
EP-PEEL (IC722v10,18v6)	\$59.95
EP-1051 (89C1051,2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95

M²L Electronics

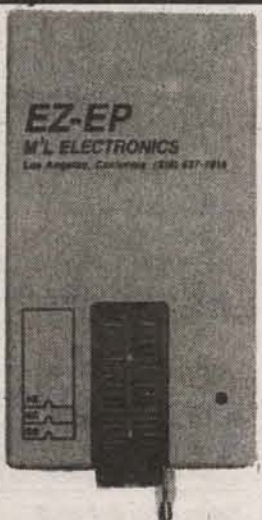970/259-0555
Fax: 970/259-0777
 S Camino Del Rio #119
 Durango, CO 81301
 All orders please add 7%
 sales tax.
<http://www.m2i.com>



Equipment Management Technology

From Acquisition to Disposition

BUY * RENT * SELL
Quality
Test and Measurement Equipment

We inventory HP, Tektronix, Fluke, Anritsu, Wiltron, Iwatsu, Wavetek, GenRad and many other manufacturers. Our product lines include RF & microwave, oscilloscopes, generators, supplies, communications, voltage and frequency standards. Call us now for a quote!

Tel 650-631-1700 * Fax 650-631-1200 * email sales@emt1.com

Carl Breuning
Dartmouth College

$t(\min) = R_1 C_1 \times 2.1 = 21 \text{ min.}$

Quick SMD Removal

Don Florida

Ring My Bell

want. According to a friend of mine at Lucent Technology, the phone line has a static line voltage of 48-54 volts DC. When the phone rings, he says, there is an additional 70 volts of AC that rides on top of the DC and rings the bell. I thought about using a 555 timer at 60 Hz feeding the secondary of a six-volt power transformer, but I'm just fishing here. Does such a circuit exist?

Skip M. Plonka via Internet

The diagram shows a 5V push-to-talk (PTT) interface circuit. It features a 5V supply connected to a 300k resistor, which is in series with a 1.3M resistor. The input signal, labeled "PRESS TO RADIO", is connected to a 10k resistor. The output of the 1.3M resistor is connected to a 300k resistor, which is in series with a 2.2k resistor. The output of the 2.2k resistor is connected to a 1N4148 diode. The output of the 1N4148 diode is connected to a 1N4733A diode. The output of the 1N4733A diode is connected to a VP2110 diode. The output of the VP2110 diode is connected to a VN2110 diode. The output of the VN2110 diode is connected to a "PHONE" input. The output of the 1N4733A diode is also connected to a 1N4733A diode, which is in series with a VP2110 diode. The output of the VP2110 diode is connected to a VN2110 diode. The output of the VN2110 diode is connected to a "PHONE" input. The output of the 1N4733A diode is also connected to a 1N4733A diode, which is in series with a VP2110 diode. The output of the VP2110 diode is connected to a VN2110 diode. The output of the VN2110 diode is connected to a "PHONE" input.

effectively grounding the green lead. When the output logic reverses, Q1 goes off and Q2 goes on, grounding the red lead; on the bottom pair, Q4 turns off and Q3 turns on, connecting the green lead to +V. This creates a 68-volt squarewave which triggers the ringer. The ringer outputs are active when both the 1.3M and 30M inputs are pulled high, either with a push-button switch (S1) or a logic gate. While the schematic shows a five-volt source, you can power the circuit from four 'C' cells without changing any values. The HV421 is available

Do You Repair Electronics?

Repair data for TV, VCR, monitor, audio, camcorder, & more.

Over 100,000 constantly updated problem/solutions plus...

- TechsChat live chat room.
- Private user discussion forums.
- Automated email list server.
- UL/FCC number lookup.
- Hot tips bulletin board.
- Manufacturer information.

To access RepairWorld, direct your internet browser to <http://www.repairworld.com>

RepairWorld.com

Electronix Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878

SOLUTIONS TO YOUR CABLING NEEDS

**Cat.5 -- Enhanced Cat.5 -- USB -- IEEE1284 / 488 / 1394
Firewire -- High-End Monitor -- Manual & Auto Switches
Apple -- Custom Ribbon Cables -- Premise Wiring -- more!
HUGE SELECTION OF SCSI CABLES & ADAPTERS**

Closeout & Overstock Specials (many more at our Website)

DB25M/CN50M SCSI cable 6ft.....\$2.40	AT motherboard power extnd.....\$1.60
IEEE-1284 A-A DB25M/F 6 feet.....\$6.00	6 inch 3.5mm M/M stereo cbl.....\$0.80
PS/2 to AT keybd. Adpt. 1 foot.....\$0.95	Serial 4-head Laplink cable 6ft...\$3.25
Cat.5 14ft. Patch cable, gray.....\$2.45	6P4C surface mount mod jack...\$0.40

Place Your Order Online 24 hrs./day

No minimum order, same day shipping on most orders. A+ and CET technician available to answer your questions.



Northwest Cable & Connector Co.

www.nwcable.com



Phone: (360) 754-3606

Fax: (360) 754-0825



from **NuHorizons Electronics** (888-747-6846; <http://www.nuhorizons.com>), as are the MOSFETs.

More On Obsolete ICs

Q. I'm unable to locate a SL952 IC that is used in the Heath model SM-2420 frequency counter. Do you have information on a source or a substitute IC?

George Rooke
Upland, CA


A. This chip was made by GEC Plessey Semiconductor. The company was recently acquired by Mitel, and the chip was dropped from production. Fortunately, this and many other obsolete and hard-to-find ICs can be obtained from: **Online Technology Exchange, Inc.**, 7100 Gulf Blvd., St. Petersburg, FL 33706. 1-800-606-8459; <http://www.onlinetechx.com>

Video Game Schematics

Q. I have a Sega Genesis game controller with what appears to be a nine-pin female serial connector. My goal is to build an adapter which will allow me to connect my Sega game controller to the joystick port of my PC. The project seems simple enough if I had the pinout diagrams for the Sega Genesis game controller and the joystick port of a SoundBlaster-compatible sound card. Can you provide me with this information or direct me to someone who can?

Dom Franzo
via Internet

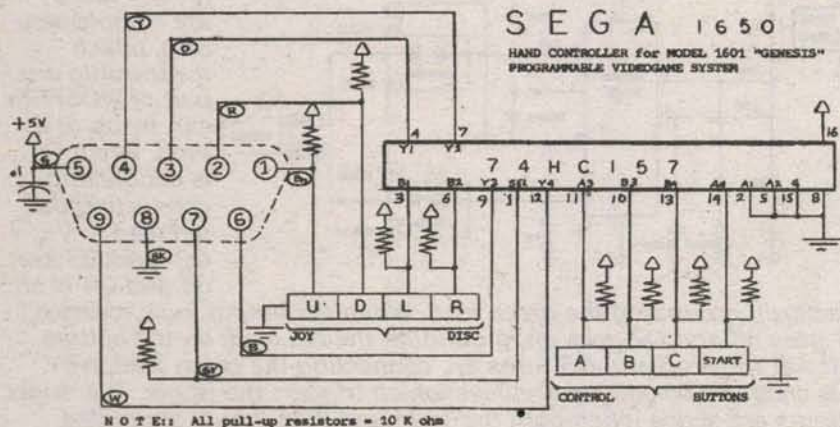A. I'm not so sure it's as simple as wiring one connector to another, but you definitely have to start there. I stumbled across an amazing service, called **Bomarc Services** (307-234-3488; <http://w3.trlb.com/~rollo/bomcat.htm>), that publishes schematics for many consumer products, from radios to TVs to radar — and game controllers. They generate schematics the old-fashioned Howard Sams way — by dismantling the product piece by piece. It's called reverse engineering. If they don't have your particular schematic in stock, they'll gladly create one for you at about \$20.00/hr. if you supply the device (which you get back in working order). For example, a typical two-chip remote control will cost you about \$35.00 to reverse engineer. Here's a sample of their work, which not coincidentally, is a schematic of your Sega Genesis game controller.



Many more like this are available for a reasonably priced \$1.50 each. The product catalogs, divided into 21 categories, cost three for

\$5.00 (refundable with order). Using the schematic above and a quick search of my pinout files produced the following two tables.

SoundBlaster Game Port Pinout

Pin	Function
1	+5V
2	X button, joystick A
3	X potentiometer, joystick A
4	GND
5	GND
6	Y potentiometer, joystick A
7	Y button, joystick A
8	+5V
9	+5V
10	X button, joystick B
11	X potentiometer, joystick B
12	MIDI out
13	Y potentiometer, joystick B
14	Y button, joystick B
15	MIDI in

Sega Genesis Game Controller

Pin	Function
1	UP switch
2	DOWN switch
3	Y1
4	Y2
5	+5V
6	Y3
7	SELECT
8	GND
9	Y4

Now you have to write software to sort the signals out because the Sega controller is programmable. That is, it can do many things depending on how you define the buttons. Fortunately, an engineer in Japan has posted some software clues for the Sega controller at <http://www.hongo.ecc.u-tokyo.ac.jp/~t50942/md6bpad-e.html>. However, I've found this Web link to be unreliable at times, so I took the liberty of posting the opening page, with the software commands, on our Web site (<http://www.nutsvolts.com>) under the original name of md6bpad.htm. This file can be viewed with Microsoft Explorer. While you're at it, check out this Web site (<http://hiwaay.net/~jfrohwel/tech/repair.html>), too.

Mile High PCs

Q. I work for an airline and have a question about power supply frequency, specifically about using aircraft outlets for computers. Most of the 115 VAC outlets look just like house outlets, so the computer can plug in okay. However, the aircraft frequency is 400 Hz, not the 60 Hz you find in homes. I think I once heard you can use transformer-powered 60 Hz equipment on 400 Hz, but not vice versa. Also how would this affect switching power supplies that many PCs now use?

Wayne Anderson
via Internet

A. It's true that most 60 Hz power transformers will work on 400 Hz without a hitch, but not the other way around. Why? It has to do with the metal core. As the frequency decreases, you need more metal. That's why the airlines have gone to 400 Hz. The higher frequency means less metal, which weighs less and takes up less space. Obviously, a 60 Hz transformer has more than enough metal for 400 Hz operation. However, that's presupposing that the AC is converted to DC, and that a 60 Hz timing pulse isn't a requirement. As far as I know, notebook wall chargers will run off 400 Hz.

As for switching power supplies, they are DC-operated, too. Which means, the AC voltage is first converted to high-voltage DC, then to high-frequency AC, and finally back to low-voltage DC.

Mr. NiCd

April 99 SUPER SPECIALS!

THE BEST BATTERIES IN AMERICA!

Packs & Charger for YAESU FT-50R / 40R / 10R:

FNB-40xh 500mAh 7.2v 650mAh \$41.95

FNB-47xh 1800mAh 7.2v 1800mAh \$49.95

FNB-41xh (5w NiMH) 9.6v 1000mAh \$49.95

For YAESU FT-51R / 41R / 11R:

FNB-38 pack (5w) 9.6v 700mAh \$39.95

For YAESU FT-530 / 416 / 816 / 76 / 26:

FNB-26 pack (NiMH) 7.2v 1500mAh \$32.95

FNB-27s (5w NiMH) 12.0v 1000mAh \$45.95

For YAESU FT-411 / 470 / 73 / 33 / 23:

FNB-11 pack (5w) 12.0v 600mAh \$24.95

FBA-10 6-Cell AA case \$14.95

Packs for ALINCO DJ-580 / 582 / 180 radios:

EBP-20ns pack 7.2v 1500mAh \$29.95

EBP-22nh pk (5w) 12.0v 1000mAh \$36.95

EDH-11 6-Cell AA case \$14.95

For ICOM IC-21A / T22-42A / W31-32A / T7A:

BP-180xh pk (NiMH) 7.2v 1000mAh \$39.95

BP-173 pack (5w) 9.6v 700mAh \$49.95

For ICOM IC-W21A / 2GXA7 / V21AT (Black or Gray):

BP-132s (5w NiMH) 12.0v 1500mAh \$49.95

For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:

BP-83 pack 7.2v 600mAh \$23.95

For ICOM 02AT etc & Radio Shack HTX-202 / 404:

BP-8h pack 8.4v 1400mAh \$32.95

BP-202s pack (HTX-202) 7.2v 1400mAh \$29.95

For KENWOOD TH-79A / 42A / 22A:

PB-32xh pack (NiMH) 6.0v 1000mAh \$29.95

PB-34xh pack (5w NiMH) 9.6v 1000mAh \$39.95

For KENWOOD TH-78 / 48 / 28 / 27:

PB-13 (original size) 7.2v 700mAh \$26.95

For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:

PB-6X (NiMH, w/chg plug) 7.2v 1200mAh \$34.95

Mail, phone, & Fax orders welcome! Pay with Mastercard / VISA / DISCOVER / American Express

Call 608-831-3443 / Fax 608-831-1082

Mr. NiCd - E. H. Yost & Company
2211-D Parview Road, Middleton, WI 53562
CALL OR WRITE FOR OUR FREE CATALOG!
Cellular / Laptop / Videocam / Commercial & Aviation packs too!
E-mail: ehyost@midplains.net

5 Axis Robotic Arm Kit

\$195.00 Plus S&H

We make it easy!

You can build this Robotic Arm!


Impressive, fast, accurate, and repeatable motion. Any computer capable of sending 2400 or 9600 baud serial data can control the arm, even a Basic Stamp. This arm makes a great foundation for AI and motion control experiments. Position the arm in an X, Y, Z, grid with a joystick or keyboard using the new RoboMotion for Windows. The kit includes the hardware, structural components, Hitec servos, pre-assembled SSC servo controller, DOS and Windows software, and an illustrated assembly manual. Camouflage paint not included.

We have many more cool robots, check out our web page or ask for our free catalog!

3 Axis Version \$155.00 • Mobile Version \$250.00 • Mobile Robots Book \$48.00

Lynxmotion, Inc.
104 Partridge Road
Pekin, IL 61554-1403 USA
<http://www.lynxmotion.com>

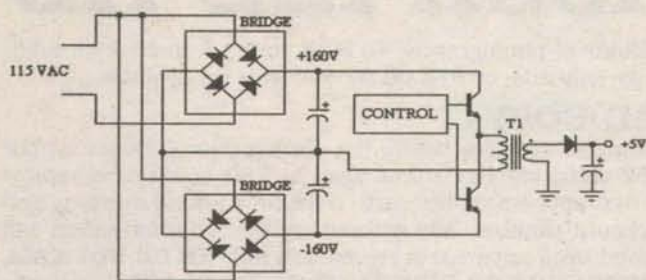Tel: 309-382-1816
Fax: 309-382-1254
sales@lynxmotion.com
tech@lynxmotion.com



This time, the 60 Hz AC is converted to a higher-frequency AC so that the transformer is again smaller and lighter. Since there isn't an input transformer involved, just rectifying

diodes, the switching power supply doesn't care what frequency you input. Will it work off 400 Hz? I don't see why not.

Triplett Manuals and Parts

Q. I have a Triplett Model 801 FET multimeter (analog needle display) which recently died. I suspect that one of the transistors is bad, but few of them have any markings. What I really need is a technical reference manual or schematic to fix it. Unfortunately, I have not been able to locate the Triplett company. Any suggestions?

O.C. Powell WB4WAA
Rocky Mt., NC


A. Triplett Corp., One Triplett Dr., Bluffton, OH 45817 (1-800-874-7538; <http://www.triplett.com>) will send you a copy of the schematic for free. Triplett can also repair your meter (write or call for a quote), or you can order replacement parts and do it yourself (there's a nominal fee for shipping and handling, usually about \$3.00). Before tearing into the instrument, though, see if the problem isn't as simple as a blown fuse. Most Triplett multimeters have two fuses, at least one of which is soldered to the circuit board. Next, look for burned (vaporized) traces, leading to a trail of scorched resistors; this is the second leading cause of failure. Good luck!

Special Effects Timer

Q. I'm in need of a digital timer that has multiple outputs. I want to use it to control the sequence of events in a portable special effects project. It has to be battery operated, or able to use a DC wall transformer, and must have a digital display of the sequence in progress. The output level isn't critical, because all I need is a relay to trigger the event. Two to five outputs would be ideal.

L. Bearden
via Internet

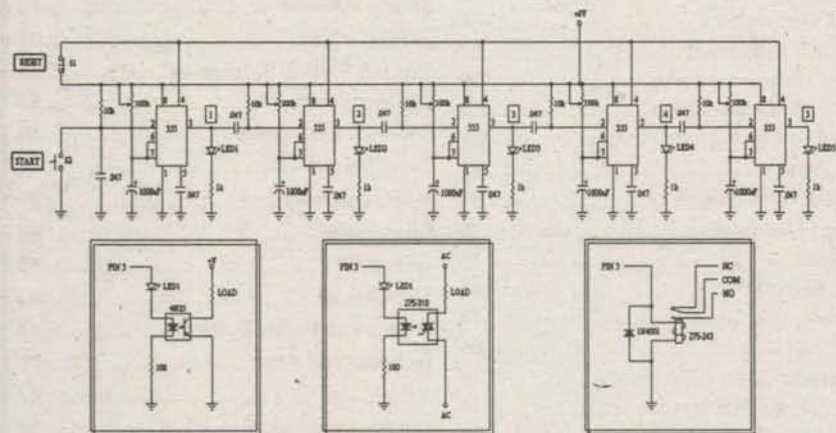A. Not a tall order, but one that you'll have to be careful putting together. First, I'd use a string of CMOS 555 timers (TLC555 or equivalent) for the sequencer. They consume virtually no power, and are inexpensive (less than a buck). A five-stage sequencer looks like this.



Pressing S2 starts the sequencer, and S1 resets it. As each stage times out, the falling edge triggers the next stage. The time between stages is determined by the 100K pot and 1000 uF capacitor, which has a range of a couple of seconds up to about three minutes. As the sequence progresses, one stage turns off, and the next turns on, as indicated by the LED on the output pin (pin 3). This LED can also be used to trigger an optoisolator, to close a relay, or to control an SCR or triac. If you want both a digital indicator and an optoisolator, simply wire the two LEDs in series with an appropriate current-limiting resistor, as shown in the insert boxes. The precaution is that you must very carefully bypass each and every Vcc pin (pin 8) with a 0.1 uF capacitor and the Voltage Control pin (pin 5) with a 0.047 uF capacitor as close to the IC as possible, as shown on the schematic. Also, return all the digital grounds to one point, and the analog (LED or relay) grounds to another, then connect the two grounds together via a single wire. The circuit can be powered with four 'C' cell batteries, or from a six-volt wall transformer, like RadioShack's 273-1454.

Video RAM Requirements

Q. I'm confused about the amount of memory I need on my video card. One sales person tells me 4MB, yet another says 8MB. Can you set the record straight?

Anonymous
via Internet

A. The amount of video RAM needed is directly related to the number of colors and the number of pixels (screen resolution). The wider the color range and the more numerous the pixels, the more memory needed. As a rule, 2MB is the absolute minimum, with 8MB preferred when working in 3D color rendition. Here's a handy chart that spells it out.

Video Graphics Requirements

Palette	Refresh	Resolution	Video RAM
16-bit color	72 Hz	768 x 1024	1.5MB
24-bit color	72 Hz	768 x 1024	2.3MB
32-bit 3D	72 Hz	768 x 1024	6MB
16-bit color	72 Hz	1280 x 1024	2.5MB
24-bit color	72 Hz	1280 x 1024	3.8MB
32-bit 3D	72 Hz	1280 x 1024	10MB
16-bit color	72 Hz	1600 x 1200	3.7MB
24-bit color	72 Hz	1600 x 1200	5.6MB
32-bit 3D	72 Hz	1600 x 1200	14.7MB

MAILBAG

Dear TJ:

For a simpler, less-expensive natural gas/propane conversion mentioned in your Jan. '99 answer ("Push My Button"), look at the <http://www.uscarb.qpg.com/> Web site by **US Carburetion, Inc.**, Atlanta, GA (1-800-553-5608). I haven't used them, but wish I had found the site before buying a natural gas generator.

Jim Edwards
via Internet

Dear TJ:

I just read your Jan. '99 column, and as a licensed electrician would like to comment on Howard Epstein's unattended generator starting situation. Over the years, I've seen several "do-it-yourself" emergency power systems and most are real "time bombs." Specifically, if he's planning to connect the generator to the building's wiring system, then he must use a "Transfer Switch" (either manual or automatic). Without one, a dangerous "Backfeed" situation can occur that will feed his generated power back into the utility grid. This can injure utility workers and damage the generator (remember, you'll essentially be feeding other customers via the common grid) not to mention the problems caused if the utility returns and bucks his "plant." An alternative is to install a totally separate wiring system dedicated to the generator. In both cases, he should have a qualified electrician handle the work, follow the National Electric Code, and be inspected by the local Electrical Inspector (or Building Department).

John Henshaw
via Internet

Weeder Technologies

ON-LINE
CATALOG

www.weedtech.com

Pro-Kit

PO Box 2426, Ft. Walton Beach, FL 32549

Voice/Fax 850-863-5723

Stackable RS-232 Kits

Digital I/O - 12 I/O pins individually configurable for input or output. DIP switch addressable; stack up to 16 modules on same port for 192 I/O points. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. **\$32**

Analog Input - 8 input pins. 12-bit plus sign self-calibrating ADC. Returns results in 1mV steps from 0 to 4095. Software programmable alarm trip-points for each input. DIP switch addressable; stack up to 16 modules on same port for 128 single-ended or 64 differential inputs. **\$49**

Home Automation (X-10) - Connects between a TW523 and your serial port. Receive/transmit all X-10 commands with your home-brewed programs. Full collision detection with auto re-transmission. **\$39**

Caller ID - Decodes the caller ID data and sends it to your serial port in a pre-formatted ASCII character string. Example: "12/31 08:45 850-863-5723 Weeder, Terry <CR>". Keep a log of all incoming calls. Block out unwanted callers to your BBS or other modem applications. **\$35**

Touch-Tone Input - Decodes DTMF tones and sends them to your serial port. Keep a log of all outgoing calls. Use with the Caller ID kit for a complete in/out logging system. Send commands to the Home Automation and/or Digital I/O kits using a remote telephone. **\$34**

IR Remote Control Receiver

Learns and responds to the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. 7 individual output pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action. **\$32**

Telephone Call Restrictors

Two modes of operation: either prevent receiving or placing telephone calls (or call prefixes) which have been entered into memory, or prevent those calls (or call prefixes) which have "not" been entered into memory. Use touch-tone phone to program.

Block out selected outgoing calls. Bypass at any time using your password. **\$35**

Block out selected incoming calls. Calls identified using Caller ID data. **\$46**

Phone Line Transponder

7 individual output pins are controlled with buttons 1-7 on your touch-tone phone. Automatically answers telephone and waits for commands. Monitor room noises with built in mic. "Dial-Out" pin instructs unit to pick up phone and dial user entered number(s). Password protected. **\$49**

DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Decodes all touch-tones and displays them on a 16 character LCD. Holds the last 240 digits in non-volatile memory. Connect directly to radio receiver's speaker terminals for off-air decoding of repeater codes, or numbers dialed on a radio program. **\$55**

HOW TO PLACE A CLASSIFIED AD

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

NUTS & VOLTS MAGAZINE, 430 Princeland Ct., Corona, CA 91719.

RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00 minimum** charge per ad per insertion.

WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. Add a one-time charge of **\$5.00** to enlarge, reduce, or duplicate line

art, or **\$8.00** for halftone of photographs. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the **5th**) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your *Nuts & Volts* account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in *Nuts & Volts* is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you clearly print or type your ad copy.

Choose a category for your ad from the classifications listed below.

10. Ham Gear For Sale	80. Test Equipment	120. Components	155. Manuals/Schematics Wanted
20. Ham Gear Wanted	85. Security	125. Microcontrollers	160. Misc. Electronics For Sale
30. CB/Scanners	90. Satellite Equipment	130. Antique Electronics	170. Misc. Electronics Wanted
40. Music & Accessories	95. Military Surplus Electronics	135. Aviation Electronics	175. BBS & Online Services
50. Computer Hardware	100. Audio/Video/Lasers	140. Publications	180. Education
60. Computer Software	110. Cable TV	145. Robotics	190. Business Opportunities
70. Computer Equipment Wanted	115. Telephone/Fax	150. Plans/Kits/Schematics	200. Repairs/Service

ADVERTISER'S INDEX

Abacom Technologies	48	Digital Products Co.	80	Lifeline Electronix, Inc.	72	Roger's Systems Specialist	44
ABC Electronics	51	DMD Systems Recovery, Inc.	81	Linear Systems	15	Saelig Company	43
ACP Super Store	86	Earth Computer Technologies	43	LLH Technology Publishing	20	Sam's Electronics	61
Advanced Educational Systems	50	Edlie Electronics, Inc.	42	Lynxmotion, Inc.	76	Scott Edwards Electronics	85
Alfa Electronics	57	E.H. Yost & Co.	76	M2L Electronics	74	Seabird Technical	81
All Electronics Corporation	54	Electro Mavin	71	Matco, Inc.	81	Shreve Systems	80
Allison Technology Corporation	51, 80	Electro Tool, Inc.	53	MCM Electronics	65	SiGEM	81
Alltech Electronics	24	Electronic Design Specialists, Inc.	66	Meredith Instruments	57	Skycraft Parts & Surplus, Inc.	34
Alltronics	17	Electronic Goldmine	19	Metric Equipment Sales, Inc.	69	Sky Electronics, Inc.	53
American Technologies Network Corp.	86	Electronic Rainbow Ind., Inc.	46	M.F.M. Communications.....	58	Square 1 Electronics	33
AM Research, Inc.	31	Electronix Corp.	75	microEngineering Labs	28	SuperCircuits	51
Andromeda Research.....	16	Electronix Express	39	Micromint	31	Surplus Traders	80
Antique Radio Classified	81	EMAC, Inc.	32	Midland Technologies	80	Synergetics	83
A.S. Electronics	48	EPS	81	Motron Electronics	25	Tech 2000	58
AST Global Electronics	70	Equipment Management Technology	74	Mr. NiCd	76	Techniks, Inc.	80
Aventrade	80	ExpressPCB	33	MSC Electronics	81	Techno Lab Digital Systems	47
Baylin Publications.....	21	Fair Radio Sales Co.	49	Netcom	13	Technological Arts	60
Bilocon Corp.	81	Foss Warehouse Distributors.....	80	Norcomm	91	Telulex, Inc.	47
Bisme Computers Outlet	57	Gateway	55	Northwest Cable & Connector Co.	75	The RF Connection	38
Black Feather Electronics	88	General Device Instruments	80	Ocean State Electronics	40	Timeless Products	64
Brigar Electronics.....	12	Glentech, Inc.	80	Optoelectronics.....	4	Trenton Computer Festival.....	39
C & S Sales, Inc.	82	Graymark	28	Parallax, Inc.	Back Cover	Unicorn Electronics	67
C and H Sales Company	72	Halted Specialties Co.	3	PARAMAX, INC.	63	USI Corp.	53
Chaffin Electronics	60	H.T. Orr Computer Supplies.....	86	Patco Service, Inc.	25	Utopia Tools	38
Chenesko Products, Inc.	32	IndustroLogic	50	PCW, Inc.	34	V&V Mach. & Equipment, Inc.	80, 81
Circuit Specialists, Inc.	94	Information Unlimited	29	Phelps Instruments	68	Velleman	41
Communications Surplus.....	81	Inkjet Southwest	52	Pioneer Hill Software	73	VersaTech Electronics.....	47
Comtrad Industries	8	Intronics, Inc.	84	Polaris Industries	49	Vesta Technology, Inc.	81
Consumertronics	18	Jade Products, Inc.	80	Prairie Digital, Inc.	81	Viking International	21
Corporate Systems Center	2, 95	James' Electronic Services, Ltd.	50	Pulsar, Inc.	88	Visitect, Inc.	59
Cruising Equipment	71	JK microsystems.....	81	Quality Kits	14	Weeder Technologies	77
Cunard Associates.....	84	J-Works, Inc.	61	R & D Books	15	Western Test Systems	22-23
Cyber-Test Incorporated	66	KDE Electronics Corp.	69	R & S Surplus	35	Wholesale Cable	16
Davilyn Corp.	11	La Paz Electronics Int'l.	72	Ramsey Electronics, Inc.	45		
Decade Engineering	80	Lemon-Pladd, Inc.	14	Resources Un-Ltd.	36		
DeMar Electronics	81	Lemos International Co., Inc.	73	R.E. Smith	80		

AMATEUR RADIO & TV

Abacom Technologies	48
Alltronics	17
Communications Surplus	81
Gateway	55
Jade Products, Inc.	80
Lemos International Co., Inc.	73
Norcomm	91
Ocean State Electronics	40
Ramsey Electronics, Inc.	45
The RF Connection	38

BATTERIES/CHARGERS

Aventrade	80
Cruising Equipment	71
Cunard Associates	84
E.H. Yost & Co.	76
Jade Products, Inc.	80
Mr. NiCd	76

BUSINESS OPPORTUNITIES

Cheneko Products, Inc.	32
------------------------	----

BUYING ELECTRONIC SURPLUS

ABC Electronics	51
Alltech Electronics	24
Black Feather Electronics	88
C and H Sales Company	72
Earth Computer Technologies	43
EPS	81
Equipment Management Technology	74
Metric Equipment Sales, Inc.	69
Roger's Systems Specialist	44
Skycraft Parts & Surplus, Inc.	34

CABLE TV

Foss Warehouse Distributors	80
James' Electronic Services, Ltd.	50
KDE Electronics Corp.	69
PCW, Inc.	34
Sam's Electronics	61
Tech 2000	58
Timeless Products	64
Wholesale Cable	16

CB/SCANNERS

Norcomm	91
USI Corp.	53

CCD CAMERAS/VIDEO

American Technologies Network Corp.	86
Black Feather Electronics	88
Circuit Specialists, Inc.	94
Decade Engineering	80
MSC Electronics	81
Polaris Industries	49
Ramsey Electronics, Inc.	45
Resources Un-Ltd.	36
Seabird Technical	81
SuperCircuits	51
USI Corp.	53

COMPONENTS

Communications Surplus	81
Electronic Goldmine	19
EPS	81
La Paz Electronics Int'l.	72
Linear Systems	15
Ocean State Electronics	40
Pulsar, Inc.	88
SIGEM	81
Skycraft Parts & Surplus, Inc.	34
Unicom Electronics	67
Visitec, Inc.	59

COMPUTER

Hardware	
ACP Super Store	86
Allison Technology Corp.	51, 80
Alltech Electronics	24
AM Research, Inc.	31
Bismar Computers Outlet	57
Chaffin Electronics	60
Consumertronics	18
Corporate Systems Center	2, 95
DMD Systems Recovery, Inc.	81
Earth Computer Technologies	43
Electro Mavin	71
General Device Instruments	80
Halted Specialties Co.	3
La Paz Electronics Int'l.	72
MCM Electronics	65

Northwest Cable & Connector Co.	75
Roger's Systems Specialist	44
Shreve Systems	80
Techniks, Inc.	80
Techno Lab Digital Systems	47

Software

AM Research, Inc.	31
Bismar Computers Outlet	57
Electronix Corp.	75
Pioneer Hill Software	73
R & D Books	15

Microcontrollers / I/O Boards

Abacom Technologies	48
Advanced Educational Systems	50
AM Research, Inc.	31
Bismar Computer Outlet	57
EMAC, Inc.	32
IndustroLogic	50
JK microsystems	81
La Paz Electronics Int'l.	72
Lemon-Pladd, Inc.	14
Micromint	31
Motron Electronics	25
Parallax, Inc.	Back Cover
PARAMAX, INC.	63
Prairie Digital, Inc.	81
R.E. Smith	80
Scott Edwards Electronics	85
Square 1 Electronics	33
Technological Arts	60
VersaTech Electronics	47
Vesta Technology, Inc.	81

Printers/Printer Supplies

Cheneko Products, Inc.	32
H.T. Orr Computer Supplies	86
Inkjet Southwest	52

DESIGN/ENGINEERING SERVICES

ExpressPCB	33
Midland Technologies	80
Pulsar, Inc.	88
Sky Electronics, Inc.	53
V&V Mach. & Equipment, Inc.	80, 81

EDUCATION

Advanced Educational Systems	50
Electronix Corp.	75
EMAC, Inc.	32

EVENTS/SHOWS

ACP Super Store	86
Trenton Computer Festival	39

KITS

Alltronics	17
C & S Sales, Inc.	82
Digital Products, Inc.	80
Earth Computer Technologies	43
Edlie Electronics, Inc.	42
Electronic Goldmine	19
Electronic Rainbow Ind., Inc.	46
EMAC, Inc.	32
Gateway	55
Information Unlimited	29
Inkjet Southwest	52
Jade Products, Inc.	80
Lemon-Pladd, Inc.	14
Ocean State Electronics	40
Quality Kits	14
Ramsey Electronics, Inc.	45
Scott Edwards Electronics	85
SIGEM	81
USI Corp.	53
Velleman	41
Weeder Technologies	77

LASERS

Information Unlimited	29
Meredith Instruments	57
Resources Un-Ltd.	36
Unicom Electronics	67

MISC./SURPLUS

All Electronics Corporation	54
Alltech Electronics	24
Black Feather Electronics	88
Brigar Electronics	12
C and H Sales Company	72
Chaffin Electronics	60
Communications Surplus	81
Consumertronics	18
Cyber-Test Incorporated	66
DeMar Electronics	81
Electronic Goldmine	19
Electronic Rainbow Ind., Inc.	46
EPS	81

FIND
what you need...

FAST
BY PRODUCT
OR
CATEGORY

Equipment Management Technology	74
Fair Radio Sales Co.	49
Gateway	55
Halted Specialties Co.	3
Lifeline Electronics, Inc.	72
Linear Systems	15
Resources Un-Ltd.	36
Shreve Systems	80
Skycraft Parts & Surplus, Inc.	34
Surplus Traders	80
Unicom Electronics	67
Viking International	21
Visitec, Inc.	59
Weeder Technologies	77

PROGRAMMERS

Andromeda Research	16
General Device Instruments	80
Intronics, Inc.	84
M2L Electronics	74
microEngineering Labs	28

PUBLICATIONS

Antique Radio Classified	81
Consumertronics	18
LLH Technology Publishing	20
Netcom	13
R & D Books	15
Square 1 Electronics	33
Synergetics	83

ROBOTICS

Abacom Technologies	48
Lemos International Co., Inc.	73
Lynxmotion, Inc.	76
PARAMAX, INC.	63
SuperCircuits	51

SATELLITE

Baylin Publications	21
SIGEM	81

SECURITY

American Technologies Network Corp.	76
A.S. Electronics	48
Information Unlimited	29
Lemos International Co., Inc.	73
Lifeline Electronics, Inc.	72
Matco, Inc.	81
MSC Electronics	81
Norcomm	91
Polaris Industries	49
SuperCircuits	51
Visitec, Inc.	59

SOLAR EQUIPMENT

Cruising Equipment	71
--------------------	----

STEPPER MOTORS

Alltronics	17
PARAMAX, INC.	63

TELEPHONE

Bilocon Corp.	81
Digital Products, Inc.	80
M.F.M. Communications	58
Telulex, Inc.	47
Weeder Technologies	77

TEST EQUIPMENT

ABC Electronics	51
Alfa Electronics	57
Allison Technology Corp.	51, 80
AST Global Electronics	70
C & S Sales, Inc.	82
C and H Sales Company	72
Circuit Specialists, Inc.	94
Cruising Equipment	71
Davilyn Corp.	11
Digital Products, Inc.	80
DMD Systems Recovery, Inc.	81
Electronic Design Specialists, Inc.	66
Equipment Management Technology	74
Electro Tool, Inc.	53
Glentech, Inc.	80
Intronics, Inc.	84
J-Works, Inc.	61
MCM Electronics	65
Metric Equipment Sales, Inc.	69
Optoelectronics	4
Phelps Instruments	68
Pioneer Hill Software	73
R & S Surplus	35
Saelig Company	43
Seabird Technical	81
Telulex, Inc.	47
Western Test Systems	22-23

TOOLS

C & S Sales, Inc.	82
Electro Tool, Inc.	53
Graymark	28
Lemon-Pladd, Inc.	14
Patco Service, Inc.	25
The RF Connection	38
Utopia Tools	38

WIRE/CABLE & CONNECTORS

Northwest Cable & Connector Co.	75
Roger's Systems Specialist	44
The RF Connection	38

A/D CONVERTERS with SERIAL OUTPUT

Tiny (1.75"x1.41") fully assembled and tested printed circuit board includes two 8-bit A/D converters and one digital input. Up to 16 units addressable (DIP switch setting) totalling 32 converters on a single serial port. Output is ASCII encoded bit count (0 to 255) at 2400 BPS via RJ-11 interface. Fully programmed PIC16C71 installed in IC socket. Sample software in BASIC included. Requires 8-28Vdc At 1-2mA.
\$49.95. Optional DC adapter \$19.95.
Add \$5.00 shipping.



Tele: 847-891-2584
Fax: 847-891-2587
www.glentech-rf.com

SURPLUS SALE

1,000,000 WALL
TRANSFORMERS



3VDC/100MA CX099 \$0.75
6VDC/100MA CS039 \$1.45
9VDC/100MA CR314 \$1.45
12VDC/200MA CS033 \$0.99
13.5VAC/400MA.. CR574 \$1.29
24VDC/500MA CR174 \$3.40

Min 1000/type -- Call for other types

SURPLUS TRADERS

PO Box 276,
Alburt, VT 05440
Tel: (01) 514-739-9328
Fax: (01) 514-345-8303
http://www.73.com/w

FREE CATALOG!

PROGRAMMERS

ADVANTECH EETOOLS NEEDHAM DATA I/O TECHNOLOGY HILO
SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



CALL ADVANTECH LABTOOL 599 EETOOLS SIMMAX
629 ICE TECH MICROV 795 CHROMA SIMM/SIP
650 EETOOLS ALLMAX + 359 MOD-MCT-EMUP/R
409 EETOOLS MEGAMAX 279 MOD-MCT-EMUP/R
509 EETOOLS MEGAMAX4 49 EPROM 1G TO 512K
369 XELTEK SUPERPRO II 69 EPROM 1G TO 1MEG
409 XELTEK SUPERPRO II P 99 EPROM 4G TO 1MEG
249 XELTEK SUPERPRO L 199 EPROM 16G TO 1 MEG
165 XELTEK ROMMASTER II 89 EPROM 1G TO 8MEG
479 MOD-MCT-EMUPA 129 EPROM 4G TO 8MEG
739 STAG ORBIT-32 250 EPROM 8G TO 8MEG



General Device Instruments

Sales 916-393-1655 Fax 916-392-4949
Web www.generaldevice.com E-Mail idevice@best.com

BATTERY — YUASA



Sealed Lead-Acid/Gel-Cell
12V: 7AH \$19, 2.3/4AH \$16
18AH \$39, 1.2AH \$13
6V: 4AH \$9, 10AH \$13

Quantity Discounts Available
Call for other models

Aventrade

4518 Temple City Blvd., Temple City, CA 91780
Tel. 626-286-0118 Fax 626-287-9618
E-Mail: sales@aventrade.com
www.aventrade.com

Serial Problems???

Use your PC compatible desktop or laptop computer to debug serial communications problems with Serial, our test tool for serial communications.

Serial works with the standard data rates and asynchronous serial formats commonly found in modern office and industrial environments. Suitable for development, service work, and end-user problem diagnosis.

- Easy to Use
- Menu and Windows
- Highly Configurable
- Contextual Help
- Autobaud Detect
- Time Stamping
- Custom font editor for EGA/VGA Screens
- Saves Configurations
- Extensive Manual
- Block transmit ability
- CRC/LRC generation

Serial, with manual \$99.95
Cable for full duplex monitoring \$49.95

For Orders and Inquiries Call: 1-800-980-9806
Allison Technology Corporation

2006 Finney Valley Rd., Rosenberg, TX 77471
281-239-8500 • 281-239-8006 FAX

"SMART" BATTERY CONTROLLERS:

APRIL SPECIAL

5A 110 VAC ... \$214.95 PP
6 A SOLAR ... \$193.00 PP

BUY NOW RECEIVE LOW
VOLTAGE DISCONNECT FREE! SAVE \$18.

MARCONI ANTENNA 700W 50 Ω

THE BEST "LITTLE" LOW BAND ANTENNA
80M: 67' OVERALL \$46.95 PP
160M: 130' OVERALL \$53.95 PP

SHIELDED LOOP RECEIVER

30M, 40M KITS WITH
ANTENNA. VERY SENSITIVE.
HAS HIGH IMMUNITY TO
LOCAL AM BROADCAST
AND QRN. \$101.50 PP

CODE PRACTICE OSCILLATOR. \$23.45 PP

SEND FOR FREE CATALOG

1-800 JADE PRO (523-3776)

www.jadeprod.com/

email: jadepro@jadeprod.com

JADE PRODUCTS E. HAMPSTEAD NH 03826-0388

PCB's in Minutes From LaserPrint!*

8 1/2" x 11"
Sheets

* Or Photocopier
Use household
iron to apply.



PnP BLUE or PnP WET

For High Precision
Professional PCB Layouts

1. LaserPrint
2. Iron-On
3. Peel-Off
4. Etch

Adds on Extra Layer of
Resist for Super Fine
Lines on Std Clad Bds

Easy Hobby
Quality PCB's

1. LaserPrint
2. Iron-On
3. Soak-Off w/ Water
4. Etch

Transfers Laser Printer
or Copier Toner as
Resist to Std Clad Bds

20Sh \$30/40Sh \$50/100Sh \$100 Blue/Wet (No Mix)

Sample Pack 5 Shets Blue + 5 Shets Wet \$20

VISA/MC/PO/CH/MO \$4.50H -- 2nd Day Mail


Techniks Inc. P.O. Box 463 Ringoes NJ 08551

(908)788-8249

100% Money Back Guarantee-Dealer Inquiries Invited

Convert RS-232 to RS-485
or TTL/CMOS for Only \$49.00

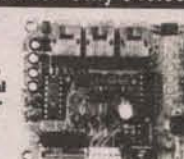Communicate up to
1,000 feet, at up to
1 MEGA-bps, full
or half duplex, up to
32 units on one serial
link, with 31 jumper
options for flexible
configuration, LED
indicators.



COMMUNICATIONS CONVERTER

- FULL SCHEMATIC AND DOCUMENTATION
- FULL FAMILY OF MODULAR DESIGNS
- RS-485/RS-422 REMOTE I/O MODULE KITS
- NETWORK SOFTWARE AND SOURCE CODE
- AUTOMATIC OR RTS UNITS AVAILABLE
- RJ-11/12 CONNECTORS OR TERMINAL STRIP
- TURN YOUR PC INTO A DISTRIBUTED DATA ACQUISITION AND CONTROL SYSTEM

R.E. SMITH

(513) 874-4796

4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011

www.rs485.com

TV 85 PJ & TV 86
CABLE CONVERTERS
VOLUME &
NON-VOLUME CONTROL

SALES/SERVICE
VOICE 1-800-473-0506
FAX 1-800-488-0525

FOSS WAREHOUSE DISTRIBUTORS

285 Schenck St.
N. Tonawanda, NY 14120
www.fossw.com

PCBs

PER SQIN
\$100.00 SETUP

WE SPECIALIZE IN SINGLE SIDED, 1 OZ, PC75

9¢

PCB LAYOUT

PER COMPONENT PIN \$100.00 MINIMUM

59¢

ENGINEERING DIAGRAMS

PER COMPONENT PIN \$100.00 MINIMUM

39¢

V&V MACH. & EQUIP., INC. (HOUSTON, TX OFFICE)

PH (281) 397-8101 FAX (281) 397-6220

MARKETING TECH. S.A. (MEXICO/PLANT)

PH 011 (525) 361-3351 FAX 011 (525) 361-5996

Peltier Junction

While They Last!

1 3/16" x 1 3/16"
cooling area

Quantity Pricing
Available

WITH HEATSINK AND LEADS
\$10 EACH
OR THREE FOR \$25

SHREVE SYSTEMS
318-424-9777

Ask for Jake

RGB Color
Composite Displays
ON SALE!



*refurbished with 90-day warranty

ONLY \$49!!

Excellent for studio, lab or
surveillance applications

640x480 resolution, RCA-style connectors

Returns subject to a 15% restocking fee. Prices are
subject to change without notice.

WE ACCEPT VISA, MASTERCARD, AMEX, DISCOVER

HTTP://WWW.SHREVESYSTEMS.COM

Telecom Hardware/Software Developers

STOP using your phone lines to test and demonstrate your telecom devices. Our affordable telephone line simulators offer authentic USA dial tone, busy signals, ringing, and exceptional speech quality.



RING-IT! TELCO SIMULATOR
• Single Line (two RJ-11 Jacks)
• LED Display
• DTMF Operation
• Automatic Ring-up Mode
• \$325 (\$149 kit available)

PARTY-LINE TELCO SIMULATOR

- Six Extensions
- Caller-ID (Name/Nbr)
- Distinctive Ringing

• \$425 (\$199.95 kit avail)



Digital Products COMPANY

134 Windstar Circle

Folsom, CA 95630 USA

Tel: 916-985-7219

Fax: 916-985-8460

http://www.digitalproductsco.com

NEW 3 AMAZING NEW PRODUCTS

12-HOUR VOICE ACTIVATED MULTI RECORDER MC-4



CAN BE USED AS:
1. ROOM MONITOR
2. TEL LINE RECORDER
3. MULTI-LINE HANDSET
RECORDER
4. REGULAR 12-HOUR
RECORDER
\$95
INCLUDING
SHIPPING



THE PRIVACY ENFORCER
STOPS
1. VOICE ACTIVATED AND
VOLTAGE SENSITIVE
RECORDERS
2. ALERTS YOU WHEN
SOMEONE ELSE IS LISTENING
IN FROM ANOTHER EXTENSION
\$49
INCLUDING
SHIPPING



THE BUG BUSTER
1. DETECTS AND LOCATES
FM TRANSMITTERS (BUGS)
\$79
INCLUDING
SHIPPING

CALL 1-905-820-8020

PC BOARD SERVICES

PCB Design Layout

Thru Hole

SMT

Multilayer

PCB FABRICATION

In-house Prototypes

Single and Double Side

Plate Thru Hole

ASSEMBLY

Thru Hole

Small Project Specialists

Serving Engineers and Hobbyists
for 16 Years

MIDLAND TECHNOLOGIES

800-726-8871 Voice

406-586-0300 FAX

VIDEO CHARACTER OVERLAY GENERATOR

New BOB-II superimposes up to 308
characters on standard video or gener-
ates video. 30-pin SIMM design, RS-
232 interface, easy to use for:

- Video Inspection - NDT
- Home Automation Display
- ATV - CCTV Security - CATV
- Remotely Piloted Vehicles
- Gaming - Racing - Sports
- Process/Experiment Monitor
- Robotics - Electronic Signs

Single units only \$79.95

DECADE ENGINEERING

5504 ValView Dr. SE, Turner, OR 97392

Tel: 503.743.3194 ~ Fax: 503.743.2095

mikeh@decadenet.com ~ www.decadenet.com

EMBEDDED DOS Flashlite-V25

- 2 Serial Ports
- 2 DMA Channels
- 2 Timer Channels
- 20 Parallel I/O Lines
- 5 Volt Operation
- 4 Hardware Interrupts
- 8 Analog Comparators
- Low Power Consumption



qty 1 \$119
qty 100 \$99
qty 1000 \$85

Development Kit - \$159 Includes:

- Flashlite V25, 10MHz, 512K Ram/ 512K Flash
- Borland C/C++ 4.52 Development Software on CD
- Telecommunications Program & Sample Programs
- AC Adapter and Cables

www.jkmicro.com

Call 530-297-6073 Fax 530-297-6074

JK microsystems

ATTENTION DEALERS WHOLESALE ONLY!

• ANY CABLE MFRG CONVERTERS & ACC

• BEST PRICING & SERVICE

• SHOP US NOW

PANASONIC • NOVA, ETC.

800-777-7731

10 Hr. Telephone Recorder \$69

+\$6.95 S/H



Automatically starts recording when the phone is picked up and stops when you hang up. Records both sides of the conversation!
BEST PRICE AROUND!

FREE CATALOG
www.mscelectronics.com

MSC Electronics
PO BOX 461 Jessup, MD 20794
(301) 497-1600
FAX (301) 497-1925



EPS EPROMS AS LOW AS 25¢

27C256	27C040	27C1024	87C51
27C512	27C400	28F010	8751
2732A	27C4096	28F020	8755
27C32	274000	28F040	MC68HC70
27C128	574200	8749H	5C8A
27C64	27C402	8748H	PIC16C56
2716	27C020	8741	PIC16C54
2708	27C210	8742	PIC16C622
27C512-90	27C010	8744	GAL16V8

STATIC RAM
HM628128
62256
6264
6116

PROCESSOR
8255
8254
80C31

• Many more parts in stock
• All major brands
• All guaranteed
E-Mail: eproms@aol.com

TEL: (818) 774-9444 • FAX: (818) 774-0822
WE BUY EXCESS INVENTORY

FREE SAMPLE COPY!

ANTIQUE RADIO CLASSIFIED

Antique Radio's Leading Monthly Magazine

Articles - Classifieds - Ads for Parts & Services. Also: Ham Equip. - Books - Telegraph - 40's, 50's & 60's Radios - Early TV - Auction Reports & more...

1-Year: \$39.49 (\$57.95 by 1st Class)
6-Month Trial - \$19.95. Foreign - Write.

A.R.C., P.O. Box 802-G23
Carlisle, MA 01741
Call: 978-371-0512 - Fax: 978-371-7129
Web: www.antiqueradio.com

TOGGLE SWITCHES - All sizes and types Commercial Quality

TYPE	MODEL	RATING	LEAD	PRICE
SPST	D125	6A/125V	6" wire	.77 .67
SPST	D128	4A/125V	Solder	.57 .47
DPDT	D126	5A/125V	Solder	.77 .67
DPDT	D127	10A/125V	Solder	1.17 1.06

TYPE	MODEL	RATING	LEAD	PRICE
SPST	D131	6A/125V	Solder	.57 .47
SPST	D132	6A/125V	Solder	.61 .51
SPST	D129	6A/125V	Solder	.77 .67

TYPE	MODEL	RATING	LEAD	PRICE
mom-off-mom	D134	3A/250V	Solder	.77 .67
on-off-on	D133	6A/125V	Solder	.77 .67
DPDT	D135	6A/125V	Solder	.92 .82

TYPE	MODEL	RATING	LEAD	PRICE
on-off-on	D130	3A/250V	Solder	.92 .82
mom-off-mom	D130	3A/250V	Solder	.92 .82


MOMENTARY PUSHBUTTON SWITCHES 1/4" DIA.				
SPST Nor Open DM1	3A/125V	Solder	.30	.25
SPST Nor Close DM2	3A/125V	Solder	.30	.25

ANY ORDERS LESS THAN 100, ADD 20¢ EACH
LEDs Red, Yellow, Green - \$12.00/100 \$10.00/1,000

DEMAR ELECTRONICS
P.O. Box 7215, Algonquin, IL 60102
Toll Free 877-655-6433
Fax 847-854-4434

CABLE BOXES

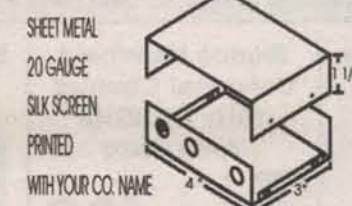
CUT MANUFACTURING COST!
WE ACCEPT SMALL ORDERS TOO.



ALSO PCB, SMT, PROTOTYPES, ASSEMBLY,
PLASTIC MOLDS, INJECTION MOLDING.

USA Office: V&V Mach. & Equipment, Inc.
Ph: (281) 397-8101, Fax: (281) 397-6220.
Mexico Plant: Marketing Tech.
Ph: 011 (525) 361-3351, Fax: 011 (525) 361-5996.

2.4 GHz Wireless Transmitter & Receiver

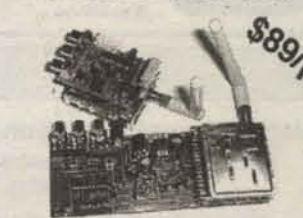

2.4 GHz - 2.48 GHz User Selectable
Over 700' Range and 4 Chl Auto-scan
NTSC, PAL, Composite video B/W or Color
2 Audio Input may be used for digital data
Customizations including battery packs available

Matco Inc.
(800)440-0299 or (800)719-9605
www.mat-co.com

ASSEMBLY & ENGINEERING

Producible designs since 1970 Contract Engineering

Embedded Microprocessors
PCB Layout and Packaging Design
Analog Including RF to 1 GHz
Instrumentation
A/D and D/A

Contract Assembly
High-Speed Fuji Surface Mount
Through hole
Turn-key or Kit
Run sizes one through thousands
Test and burn-in available

Bilocon Corp.
800-736-5927
425-353-2276
www.bilocon.com

Stereo Microscopes

- 10X & 30X
- Top and bottom Light
- Dust cover
- Eyeguards
- 1 year warranty
- ST241A - \$275.00
- Catalog available

jlittle@netwizards.
3580 Haven Ave. Redwood City, CA 94063
4603 650/367-8320 Fax 365-5845

CONTROL • MEASURE • INPUT

MODEL 40-\$109
• RS-232 interface
• 28 lines digital I/O
• Eight analog inputs
• PWM output
• Three stepper ports

MODEL 100-\$279
• 12-bit 100KHz A/D • Four analog outputs
• Three timer counters • 24 digital I/O



PRAIRIE DIGITAL, INC.
920 SEVENTEENTH ST., INDUSTRIAL PARK
PRAIRIE DU SAC, WI 53578
TEL: (608) 643-8599 • FAX: (608) 643-6754

the only place
to go for
computer &
computer &

dmdsystems.com

test equipment parts,
spares, systems
and components

DMD SYSTEMS RECOVERY, INC.
602 305-8485
fax 602 305 8490 • email info@dmdsystems.com



GPS Design Kit - \$379

The design kit SGM5600KS is a complete and immediately usable means of evaluating the SiGEM GPS receiver module and high performance GPS antenna, which are included in the kit. Software running on the GPS receiver module communicates to a user supplied computer via NMEA 0183 formatted messages. Advanced PC software provides map integration and a demonstration of tracking. Provision has been made for DGPS inputs.
SiGEM Inc.
50 Hines Road
Kanata, Ontario
Canada K2K 2M5
Tel: (613) 271-1601 (Can)
(541) 923-3733 (USA)
Fax: (613) 271-1896

SiGEM

Web: www.sigem.ca
Email: info@sigem.ca


CUSTOM PLASTIC PARTS

- MODELS (WOOD AND RESIN). TO EVALUATE YOUR PARTS BEFORE COMMITTING TO MANUFACTURE A MOLD.
- MOLD DESIGN AND BUILDING.
- PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TO SMALL OR TO BIG.
- VERY COMPETITIVE ON HIGH LABOR PARTS.

We also have manual low pressure machines for injection molding of very small runs or prototypes of parts up to 2 oz. At a surprisingly low price.

USA Office: V&V Mach. And Equip. Inc.
Tel: (281) 397-8101, Fax: (281) 397-6220.
Please send blue prints or samples to:
Marketing Tech. S.A. • Alamo 93, 4 Piso • Sta. Monica,
Tlal • Eco. De Mexico 54040 • Tel. 011 (525) 361-3351.
Fax: 011 (525) 361-5996. ATTN: VICTOR M. MENDOZA
e-mail: marktech@infonet.net.mx

SBC2000-074

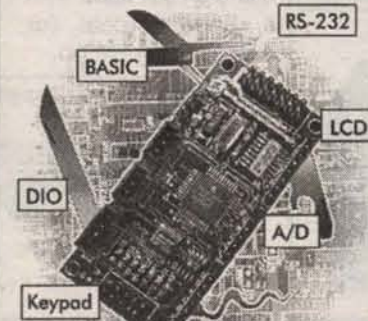

Versatility starting at \$64 each.

Voice: 303.422.8088 Fax: 303.422.9800
www.sbc2000.com
Vesta Technology, Inc.

GPS Units

Trimble Placer 400
6 Channel
No Antenna **\$49.95**
Trimble SVeeSix
6 Chan w/ Diff. & Magnet Mt. Antenna
\$89.95
Rockwell MicroTracker LP
5 Channel, Module w/ Differential
No Antenna **\$69.95**

Communications Surplus
713-526-8000 or 1-877-878-6GPS
lshaefer@flash.net Fax to 713-522-6309

CALL TOLL FREE

(800) 292-7711
Orders Only

Se Habla Español

C&S SALES

Excellence in Service

**CALL OR WRITE
FOR OUR
FREE**

**64 PAGE CATALOG!
(800) 445-3201**

Digital Multimeters

Elenco Model M-1740



\$39.95

- 11 Functions:**
- Freq. to 20MHz
 - Cap. to 20µF
 - AC/DC Voltage
 - AC/DC Current
 - Beeper
 - Diode Test
 - Transistor Test
 - Meets UL-1244 safety specs.
- Model M-2760 - \$24.95**
(9 functions)

Elenco Model LCR-1810



\$99.95

- Capacitance .1pF to 20µF
- Inductance 1µH to 20H
- Resistance .01Ω to 2000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

Fluke 87III



\$299

Features high performance AC/DC voltage and current measurement, frequency, duty cycle, resistance, conductance, and capacitance measurement.

Series II (limited qty.)
\$289

Generators and Counters

Elenco Sweep Function Generator with built-in frequency counter Model GF-8036



\$225

This sweep function generator with counter is an instrument capable of generating square, triangle, and sine waveforms, and TTL, CMOS pulse over a frequency range from 0.2Hz to 2MHz.

20MHz Sweep / Function Generator with Frequency Counter Model 4040

\$399



- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep

BK PRECISION

10MHz Model 4017 \$309

5MHz Model 4011 \$239

Elenco Handheld Universal Counter Model F-2800



\$99

- Sensitivity:**
- <1.8mV @ 100MHz
 - <8mV @ 250MHz
 - <8mV @ 10Hz
 - <100mV @ 2.4GHz

Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter.

B&K Frequency Counter Model BK-1875



**1Hz - 2.8GHz
3 Channels**

\$189

- Sensitivity:**
- <0.8mV @ 100MHz
 - <8mV @ 300MHz
 - <7mV @ 1GHz
 - <100mV @ 3GHz

Ultra sensitive synchronous detector bargraph and RF strength.

Elenco RF Generator with Counter (100kHz - 150kHz) Model SG-9500



Features internal AM mod. of 1kHz, RF output 100MV - 35MHz. Audio output 1kHz @ 1V RMS.
SG-9000 (analog, w/o counter) \$119.95

Elenco 10Hz - 1MHz Digital Audio Generator Model SG-9300




\$175

Features built-in 150MHz frequency counter, low distortion and sine/square waves. SG-9200 (w/o counter) \$119.95

Elenco Oscilloscopes

Free Dust Cover and 2 Probes

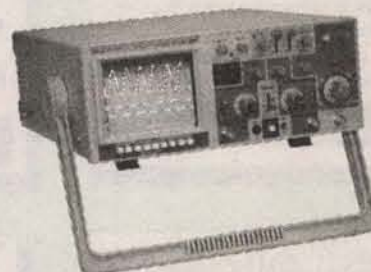

S-1325	25MHz	Dual Trace	\$325
S-1330	25MHz	Delayed Sweep	\$439
S-1340	40MHz	Dual Trace	\$475
S-1345	40MHz	Delayed Sweep	\$569
S-1360	60MHz	Delayed Sweep	\$749
S-1390	100MHz	Delayed Sweep	\$995

DIGITAL SCOPE SUPER SPECIALS

DS-203	20MHz/10Ms/s Analog/Digital	\$695
DS-303	40MHz/20Ms/s Analog/Digital	\$995
DS-603	60MHz/20Ms/s Analog/Digital	\$1295

Four Functions in One

Elenco Model MX-9300



\$459.95

Features:

- One instrument with four test and measuring systems:
- 1.3GHz Frequency Counter
- 2MHz Sweep Function Generator
- Digital Multimeter
- Digital Triple Power Supply - 0-30V @ 3A, 15V @ 1A, 5V @ 2A

Elenco Educational Kits

Model AR-2N6K



2 Meter / 6 Meter
Amateur Radio Kit
\$34.95

Model AM/FM-108K

Transistor
Radio Kit
\$29.95



Model AK-700
Pulse/Tone
Telephone Kit
\$15.95

Model AK-870
Radio Control Car Kit
\$24.95



Model M-1005K
Digital Multimeter Kit
\$19.95

Model XP-720K
Power Supply Kit
\$54.95



Model XK-150
Digital / Analog
Trainer
\$89.95

Model EP-50
Electronic
Playground and
Learning Center
\$19.95



Tekk Radios

Pro-Sport FRS Two-Way Radio Model PRO-SPORT+

- 14 Channels
- Battery Monitor
- Key Lockout
- Monitor Button
- Lightweight
- Palm Sized
- Large LCD Display
- Removable Belt Clip
- Removable Antenna
- Two Radio Call Tones
- Busy Channel Lockout
- Accessory Connector
- Highly Water Resistant

\$79 each
or
\$149.95
Set of 2

Talk up to
2 miles!



PRO SPORT Model
\$109.95 set of 2

Miscellaneous

Elenco Technician Tool Kit Model TK-1500

28 tools plus a DMM contained in a large flexible tool case with a handle ideal for everyone on the go.



Elenco Quad Power Supply Model XP-581



\$89.95
4 Fully Regulated DC Power Supplies in One Unit
4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A
1 Variable - 2.5 - 20V @ 2A

Dual-Display LCR Meter w/ Stat Functions B&K Model 878



\$219.95
Auto/manual range
Many features
with Q factor
High Accuracy

Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents add 8.25% Sales Tax

SEE US ON THE WEB

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710

<http://www.cs-sales.com>

15 DAY MONEY BACK GUARANTEE

2 YEAR FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Don Lancaster's

RESOURCE BIN

number eighty seven

Exploring used test equipment options.

Our usual reminder here that the *Resource Bin* is a two-way column. You can get tech help, consultant referrals, and off-the-wall networking on nearly any electronic, *tinaja* questing, personal publishing, money machine, or computer topic by calling me at (520) 428-4073 weekdays 8-5 Mountain Standard Time.

Finding Decent Used Test Equipment

You'll find a lot of incredible buys in used test equipment if you shop around. Brought about by military and aerospace cutbacks, those schools dropping their electronics programs, and the big shift towards modeling, simulation, and computer control. On the other hand, there sure is a lot of outrageously heavy and ridiculously oversized junk out there.

Much of it totally useless.

How do you separate the goodies from the grunge?

A better home lab should have at least a good power supply or two, a multimeter, a scope, a *BASIC Stamp* by Parallax, and a function generator. For "level II," you'll add such goodies as frequency counters, signal generators, computer emulators, some RF gear, and more specialized devices.

Your first and foremost choice for used electronic test equipment should be right here in *Nuts & Volts*. Where you will find hundreds of ads spread out over dozens of categories. But let us take a tour of your other options in pinning down superb prices on used test gear. Let's start with ...

The Blue Book

The closest thing I have found to a used test equipment blue book is the *Test Equipment Connection* free catalog. From www.4testequipment.com.

This *essential* catalog instantly tells you which equipment stays popular. Along with relative prices. Primarily for H-P and Tek, of course. But *Fluke*, *Racal*, *Wavetek*, and a few dozen or so

other sources are also included.

If a piece of gear is not in this catalog, the chances are it is not worth buying.

I'll typically divide their prices by 30 to come up with reasonable bids on skidded surplus lots. Never go to any auction or a hamfest without at least one copy of their catalog.

But do keep it well hidden.

NEXT MONTH:
Don finds the hydrogen scene is a gas.

Some Sources

As with most any field, you'll get what you pay for. Depending on how price limited you are and how much risk you are willing to take, there are several choices here ...

Prime Suppliers — These firms provide like new condition, full manuals, support, leads, accessories, and even standards tracability. Typical outfits are *Danbar*, *Davilyn*, *Tucker*, *Test Equipment Plus*, *Naptech*, the *Test Equipment Connection*, *TestEquity*, *ValueTronics*, *Western Test Systems*, and a dozen others.

Bargain Sources — The bargain sources typically charge only one-half to one-third of the regular price. But all you could end up with is the instrument itself, reasonably clean, and checked only for obvious faults. Manuals are usually extra, and guarantees may be limited. Availability may be restricted to stock on hand, rather than what you really want. The lower prices are possible because of lower ad staff, and overhead costs.

Hamfests and Newsgroups — These are often your cheapest sources for single quantities of useful test gear. But they are also the ones with the highest risk. And possibly the highest rewards. We will see more on these shortly.

Wholesale Auctions — The lowest prices are gotten by buying blind in skid lots from military auctions and industrial distress sales. High quantities and high risks are involved. The process may take many weeks and involve truck rentals and travel to places you really did not want to go to. Again, we'll see more details below.

Hamfests

Hamfests are technical flea markets and tailgating parties put on by local amateur radio clubs. You should find hundreds of these yearly, ranging from a few locals gathering together to statewide regional meets. On up to their huge yearly Dayton show.

A wide variety of bargain priced test equipment is often featured from dozens to hundreds of individuals or commercial vendors. Admission is from free to nominal for buyers. Keep in mind that what you see is what you get. And that the ultra low prices can represent higher risks. If you don't know what you are buying, ask for expert help. There's always bunches of it nearby at a hamfest.

Really great buys are the norm.

Speaking of which, you'll always get the best buys before sun-up or very late in the day. Very early to grab the goodies ahead of the hoarders. And late because a seller may be under a "get rid of all that junk or don't come back" edict.

These days, there are also lots of *virtual hamfests* that are simply online classifieds that happen to cater to the amateur radio needs.

There's also a lot of hamfest info on the web. Just punch "hamfest" into www.hotbot.com to get many thousands of links. Add a state name to narrow your search.

Or, you can start off with these real hamfest directory sites ...

www.arl.com/field/hamfests
www.seanet.com/~bobjr/hfest.htm
www.vartel.com/hamfest.htm

Or these virtual ones ...

www.hamfest.net
<http://vhamfest.com>

Lots of hamfests are in the monthly *Nuts & Volts* events calender.

Newsgroups

Some of the best test equipment bargains of all can usually be found in the Usenet newsgroups. Your most useful one is *sci.electronics.equipment*. But also check *sci.electronics.repair*

new from
DON LANCASTER

ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. **\$28.50**

CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. THE two books for digital integrated circuit fundamentals. About as hands-on as you can get. **\$28.50 each.**

RESEARCH INFOPACKS

Don's instant cash-and-carry flat rate consulting service. Ask any reasonable technical question for a detailed analysis and complete report. See www.tinaja.com/info01 for specifics. **\$75.00**

INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. **\$18.50**

LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. **\$119.50**

LOTS OF OTHER GOODIES

Test Musings V or VI	\$24.50
Ask the Guru I or II or III	\$24.50
Hardware Hacker II, III or IV	\$24.50
Micro Cookbook I	\$19.50
PostScript Beginner Stuff	\$29.50
PostScript Show and Tell	\$29.50
Intro to PostScript Video	\$29.50
PostScript Reference II	\$34.50
PostScript Tutorial/Cookbook	\$22.50
PostScript by Example	\$32.50
Understanding PS Programming	\$29.50
PostScript: A Visual Approach	\$22.50
PostScript Program Design	\$24.50
Thinking in PostScript	\$22.50
LaserWriter Reference	\$19.50
Type 1 Font Format	\$16.50
Acrobat Reference	\$24.50
Whole works (all PostScript)	\$380.00
Technical Insider Secrets	FREE

BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. **\$39.50**

THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set shows you Don's tested and proven real-world alternatives. **28.50**

BLATANT OPPORTUNIST I

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. **\$24.50**

RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. **\$24.50**

FREE SAMPLES

Check Don's Guru's Lair at <http://www.tinaja.com> for interactive catalogs and online samples of Don's unique products. Searchable reprints and reference resources, too. Tech help, hot links to cool sites, consultants. email: don@tinaja.com
FREE US VOICE HELPLINE VISA/MC

SYNERGETICS

Box 809-NV
Thatcher, AZ 85552
(520) 428-4073

and *sci.electronics.misc*.

But buyer beware, empty cravats, and all that other stuff.

The newsgroup access is sometimes free with your Internet account. Other times, there is a low extra monthly charge. Be sure to ask your ISP if you are having access problems.

If you can't access a newsgroup any other way, use www.dejanews.com.

Auctions

Auctions are interesting but

RESOURCE BIN

SOME USEFUL TEST EQUIPMENT RESOURCES

ABC Electronics 315 7th Ave N Minneapolis MN 55401 (612) 332-2378	Cruising Equipment 5245 Shilshole Ave NW Seattle WA 98107 (206) 782-8100	Fluke PO Box 9090 Everett WA 98206 (800) 443-5853	OptoElectronics 5821 NE 14th Ave Ft Lauderdale FL 33334 (954) 771-2050	Telulex Inc 2455 Old Middlefield Way S Mountain View CA 94043 (650) 938-0240
Alfa Electronics Inc PO Box 8089 Princeton NJ 08543 (609) 897-1135	Danbar 14455-C N 79th St Scottsdale AZ 85260 (602) 483-6202	Glentech Inc 731 W Lunt Ave Schaumburg IL 60193 (847) 891-2584	Parallax 3805 Alherton Rd #102 Rocklin CA 95765 (916) 824-8333	Test & Measure World 275 Washington St Newton MA 02158 (617) 558-4671
Allison Technology Corp 2006 Finney Valley Rd Rosenberg TX 77471 (281) 239-8500	Davilyn Corp 13406 Saticoy St North Hollywood CA 91605 (818) 787-3334	Stan Griffiths 18955 SW Blanton Aloha OR 97007 (503) 649-0837	Phelps Instruments 2631 Hillside Ave Norco CA 91760 (909) 279-7347	Test Equip Connection 525 Technology Park Lake Mary FL 32746 (800) 615-8378
AST Global 24529 St Hwy 408 Cambridge Springs PA 16403 (814) 398-8080	Digital Products Inc 134 Windstar Cir Folsom CA 95630 (916) 985-7219	Intronics Inc Box 13723/612 Newton St Edwardsville KS 66113 (913) 422-2094	Pioneer Hill Software 24460 Mason Rd Poulsbo WA 98370	Test Equipment Plus 3331 W Bright Terrace Tucson AZ 85741 (520) 575-6967
Auction Advisory Box 61104 Phoenix AZ 85082 (602) 994-4512	Electronic Design Specialist Inc 4647 Appalachian St Boca Raton FL 33428 (561) 487-6103	J-Works Inc 12328 Gladstone St #4 Sylmar CA 91342 (818) 361-0787	R&S Surplus 1050 E Cypress St Covina CA 91724 (626) 967-0846	TestEquity 2450 Turquoise Circle Thousand Oaks CA 91320 (800) 228-3457
Bentley Auctioneers 3801 Academy Pkwy NE Albuquerque NM 87109 (505) 344-1812	eBay 2005 Hamilton Ave, #350 San Jose CA 95125 www.ebay.com	Jnl of Electronic Test 101 Philip Dr Norwell MA 02061 (781) 871-6600	Racal Instrument PO Box C-19541 Irvine CA 92718 (949) 859-8999	Tucker 1717 Reserve St Garland TX 75042 (800) 527-4642
C&S Sales Inc (Elenco) 150 W Carpenter Ave Wheeling IL 60090 (847) 541-9904	Electro Tool Inc 9103 Gilman Livonia MI 48150 (734) 422-1221	Levy Latham 6263 N Scottsdale #371 Scottsdale AZ 85250 (602) 367-1100	Saelig Company 1193 Moseley Rd Victor NY 14564 (716) 425-3753	ValueTronics 1925 S Wright Blvd Schaumburg IL 60193 (800) 552-8258
C & H Sales Inc 2176 E Colorado Blvd Pasadena CA 91107 (800) 325-9465	EMF-EMI Control PO Box D Gainesville VA 20156 (540) 347-0030	Metric Equipment Sales 3486 Investment Blvd Hayward CA 94545 (800) 432-3424	Seabird Technical 3580 Haven Ave Redwood City CA 94063 (650) 367-8320	Wavetek 9054 Balboa Ave San Diego CA 92123 (619) 279-2200
Circuit Specialists Inc 220 S Country Club Dr Mesa AZ 85210 (602) 464-2485	Equipment Management Technology 837A Industrial Rd San Carlos CA 94070-3312 (650) 631-1700	Naptech 11270 Clayton Creek Rd Lower Lake CA 95457 (800) 336-7723	Synergetics Box 809 Thatcher AZ 85552 (520) 428-4073	Western Test Systems 530-C Compton St Broomfield CO 80020 (303) 438-9662
Compliance Engineering 629 Massachusetts Ave Boxborough MA 01719 (508) 264-4208	Evaluation Engineering 2500 Tamiami Trail North Nokomis FL 34233 (941) 966-9521	Nuts & Volts 430 Priceland Ct Corona CA 91719 (909) 371-8497	Tektronix PO Box 500 Beaverton OR 97077 (800) 835-9433	

risky places to pick up used test equipment. Their prices will sometimes end up extremely low. Particularly when you choose obscure enough auctions, the weather is lousy, it is midweek, and you are the only one bidding. And if you do not commit to excessive time, dollars, and ego

while attending. The usual trick is to try and score several identical units so you can make a few good instruments out of the lot.

If you are doing this commercially, the object of surplus is to buy for a penny on the dollar, sell for a dime, and try to make a nine percent profit while doing so. Lean

and mean is the *only* route that works here. Auction sources include community colleges, commercial test equipment auctions, business liquidations, mil surplus, and live online venues ...

Community Colleges — Many of these colleges are phas-

ing out or sharply cutting back on electronics programs. A few years back, I bought an *entire* electronics department at auction for an obscenely low price. And made more from it than I did in 10 years of teaching for them.

Ask *all* the schools even remotely near you for ongoing auction info. You'll do best with outlying schools in small rural communities.

For higher profile examples, see www.dist.maricopa.edu.surplus or check w3.arizona.edu/~surplus/public/index.html.

Commercial Test Equipment — Several auctioneers specialize in commercial test gear. Mountains of stuff are often available, but the competition can also be fierce. Many of these are held in high tech areas. Albuquerque shows by *Bentleys* are examples.

At www.bentleysauction.com.

Business Liquidations — The listings of these often do appear in the regional auction directories. My favorite here is the Southwest *Auction Advisory*. It is also located online at, of all places, www.auctionadvisory.com. I've found best results when a few odd test items are included in an auction that moves lots of non-technical stuff.

Military Surplus — We have seen in previous columns how outstanding buys in mil surplus test equipment are easily gotten. You can now bid and pay online, and certain sales even deliver. The website is www.drms.com. Some mil stuff is now being handled commercially. See www.levy-latham.com.

Live Online Auctions — The real biggie here, of course, is www.ebay.com. Who are now milking auction addicts for all they are worth. And then some. eBay is strongest in collectibles, but more and more test equipment is now starting to appear. I found 313 power supplies, 68 oscilloscopes, and 42 meters listed on a recent check. Sadly, a lot of these were ancient junk. Or were otherwise second rate. This also seems more of a place to sell than buy, because I've found many of their prices tend to end up higher than you can find elsewhere. Be sure to watch your time and energy commitment.

I do prefer sealed bid sales to live auctions because you'll have less time commitment and you are more likely to score genuine bargains. Especially when you intentionally bid low and expect very few hits. A "never be underbid"

PRIMECELL

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT
DON'T PITCH EM! - SEND THEM FOR REBUILDING! - SAVE \$\$\$

CUNARD ASSOCIATES, R.D. 6 Box 104, Bedford, PA 15522

- WE INSTALL NEW NI-CAD OR NI-MH BATTERIES INTO YOUR ORIGINAL CASE.
- WE IMPROVE CAPACITY TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE. / EXTENDED LIFE FOR OLDER EQUIPMENT
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US / 12 YEARS IN BUSINESS.
- WE SAVE YOU **** MONEY **** \$\$\$\$



- NO JOB IS TOO LARGE OR TOO SMALL. WE OFFER VOLUME DISCOUNTS TO LAW ENFORCEMENT / COMPANIES / FIRE DEPARTMENTS / UNIVERSITIES

GENERAL ELECTRIC	UNIDEN	BENDIX KING
MPD/PLS - MPR/MPX/MPX	APH56 APX500 \$ 21.95	KR105/LAA125 \$ 34.95
19A704850P(1200mAh) \$ 34.95	APX690 1050 \$ 29.95	
19A704860P(1800mAh) \$ 39.95	1000 1100 1200 \$ 34.95	KENWOOD
PL190429763(777)G1/3 \$ 37.95	BP100/200/205 \$ 14.95	PB2 / KNB3 \$ 29.95
	205 Inc to 1350 \$ 22.95	PB21/21H \$ 14.95
MAXON SA-1156 1160 \$ 39.95		PB25/H26 \$ 24.95
TAD 1450 1510 1520 \$ 21.95	ICOM	CORLESS DRILLS
	BP2 / BP3 / BP22 \$ 18.95	Any brand 7.2V \$ 18.95
MOTOROLA	BP6 / BP23 / 24 \$ 24.95	Any brand 9.6V \$ 29.95
P200 HT600 MT1000	BP7 / CM7 / BP6 \$ 34.95	Any brand 12.0V \$ 32.95
NTN 4585 4824 5414 \$ 37.95	YAESU	Any brand 14.4V \$ 37.95
NTN 5447 5521 5545 \$ 37.95	FNB 3 4 12 14 16 \$ 32.95	
MIDLAND	FNB19 21 26 27 38 \$ 32.95	SURVEYING EQUIP.
70-B10 B16 B19 B21 \$ 39.95	FNB 17 25 35 \$ 23.95	COMPUTERS - PHONES
70-B32 70-B36 \$ 39.95		Send battery for quote.


FOR INFORMATION ABOUT YOUR REQUIREMENTS CONTACT US:
PHONE OR FAX : (814) 623-7000 E-MAIL TO: PRIMECELL@AOL.COM
SEND YOUR PACKS FOR FREE QUOTATION VIA UPS, RPS OR US MAIL
DOWNLOAD OUR CATALOG, WEB SITE: <http://users.aol.com/PrimeCell>

BATTERY REBUILD SERVICE

MANY OTHERS AVAILABLE - WRITE OR CALL
FREE CATALOG
ADD \$4.50 SHIPPING & HANDLING PER ORDER



The Pocket Programmer

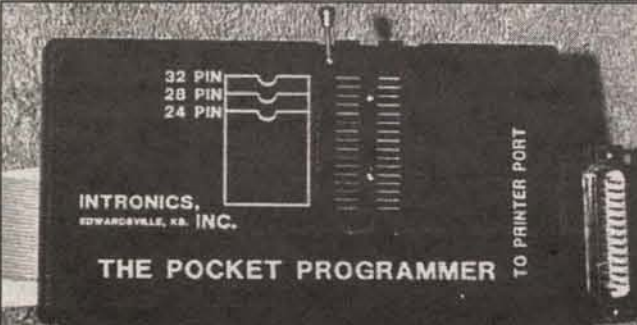

The portable programmer that uses the printer port of your PC instead of a internal card. Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)/28F/ 29F/29CXXXX & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, MCU's 874X, 875X, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang, 82/74 Prom's and Eprom Emulator to 32K X 8.
Only \$129.95

Same Name, Address & Phone Number for 16 Years....
Now isn't that Amazing ?

Intronics, Inc.

Box 13723 / 612 Newton St.
Edwardsville, KS 66113 Add \$5.00 COD
Tel. (913) 422-2094 Add \$4.00 Shipping
Fax (913) 441-1623 Visa / Master Charge / Amex

RESOURCE BIN

play will sometimes work amazingly well. The time and energy spent on pickup can also be adjusted to the value of the goodies.

It also pays to line up "associates" or "agents" who you might trade off inspection and shipping with. This can minimize non-productive travel.

For More Help

There's also a freebie trade journal called *Test & Measurement World* that sometimes has useful ads and info in it. Some more specialized instruments also appear in *Compliance Engineering*.

More obscure titles are *EMF-EMI Control*, *Evaluation Engineering*, and the pricey *Journal of Electronic Testing*.

Oscilloscopes — Restoring a Classic is your definitive Stan Griffiths book on this.

I can try to answer most simple test equipment questions free by E-Mailing me at don@tinaja.com.

The older personal computers can sometimes substitute for test gear and signal generators. You can usually make them do exactly what you want. I've got great

heaping bunches of Apple IIe and Mac LC computers available at very low cost if you want to explore these areas.

This Month's Contest

As our contest for this month, just tell me about some bargain source of electronic test equipment that I don't know about and that you can strongly and honestly recommend.

There'll be a dozen or more of my new *Incredible Secret Money Machine III* books going to the better entries. And an all expense paid *tinaja quest* for two (FOB Thatcher, AZ) going to the very best entries of all.

Send your written and snail-mailed entries on this contest directly to me here at Synergetics. NV

Don is the webmaster of his Guru's Lair found at <http://www.tinaja.com>. You can reach Don at Synergetics, Box 809, Thatcher, AZ 85552. Or send any messages to don@tinaja.com.

Scott Edwards Electronics

NEW! Graphics LCD Module with Serial Interface



The new G12864 makes it easy to display text and graphics on a 128-by-64-pixel LCD. It interfaces with a computer through a 2400 or 9600-baud RS-232 serial hookup.

Text Features

The G12864 works like a serial-receive terminal. It displays text in a 4-line by 16-character format. Text is displayed in a large 8- by 16-pixel font, which can be edited to include custom symbols.

Graphics Features

The display lets you plot points, draw lines, and display full-screen graphics using easy instructions. Its flash memory stores the text font plus 14 screens. You can create fonts and graphics on your PC, then download them to the G12864 using the included software.

Convenience Features

A power supply and DB9 serial-port connector are built in. Connect the display to the (included) AC adapter; plug the (included) serial cable into your PC or other computer, and you're ready to go. Current draw ranges from 15mA (typical, backlight off) to 100mA (max, backlight on). For complete specifications, see our web site: www.seetron.com.

Display, with starter pack: \$199 Display alone (OEM qty 1): \$179

Scott Edwards Electronics • PO Box 160 • Sierra Vista • AZ • 85636-0160
ph: 520-459-4802 • fax: 520-459-0623 • e-mail: info@seetron.com
Internet: www.seetron.com

Write in 110 on Reader Service Card.

You Win



with Nuts & Volts

Subscribe today and be automatically entered in our new MONTHLY PRIZE DRAWING!!!

February Winners:

Tony Wade

of Idaho Falls, ID

John V. Walton

of Halstead, KS

APRIL DRAWING HOSTED BY

ALLTRONICS

(see page 17)

\$50 Gift Certificate

(Towards Purchases)

SPECIAL BONUS:

NETCOM (page 13)

WILL FURNISH PRIZES MONTHLY!!

If you do not wish to order a subscription, but would like to be entered in our drawing, simply **send or E-Mail** your name, address, and telephone number, to NUTS & VOLTS, 430 Princeland Court, Corona, CA 91719, drawing@nutsvolts.com. No phone entries accepted. All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

As a current, paid subscriber, you will be automatically entered each month in our drawing.

To Subscribe — Just fill in and mail the enclosed subscription card or call our toll free order line at (800) 783-4624 with a Visa or MasterCard.

Check us out on the web!
<http://www.nutsvolts.com>

Our growing list of contributors includes ...

Parallax (back cover)

Corporate Systems Center (pages 2, 95)

HSC (page 3)

Resources Unlimited (page 36)

Timeline, Inc. (page 43, March issue)

Alltronics (page 17)

Electro Mavin (page 71)

All Electronics (page 54)

Roger's Systems Specialist (page 44)

Electronic Goldmine (page 19)

MCM Electronics (page 65)



REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Success guaranteed. Available for the following:

CANON BC-01, BC-02 CANON BJ10e, APPLE STYLEWRITER, BJ-200 Single Black Refill \$8.00; Triple Refill \$19.00. **CANON BJC-600 (BC-201)** Single Black or Single Colors (3 refills) \$8.00. **CANON BJ-130/300/330 & IBM Exec Jet** (Cart #BJI-481 & BJI-642) Black - 3-bottle kit \$22.00. **CANON BJC-210/240 (BC-05 Cart)** 3-color kit (3 refills each color for BC-05) \$24.00. **CANON BJC-4000** and Apple Stylewriter 2400 Black 3-bottle kit (3 refills BC-20, 9 refills BCI-21 black, 30 refills BCI-11 black, 10 refills BCI-10) \$19.00. **CANON BJC-4000/BJC70 and Apple Stylewriter 2400** Tri-color kit - 6 refills each color for BCI-21 or 15 refills each color for BCI-11 \$24.00. **CANON BJC-800/820/880** 3-bottle kit (for BJI-643B) \$19.00. **CANON BJC-800/820/880** 3-bottle tri-color kit (Cart #BJI-643CMY) \$24.00. **EPSON STYLUS COLOR PRINTER** - (Cart S020034) Single Triple black \$19.00; Tri-color kit (Cart S020036) 2 refills each color \$24.00. **EPSON STYLUS COLOR II** - (S020047) Triple Black \$19.00 (S020049) Tri-color (2 refills each color) \$24.00. **EPSON STYLUS COLOR 400, 500, & 600 (S020093)** Triple black (7 refills total) \$19.00; **EPSON STYLUS COLOR 200, 500 (S020097)** Tri-color 3 refills each color \$24.00. **EPSON STYLUS COLOR 400, 600, 800, 1520** Tri-color (S020089) 3 refills each color \$24.00. **EPSON STYLUS 800/1000 (S020025)** 3-refill kit, black, \$19.00. **HP DESKJET 500/550/560 (51608A, 51633A, 51626A)** Black single refills \$8.00. **HP DESKJET 500/550/560** Black 3-bottle kit \$19.00. **HP DESKJET 500C/550C/560C** - Tri-color kit (5 refills each color) \$24.00. **HP DESKJET 1200C, DESIGNJET 650 (Cart #HP 51640B)** Black Three pack (3 refills) \$19.00. **HP DESKJET 1200C/1600C, DESIGNJET 650 (Cart #HP 51640 C,M,Y)** Tri-color kit (one refill each color) \$24.00. **HP DESKJET 600/660 (HP 51629A)** Black three pack \$19.00. **HP DESKJET 600C/660C (HP 51649A)** Tri-color (5 refills each color) \$24.00. **HP DESKJET 855C/1600C (HP 51645A)** Black three pack \$19.00. **HP DESKJET 855C (HP 51641A)** Tri-color kit (2 refills each color) \$24.00. **HP DESKJET 720, 722, 890, OFFICE JET 1170 & 1175 (C1823A)** Tri-color kit (2 refills each color) \$24.00. **HP PAINTJET and PAINTJET XL (51606A)** Black 3-bottle kit \$19.00. **HP PAINTJET and PAINTJET XL (51606C)** Tri-color kit \$24.00. **HP PAINTJET XL300 (C1645A & C1656A)** Black 3-refill kit \$19.00. **HP PAINTJET XL300** Tri-color kit (1 refill each color) HP 51639C,M,Y \$24.00. **HP THINKJET, QUIETJET, KODAK DICONIX 150 (51604A or 92261A)** black 5 refills \$9.00. **IBM/Lexmark/Execjet/4076 (1380620)** black 3-refill kit \$19.00. **IBM/Lexmark/Execjet IIC, WinWriter 150 C (Cart #1380619)** 4 refills each color \$24.00. **SNAP AND FILL SYSTEM** - Permits refilling HP 51626A (black for HP 500-series) and HP 51629A (black for HP 600-series) cartridges without making a hole in the cartridge. Consists of special cartridge holder, syringe, plastic tubing, and directions. **STARTER KIT** - with ink for 3 refills \$28.00. **EXTRA INK FOR SNAP & FILL SYSTEM** (black only) 4-oz. bottle \$18.00; 8-oz. bottle \$34.00. Specify whether for HP 51626A or HP 51629A.



HARD-TO-GET PRINTER RIBBONS

Gorilla Banana, Commodore 1525 \$8.00; Adam Coleco \$12.00; TI-850/855 \$6.00; Centronics 700 Zip Pack \$5.00; C. Itoh Prowriter Jr., Riteman C+/F+ \$6.00; Riteman Informer \$8.00; Commodore MPS-801 \$5.00; MPS-803 \$7.00; Decwriter LA30/36 \$4.00; Apple Scribe \$4.00; Mannisman Tally Spirit 80, Commodore 1526 \$5.00; Epson JX-80 4-Color \$14.00; Printronix P-1013 \$11.00; Star SJ144 color 3-pack \$29.00.

ALSO HEAT & TRANSFER RIBBONS AND PAPER FOR PRINTING T-SHIRTS.

Over 300 different ribbons in stock. All ribbons new, not re-inked. Fully guaranteed.

Order directly or send SASE for complete list.

Add \$4.00 per order shipping. California residents add 7.75% sales tax. On ribbon orders over \$50.00 deduct 10% discount.

H.T. ORR Computer Supplies

249 Juanita Way, Placentia, CA 92870-2216

714-528-9822 • 800-377-2023 • FAX 714-993-6216

<http://www.extremepay.com/occomp/orr.htm>

Write in 114 on Reader Service Card.

ATTENTION DEALERS/DISTRIBUTORS

BUY DIRECT FROM THE MANUFACTURER

THESE AND OTHER VIDEO SECURITY PRODUCTS NOW AVAILABLE!!! (DEALERS/DIST. ONLY) Minimum Order.

	Qty	Qty	Qty	Qty
CCD Cameras	5	10	20	50+
B&W Board	\$57	\$52	\$47	Call!
B&W Board/sound	\$62	\$57	\$52	Call!
B&W Mini	\$65	\$60	\$55	Call!
Color - Mini	\$150	\$142	\$135	Call!

*B&W CCDs use Sansone Chips. Color CCDs use Sony.

Guardian Eye

CCD Camera Hidden Inside a "Magnavox" Clock

	Qty	Qty	Qty	Qty
CCD Clock	5	10	20	50+
B&W Wired	\$144	\$129	\$114	Call!
B&W Wireless	\$289	\$264	\$248	Call!
Color Wired	\$234	\$218	\$199	Call!
Color Wireless	\$387	\$362	\$345	Call!

Wireless use 2.4Ghz standard transmitters and receivers.

Call ATN Today for the Best Prices and Quality Security Products.

American Technologies Network Corp.
20 S. Linden Ave. #1B
S. San Francisco, CA 94080
www.atncorp.com

(800)910-2862
(650)875-0130
fax: (650)875-0129
sales@atncorp.com

Write in 115 on Reader Service Card.

Events CALENDAR

Continued from page 57

MAY 16

MA - CAMBRIDGE - Flea Market. Kendall Square area. MIT. Nick Altembernd KA1MQX, 617-253-3776. Web: <http://web.mit.edu/w1mx/www/swapfest.html>

NH - LONDONDERRY - Hamfest. Paul KILL, 603-432-1538

MAY 22

NH - DERRY - Hamfest. Londonderry Lions Club, Mammoth Rd. Rt. 128. 8am-1pm. The Interstate Repeater Society ARC, Paul 603-432-1538. E-Mail: killx@juno.com

MAY 22-23

WA - YAKIMA - WA State Convention. Yakima ARC, C. Jo Whitney KA7LJQ, 509-965-3379. E-Mail: kb7hdx@televar.com Web: <http://eagle.yk.com/~w7aq/hamfest.html>

MAY 23

CA - SACRAMENTO - Hamfest. North Hills RC, Earl Mead K6ESM, 916-331-1115. E-Mail: nhrc@k6is.org Web: <http://www.k6is.org>

MAY 29

CANADA - MANITOBA - WINNIPEG - Hamfest. Winnipeg ARC, Ed Henderson VE4YU, 204-694-0667. E-Mail: edve4yu@pangea.ca

CT - VERNON - Hamfest. Natchaug ARC, Wayne Rychling N1GUS, 860-487-1921. E-Mail: wrych@neca.com

NC - DURHAM - Hamfest. Durham FM Assn., Joseph Fields KF4QYY, 919-596-3738. E-Mail: dfma@vramp.net

Web: <http://www.vramp.net/~dfma>
NY - PLATTSBURGH - Hamfest. Champlain Valley ARC, Bernhard Jakobetz KC2ALG, 518-643-9657

MAY 29-30

WY - CASPER - State Convention. Casper ARC, Warren "Rev" Morton WS7W, 307-235-2799 (H), 307-237-9301 (W). E-Mail: mortonwg@aol.com Web: <http://w3.trib.com/~carc/hamfest.html>

MAY 30

CA - SANTA ANA - Swapmeet. ACP parking lot. Mary Russo 714-558-8813

CANADA - QUEBEC - SOREL-TRACY - Hamfest. Le Club RA, Jean Gadoury VE2UL, 450-836-3072. E-Mail: alaing@autray.net

JUNE 1999

JUNE 4-5

NE - SOUTH SIOUX CITY - Convention. 3900 Club & Sooland ARA, Mike Nickolaus NF0N, 402-494-6070. E-Mail: nf0n@avalon.net

JUNE 4-5-6

NY - ROCHESTER - Convention. Monroe County Fairgrounds. Fri: 12pm-5:30pm, Sat: 8:30am-5:30pm, Sun: 8:30am-1:30pm. Harold Smith K2HC, 716-424-7184. E-Mail: rochfst@frontier.net Web: <http://www.rochesterhamfest.org>

JUNE 5

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

IL - SPRINGFIELD - Hamfest. Sangamon Valley RC, Ed Gaffney KA9ETP, 217-628-3697. E-Mail: egaffney@fgl.net

Web: <http://www.skylight1.com/svrc>

ME - HERMON - Hamfest. Hermon High School. 8am-1pm. VE Exams. Talk-in: 146.34/94, 146.52. Pine State ARC, Roger Dole KA1TKS, 207-848-3846. E-Mail: dolerw@juno.com

MI - GRAND RAPIDS - Hamfest. Hudsonville Fairgrounds. VE Exams. Talk-in: 147.160 link repeater system. Independent Repeater Assn., Kathy KB8KZH, 616-698-6627 4-7pm.

MN - ST. PAUL - Hamfest. TwinsLan ARC, Ann Foster NOLL, 612-706-1761. E-Mail: tailgate@twinslan.org

JUNE 5-6

GA - MARIETTA - Hamfest. Jim Miller Park.

Atlanta Radio Club, Ben Dasher KE4YZX, 404-869-6959. E-Mail: bendasher@mindspring.com Charles Golsen N4TZM, 404-252-3303. E-Mail: cgolsen@atlanta.com

OR - SEASIDE - SEAPAC Ham Convention. Seaside Convention Center. VE Exams. Randy Stinson K27T, 503-297-1175. E-Mail: rastinson@att.net Web: <http://www.otvarc.org/events/hamfairs/seapac/index.htm>

JUNE 6

IL - PRINCETON - Hamfest. Starved Rock RC, Frank Carraro KF9NZ, 815-856-3773. E-Mail: w9mks@qsl.net Web: <http://www.qsl.net/w9mks/>

NY - QUEENS - Hamfest. Hall of Science parking lot, Flushing Meadow Park Corona, 47-01 111th St. 9am-3pm. Talk-in: 444.200 repeat, PL 136.5, 146.52 simplex. Hall of Science ARC, Stephen Greenbaum WB2KDG, 718-898-5599. E-Mail: WB2KDG@Bigfoot.com

OH - MEDINA - Hamfest. County Fairgrounds, Community Center, 735 Lafayette Rd. 8am-3pm. Talk-in: 147.630 in, 147.030 out. Medina 2 Meter Group, Mike Rubaszewski N8TZY, 330-273-1519. E-Mail: m2mggroup@aol.com

VA - MANASSAS - Hamfest. Ole Virginia Hams ARC, Mary Lu Blassell KB4EFB, 703-369-2877

JUNE 11-12

GA - ALBANY - Convention. Albany ARC, Ricky McCrary KD4OZR, 912-438-9714. E-Mail: rmcrary@plantel.net Web: <http://www.isoa.net/aarc>
TX - ARLINGTON - Convention. HAMCOM, Jim Haynie W5JPB, 214-351-3271. E-Mail: jimhaynie@aol.com

JUNE 12

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

CANADA - ONTARIO - FERGUS - Hamfest. Guelph & Kitchener-Waterloo ARCs, Bill Smith VE3WHS, 519-821-6642. E-Mail: smith.ve3whs@sympatico.ca Web: <http://www.kwarc.org/fleamarket>

CT - GOSHEN - Hamfest. Southern Berkshire ARC, Lee Collins K1LEE, 860-435-0051. E-Mail: collins@li.com

MA - FALMOUTH - Hamfest. Falmouth ARA, Ralph Swenson N1YHS, 508-548-6405. E-Mail: depsher911@aol.com Web: <http://www.falara.org>

MO - MACON - Hamfest. Macon County ARC, Dale Bagley K0KY, 660-385-3629. E-Mail: dbagley1@istmacon.net Web: <http://www.istmacon.net/~kfoster/hamfest.htm>

NC - WINSTON-SALEM - Hamfest. Tom Gallagher N4IOZ, 336-723-7388. E-Mail: n4ioz@ibm.net Web: <http://members.xoom.com/w4nc/>

PA - BLOOMSBURG - Convention. Columbia-Montour ARC, Dave Schack WC3A, 717-752-6851. E-Mail: kev17815@epix.net Web: <http://www.bafn.org/~cmarc>

ACP's 91st GIANT COMPUTER SWAP★MEET

Orange County's Original! All Day Sunday 8am-2pm

Be a Seller...for your space Call Mary

May 23rd FREE Admission & Parking Shop 100's of Sellers

in ACP's Giant Parking Lot !!!

Advanced Computer Products, Inc.


ACP SUPER★STORE Since 1976

1310 E. Edinger Santa Ana, CA 714-558-8813

You can now read the entire events calendar online at www.nutsvolts.com with listings for shows upcoming throughout the year.

MARINE ELECTRONICS FOR THE LAND RV MARKET

by Gordon West

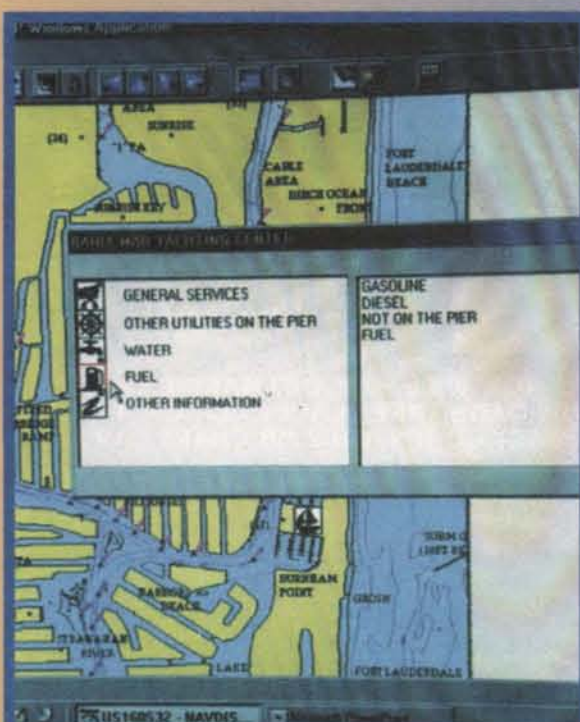

**MARINE AND LAND SOFTWARE FOR
BOATS AND RVs WITH A LAPTOP
COMPUTER ON BOARD.**

Electronics that go into boats and vehicles share a lot of common applications. Both boats and cars run on 12 volts. Boats and RVs are regularly plugged into 110 VAC when at the dock or at the campsite. Both types of moving vehicles may generate radio reception interference, and both the sailor, as well as the RVer want to know exactly where they are at anytime. Both sailors and RVers are always interested in upcoming weather conditions, and both the boat, as well as the vehicle may require special grounding techniques in order to make the radio and navigation receiving equipment work properly.

If you compare a big, thick marine electronics discount catalog to a big, thick RV accessories catalog, you will see many manufacturers displaying similar equipment for both markets.

And this is good for us. The more avenues of sales and distribution, the greater the volume of equipment sold, and individual equipment prices become quite affordable.

There is also the advantage of technology exchanges between both mobile markets. Portable electronics for boats must be absolutely waterproof to the point of passing a submersion test. For the RV market, this means you can take your little portable radio or navigation receiver out on the snowmobile or in a driving rainstorm, and have it survive without water damage. And this same piece of equipment might show land navigation streets and freeways when you are in the RV, and then double

as a marine electronic charting device when out on the waves. So, here are some double-duty electronics that can very well satisfy the requirements of both sailors, as well as land rovers.

HIP-POCKET GPS

Garmin and Magellan are the undisputed GPS pace-setters. Both companies were one of the first to offer a marine low-cost, portable GPS receiver well before the entire GPS constellation was in place. In fact, during Desert Storm, civilian receivers were in high demand by the military, even though they lacked the secondary military receiving frequency for a more precise position fix. As you may remember, the military turned Selective Availability to zero during much of the Crisis. (Selective Availability is the military's on-purpose dithering of clock time to deny unfriendly use of this worldwide navigation system by the enemy.)

Magellan has just announced a \$50 million joint-venture with Hertz to equip 50,000 rental cars in the United States, Europe, and Canada with next-generation navigation technology. The Magellan "Smart Car" navigation technology allows users to simply input a local street address, or choose from a range of destinations including hotels, airports, restaurants, and points of interest.

Magellan then transforms this technology into their portable marine navigation receivers, putting in marine "points of interest" such as fuel docks, buoys, lighthouses, and yacht clubs.

But Garmin counters with a \$300.00 portable that lets you upload from CD-ROM cartography street-level mapping, and without any cartography upload, a base map showing major highways and secondary roads including information about available lodging, food, and service stations in their GPS III.

But Garmin is best-known for their StreetPilot that can be ordered in a monochrome readout or, for in-vehicle use, color LCD readout. The StreetPilot sells for around \$550.00, and includes the embedded base map that gives you sufficient detail and guide to services to easily get you across the United States.

The StreetPilot is more designed for the RVer than the mariner because coastline detail is not intended for navigating in and out of harbors on the screen. Freeways yes, harbors no.

To get down to street level, you need to purchase a local area Garmin street map cartridge using ETAK cartography that has been updated to 1998 roads. The cartridges could cost anywhere from \$100.00 to \$300.00, depending on how many MB to cover a specific geographic area. ETAK and Garmin have done a good job to structure their cartography so as not to drop out in an important area when leaving or entering town.

"When comparing the StreetPilot plug-in cartridges to the CD-ROM cartography, we see many more new roads and new freeways appearing on the little expensive cartridges than what we see coming from the CD-ROM," comments Joel Levy, an avid mariner and RVer.

Lowrance is also bridging the land and ocean markets with a GPS charting receiver called GlobalMap 1600. "We have designed this product for both the land and marine markets," comments Chad Worford of Lowrance. "Our MapSelect/MapCreate software enables sailors and RVers to selectively upload street-level cartography for driving in any city in the USA, worldwide cartography of major highways, inland lakes and rivers cartography for freshwater fishermen, and marine cartography for US coastal wrecks, obstructions, and selected navigational aids," adds Chad. You upload a specific 2 MB of marine or land street detail by connecting the dots seen on your laptop screen on the Lowrance fixed or portable GPS charting equipment. A small city takes under 1 MB of memory, yet a big city like Los Angeles gobbles up almost 2 MB. The upload takes place at 57,600 baud, so it takes about 10 minutes for a complete memory upload of your desired cruising or driving location.

"You simply draw the border around the area of interest by clicking on grid marks, and each click draws part of the box around an area of the map. When the box is complete, you simply click on the create map icon and save it to the hard drive, or upload it to the Lowrance dis-



**NEW COLOR LCD SCREENS WORK WELL
IN A BRIGHT AND WET COCKPIT.**



**THIS RADIO CAN TAKE RAIN, AS WELL
AS AN UNDERWATER BATH.**



**AUTHOR WEST (R) GETS THE STRAIGHT
SCOOP ON GPS AT THE MAGELLAN
BOOTH AT A COMBO MARINE/RV SHOW.**



THE UPLOAD BLANKS OUT WHEN MEMORY IS FILLED TO CAPACITY ON THE PORTABLE GPS.



LAND CARTOGRAPHY IS NOT SUITABLE FOR DETAILED OCEAN AND HARBOR NAVIGATION.



HOW WILL MAP AND MARINE CHART UPLOADS TAKE PLACE? CD-ROM, PCMCIA CARTRIDGES, OR 2 MB CHART CARDS?

play unit," comments Julian Frost, a computer expert who advises me on the latest in GPS technology.

When viewing the Lowrance street cartography, there is plenty of detail, down to 500 feet, but the streets don't have quite the finished look that you would get on the Magellan or Garmin land units. We also saw some overlay discrepancies where streets extended out into the ocean, rather than ending at a cul-de-sac on a bluff. But this is a relatively inexpensive (under \$500.00) unit, and you really can't compare it to those in-vehicle, permanently-installed mapping devices which cost over \$1,000.00 plus additional costs to unlock specific areas on the CD-ROM.

So will we end up with cartography on a chip or on CD-ROM? Will CD-ROM providers give us the entire United States, or give us specific cities that must be electronically purchased by unlocking portions of a CD-ROM? Manufacturers and CD-ROM mapping companies are still working on the best way to present these products to both sailors, as well as land users.

WET TALK

Handheld two-way radio manufacturers have now developed methods to keep water out of the insides of their equipment. Standard Communications, the marine electronic giant who first pioneered a Japanese VHF handheld transceiver, offers a submersible Model HX350 for around \$275.00 that works on all marine domestic and international channels. They also have a new fixed-mount marine VHF that can actually float — although I can't imagine why any mariner would want a floating 25-watt radio still hooked up to their 12-volt battery system aboard!

Standard Communications has just been acquired by amateur radio giant Yaesu, and this

means ham operators may soon find submersible handheld equipment sharing the design from Standard's marine radio line. We will also see Standard Communications ending up with a dandy long-range, single-sideband radio, designed by Yaesu.

But no one knows what may happen to the popular Standard radio line of ham equipment, marketed out of Chicago, and principally sold by TechAmerica. Yaesu's buy-out of Standard was just their marine and land-mobile divisions, not the ham division. You figure it out!

Garmin is now in the submersible market, and under \$160.00 with their Model VHF720 all-channel marine VHF handheld. And Garmin JUST announced a new cellular phone product that incorporates a GPS receiver and GPS charting so you can call up another Garmin cell phone, and you can each look on your own display and see where the called party is located.

Garmin also offers a service that would allow RVers and boaters to call a designated Garmin service provider; and as soon as the Garmin cell phone rings through, they know your location by an embedded GPS datastream, and can send help to you whether you are on the freeway or in mid-channel taking on water.

Or maybe you are out skiing, and a white-out gets you completely turned around. You can either watch your combined cellular/GPS screen for a track back to civilization, or dial an emergency help number and let them see your position to arrange help to be brought in. And yes, this equipment is also waterproof, too, against waves, snow, and driving rain.

COMS AND NAV

There is no comparison between factory-installed vehicle GPS navigation systems offering incredible local advantages over portable equipment that does double-duty aboard boats

and land yachts. However, the double-duty portable equipment is far less expensive, and can be taken virtually anywhere without a hard-wire vehicle system. The portables can also work the trails, the ski slopes, snowmobile paths, and could even survive an accidental shallow-water dunking.

But the big question is how the cartography will ultimately upload into portable equipment. Will the relatively expensive 1 MB, 2 MB, and 3 MB chip cards remain in our future, or will we buy cartography off of the web by unlocking CD-ROM mapping and charting fields? Or maybe the cartography will be absolutely free, and you can load as much from your computer to your GPS set as your portable equipment can hold. But what are you going to do when you are out there in one region, and now move into another region, and your laptop has been left behind? Now the chart cartridges which you can keep in your backpack begin to have field-interchangeable benefits. Or will we see portable mapping GPS equipment with increased memory to give us 5 to 10 states of street-level mapping capabilities? Right now, portable street-level detail may only give you one or two cities, certainly not five or six states.

Marine cartography vector chart makers like C-Map and Navionics are still considering their options. What will the market demand when it comes to street-level cartography and boat harbor ports and services detail?

One of the most complete catalogs on low-cost marine electronics is available from Consumers Marine Electronics, located in Wahl, NJ. You may visit them on the web at www.cmelectron.com, or phone them for their all-color, 175-page, marine electronics catalog at 732-681-9025. This catalog has about the lowest prices mail order for marine equipment that can do double-duty in an RV or in your car.

NV

PRINTED CIRCUIT BOARDS

**QUALITY PRODUCT
FAST DELIVERY
COMPETITIVE PRICING**

- * UL approved
- * Single & Double sided
- * Multilayers to 8 layer
- * SMOBC
- * LPI mask
- * Through hole or SMT
- * Nickel & Gold Plating
- * Routing or scoring
- * Electrical Testing
- * Artwork or CAD data
- * Fast quotes

PROTOTYPE THROUGH PRODUCTION

PULSAR, INC

9901 W. Pacific Ave.
Franklin Park, IL 60131
Phone 847.233.0012
Fax 847.233.0013
Modem 847.233.0014
www.pulsar-inc.com

PRODUCTS FEATURES ORDER NEWS LINKS

Black Feather ELECTRONICS

Black Feather Electronics
10841 Noel St. #106
Los Alamitos, Ca. 90720

DIRECT DIAL: (714) 236-1776 FAX: (714) 236-1778 E-MAIL: blkfea@juno.com
WWW.BLKFEATHER.COM
 WE BUY EXCESS/SURPLUS ELECTRONIC SUPPLIES

AMATEUR ROBOTICS

NOTEBOOK

by Robert Nansel



Last month, I was only able to give you a few glimpses of Parallax's new GrowBot kit. My first child had just been born — a healthy nine-pound boy! My in-laws and parents were in town to help out and to coo at my son Yonatan. And to take hundreds of pictures of him; at one point, there were so many flashes going off, it was like our household had been invaded by paparazzi. Things were sorta hectic around the robot ranch, see?

Nonetheless, I was able to put a GrowBot together on my kitchen table in between miscellaneous baby crises and photo-ops. However, I wasn't able to get downstairs to fire up Igor, the ancient 386 I keep locked up down in my basement. That meant I couldn't try out any of the software that comes with the GrowBot kit since, alas, Parallax doesn't have a version of their PBASIC development tool that runs on the Mac.

GrowBot through its paces. I also have some new web sites to recommend and a contest announcement later, but first I want to talk about GrowBot.

A Growing Bot

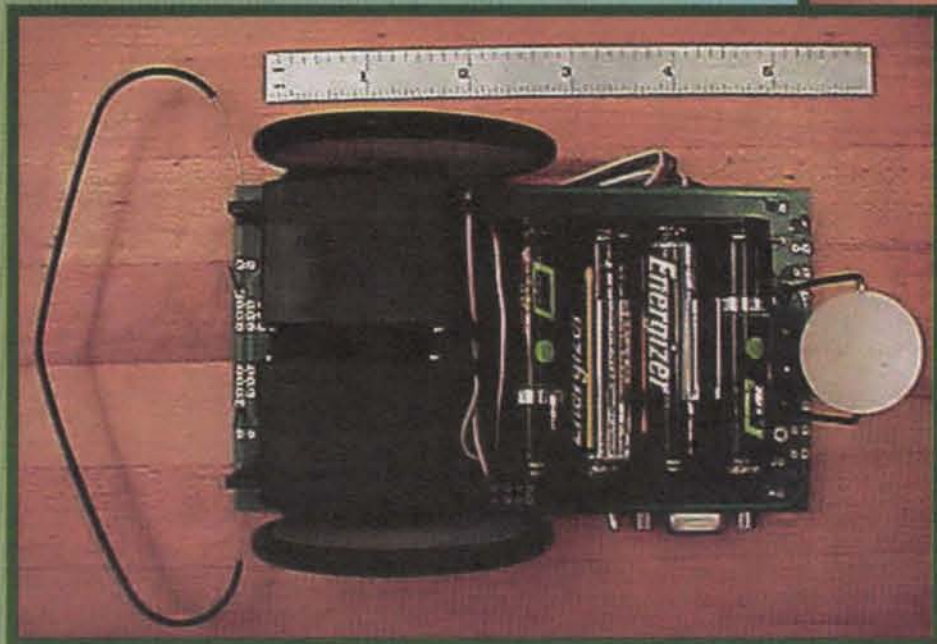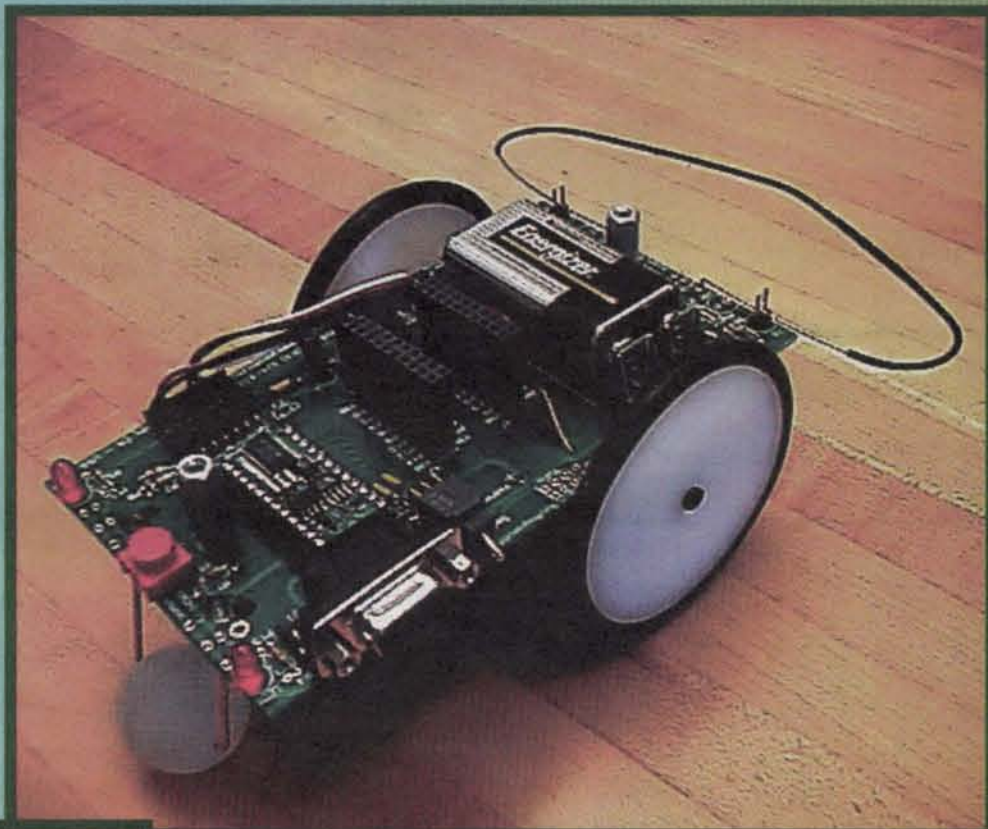GrowBot is \$179.00 and for that you get an unassembled kit of parts (see photos) — everything you need to build a compact desktop-class robot. It uses standard hobby servos (included) for its drive-train. A 3" x 5.25" PCB serves as its chassis on which all other parts are mounted. Its wheels are 2-5/8" diameter, and its width overall (without the bow-tie bumper) is 3.75". With the bow-tie bumper,



(I know, I could run it with a DOS or Windows emulator on my Mac, but the idea of intentionally running DOS code on my Mac somehow seems evil and wrong.)

Anyway, some of last month's chaos has finally subsided. The grandparents have gone home; Yonatan is six weeks old and now weighs nearly 13 pounds (honest, milk is all we feed him, not steroids). While Yonatan doesn't sleep through the night yet, my wife and I have settled into something of a routine. I can get down to my workshop regularly enough to work on robots again, and I used my time this month to run

it's about 5.25" wide, and its overall length is 7.25". Its height without any AppModules installed is 2-5/8".

The GrowBot kit includes a prefabricated bow-tie bumper sensor. Unlike Breadbot, GrowBot doesn't have side whisker sensors; it makes do with just two input bits to distinguish left, right, and center.


Other running hardware includes a user-programmable push-button switch, a small speaker, and two rear "tail light" LEDs. The speaker

circuit can also be used to monitor servo battery voltage, though the manual doesn't show how to use this function. I measured the impedance of the sounder with a DVM: It's about 50 ohms, a dead short to ground compared to the 220K ohm pullup and 100K pulldown resistors. Combined with the speaker's 10 uF coupling capacitor, I imagine it's intended to be used with

PBASIC's RCTIME command to digitize the level of Vservo, though the manual doesn't talk about this.

AppMods

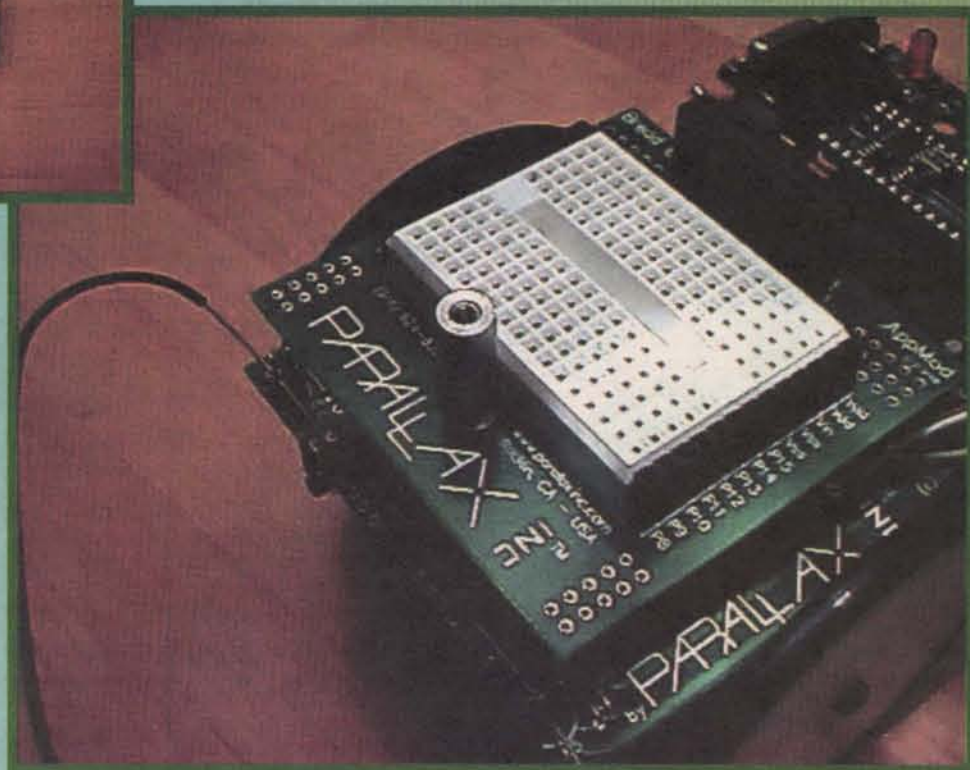
In the middle of the PC board are two 20-pin female header connectors that allow customization and expansion of GrowBot with what Parallax calls AppMods. These are 2.5-inch-square stacking daughterboards. One end of an AppMod





has the 20-pin stacking connector, and the other end has a hole for a 4-40 male/female aluminum hex standoff that ties the AppMod rigidly to the GrowBot chassis or to

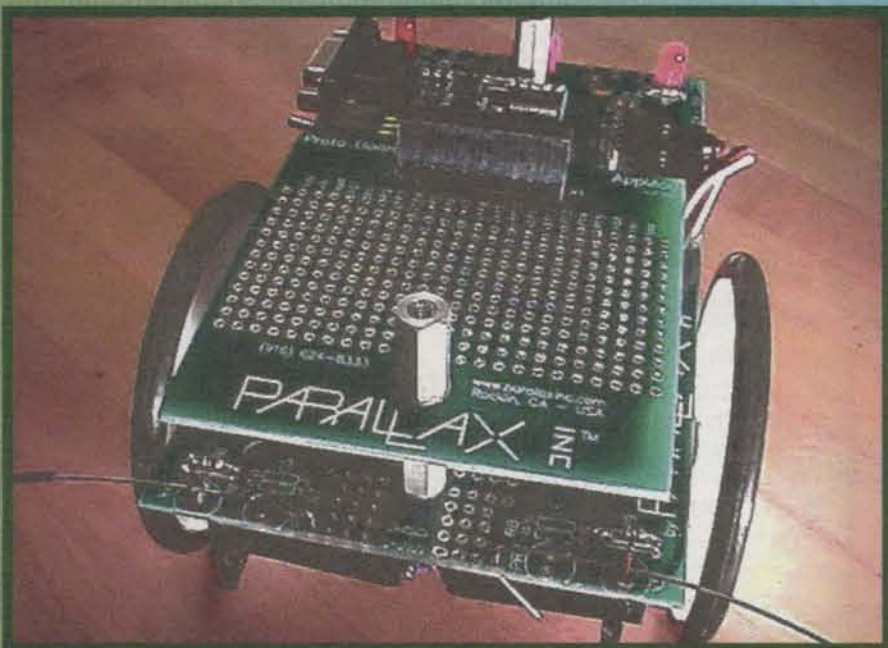brought out on GrowBot's AppMod connectors. There are currently two module types available: the solderless Breadboard (P/N 29114, \$29.00 US) and the lower



another AppMod below.
All 16 of the BS2-IC I/O lines, plus Gnd, Vss, and Vdd, are

profile Prototype Board (P/N 29110, \$19.00 US). The Prototype Board has a stacking clearance



height of 1/2", so you won't be able to use standard wirewrap construction, but point-to-point will work just fine. The Bread Board module has enough room for a couple 16-pin DIPs. It has a 5/8" stacking clearance, but all components you plug into the solderless breadboard have less than 1/4" clearance if you plan to stack another AppMod on top.

The Prototype Board has a 13-column by 24-row grid of pads but, for some reason, Parallax chose to bus together the second, third, and fourth columns on both the left and right edges of the board for Gnd, Vin, and Vdd. Not only that, they left the single columns of pads closest to the edges isolated from all the other pads. Most of the two rows of pads closest to the stacking connector are committed to the expansion bus, effectively reducing the uncommitted prototyping area to a grid of just 11 columns by 16 rows.

My preference would have been to lay out power and ground on either the left or the right side (but not both), and to start with that first column. This would have given an effective 11-column by 21-row grid — much more useful. You'd be able to prototype with a 40-pin DIP, for instance, or a couple 16-pin DIPs end-to-end.

Another style of prototype board would be a simple PC board version of the Bread Board AppMod so you could transfer circuits you breadboard directly to a more permanent (and cheaper) AppMod. If this sounds like I'm complaining, I'm not. I'm hoping Parallax will eventually come out with more AppMods that address these concerns.

Some upcoming AppModules include the "ISD Mobile Recording Studio" (P/N 29111) and the "LED Display Terminal" (P/N 29112). These should be available by the time you read this, though I don't know what the pricing will be.

The Civilized Robot

One nice feature of GrowBot is that it uses separate batteries to power the BS2-IC and the servos, thus increasing battery life and system reliability. The kit also includes a three-position power switch. When the switch is in the center position, this allows programming and debugging your software without servo power applied. No more runaway robots and no more yanking the servo connectors off every time you want to test code.

Another civilized feature is that the kit comes with a standard DB-9 serial connector for programming the BASIC Stamp. And a cable so you can connect directly to your PC. All in all, GrowBot is an elegant, well-thought-out kit.

Some Assembly Required

The only tools you need are a soldering iron, a small Phillips screwdriver, a small pair of diagonal cutters, and a pair of needle-nose pliers. A pair of scissors and a hobby knife come in handy, too.

The assembly manual gives a definite order of assembly which I highly recommend you follow since some components (the AA-cell battery holder and the velcro servo mounting pads) must be installed on the underside of the board only after all the components on the other side are soldered in. The only place I deviated from their suggested order was with the photoconductive cells.



I was eager to get the basic system up and running, and since the photocell sensors aren't used by the ROVER.BS2 program, I left them out. They are no trouble to add later when you want to run EDGE.BS2 (which does make use of the photocells), and they are somewhat fragile and tend to get in the way. I have come up with a couple suggested changes to the way these sensors are mounted, but I'll get back to that in a moment.

Servo Mods

The only part of assembly that can be considered tricky is the modification of the servos included with the kit. These are stock Futaba FP-S148 servos, so they must, of course, be modified for continuous rotation. There are several ways to modify servos, but the way I've always done it is to open the servo, remove the position feedback potentiometer from the circuit board, and replace the pot with a fixed resistor divider network — very simple and rugged (see <http://www.seattlerobotics.org/guide/> for a good illustration of this method).

Parallax chose another method, one which I'd known about but had never tried before I built GrowBot: they keep the potentiometer in place, but mechanically disengage the potentiometer shaft from the servo output shaft. This is accomplished by removing a plastic coupler that links the potentiometer to the output shaft, an operation that is more easily reversed than the fixed resistor method. Since no desoldering is involved, the servos don't have to be disassembled as far (only the gear case cover needs to be removed).

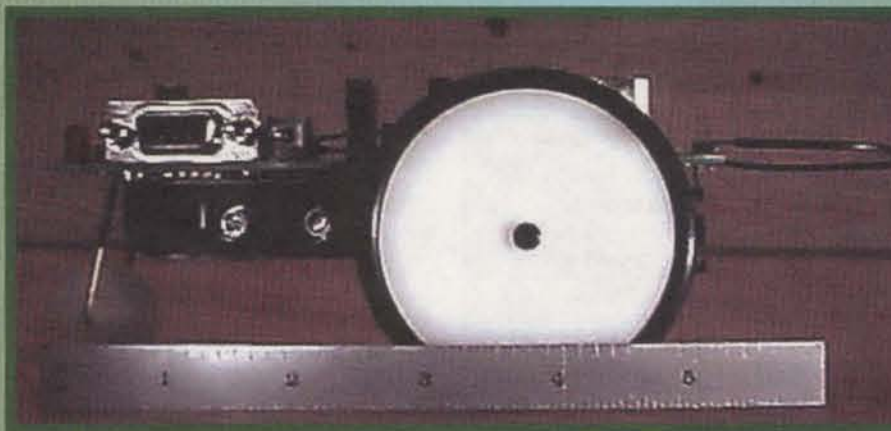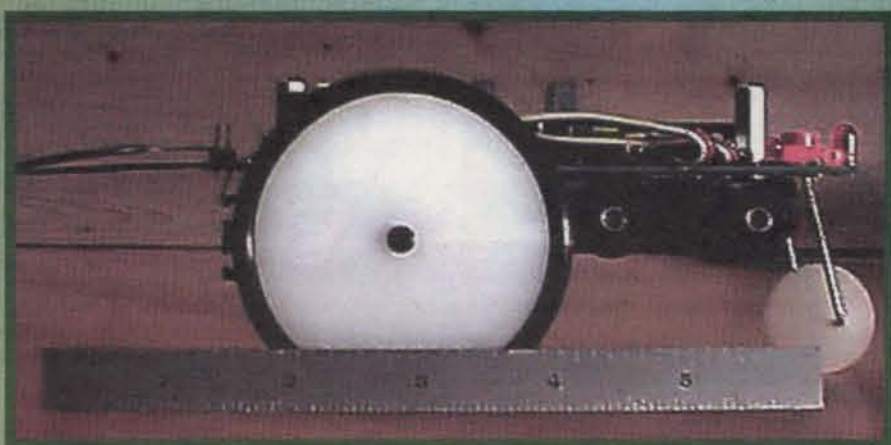Also, it's a snap to calibrate the stop ranges of the servos. While the gear case cover is off, you simply feed 1.5 msec pulses to each servo and then adjust the potentiometer until the motor stops turning. The nifty thing Parallax did was to pre-program the BS1-IC controller included with the kit to pro-



duce these 1.5 msec pulses on the servo ports.

The test software (GROWTEST.BS2) also facilitates testing the rest of GrowBot's hardware, the bumper sensors, the push-button switch, the speaker, and the rear "tail light" LEDs.

Roll Over, Rover

ROVER.BS2 was the program I was really eager to try. It is broadly similar in behavior to Breadbot's WANDER.ASM program from last month. One difference is that GrowBot doesn't pick a random direction to turn after it backs up from a head-on collision; it always turns the same direction, a backing left turn.

Another difference is that GrowBot uses its LED tail lights to show which bumper switch closed

(left, right, or both), and consequently what evasive maneuver it is performing. It also chirps on completing a turn after a head-on collision. Though I generally consider myself immune to such cosmetic details as blinky lights on robots, I must admit that they imbue GrowBot with a certain personality. It also makes it simple to tell what GrowBot is up to at any moment.

GrowBot's bow-tie bumper also performs very well; it is fully up to the task of determining whether a collision occurred on the left, right, or center, even though it lacks separate left and right whiskers. I suppose this means that if I rewired Breadbot's own bow-tie bumper to use two I/O bits instead of just one, and modified the software accordingly, I could get Breadbot to resolve five collision directions: left, front-left, front, front-right, and

right (that will have to be a project for a future column, though).

GrowBot on the Edge

The second major program included with the GrowBot kit is EDGE.BS2, which performs two functions: First, it uses the bumper to change direction when it runs into objects; second, it uses the photoresistors in front to avoid falling off the edge of the table (or crossing dark areas on a surface).

On my table, at least, EDGE isn't too successful. It runs GrowBot a little too fast, first of all, which tends to make the photo-sensing flaky, but that's just a matter of tweaking the code.


The more serious problem is that, even when the sensors work as planned, it's physically impossible for a robot with only two front-mounted sensors to avoid backing off the edge of the table at some point in its maneuvering.

Make no mistake; it's nice to be able to experiment with photocells as drop-off detectors; just don't bet your robot on that capability. I had to catch my GrowBot from tumbling off my kitchen table several times during my tests. There are several uncommitted pads along the rear edge of GrowBot's PC board, though, so rear-mounted drop-off detectors are a definite possibility and would make an excellent add-on project (yet another project for a future column).

If you start tweaking the code for EDGE, it will soon become apparent that it would be relatively straightforward to change the steering logic in the program to transform GrowBot into what's known as a *photovore* (a robot that steers toward light). By reversing the logic or the sensors in software, you'd get a *photophobe* (a robot that steers away from light).

You would probably want to bend the photoresistor leads so the sensors faced forward, and you might want to add some mechanical support and insulation so the leads won't short out against each other or the bow-tie bumper.

Hint: Plastic coffee stirrers work very well as mechanical supports and insulation. Visit a donut shop and get the kind that are like tiny, two-tubed drinking straws. Before soldering your photocells to the PC board, cut two lengths of coffee stirrer to about 1-1/4" each, about a quarter-inch shorter than the lead length of the photocells. Insert the leads of each photocell into the holes of its coffee stirrer. If you want the photocell to face forward, all you do is heat the middle of the stirrer for a few seconds with a heatgun or can-

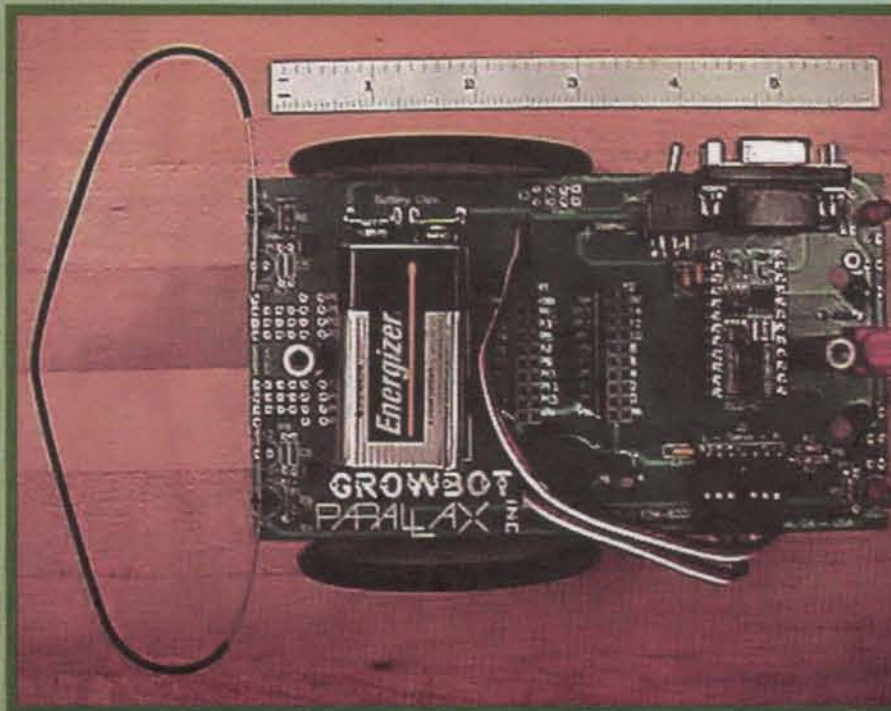

D.T.M.F. DECODER

For interconnect and remote control applications

Model NC401

The Model NC401 is a micro-miniature DTMF

decoder, designed for selective control of local or remote applications.

\$59.95

Measuring .80"Wx1.37"Lx.23"H, the NC401 combines three distinct, multi-addressing decoders offering multiple user-configurable functions. All programmed features are stored in non-volatile E2Prom memory and are easily programmed by means of a conventional DTMF encoder or the Model NC500 Universal/P.C. programmer. This highly engineered decoder is ideal for portable radio applications having limited space for accessories. The NC401 comes complete with micro-miniature 14 pin header and 12" color coded cable assembly.



VOICE SECURITY ENCRYPTION

The Model NC802 is a miniature inversion scrambler designed to provide

intermediate level security for two-way radio voice communication systems and is a perfect, cost-effective solution to entry-level voice scrambling as a defense against unauthorized or casual listeners. The NC802 provides eight user selectable carrier codes commonly used by other manufacturers and interfaces easily to most radios with near transparency to the user.

\$59.95




Nor-fax Doc. #5759

For Detailed Specifications or Product Catalog call our 24-Hour NorFax retrieval system at 530-477-8403 or on our Web Site at www.norcommcorp.com



800-874-8663

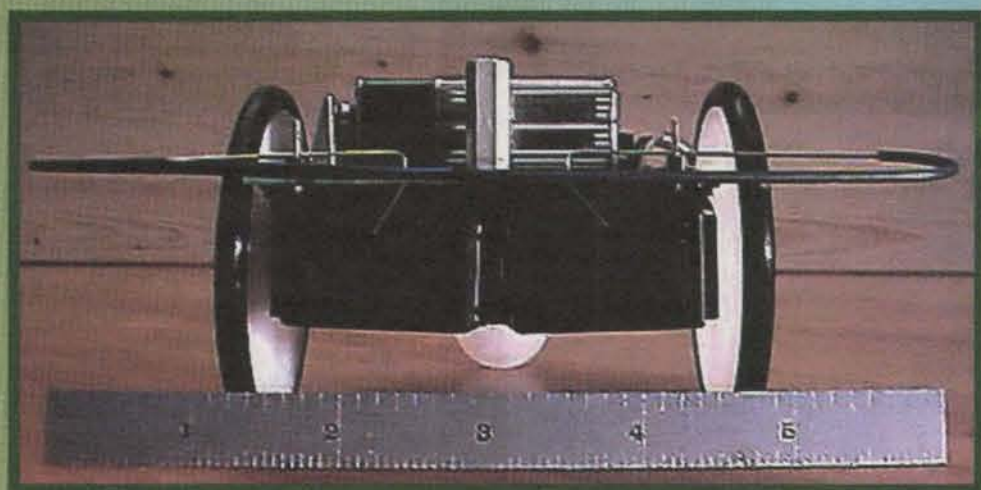15385 Carrie Drive
Grass Valley, CA 95949 USA



dle flame until the plastic is soft enough to bend; make a quarter twist and then make a 90 degree forward bend. Set aside to cool. This is also a good time to eat the donuts you bought.

Another useful modification to make in conjunction with the above is to modularize the photocells by soldering two-pin male header connectors in the pads meant for the photosensors. Where the manual says to solder the photocells, solder in the headers instead so they stick

down from the underside of the board. Then solder the leads of each photosensor to its own two-pin female header. Now you can easily remove and replace the photoresistor sensors. Or, even entirely change the type of sensor.

What's Missing

I'd like to see more examples of robot programming techniques in the manual — not necessarily complete programs such as EDGE

and ROVER. But at least program fragments that show you how to accomplish various functions. One example that immediately comes to mind is how to program the battery monitor function.

I'd also like to see a few hardware project examples. There are a number of uncommitted pads on the PC board, so some simple project examples that you could do by wiring in a few components from

RadioShack would be ideal. Of course, any large-scale projects would more properly be done with AppMod boards. I don't know if Parallax intends to include suggested project booklets with the Bread Board or Prototype Board AppMods, but it would certainly be a good idea.

Perhaps Parallax could sponsor a project competition to encourage folks to design their own AppModule projects, then publish the projects they receive in a booklet. Everybody wins. Whatever they ultimately do, I do plan to present my own AppMod projects in this column from time to time in the future. And if any of you out there with GrowBots build projects of your own, I'd love to hear about them.

Breadbot Code Online

A couple weeks ago I got a note from Kevin Coble, the author of MacPIC, a superb Macintosh integrated development environment for PIC chips. Kevin has started a webpage devoted to those of us gearheads who prefer to use Macs as our main development machines, and it's called the MacRobotics webpage.

The best part is that Kevin has graciously offered to make Breadbot's PIC assembly source files available online from MacRobotics (<http://www.MacRobotics@MacRobotics.com>). For the most part, MacPIC is compatible with all of the MPASM and MPLAB directives, but he does have to make some slight modifications to the files so they will assemble correctly with MacPIC. All the changes he makes are clearly marked, though, and any DOS or Windows specific stuff is merely commented out, so the changes are easily reversed for those of you DOS or Windows users who don't want to retype the files. Thanks, Kevin.

DiaperBot

I wish. I daydream about such a machine, but my son will probably be in college by the time I get

DonTronics
P.O. Box 595
Tullamarine 3043
Australia
Tel: 613+9338-6286
Fax: 613+9338-2935
dontronics.com
(SIMMStick PC boards, development systems, & software)

MacPIC, by Kevin Coble
<ftp://ftp.srv.net/pub/users/kxc/>
(Macintosh shareware: integrated editor, assembler, simulator/debugger, & programmer for PIC microcontroller)

MacRobotics Webpage
www.MacRobotics@MacRobotics.com

Parallax, Inc.
3805 Atherton Road, Ste. # 102
Rocklin, CA 95765
Tel: 1-800-512-1024, 1-916-624-8333
www.parallaxinc.com
(GrowBot, SX-Key debugger/programmer, BASIC Stamps)

The SIMMStick Webpage
www.simmstick.com

something like this worked out. Oh, well.

In the meantime, I have plenty to keep me busy. Another note I received recently was a contest announcement from Don McKenzie of Dontronics fame. He and other SIMMStick Dealers around the world are sponsoring SIMMStick Design Contest99. Design your system using SIMMStick products (of course) and you could win up to \$500.00 US. Many other prizes such as SIMMStick boards, regional prizes, etc.



SIMMStick products currently support PICmicro and Atmel Micro controllers (8051/AVR). However, you may use any microcontroller or peripheral you like, provided it is mounted on a SIMMStick board. The deadline for contest entry is November 1, 1999. For more information, check out <http://www.simmstick.com>.

That's it for this month. Next time, we'll talk about wheel speed sensing and odometry techniques.

NV

As always, if you have suggestions for improving Breadbot, if you've built a Breadbot, or if you have questions or comments about amateur robotics topics, you can reach me at:

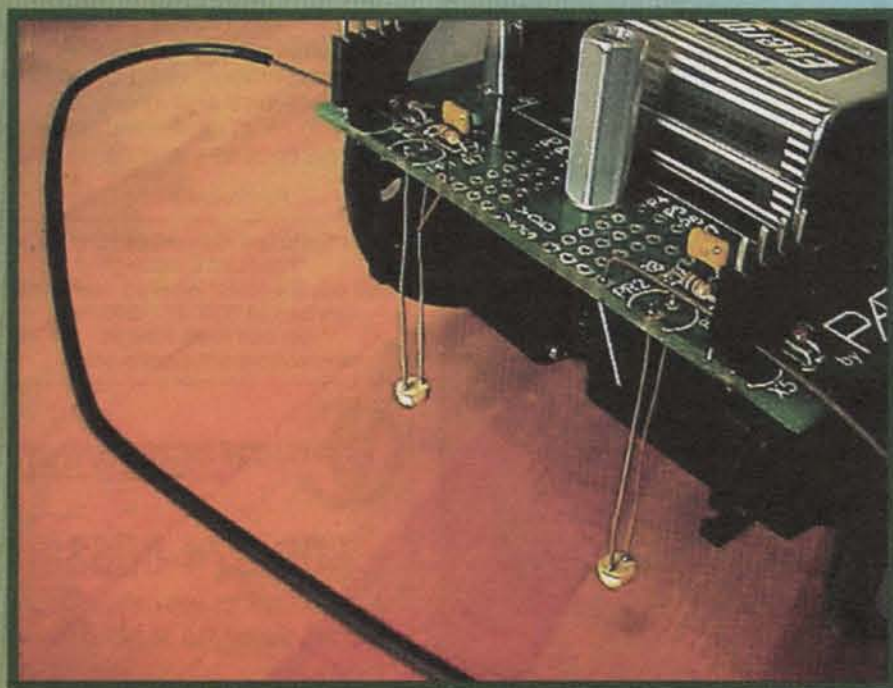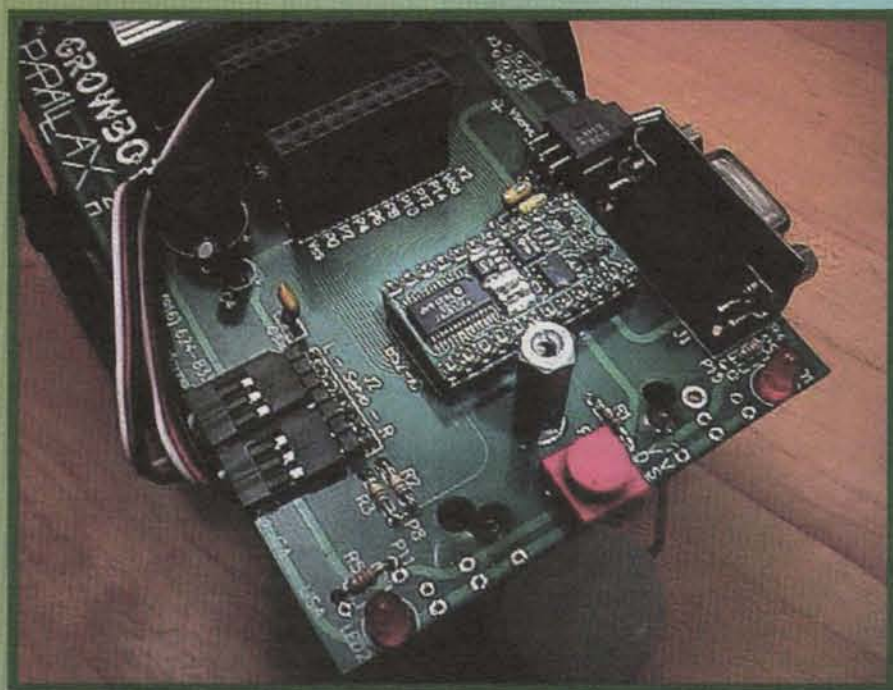Robert Nansel
69 S. Fremont Ave. #2
Pittsburgh, PA 15202
E-Mail: bnansel@nauticom.net



New Product News



QUAD COMPRESSOR

American Innovations, Inc. introduces the CQ-204 Color Quad Compressor. This color quad compressor will enable you to view and/or record up to four cameras in real time on one monitor or VCR.

The compressor has four BNC video inputs, one alarm input remote control that supports up to four sensors, and two video outputs.

The compressor works in real time 60 fields/sec for NTSC and 50 fields/sec for PAL. The compressor features high resolution – (1024 x 512 pixels), quad and full screen selection, freezes individual quadrant function,

manual and automatic switching with programmable dwell time, and video loss detection with on-screen warnings.

The CQ-204 Color Quad Compressor measures 14 x 10 x 2 inches, and weighs 5 pounds.

The special introductory price is only \$325.00.

For more information, contact:

AMERICAN INNOVATIONS
119 ROCKLAND CENTER #315
DEPT. NV
NANUET, NY 10954
914-735-6127 FAX: 914-735-3560

WORLD PACK™

Cutting Edge Enterprises has come to the rescue of the vacationing HAM.

The World Pack™ lets you carry your 100-watt station on your back. Bring the radio easily on planes, trains, or safe and compact in your car.



The specifically designed man-pack will carry the new mobile HF rigs, such as the ICOM-706 or Yaesu FT-100 securely on your back with a compartment below for a rechargeable power supply and a pocket on the side to secure your mobile antennae.

The backpack is constructed of laminated heavy-duty black nylon with 1/4" foam padding. The construction is sturdy, well-padded, and weather resistant.

The radio is secured in the upper compartment in an adjustable radio sling that allows the unit to be raised or lowered easily for access. A lower compartment is designed to hold a rechargeable battery power supply.

The price of the World Pack is \$57.95, P/N HMP. The cost of the power supply kit is \$63.95, P/N HPP9A.

For more information, contact:

CUTTING EDGE ENTERPRISES
1803 MISSION ST., STE. 546, DEPT. NV
SANTA CRUZ, CA 95060
1-800-206-0115 FAX: 831-426-0115
E-MAIL: cee@cruzio.com

Showcase your New Products here! Send all press releases or information/photos to:

Nuts & Volts Magazine
New Product News
430 Princland Court,
Corona, CA 91719
or E-Mail to
newproducts@nutsvolts.com

10-METER SSB TRANSCEIVER

The MFJ-9410X is a 20-watt PEP USB transceiver designed for fixed or portable radio communication in the 10-meter band. It uses a single-conversion mixing format and a low-noise heterodyne VFO for enhanced weak-signal performance.

The transmitter features a built-in seven-element lowpass filter to help reduce interference at TV and FM broadcast entertainment frequencies.

Other features include an HF-communication grade crystal, IF bandpass filter, built-in heavy duty speaker, full analog mechanical S-meter, optional semi-break-in CW module, and easy-to-operate controls.

Low drain lets you operate from a three-amp AC supply or 12-volt battery. All-analog circuitry



encourages high energy efficiency. The MFJ-9410X costs \$259.95 and comes with a rugged 3-1/2" top mount speaker.

MFJ ENTERPRISES, INC.
P.O. BOX 494, DEPT. NV
MISSISSIPPI STATE, MS 39762
601-323-5869 FAX: 601-323-6551

MICROPAC HC16 SBC WITH 1 MEG OF FLASH MEMORY

EMAC, Inc., announces that the MicroPac HC16 SBC now has 1 Meg of flash memory. The MicroPac HC16 can also have up to 1 Meg of RAM.

The processor utilizes the Motorola 68HC1621 16-bit microprocessor which is code-compatible with 68HC11 controllers.

This high-integration processor features integer DSP capability, programmable I/O ports, interrupt controller, watchdog timer, A/D converter, pulse width modulation (PWM) capability, and timer/counters.

EMAC integrated this powerful processor onto a board that contains 24 digital I/O lines, two serial RS232/485 ports, battery backed real-time clock/calendar, LCD interface, keypad interface, eight channels of A/D, and eight channels of D/A.

The MicroPac HC16 comes equipped with a Background Debug Mode (BDM) port. Through this port, programs can be downloaded and debugged. The BDM when used with the battery backed RAM and development software provides a full featured development system with features comparable to those of an In-Circuit Emulator.

DSP capability, fast analog conversions, and low interrupt latency time make

this board ideal for demanding real-time applications.

The cost of the MicroPac HC16 is \$249.95 US dollars in quantity of one.

WINDOWS CE CERTIFIED SBC-456/E

EMAC, Inc., announces that the SBC-456/E – a 486 PC compatible Single Board Computer – is now certified for Windows CE. This allows customers to utilize their knowledge of Windows API so they can develop embedded applications with minimal size and complexity.

The SBC-456 (non-Ethernet) and SBC-456E (with Ethernet) are half-sized AMD DX5-133 CPU cards with VGA/LCD interface. These boards offer an ISA bus and a PC/104 bus, DiskOnChip, and two COM ports.

The cost of the SBC-456 is \$387.00 and the SBC-456E is \$411.00 (US dollars) in quantity of one, including the CPU, but without memory.

For more information, contact:

EMAC, INC.
11 EMAC WAY, DEPT. NV
CARBONDALE, IL 62901
618-529-4525 FAX: 618-457-0110
WEB: <http://www.emacinc.com>



Fantastic DMM Offer!

Don't let this price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch. **Rubber Boot Included!** Display: 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity. Overrange Indication: 3 Least Significant Digits Blank. Temperature for Guaranteed Accuracy: 23°C ±5°C RH<75%.

Temperature Ranges:
Operating: 0°C to 40°C (32°F to 104°F)
Storage: -10°C to 50°C (14°F to 122°F)
Power: 9V Alkaline or Carbon-Zinc Battery (NEDA 1604)
Low Battery Indication: BAT on Left of LCD Display.
Dimensions: 188mm(L) x 87mm(W) x 33mm thick
Net Weight: 400g

**ONLY \$19**

Get All the Specs From Our Web Site

7 1/2" Pro Modular Crimping Tool Kit

Includes:
• Heavy Duty Ratchet Crimp Tool
• 5 Die Sets!



#HT-330K

ONLY \$64.95

Details on our Web Site

True RMS DMM

• Full Sized, 4 1/2 Digit
• Frequency Range to 20 KHz
• Capacitance Ranges from 2000 pF to 20 uF
• hFe, Audible Continuity, 20A max 1000VDC/20A max & 700VAC max
• Selectable Data Hold Function

**ONLY \$69**

CSI-980 DMM

Removable Hard Drive Rack

For IDE/Ultra DMA Hard Drives

We Sold Over 14,000 in 1998!

This product can be used with any 3-1/2 IDE hard drive up to 1" high. It includes an electronic keylock for safe removal and insertion. Made of ABS 707 fireproof plastic. Use this product to protect sensitive hard drive data, take your hard drive between work and home or even set up different users with their own hard drives that they physically insert every time they use a PC. Other models available from C.S.I. include RH10 series and RH20 series, which are interchangeable within the same interface design (IDE or SCSI).

Other Models are Available. See www.web-tronics.com under "hard drive and accessories" for more details and pictures.

RH-10C-IDE

ONLY \$14.95**Our Most Sophisticated DMM**

We Sold Over 700 Last Year!

with RS-232 Interface & Software, 3-3/4 Digit, 4000 Count, Auto-Ranging with Analog Bargraph

• True RMS Mode
• 10MHz Frequency Counter
• Time Mode with Alarm, Clock, and Stop Watch
• Dual Display
• 10 Location Memory
• Min, Max, Avg and Relative Mode
• Decibel Measurement
• Cap and Ind. Measurement
• Temperature Mode (C/F)
• K Type Temperature Probe Included
• Pulse Signal for Logic &



Audible Test
• Continuity/Diode Test
• Logic Test
• Auto Power OFF/"Keep ON" Mode
• Fused 20A Input with Warning Buzzer
• Back Light
• Data Hold/Run Mode
• Safety Design UL1244 & VDE-0411
• Protective Holster
• Silicon Test Leads

PROTEK 506

SALE \$139

Reg. \$169

Auto-Temp Solder Station with Ceramic Element

• With Ceramic Heating Element for More Accurate Temp Adjustment
• 3 Conductor Grounded Power Cord
• 250°C-480°C (470°F-900°F)
• Fast Heating Feature



SR-976 Extra Tip Options Available. See Web!

ONLY \$39

CTRL - D to bookmark this site

www.web-tronics.com

Don't forget the dash

Circuit Specialists Inc.

Easy to Navigate
• Includes a Search Engine
• That Really Works
• New Items Added Constantly

In Business Since 1971

CCD B&W Board Cameras

• ASIC CCD Area Image Sensor
• Extremely Low Power Consumption
• 0.5 Lux Min Illumination
• Built-In Electronic Auto Iris for Auto Light Compensation

Detailed Specs on the Web




VM1030PA
Pinhole lens with audio, 30mmx30mmx25mm, 12V, 430 horz & vert TV lines
\$59.00 \$49.00
5 or more

Infra-Red!

VMCB21
44mmx38.5mmx28mm with 6 infra-red LEDs, 12V, 380 horz TV lines
ON SALE \$59.00 any qty.
Reg. \$69.00



VM1035A
Standard lens with audio, 42mmx42mmx25mm, 12V, 430 horz & vert TV lines with back light compensation
\$77.00 \$68.00
5 or more

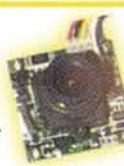

VM1030A
Standard lens with audio, 30mmx30mmx26mm, 12V, 430 horz & vert TV lines
\$59.00 \$49.00
5 or more



VM1036A
Standard lens with audio, 32mmx32mmx25mm, 12V, 430 horz & vert TV lines, reverse mirror image feature
\$69.00 \$63.00
5 or more

COLOR CCD Mini Board Cameras

• Low Power Consumption
• 1 Lux Illumination
• Built-In Electronic Auto Iris for Auto Light Compensation
• Internal Synchronization
• 12Volts
• 400 TV Lines



VM3011-A
Standard lens with audio, 45mmx40mmx24mm, single board
\$147.00 \$139.00
5 or more



VM3010PA
Pinhole lens with audio, 33mmx33mmx18mm
\$149.00 \$137.00
5 or more



VM3010-A
Standard lens with audio, 33mmx33mmx32mm
\$144.00 \$129.00
5 or more

Detailed Specs on the Web

Bullet CCD Cameras

• B&W and Color
• Smart Rugged Metal Housing
• Extremely Low Power Consumption
• 12 Volt
• CCD Area Image Sensor for Long Camera Life
• Built-In Electronic Auto Iris for Auto Light Compensation
• No Blooming, No Burning
• 0.1 Min Lux Illumination (B&W), 1 Lux Min Lux Illumination (color)



VMBLT3025W
Digital Color, Weatherproof, 20mm(D)x83mm(L)
\$219.00 \$199.00
5 or more

VMBLT1020W
B&W Weatherproof, 21mm(D)x58.5mm(L)
\$96.00 \$89.00
5 or more



VMBLT1020A
B&W with audio, 21mm(D)x55mm(L)
\$85.95 \$77.00
5 or more

Detailed Specs on the Web

Protek Amazing Test Equipment Offers

Series 6500 Deluxe
20MHz/40MHz/60MHz/100MHz
Dual-Trace Oscilloscopes

• Alternate Trigger
• Internal Sync Separator Circuit
• Alt-Mag Sweep
• Delay Sweep (6510)

LATEST DESIGNS!

Asia's currencies are devalued against U.S. dollars. Take advantage of GREAT prices while they last!



#6502 - 20MHz \$289

#6504 - 40MHz \$569

#6510 - 100MHz \$799

#6506 - 60MHz \$689

Part No.	Bandwidth	6510	6506	6504	6502
Bandwidth	100MHz	100MHz	60MHz	40MHz	20MHz
Vert. Sensitivity	1mV/DIV to 5V/DIV	1mV/DIV to 5V/DIV	1mV/DIV to 5V/DIV	1mV/DIV to 5V/DIV	1mV/DIV to 5V/DIV
Max Sweep Rate	2nS/DIV to 0.2S/DIV	2nS/DIV to 0.2S/DIV	0.1uS/DIV to 0.2S/DIV	0.1uS/DIV to 0.2S/DIV	0.2uS/DIV to 0.5S/DIV
Delay Sweep	YES	YES	YES	YES	YES
Vert. Mode Trig.	YES	YES	YES	YES	YES
Cursor Readout	NO	NO	NO	NO	NO
CRT Volts	12KV	10KV	10KV	10KV	2KV

For More Information See www.web-tronics.com**Amazing Test Equipment Offers**

10MHz Pulse Generator

• Max. 10MHz Rate
• Adjustable Delay Time & Pulse Width
• External Oscillator Input
• Variable Output Level Control
• Delay Function
• Frequency Counter

B1010
\$269 See the web site for details



2GHz Universal Counter

• Frequency, Period, Totalize Ratio Measurements
• Low Pass Filter
• 3 Channel Input (CH A, CH B, CH C)
• Variable Trigger Level
• 8 Digit LED Display
• 4 Step Gate Time Control
• FI/IO Input Attenuator
• Self Test

U2000A
\$319 See the web site for details



1GHz Multifunction Counter

• Frequency, Period, Totalize Measurements
• Low Pass Filter
• 2 Channel Input (100MHz, 1GHz)
• 8 Digit Gate Time Control
• 1/20 Input Attenuator

B-818
\$209 See the web site for details



Digital Multimeter

• AC/DC Voltage, AC/DC Current, Resistance Measurement
• 4 1/2 Digit Display
• Over Range Indication
• 7 Functions
• Data Hold Function

9902A
\$189 See the web site for details



10MHz Sweep Function Generator

• Sine, Triangle, Square, Ramp, Pulse Waveform
• Gate & Trigger Output
• Burst Waveform Output
• Sweep Function (Linear/Logarithmic)
• VCG Input
• GCV Function
• AM Modulation
• Variable Symmetry
• Output Attenuator
• DC Offset
• Frequency Counter

B-810
\$559 See the web site for details



2MHz Sweep Function Generator

• Sweep Function Width: 1:1 to 1000:1
• Sweep Rate: 0.5Hz to 50Hz
• Attenuation: -20dB
• Frequency Range: 0.02Hz to 2MHz in 7 Ranges
• Outputs: Sine, Triangle, Square Wave, Pulse, Ramp, Slew Sine Wave
• Sync Out: TTL Square Wave

9205
\$219 See the web site for details



20 Amp Switching Power Supply With Overvoltage Protection and Variable DC Output

Specifications
Input Voltage: AC 110V ±15%, 50Hz/60Hz
Output Voltage: DC 9V - 15V variable
Polarity: Negative ground
Current (13.8V): 25A peak, 20A continuous
Overvoltage Protection
Cooling fan inside chassis

\$99
See the web site for details #SPS-1020G



2MHz Sweep Function Generator

• Sine, Triangle, Square, Pulse, Ramp, Slew Sine Waveform
• Sync. Output (TTL Square Waveform)
• Sweep Function
• VCG Input
• DC Offset
• Variable Symmetry

9205C
\$279 See the web site for details

**PC Based Digital Storage Oscilloscope**

With Easy to Use Software

• Auto Setup
• Pre Trigger
• Voltage Range: 50mV to 5V, 7 steps
• Time Range: 50ns/div to 0.5s/div, 1-2-5 22 steps
• 32KB Memory Depth



#220

ONLY \$199

See the web site for details

HDD Heat Sink & Fan Heat Reduction System

• The Ultimate Heat Reduction System for Hard Drives
• Huge Aluminum Heat Sink, Plus Two Cooling Fans
• Heat Terminator Mounts in Any 5.25" F.D.D. Bay
• For All 3.5 Drives up to 1" High
• Hard Drive Heat Reduction up to 33%

HEAT TERMINATOR
\$39.00 \$35.00
10 or more

See the web site for details

2GHz RF Field Strength Analyzer

• Frequency Range: 100KHz to 2.060GHz
• Narrow Band FM (NFM), Wide Band FM (WFM), AM and Single Side Band (SSB) Modulated Signals May Be Measured
• PLL Tuning System for Precise Frequency Measurement and Tuning
• LED Backlight LCD (192x192 dots)



#3201
See the web site for details

ONLY \$1529

**COMPLETE STAND ALONE
DUPLICATION SYSTEM**

**EIGHT INDIVIDUAL
CONTROLLERS
FOR FULL
PERFORMANCE.**

**HIGH PERFORMANCE
INTEL EMBEDDED
PROCESSOR.**

**COPIES EVERYTHING:
PARTITIONS, O/S,
PROGRAMS - THE WORKS!**

**DUPLICATION
SOFTWARE ON
UPGRADEABLE CD**

COPY HARD DRIVES INSTANTLY!

"THE FASTEST WAY WE'VE FOUND TO MASS PRODUCE SYSTEMS." ANDY HSU, GENESIS TECHNOLOGY

SEVEN DRIVE DUPLICATOR

Copy entire hard drives with ease. Drive duplicators are an essential tool for dealers and system builders. Why spend hours installing and formatting drives when you can clone seven at once? This high speed, stand-alone IDE copier is easy to use and totally self-contained.

Set up any IDE or Ultra-DMA drive with all your original software. Connect blank drives and press "copy". You'll completely duplicate seven

**BUY DIRECT: \$2495
408 330-5523**

drives faster and more accurately than you can copy just one on a PC!

Notebook and desktop drives are supported. Eight separate ports let you copy drives at full speed without changing jumpers. Other copiers slow down with two or more drives attached. This true parallel transfer duplicator runs at full speed regardless of the number of drives attached.

Time is money. Get the fastest hard drive duplicator made. Performance exceeds the maximum speed of any available hard drive.




CORPORATE SYSTEMS CENTER
3310 WOODWARD AVE., SANTA CLARA, CA 95054
WWW.DRIVEDUPLICATORS.COM

This product is sold and intended for legitimate in-house duplication purposes only.
Copyright laws must be observed.

ONE SIZE FITS ALL


Super Carrier Board (#27130) for \$39

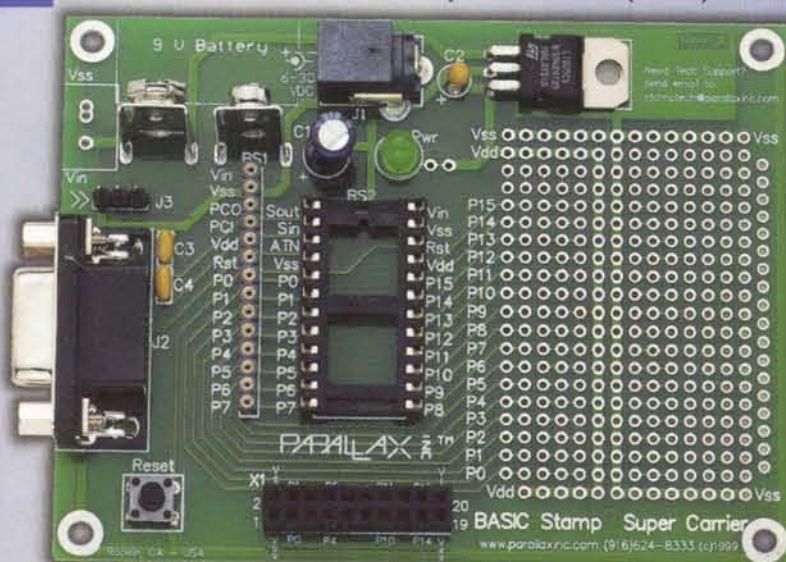

the new SUPER CARRIER BOARD from PARALLAX

DOWNLOAD the new BS2SX Win95/98/NT Interface at www.parallaxinc.com
Available April 15, 1999. Introductory prices good through June 15, 1999.

NEW!

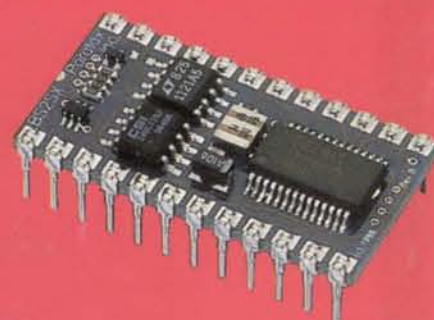

BS2SX Starter Kit

\$159 INTRODUCTORY PRICE

Using Scenix Semiconductor's SX microcontroller, the BS2SX-IC provides the highest speed, largest program memory, and fastest serial I/O in the BASIC Stamp family.

The new Super Carrier Board provides an easy means to program and prototype with the BASIC Stamp modules. The Super C also has a versatile power supply (use a 9V battery or an AC adapter) and will accommodate BS1-IC, BS2-IC, and BS2SX-IC modules. One board fits all!

Together with the new Super Carrier Board, Parallax has created the **BS2SX Starter Kit (#27206)**

The kit includes a BS2SX-IC module, the Super Carrier Board, BS2SX Win95/98/NT Interface, BASIC Stamp manual version 1.9, software and a serial cable. The BS2SX Starter Kit will be available April 15, 1999, for the introductory price of \$159.

The **Super Carrier Board (#27130)** is available separately for the introductory price of \$39.

To order call Parallax at (916) 624.8333
sales hours: Mon-Fri 8am-12pm and
1pm-5pm Pacific Standard Time.

For more information on Parallax products
visit our website at www.parallaxinc.com

PARALLAX

BASIC Stamp and the Parallax logo are registered trademarks of Parallax, Inc.

Write in 194 on Reader Service Card.

NUTS & VOLTS MAGAZINE
430 PRINCELAND COURT
CORONA, CA 91719

CHANGE SERVICE REQUESTED

BULK RATE
U.S. POSTAGE
PAID
PERMIT No. 49
LONG BEACH CA

